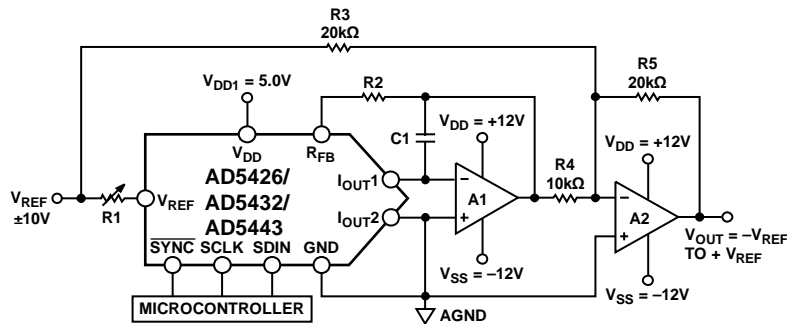


Precision, Bipolar Configuration for the **AD5426/AD5432/AD5443** 8-Bit to 12-Bit DACs

CIRCUIT FUNCTION AND BENEFITS

This circuit is a bipolar, precision dc digital-to-analog converter (DAC) configuration that employs a precision multiplying DAC and a low noise operational amplifier (op amp). The DAC is the core-programmable element and the amplifier selection dictates

the performance in terms of precision or speed. For an accurate, high precision, low noise application, the **AD8066** dual op amp can provide the current to voltage (I to V) conversion and the bipolar output.



NOTES

1. R1 AND R2 ARE USED ONLY IF GAIN ADJUSTMENT IS REQUIRED. ADJUST R1 FOR $V_{OUT} = 0V$ WITH CODE 10000000 LOADED TO DAC.
2. MATCHING AND TRACKING IS ESSENTIAL FOR RESISTOR PAIRS R3 AND R4.
3. C1 PHASE COMPENSATION (1pF TO 2pF) CAN BE REQUIRED IF A1/A2 IS A HIGH SPEED AMPLIFIER.

08270-001

Figure 1. Bipolar, Precision DC Conversion (Simplified Schematic)

TABLE OF CONTENTS

Circuit Function and Benefits.....	1	Common Variations.....	3
Revision History	2	References.....	3
Circuit Description.....	3		

REVISION HISTORY

11/2017—Rev. A to Rev. B

Document Title Changed from CN0036 to AN-1497 Universal
Changes to Circuit Description Section 3

7/2009—Rev. 0 to Rev. A

Updated Format..... Universal

CIRCUIT DESCRIPTION

Using a single op amp, this circuit can be configured to provide two-quadrant multiplying operation. When a single op amp (A1) is connected, the output voltage (V_{OUT}) of A1 is calculated by the following equation:

$$V_{OUT(A1)} = -V_{REF} \times (D/2^N)$$

where:

D is the digital word loaded to the DAC and N is the number of bits: $D = 0$ to 255 (8-bit [AD5426](#)), $D = 0$ to 1023 (10-bit [AD5432](#)), and $D = 0$ to 4095 (12-bit [AD5443](#)).

V_{REF} is the reference input voltage.

In some applications, it can be necessary to generate a full, four-quadrant multiplying operation or a bipolar output swing. To accomplish this, use another external amplifier (A2) and the R3, R4, and R5 external resistors, as shown in Figure 1. In this circuit, the second amplifier, A2, provides a gain of 2. Biasing the external amplifier with an offset from the reference voltage results in a full four-quadrant multiplying operation. The transfer function of this circuit shows that both negative and positive output voltages are created as the input data, D , is incremented from code zero ($V_{OUT} = -V_{REF}$), to midscale ($V_{OUT} = 0$ V), to full-scale ($V_{OUT} = +V_{REF}$).

Calculate V_{OUT} using the following equation:

$$V_{OUT} = V_{REF} \times (D/2^{N-1}) - V_{REF}$$

This circuit uses the [ADR01](#), a high accuracy, high stability, 10 V precision voltage reference. The reference is connected to the V_{REF} input of the circuit in Figure 1. Because the temperature coefficient and long-term drift are primary considerations for applications requiring high precision conversion, this device is ideal.

The supply voltage of the op amp limits the reference voltage that can be used with the DAC. The input bias current and input offset voltage of an op amp are important selection criteria for precision current output DACs. This circuit employs the [AD8066](#) op amp, which has ultralow input offset voltage (0.4 mV typical) and input bias current (2 pA typical).

The input offset voltage of the op amp, A1, is multiplied by the variable noise gain (due to the code dependent output resistance of the DAC) of the circuit. A change in this noise gain between two adjacent digital codes produces a step change in the output voltage due to the input offset voltage of the amplifier. This output voltage change is superimposed on the desired change in output

between the two codes and gives rise to a differential linearity error that, if large enough, can cause the DAC to be nonmonotonic. In general, the input offset voltage is a fraction of an LSB to ensure monotonic behavior when stepping through codes. For the 12-bit [AD5443](#), the LSB size is $10 \text{ V}/2^{12} = 2.44 \text{ mV}$, while the input offset voltage of the [AD8066](#) is only 0.4 mV.

Use proper grounding, layout, and decoupling techniques for proper operation of the circuit. Decouple all power supply pins directly at the pin with a low inductance, 0.1 μF ceramic capacitor. Ensure that the connection to ground is made directly to a large area ground plane. Additional decoupling using a 1 μF to 10 μF electrolytic capacitor is recommended on each power supply where it enters the printed circuit board (PCB). The decoupling capacitors are not shown in Figure 1 for simplicity.

COMMON VARIATIONS

The [OP2177](#) is another dual op amp for the I to V conversion circuit. It also provides a low input offset voltage (15 μV typical) and ultralow input bias current (0.5 nA typical). The [ADR02](#) and [ADR03](#), with 5.0 V and 2.5 V outputs, respectively, are other low noise references available from the same reference family as the [ADR01](#). Another suitable family of low noise references that are the [ADR441](#) and [ADR445](#) products. The value of the reference input voltage, V_{REF} , is restricted by the rail-to-rail output voltage swing of the operational amplifier selected.

REFERENCES

- [ADIsimPower Design Tool](#). Analog Devices, Inc.
- Kester, Walt. 2005. Chapter 3 and Chapter 7. *The Data Conversion Handbook*. Analog Devices.
- MT-015 Tutorial. *Basic DAC Architectures II: Binary DACs*. Analog Devices.
- MT-031 Tutorial. *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*. Analog Devices.
- MT-033 Tutorial. *Voltage Feedback Op Amp Gain and Bandwidth*. Analog Devices.
- MT-035 Tutorial. *Op Amp Inputs, Outputs, Single-Supply, and Rail-to-Rail Issues*. Analog Devices.
- MT-101 Tutorial. *Decoupling Techniques*. Analog Devices.
- [Voltage Reference Wizard Design Tool](#). Analog Devices.