

## Single Supply Low Noise LED Current Source Driver Using a Current Output DAC in the Reverse Mode

### CIRCUIT FUNCTION AND BENEFITS

This circuit provides a low noise, single supply current drive for an LED. Each component is selected to operate from a 3.0 V single supply while maintaining very low peak-to-peak noise. The signal chain is optimized for low power, low noise optical communications and medical applications.

In a typical pulse oximetry application, an LED is pulsed from a high level of current (e.g., 3/4 scale) to a lower level of current (e.g., 1/4 scale). The on time of these pulses is typically in the order of several hundred microseconds. Peak-to-peak 1/f noise superimposed on the LED brightness levels during the on time affects the accuracy of the overall measurement. The R-2R core of a current output DAC has inherently low 0.1 Hz to 10 Hz noise because it is only the resistive noise of the ladder that causes the noise. The AD5452 current output DAC is used in the reverse mode so it can support single supply applications. By applying 1.25 V to the IOOUT pin, a full-scale code will result in 1.25 V – 1 LSB appearing on the VREF pin, while a zero-scale code will result in 0 V on the VREF pin.

Key to maintaining low noise in the signal chain is the ADR127 reference, which has a 0.1 Hz to 10 Hz noise of only 9  $\mu$ V p-p. In addition, the AD8655 is the industry's lowest noise precision CMOS amplifier (1.23  $\mu$ V p-p). The combined circuit has a typical 0.1 Hz to 10 Hz noise of only 14.7  $\mu$ V p-p.

### CIRCUIT DESCRIPTION

**Table 1. Devices Connected/Referenced**

Product	Description
AD5452	12-bit multiplying DAC
AD8655	Low noise precision CMOS amplifier
ADR127	Low noise 1.25 V precision LDO

The signal chain in Figure 1 shows the AD5452 current output DAC in reverse (voltage switching) mode controlling the brightness of an LED. By using the current output DAC in reverse mode, described in more detail in the AD5452 data sheet, the part can take a positive low noise 1.25 V reference input and output a positive 1.25 V – 1 LSB output at full-scale. It is important to note that with this configuration, the current output DAC is limited to low input voltages (<1.5 V) because the switches in the DAC ladder do not have the same source-to-drain drive voltage. As a result, their on-resistance differs, which degrades the integral linearity of the DAC. The ADR127 is a low noise 1.25 V output precision LDO and provides this low voltage. The AD8655's high output current and low quiescent current make it ideal for handheld medical applications.

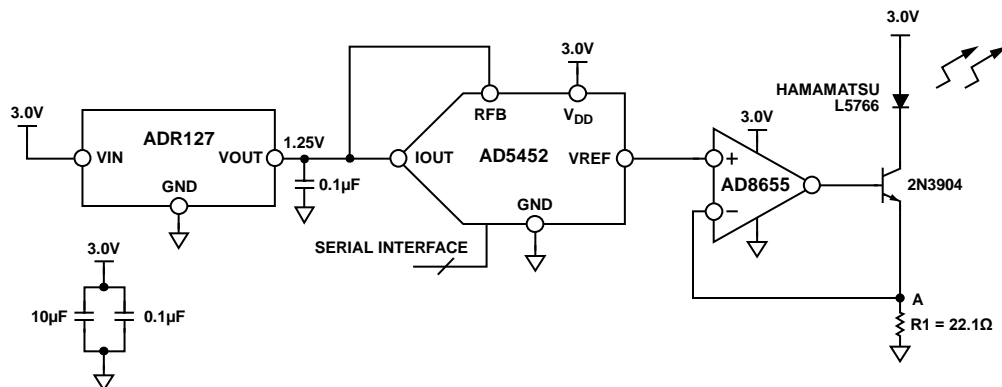


Figure 1. Low Noise LED Driver (Simplified Schematic: All Connections Not Shown)

The 12-bit [AD5452](#) DAC generates the voltage that drives the noninverting input of the operational amplifier. This voltage also appears across the R1 resistor, which should be a high precision resistor, and generates the current required at the collector of the bipolar transistor. Nominal diode current at full-scale is 56.6 mA for the circuit shown in Figure 1. A low noise [AD8655](#) is used to sense the current through R1.

The R-2R architecture of the [AD5452](#) allows for a very low noise DAC core. The dominating noise source in the signal chain is the ADR127 reference with a specified typical 1/f noise of 9  $\mu\text{V}$  p-p. The plot in Figure 2 is the 0.1 Hz to 10 Hz voltage noise at the negative terminal of the AD8655, removing the noise added by the LED, in this case a Hamamatsu L5766. A standard 2N3904 NPN bipolar transistor was used in the circuit to drive the LED.

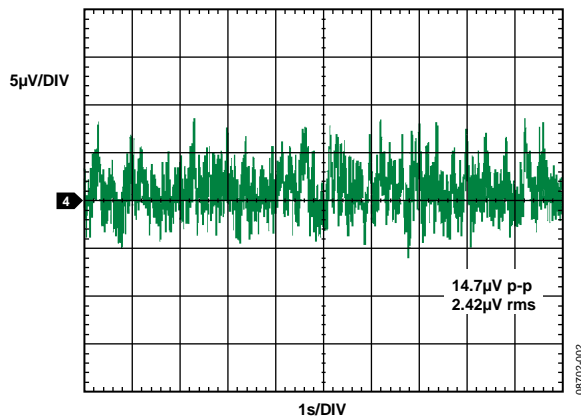


Figure 2. 0.1 Hz to 10 Hz Noise Measured at Point A

## COMMON VARIATIONS

Other suitable DACs are the 16-bit single channel [AD5543](#) or the 14-bit [AD5446](#). Dual channel DACs will also work, such as the [AD5447](#) (12-bit) and [AD5545](#) (16-bit). The [AD8656](#) is a dual channel version of the [AD8655](#).

Alternative low noise precision op amps such as the [ADA4841-1](#) and the [ADA4841-2](#) are also suitable.

## LEARN MORE

Kester, Walt. *The Data Conversion Handbook*. Chapter 3, 7. Analog Devices. 2005.

MT-015 Tutorial, *Basic DAC Architectures II: Binary DACs*. Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of AGND and DGND*. Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*. Analog Devices.

Voltage Reference Wizard Design Tool. Analog Devices

## Data Sheets and Evaluation Boards

[AD5452 Data Sheet](#)

[AD5452 Evaluation Board](#)

[AD8655 Data Sheet](#)

[ADR127 Data Sheet](#)

## REVISION HISTORY

4/12—Rev. 0 to Rev. A

Changed Document Title from CN-0139 to

AN-1212 ..... Universal

12/09—Revision 0: Initial Version