

Converting a Single-Ended Signal with the **AD7984** Differential PulSAR ADC

CIRCUIT FUNCTION AND BENEFITS

There are many applications that require a single-ended analog signal, either bipolar or unipolar, to be converted by a high resolution, differential input analog-to-digital converter (ADC). This dc-coupled circuit converts a single-ended input signal to a differential signal suitable for driving the **AD7984**, an 18-bit, 1.33 MSPS member of the PulSAR® family of ADCs. This circuit uses the **ADA4941-1** single-ended to differential ADC driver

and the **ADR435** ultralow noise 5.0 V voltage reference. The circuit can accept many types of single-ended input signals, including bipolar or unipolar, ranging from high voltage to low voltage. Direct coupling is maintained throughout. If board space is at a premium, all the ICs shown in Figure 1 come in small packages; either 3 mm × 3 mm lead frame chip scale package (LFCSP) or 3 mm × 5 mm micro small outline package (MSOP).

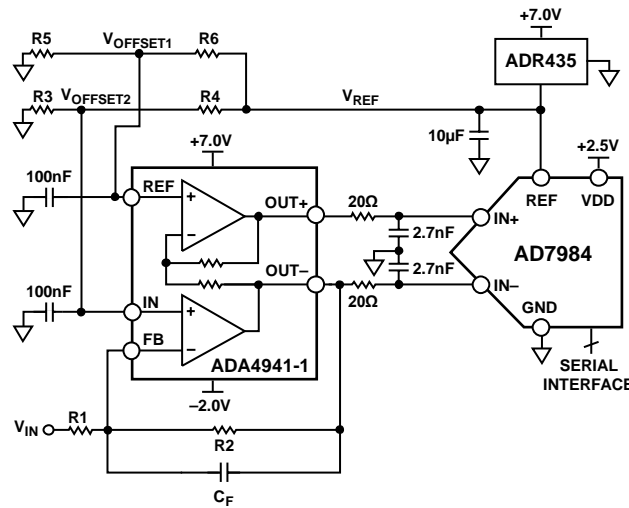


Figure 1. Single-Ended to Differential DC-Coupled Driver Circuit (Simplified Schematic)

TABLE OF CONTENTS

Circuit Function and Benefits.....	1	Common Variations.....	4
Revision History	2	References.....	4
Circuit Description.....	3		

REVISION HISTORY

12/2017—Rev. A to Rev. B

Document Title Changed from CN0033 to AN-1495.....	Universal
Changes to Figure 1	1
Changes to Circuit Description Section and Table 1	3

7/2009—Rev. 0 to Rev. A

Updated Format.....	Universal
---------------------	-----------

7/2009—Revision 0: Initial Version

CIRCUIT DESCRIPTION

The differential input voltage range of the [AD7984](#) is set by the voltage on the REF pin. For $V_{REF} = 5\text{ V}$, the differential input voltage range is $\pm V_{REF} = \pm 5\text{ V}$. The voltage gain (or attenuation) from the single-ended source, V_{IN} , to the OUT+ pin of the [ADA4941-1](#) is set by the ratio of the R2 resistor to the R1 resistor. The ratio of R2 to R1 is equal to the ratio of V_{REF} to the peak-to-peak input voltage at V_{IN} . For a peak-to-peak, single-ended input voltage of 10 V and $V_{REF} = 5\text{ V}$, the ratio of R2 to R1 is 0.5. The signal at the OUT+ pin is inverted (gain = -1) by the upper half of the [ADA4941-1](#), which supplies the opposite phase output signal at the OUT- pin. The absolute value of the R1 resistor determines the input impedance of the circuit. The C_F feedback capacitor is chosen based on the desired signal bandwidth, which is approximately $1/(2\pi R2C_F)$. The 20 Ω resistors and the 2.7 nF capacitors act as a 3 MHz, single-pole, low-pass noise filter.

Resistors R3 and R4 set the common-mode voltage on the IN- input of the [AD7984](#). The value of this common-mode voltage is $V_{OFFSET2} \times (1 + R2/R1)$, where $V_{OFFSET2} = V_{REF} \times R3/(R3 + R4)$. Resistors R5 and R6 set the common-mode voltage on the IN+ input of the ADC. This voltage is equal to $V_{OFFSET1} = V_{REF} \times R5/(R5 + R6)$. The common-mode voltage of the ADC, which is equal to $V_{OFFSET1}$, is close to $V_{REF}/2$. This presumption implies that $R5 = R6$. Table 1 shows some possible standard 1% values for the resistors for popular input voltage ranges.

The [ADA4941-1](#) operates on supply voltages of +7 V and -2 V. Because each output must swing from 0 V to 5 V, the positive supply voltage must be a few hundred millivolts greater than 5 V, and the negative supply must be a few hundred millivolts more negative than 0 V. For this circuit, supply voltages of +7 V and -2 V are chosen.

The 7 V supply also provides sufficient headroom to power the [ADR435](#). Other voltages are possible, provided the absolute maximum total supply voltage on the [ADA4941-1](#) does not exceed 12 V, and the headroom requirement of the [ADR435](#) is observed.

The [AD7984](#) requires a 2.5 V supply for VDD as well as a VIO supply (not shown in Figure 1), which can range between 1.8 V and 5 V, depending on the input/output logic interface levels.

This circuit is not sensitive to power supply sequencing. The [AD7984](#) inputs can withstand up to $\pm 130\text{ mA}$ maximum during momentary overvoltage conditions.

The [AD7984](#) serial peripheral interface (SPI)-compatible serial interface (not shown in Figure 1) has the ability to daisy-chain several ADCs on a single 3-wire bus and provides an optional busy indicator via the SDI input pin. The SPI is compatible with 1.8 V, 2.5 V, 3 V, and 5 V logic, using the separate VIO supply. For full details on the SPI interface, digital modes, and logic power options, see the [AD7984](#) data sheet.

Use proper layout, grounding, and decoupling techniques to achieve the desired performance from the circuits discussed in this application note. As a minimum, use a 4-layer printed circuit board (PCB) with one ground plane layer, one power plane layer, and two signal layers.

All IC power pins must be decoupled to the ground plane with low inductance, multilayer ceramic capacitors (MLCC) of 0.01 μF to 0.1 μF (this is not shown in Figure 1 for simplicity).

Consult the [EVAL-AD7984](#) and [EVAL-FDA-1](#) evaluation board user guides for the recommended layout and critical component placement of each product.

Table 1. Circuit Values and Voltages for Popular Input Voltage Ranges

V_{IN} (V)	$V_{OFFSET1}$ (V)	$V_{OFFSET2}$ (V)	OUT+ (V)	OUT- (V)	R1 (k Ω)	R2 (k Ω)	R4 (k Ω)	R3, R5, R6 (k Ω)
+20, -20	2.5	2.203	-0.01, 4.96	5.01, 0.04	8.06	1.00	12.70	10.00
+10, -10	2.5	2.000	0.01, 4.99	4.99, 0.01	4.02	1.00	15.0	10.00
+5, -5	2.5	1.667	0.00, 5.00	5.00, 0.00	2.00	1.00	20.0	10.00

COMMON VARIATIONS

For different reference voltages, the [ADR430](#), [ADR431](#), [ADR433](#), [ADR434](#), and [ADR435](#) family of references has a wide range of values that can interface with the ADC.

REFERENCES

Kester, Walt. 2005. Chapter 6 and Chapter 7. *The Data Conversion Handbook*. Analog Devices.

Kester, Walt. 2006. Chapter 2. *Optimizing Data Converter Interfaces*. High Speed System Applications. Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*. Analog Devices.

MT-035 Tutorial, *Op Amp Inputs, Outputs, Single-Supply, and Rail-to-Rail Issues*. Analog Devices.

MT-074 Tutorial, *Differential Drivers for Precision ADCs*. Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*. Analog Devices.

[Voltage Reference Selection Wizard](#)