

Easily Boost 12V to 140V with a Single Converter IC

Design Note 1033

Victor Khasiev

INTRODUCTION

Generating a high voltage from a much lower voltage presents a number of challenges for the classical single stage boost topology. For instance, the maximum duty cycle limitation of a boost controller may not allow the required step-up ratio. Even if it does, there is often a sharp decrease in efficiency at high duty cycles. The duty cycle can be shortened by choosing discontinuous mode of operation, but this leads to high peak input current, higher losses and EMI challenges.

An alternative to a single boost converter is a 2-stage boost converter, where the first stage produces an intermediate voltage and the second stage boosts to the final high voltage. A 2-stage converter can be produced with a single controller IC, such as the LTC®3788, a high performance 2-phase dual output synchronous boost controller, which drives all N-channel power MOSFETs.

The LTC3788 can be configured such that the first boost stage takes advantage of its synchronous rectification feature, which maximizes efficiency, reduces



Figure 1. Block Diagram of LTC3788-Based 2-Stage Boost Converter

power losses and eases thermal requirements. The maximum output voltage of this controller is 60V, when using synchronous rectification. If greater than 60V is required, the second stage can be designed to run non-synchronously, as described below.

2-STAGE BOOST PRODUCES 140V FROM 12V

The block diagram in Figure 1 shows the LTC3788 in a 2-stage boost configuration. This block diagram also reveals a few caveats that must be observed in this design:

- The output of the first stage (Q1, CINT) is connected to the input of second stage (RS2, L2). The output of the first stage should not exceed 40V, because maximum absolute rating of the SENSE pins is 40V.
- The gate drive voltage of 5V is suitable for logic level MOSFETs, but not for high voltage standard MOSFETs, with typical gate voltages of 7V to 12V. The external gate driver DR, controlled by the BG2 signal can be used as shown here to drive high voltage standard MOSFETs.
- To generate an output voltage above maximum limit of 60V, the synchronous rectification MOSFET is replaced by a single diode D1.

Figure 2 shows the complete solution. Transistors Q1, Q2, and inductor L1 compose the first stage, which generates an intermediate bus voltage of 38V. The first stage employs synchronous rectification for maximum efficiency. The output of the first stage is connected as input to the second stage, comprised of Q3, D1, L2. The output of second stage produces 140V at 1A.



Figure 2. Full Schematic of 2-Stage 140V Output, 1A Boost Converter

Transistor Q3 is standard level MOSFET, driven by the LTC4440. Here, an LDO, based on transistor Q4, biases the gate driver, but a switching regulator can be employed instead (such as one built around the LTC3536) to further increase overall efficiency.

This solution features an input voltage range from 3V to 36V, nominal 12V. To decrease components' thermal stress, the output current should be reduced when the input voltages falls below 10V. Figure 3 shows measured efficiency, and Figure 4 shows the start-up waveforms. A 93% efficiency is shown with $V_{IN} = 24V$ and with the 140V output loaded from 0.4A to 1A. This converter can operate at full load with no airflow.

CONCLUSION

LTC3788 is a high performance 2-phase dual output synchronous boost controller, suitable for high power, high voltage applications. Its dual outputs can be used in tandem to achieve extremely high step-up ratios to high voltages.

Data Sheet Download

www.linear.com/LTC3788



Figure 3. Efficiency of the 2-Stage Converter in Figure 2 $[V_{IN}\ 8V\ to\ 24V,\ V_{OUT}\ 140V]$



Figure 4. Start-Up Waveforms [from V_{IN} 12V to V_{OUT} 140V at 1A]

For applications help, call (408) 432-1900, Ext. 3161

