

E3-238
Analog and Mixed Signal
VLSI Circuit Design

Dr. Navakanta Bhat

Assistant Professor, ECE Department
Indian Institute of Science, Bangalore-560012

Email: navakant@ece.iisc.ernet.in

URL: http://ece.iisc.ernet.in/~navakant/Navakant_Bhat.html

Version 1, 26th July 2003

Dr. Navakanta Bhat

Scope of the Course-ware

“This course material has been developed to supplement the the discussions during the lectures in class. You can use this as the principal reference material. However, this course material is not a text book. You may still want to read up some of the books listed in the reference list to gain more insight or to get alternate explanation for a given topic.”

Your feedback is wel-come in terms of any corrections or any additions to be done to the course-ware to improve its utility.

Note: The emphasis in this course is to designs analog circuits on a digital CMOS technology. Some of the discussions should be viewed and appreciated with this context in mind.

List of Reference books

Due to the advent of mixed signal SOCs, numerous books have been published on Analog Design. A partial list :

1. Analog CMOS Design

Razavi, McGraw Hill Publication

2. CMOS: Circuit Design, Layout , and Simulation

Boise, Baker, Lee, Prentice Hall Publication

3. Analog VLSI : Signal and Information Processing

Ismail and Feiz, McGraw Hill Publication

4. Analysis and Design of Analog Integrated Circuits

Gray and Meyer, Wiley Publication

Topics covered

- CMOS versus Bipolar Implementation
- The Sub-micron MOS Transistor for Analog Design
- Small signal parameters for MOSFET
Cut-off frequency, Concept of Poles and Zeros, Miller approximation
- Single stage Amplifiers
Common source, Common gate, Source follower, Cascode
- Current Mirror
Cascode Current Mirror, Wilson Current Mirror, Regulated Cascode
- Layout issues
- Bandgap Voltage Reference

Topics covered

- Differential Amplifier
- Gilbert Cell
- Design of 2 stage CMOS OPAMP
 - Differential to Single ended conversion, DC and AC response
 - Frequency Compensation, Pole Splitting, Zero Cancellation
- OPAMP Performance Metrics
 - Slew rate, CMRR, Offset, Noise ...
- Output Stage
- OTA and OPAMP Circuits
- Sample and Hold
- Switched Capacitor Circuits


Topics covered

- Comparator
- Sense Amplifier
 - Voltage SA, Current SA, Latch type SA, Gain bandwidth analysis
- Impact of mismatch on Analog design
 - Offset effects in Sense Amplifier
- Statistical Design and Simulation
- Alternate Device Gallery for Low Voltage Low Power Analog Design
 - Wide common range OPAMP
 - Bulk driven OPAMP
 - Lateral BJT in CMOS Technology
 - Sub-threshold operation of MOSFET : Neural Network Application
 - Floating Gate transistor as analog memory

The First Transistor : 1947

The baby is born!


Bardeen, Brattain, Schokley @ Bell Labs

 

- First transistor was point contact Ge bipolar junction transistor, whereas the VLSI is neither based on Ge nor on BJT!
- The Bell Labs team was in fact trying to make MOS transistor, but got stuck with surface states and ended up with BJT!

Metal Oxide Semiconductor Field Effect Transistor (MOSFET)

 
- Field effect transistor concept proposed in 1930s by Lilienfeld
- First MOSFET fabricated in 1960 by Kahng and Atalla




- Early MOS technology was based on PMOSFETs

CMOS (Complementary MOS) technology

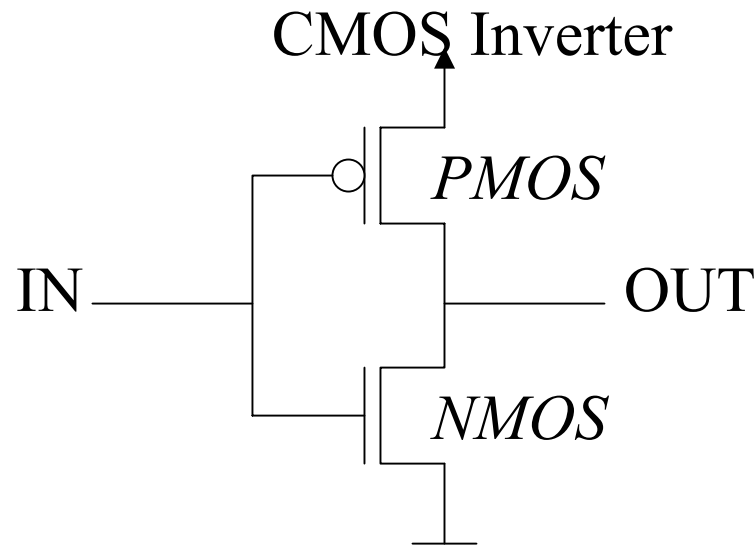- Both NMOSFETs & PMOSFETs are used
- No static power consumption
- Very high integration density
- Very good isolation
- Very low cost




Evolution from SSI to VLSI

 

- In the the Digital world, MOSFET completely displaced BJT due to all the advantages offered by CMOS

CMOS market share

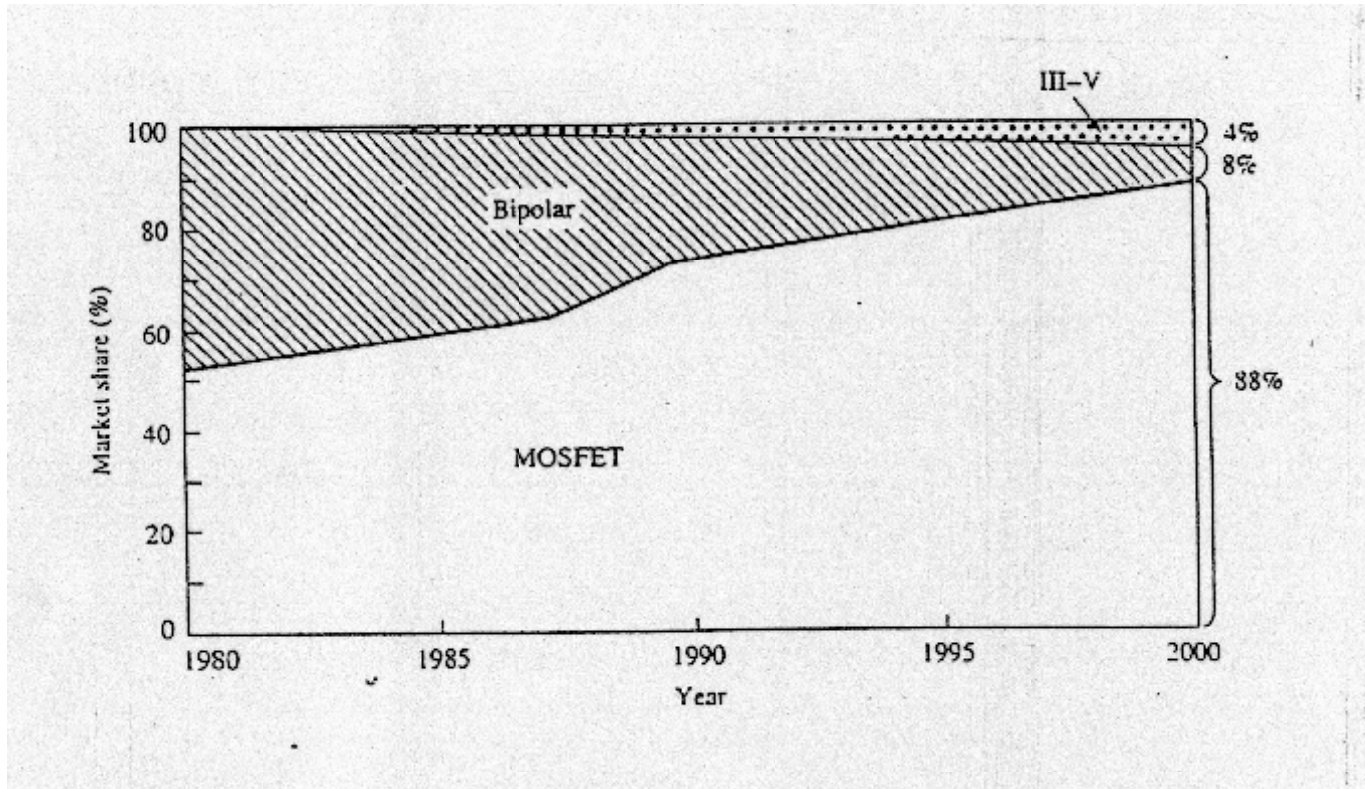

- CMOS captures more than 90% of electronics market share


Process Technology Today (2003)

- 0.13 μm digital technology in volume production
- Number of transistors per chip is \sim 1 billion(DRAMs),
 \sim 100 million (microprocessors)
- Technology scaling for future more challenging and expensive
- State of the art fab set-up costs more than US\$2 billion
- Recovering the fab cost requires a modular process technology approach capable of producing diverse products


What do we do with the technology capable of making millions of transistor on a tiny area in Si? :

Mixed Signal Systems On Chip (SOC)

BJT versus MOSFET speed

 


Base width defined by diffusion process

 

Channel length defined by Photolithography process

- Historically BJT used to be faster than MOSFET
- CMOS scaling has brought MOSFET on par with BJT

Cut-off frequency, f_T

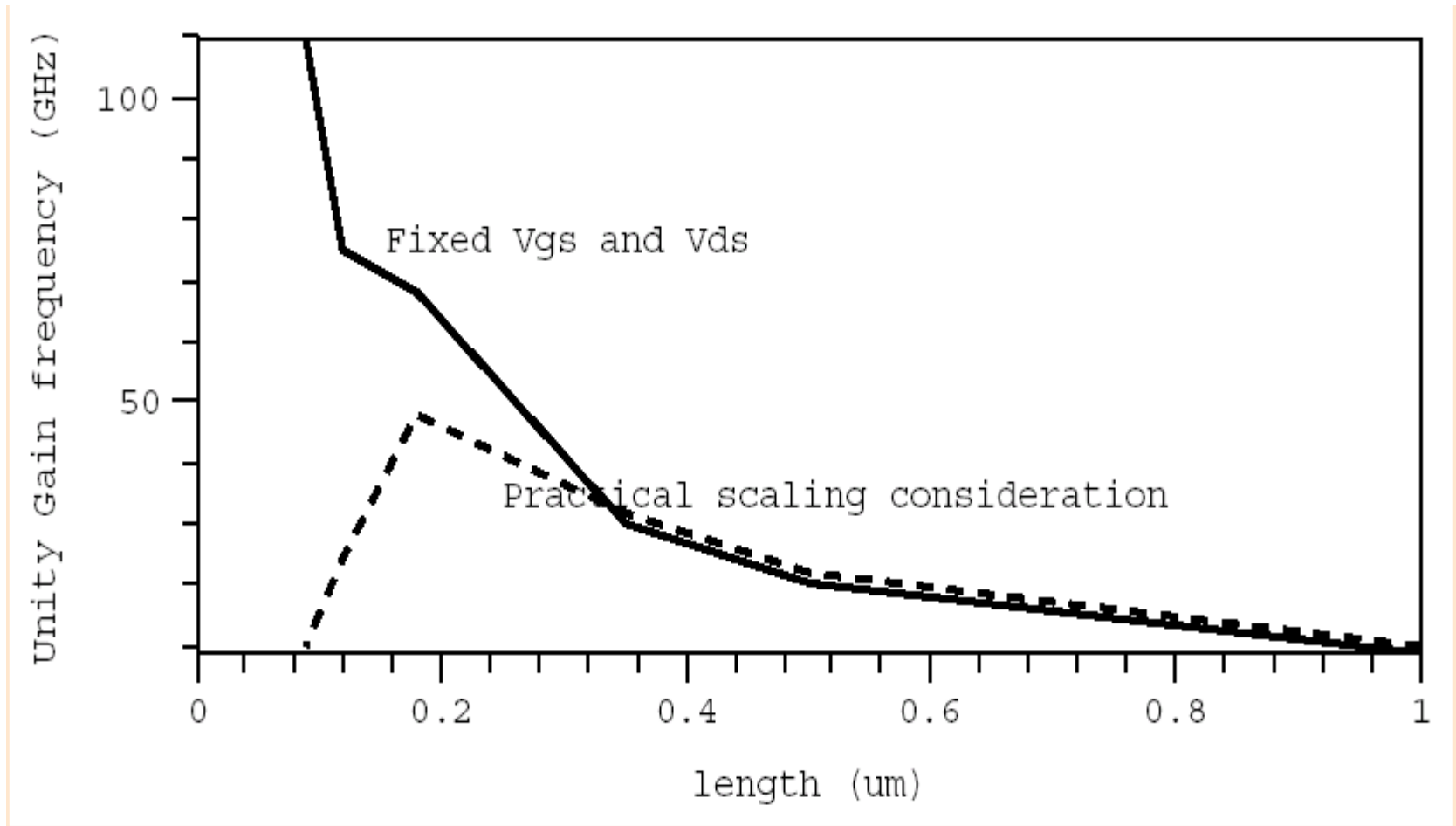





- MOSFET f_T has increased with scaling

Analog Design on Digital Technology


- Microprocessors are today's technology drivers
- The most elegant analog designs make use of the existing digital technology
- Every modification to the baseline technology adds on to the manufacturing cost
- Design For Manufacturability (DFM)
- CMOS analog circuits are logical choice

The Sub-micron MOS Transistor for Analog Design

Transistor abstraction

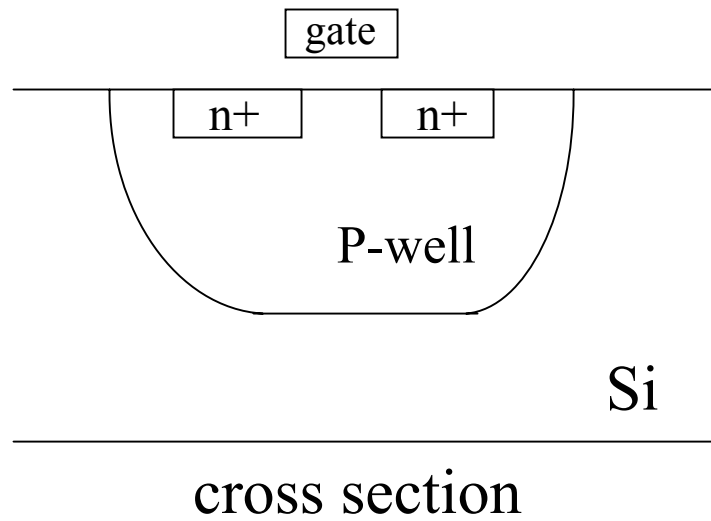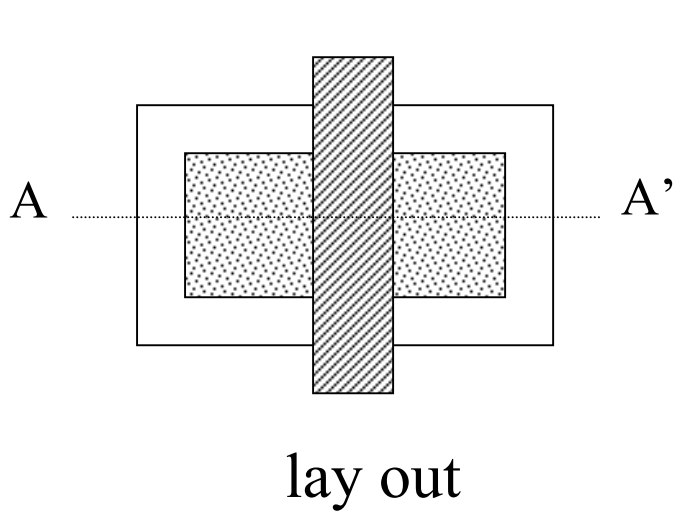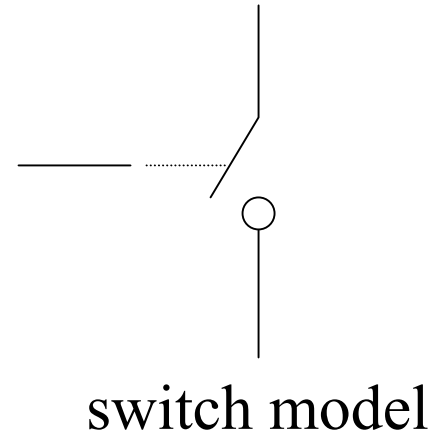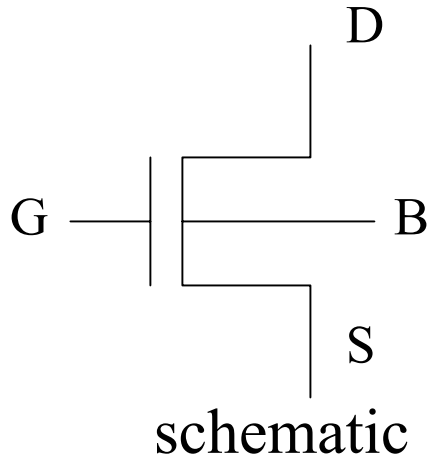

Simple 3-D picture of MOSFET

 

The 2 important dimensional parameters of MOSFET under circuit designer's control are:

$L_g = \text{Length of the gate}$

$W_g = \text{Width of the gate}$

Simple MOS Theory

$V_{gs} < V_t$, MOSFET is in cut off region

$$I_{ds} = 0$$

$V_{gs} > V_t$, $V_{ds} < V_{gs} - V_t$, MOSFET is in linear region

$$I_{ds} = \frac{\mu \epsilon_{ox} W}{T_{ox} L} \left[(V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right]$$

$V_{gs} > V_t$, $V_{ds} > V_{gs} - V_t$, MOSFET is in saturation region


$$I_{ds} = \frac{\mu \epsilon_{ox} W}{T_{ox} L} \frac{(V_{gs} - V_t)^2}{2}$$

where μ is mobility, ϵ_{ox} is permittivity of the oxide, and V_t is the threshold voltage of the MOSFET


$$V_t = V_{fb} + 2\phi_b + \frac{T_{ox} \sqrt{4\epsilon_s q N_a \phi_b}}{\epsilon_{ox}}$$

I-V characteristics

Output Characteristics

 



Transfer Characteristics

 

- I_{ds} is constant and independent of V_{ds} in saturation
- I_{ds} is zero in sub-threshold region

Both of these idealities are incorrect especially for the sub-micron MOS transistor

Channel length modulation

 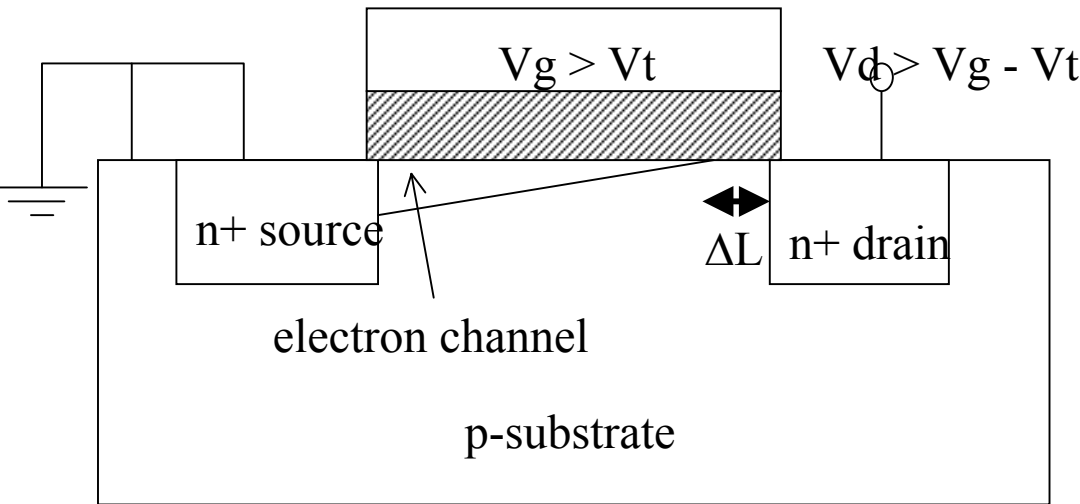

Effective channel length is $L_{eff} = L - \Delta L$, where $\Delta L = f(V_{ds})$

$$I_{ds} = \frac{\mu \epsilon_{ox} W}{T_{ox} L_{eff}} \frac{(V_{gs} - V_t)^2}{2}$$



$$I_{ds} = \frac{\mu \epsilon_{ox} W}{T_{ox} L} \frac{(V_{gs} - V_t)^2}{2} (1 + \lambda V_{ds})$$

I_{ds} increases slightly in saturation region with increasing V_{ds}

This limits the AC output resistance for analog applications

λ is channel length modulation parameter in SPICE

Sub threshold conduction

 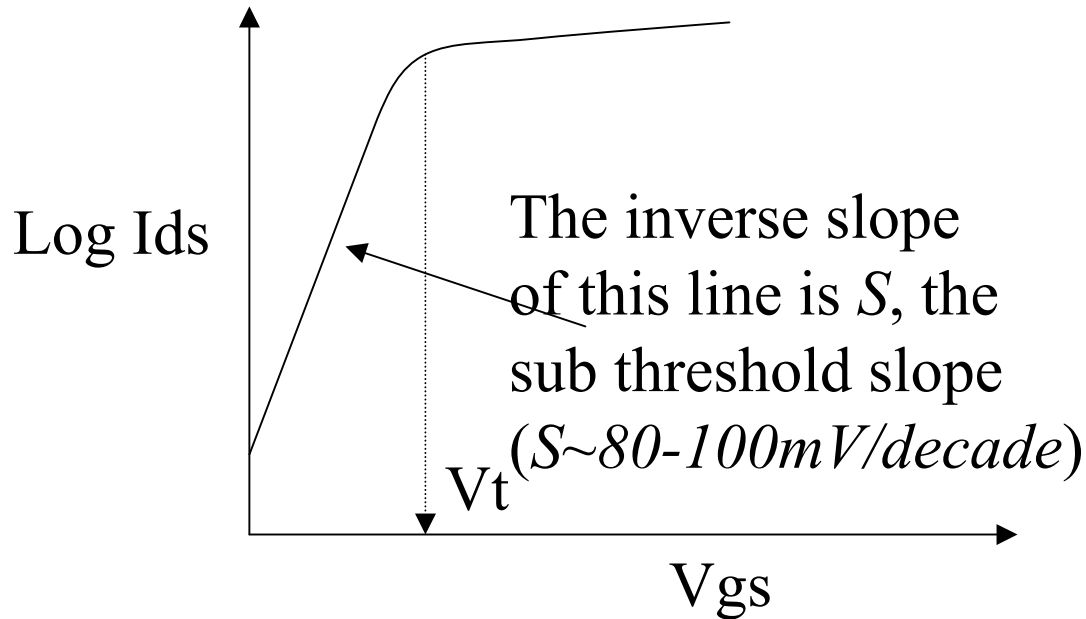

- For $V_g < V_t$, current is non zero and is exponential function of V_g
- $S = 2.3kT/q (1 + C_{si}/C_{ox})$ mV/decade
C_{si}=depletion capacitance in Si, C_{ox}=oxide capacitance, kT/q =thermal voltage
- MOSFET should be designed to have minimum possible S
- Sub threshold analog circuits work based on this principle

Sub threshold limitation on V_t scaling

Suppose $S = 100\text{mV/decade}$


Suppose MOSFET should have $I_{on}/I_{off} = 10^6$

Then for $V_{ds}=V_{supply}$,
when V_{gs} is changed from 0V (off state) to supply (on state)
 I_{ds} should change by ~ 6 decades

$$V_{tmin} = 100 * 6 = 0.6\text{V}$$

\Rightarrow The value of S will impose the lower limit on V_t scaling

Body effect

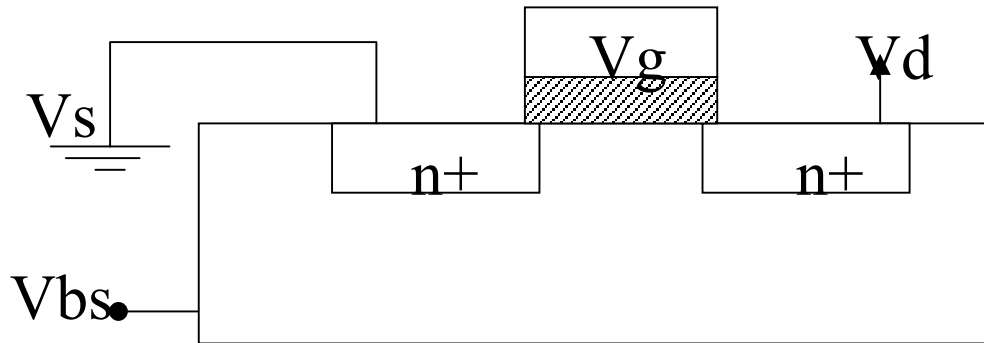


$$V_{t0} = V_{fb} + 2\phi_b + \frac{T_{ox} \sqrt{4\epsilon_s q N_a \phi_b}}{\epsilon_{ox}}$$

$$V_t = V_{t0} + \gamma \left(\sqrt{|V_{bs}| + 2\phi_b} - \sqrt{2\phi_b} \right)$$

$$\gamma = \frac{T_{ox} \sqrt{2q\epsilon_s N_a}}{\epsilon_{ox}} \quad \gamma = \text{body effect factor } (\gamma = 0.3-0.7)$$


- V_t increases due to body effect
- This results in a transconductance term

Short Channel Effect (SCE)

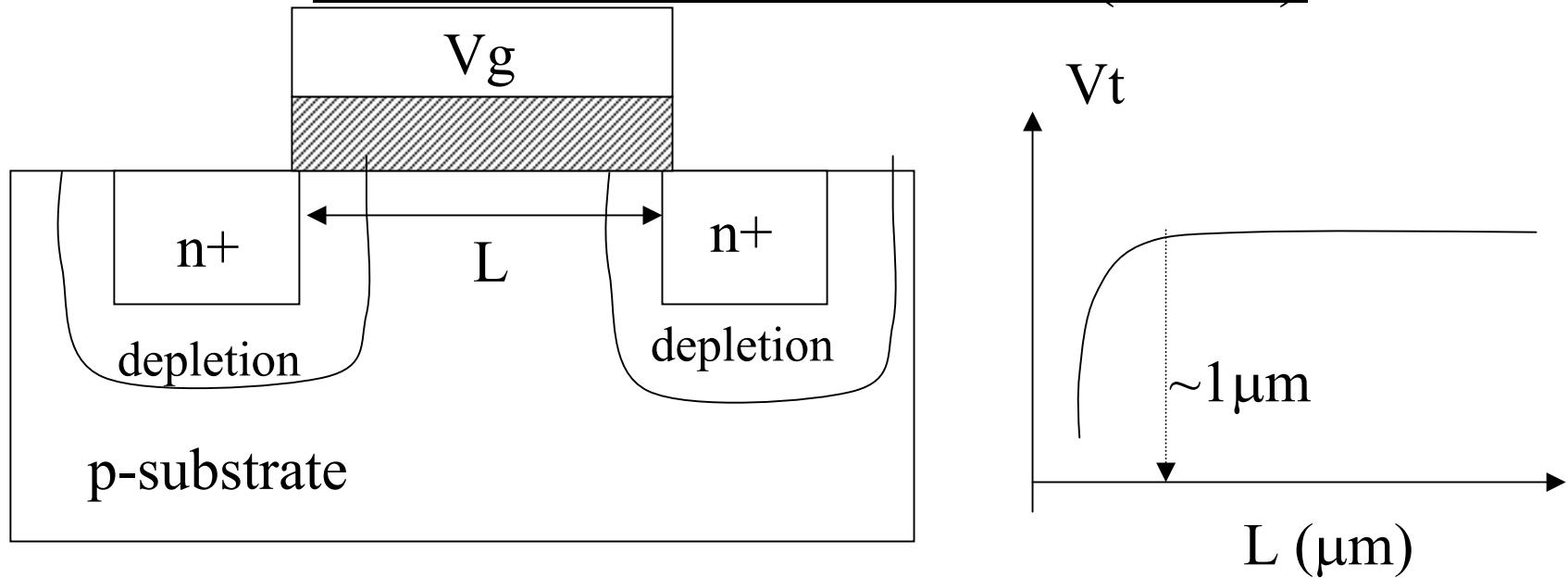


- Fraction of the depletion charge (Q_d in V_t equation) is supported by the source and drain junctions and hence V_g need not support this
 - When L is very small ($\sim 1 \mu\text{m}$) this charge becomes significant fraction of the total depletion charge and can not be neglected
- $\Rightarrow V_t$ decreases with decreasing L
- Impacts matching of transistors in analog applications

Reverse Short Channel Effect

 



- Invariably exists in almost all the sub-micron technologies
- The techniques used to suppress SCE are responsible for RSCE
- V_t becomes very sensitive function of L

Drain Induced Barrier Lowering (DIBL)

 


- V_t is also a function of drain voltage in sub-micron transistors
- DIBL effect is negligible in the long channel regime

Narrow Width Effect

 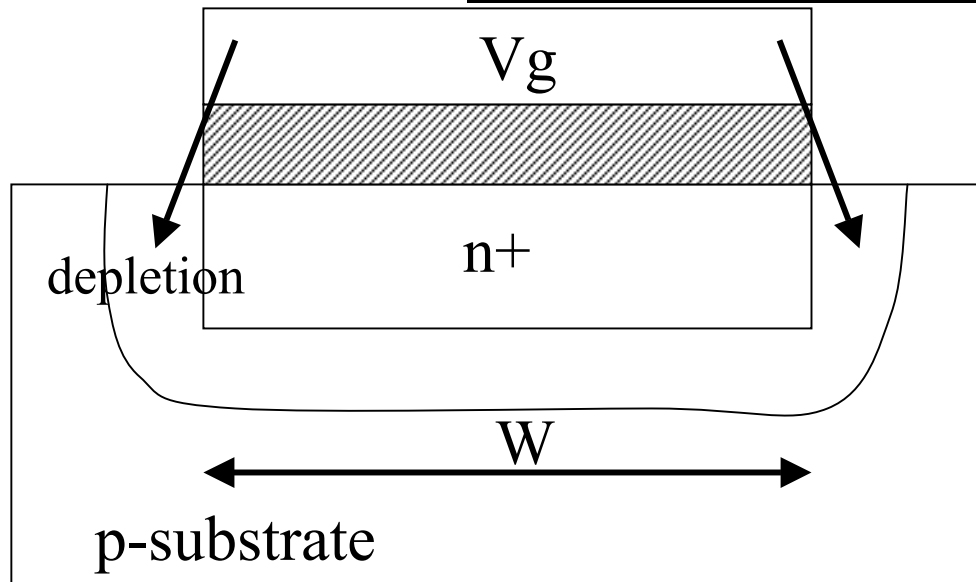


- Additional depletion charge at the edge of source & drain should be supported by the V_g before inverting the channel
 - When W is very small ($\sim 1\mu\text{m}$) this charge becomes significant fraction of the total depletion charge and can not be neglected
- $\Rightarrow V_t$ increases with decreasing W

Velocity saturation

 

 $v = \mu E$ valid only at low electric fields (E)




I_{ds} will be less than expected due to velocity saturation

- For velocity saturated transistor, the saturation drive current is

$$I_{ds} = \frac{\epsilon W (V_{gs} - V_t) v_{sat}}{T_{ox}}$$

- **Transconductance will be independent of L**
- For $L=0.1 \mu\text{m}$ transistor operating at $V_d=1\text{V}$:
 $E=10^5$ V/cm \Rightarrow transistor is velocity saturated

Punch through

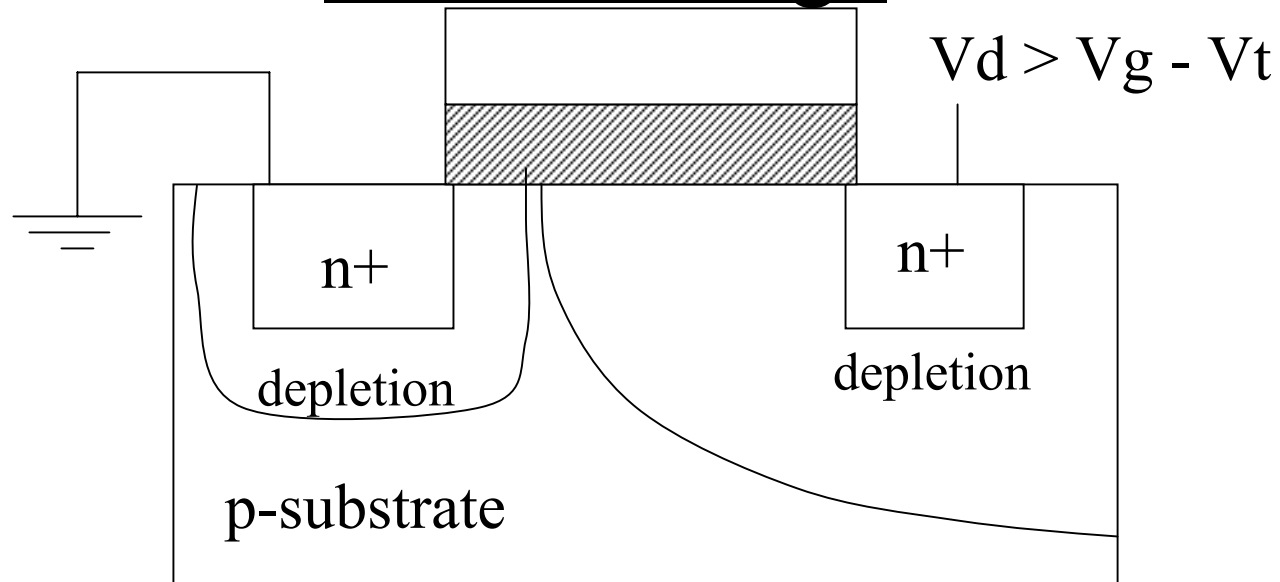


For short channel length, the drain depletion region merges with source depletion region for $V_d > V_{pt}$, punch through voltage

This results in large transistor current resulting in breakdown

Punch through voltage, V_{pt} , is one of the limiting factors on V_{dsmax}


Bipolar induced breakdown

 Parasitic Bipolar effect can trigger breakdown even before the punch through voltage is reached.



Avalanche effect at the drain generates e-h pairs. The hole current going into the bulk can turn on BJT

Hot carrier reliability

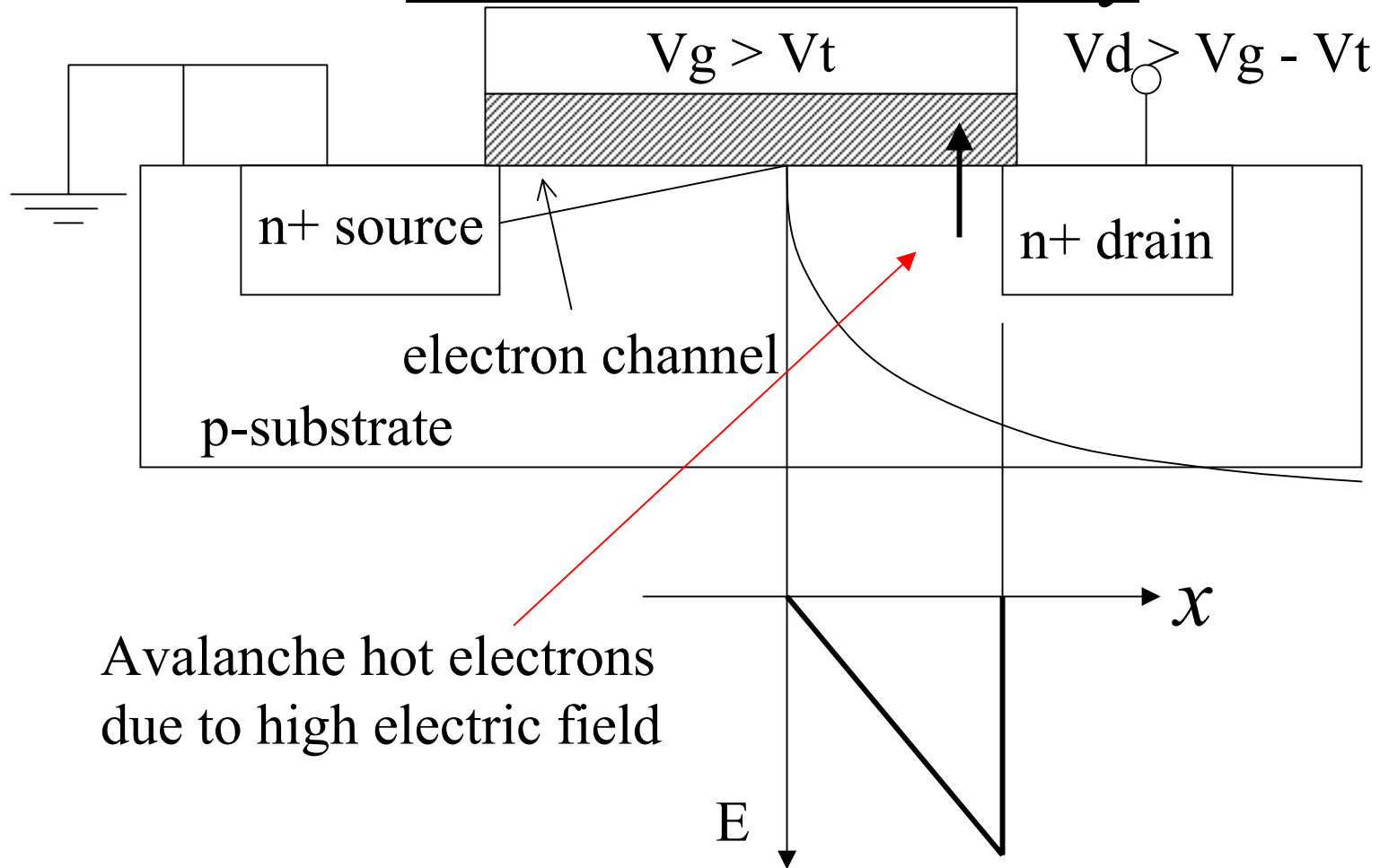

Hot electron generation is maximum when $V_g \sim V_d/2$

Transistor degradation due to hot carriers

Some of the high energy electrons are injected into the gate oxide by surmounting the barrier at Si-SiO₂ interface



Injected electrons get trapped in the oxide

The trapped electrons increase V_t , decrease mobility and decrease drain current

Transistor degradation in turn reflects in circuit behavior resulting in decreased speed and functional failure under extreme conditions

Hot carrier degradation can be significant in analog transistor biased such that $V_{gs} \sim V_{ds}/2$

Gate oxide reliability

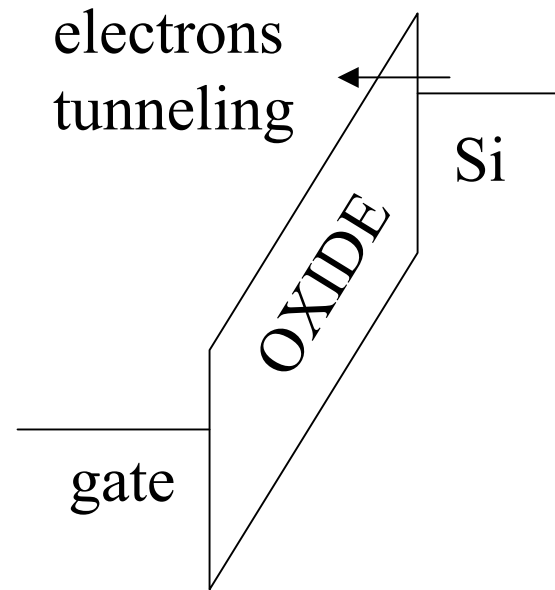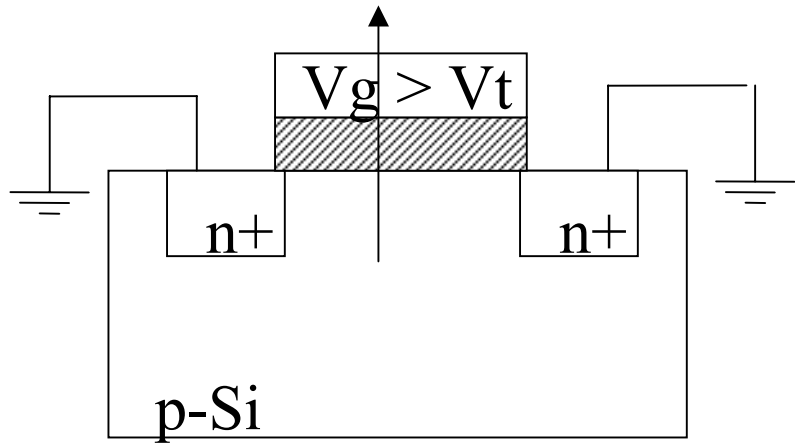


$$E_{ox} = V_{ox}/T_{ox}$$

Under high electric fields electrons tunnel through the oxide

Tunneling electrons create damage in the oxide and hence affect the transistor performance

Gate oxide reliability worsens with decreasing oxide thickness

Constant field scaling

 

Primary scaling factors:

Tox, L, W, Xj (all linear dimensions)	1/K
Na, Nd (doping concentration)	K
Vdd (supply voltage)	1/K


Derived scaling behavior of transistor:

Electric field	1
Ids	1/K
Capacitance	1/K

Derived scaling behavior of circuit:



Delay (CV/I)	1/K
Power (VI)	1/K ²
Power-delay product	1/K ³
Circuit density ($\propto 1/A$)	K ²

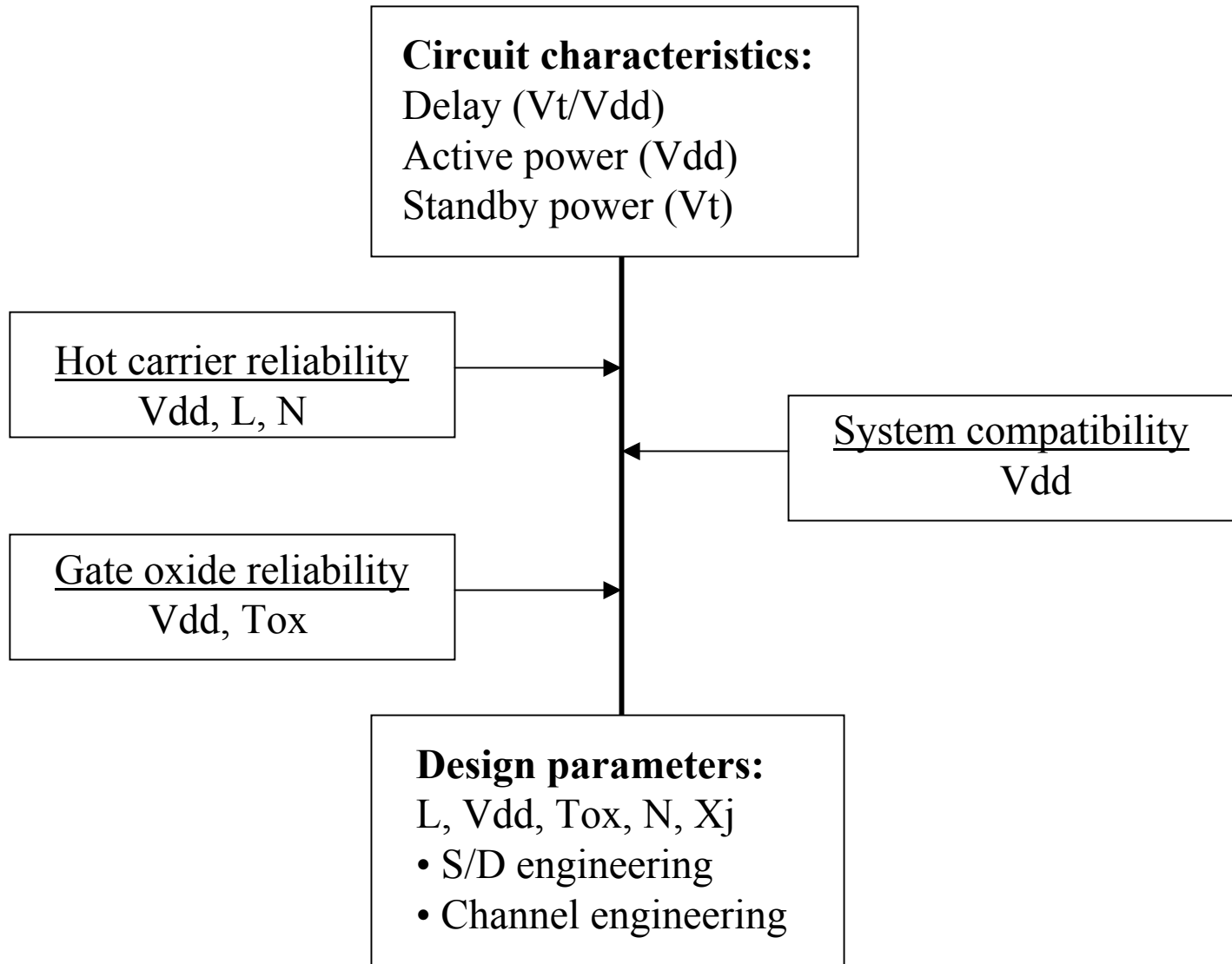Transistor design methodology for Digital Technology



Vt-Vdd design plane

Normalized delay

  

Delay increases significantly for $V_t/V_{dd} > 0.4$


$$P_{active} (P_{ac}) = CV_{dd}^2f$$

$$P_{standby} (P_{sb}) = WV_{dd}I_{off}$$

Delay and Power are the only trade-off points for digital design

Analog Circuit Performance Metrics

The Analog Octagon:

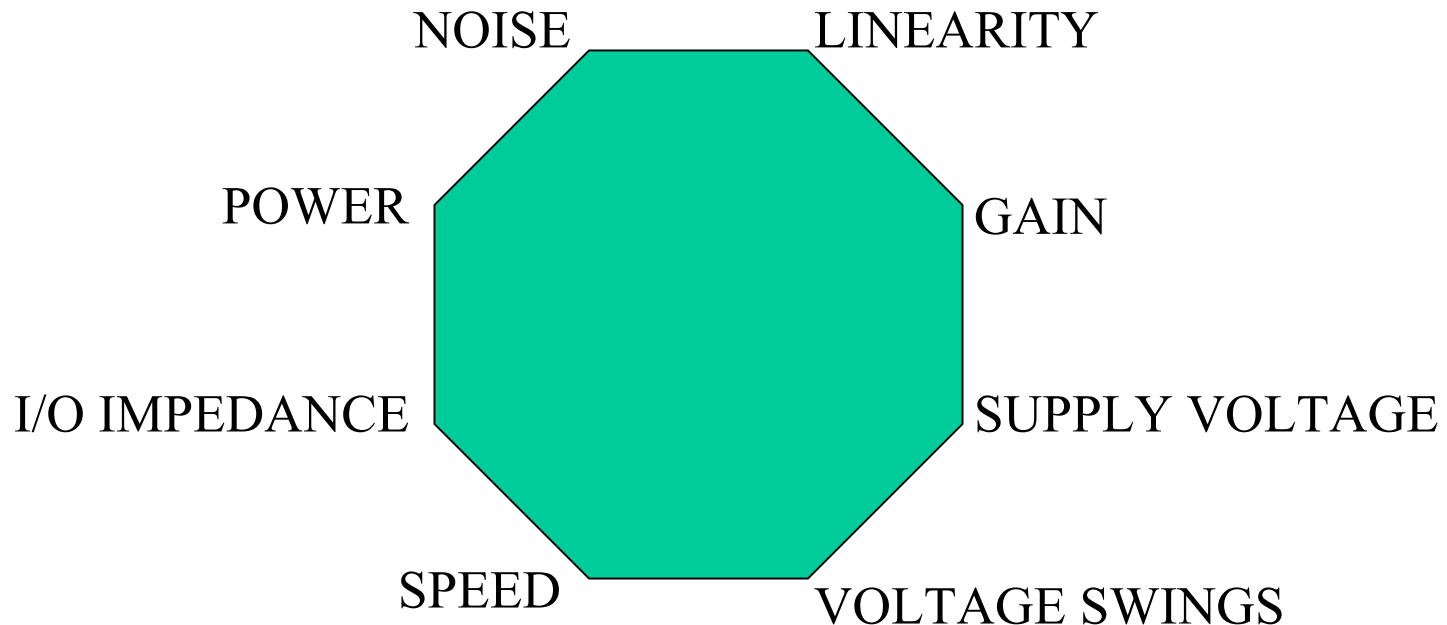

B. Razavi

Multiple trade-offs involved in Analog Design make it very complex

Small Signal parameters for MOSFET


AC Small Signal Parameters

Small signal parameters are derived from DC equations

The value of the small signal parameters is a function of the DC bias point

MOSFET is assumed to be square law device under saturation, i.e. no velocity saturation effect

 
L is metallurgic channel length, $L = L_g - 2L_D$



L entered in SPICE is L_g . Internally SPICE will subtract $2L_D$ to model the transistor

Low Frequency Model

 NEGLECT CAPACITANCES IN LOW FREQUENCY MODEL



g_m , g_{mb} and g_o are the 3 conductance parameters

Transconductance, g_m




$$g_m = \frac{i_{ds}}{v_{gs}} = \frac{\partial I_{ds}}{\partial V_{gs}}, \text{ with constant } V_{ds}, V_{sb}$$

$$g_m = \frac{\mu \epsilon_{ox} W (V_{gs} - V_t) (1 + \lambda V_{ds})}{LT_{ox}}$$

$$g_m = \sqrt{\frac{2\mu \epsilon_{ox} W I_{ds} (1 + \lambda V_{ds})}{LT_{ox}}}$$

$$g_m = \frac{2I_{ds}}{V_{gs} - V_t}$$

 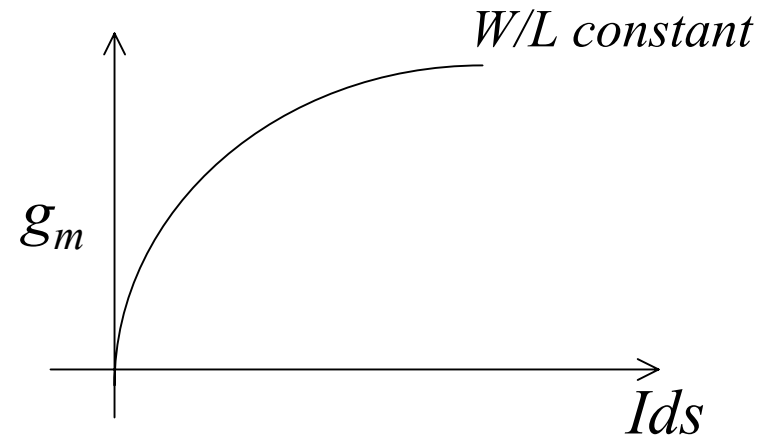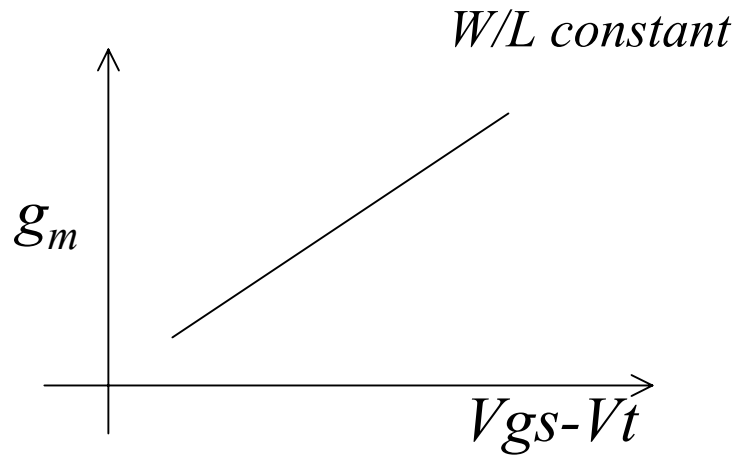g_m versus device dimension and bias point



In order to obtain large g_m ,
the input/output swing
trades-off with the transistor size


Body effect transconductance, g_{mb}

$$g_{mb} = -\frac{i_{ds}}{v_{sb}} = -\frac{\partial I_{ds}}{\partial V_{sb}} = -\frac{\partial I_{ds}}{\partial V_t} \frac{\partial V_t}{\partial V_{sb}}, \quad \text{with constant } V_{ds}, V_{gs}$$

$$g_{mb} = \frac{\gamma}{2\sqrt{2|\phi_b| + V_{sb}}} g_m = \frac{C_s}{C_{ox}} g_m = \eta g_m$$

η Is typically between 0.1 to 0.3

The back gate effect

 

- The body terminal acts as the back gate
- However, the front gate is more efficient in controlling the channel compared to back gate
- This is achieved through the proper design of the MOS transistor

Output conductance, g_o

$$g_o = \frac{i_{ds}}{v_{ds}} = \frac{\partial I_{ds}}{\partial V_{ds}} = \frac{\partial I_{ds}}{\partial L_{eff}} \frac{\partial L_{eff}}{\partial V_{ds}}, \quad \text{with constant } V_{gs}, V_{sb}$$

$$g_o = \lambda \frac{\mu \epsilon_{ox} W (V_{gs} - V_t)^2}{2LT_{ox}}$$

$$g_o = \frac{\Delta}{2(L - \Delta)(V_{ds} - V_{dsat})} I_{ds}, \quad \text{more rigorous analysis}$$

To simplify modeling, λ is assumed to be independent of V_{ds}

$$g_o \approx 0.01 g_m$$

The output conductance is inversely proportional to L

Typical values for 0.35 μ m Technology

$3.3V, L=0.35\mu m, W=0.7\mu m, T_{ox}=7nm, V_{t0}=0.6V,$

$V_{gs}-V_t=1V$

$$g_m \sim 10^{-4} \text{ A/V}$$

$$1 / g_m \sim 10 \text{ k}\Omega$$


$$g_{mb} \sim 0.1 g_m \sim 10^{-5} \text{ A/V}$$

$$1 / g_{mb} \sim 100 \text{ k}\Omega$$

$$g_o \sim 0.01 g_m \sim 10^{-6} \text{ A/V}$$

$$1 / g_o \sim 1000 \text{ k}\Omega$$

MOS Capacitances

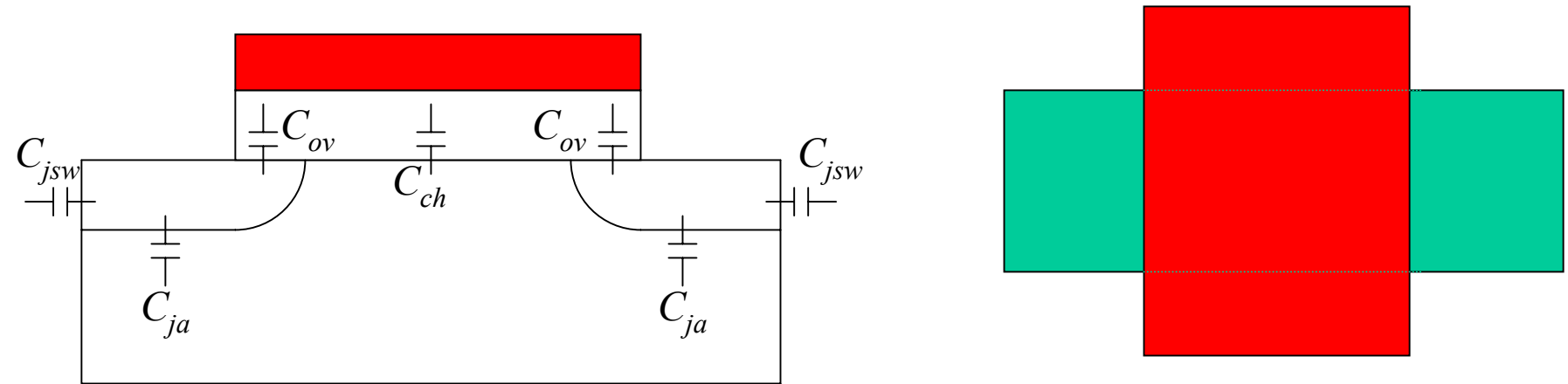

C_{ch} is split between source/drain depending on biasing condition

$C_{ov} = nWL_D C_{ox}$ where $1 < n < 2$ due to fringing and $C_{ox} = \epsilon_{ox} / T_{ox}$

C_{ja} = area component of junction depletion capacitance

C_{jsw} = side wall component of junction depletion capacitance

MOS capacitances

$$C_{sb} = AS * C_{ja}(V_{sb}) + PS * C_{jsw}(V_{sb})$$

$$C_{db} = AD * C_{ja}(V_{sb}) + PD * C_{jsw}(V_{sb})$$


AS, PS source area, perimeter; AD, PD drain area, perimeter

In saturation:

$$C_{gs} = \frac{2}{3} WL_{eff} C_{ox} + nWL_D C_{ox} \quad C_{gd} = nWL_D C_{ox}$$

In linear region:
 
$$C_{gs} = C_{gd} = \frac{WLC_{ox}}{2} + nWL_D C_{ox}$$



Typical capacitance values

For $L=0.35\mu\text{m}$ and $W=1\mu\text{m}$, Junction width = $0.7\mu\text{m}$

$$C_{ox}=4.3\text{fF}/\mu\text{m}^2 \quad \text{and} \quad C_{ja}=1\text{fF}/\mu\text{m}^2$$

$$C_{db}=C_{sb}=0.7\text{fF}$$


In saturation:

$$C_{gs}=1.1\text{fF} \quad C_{gd}=0.2\text{fF}$$

In linear region:

$$C_{gs}=C_{gd}=0.8\text{fF}$$

Small signal equivalent circuit

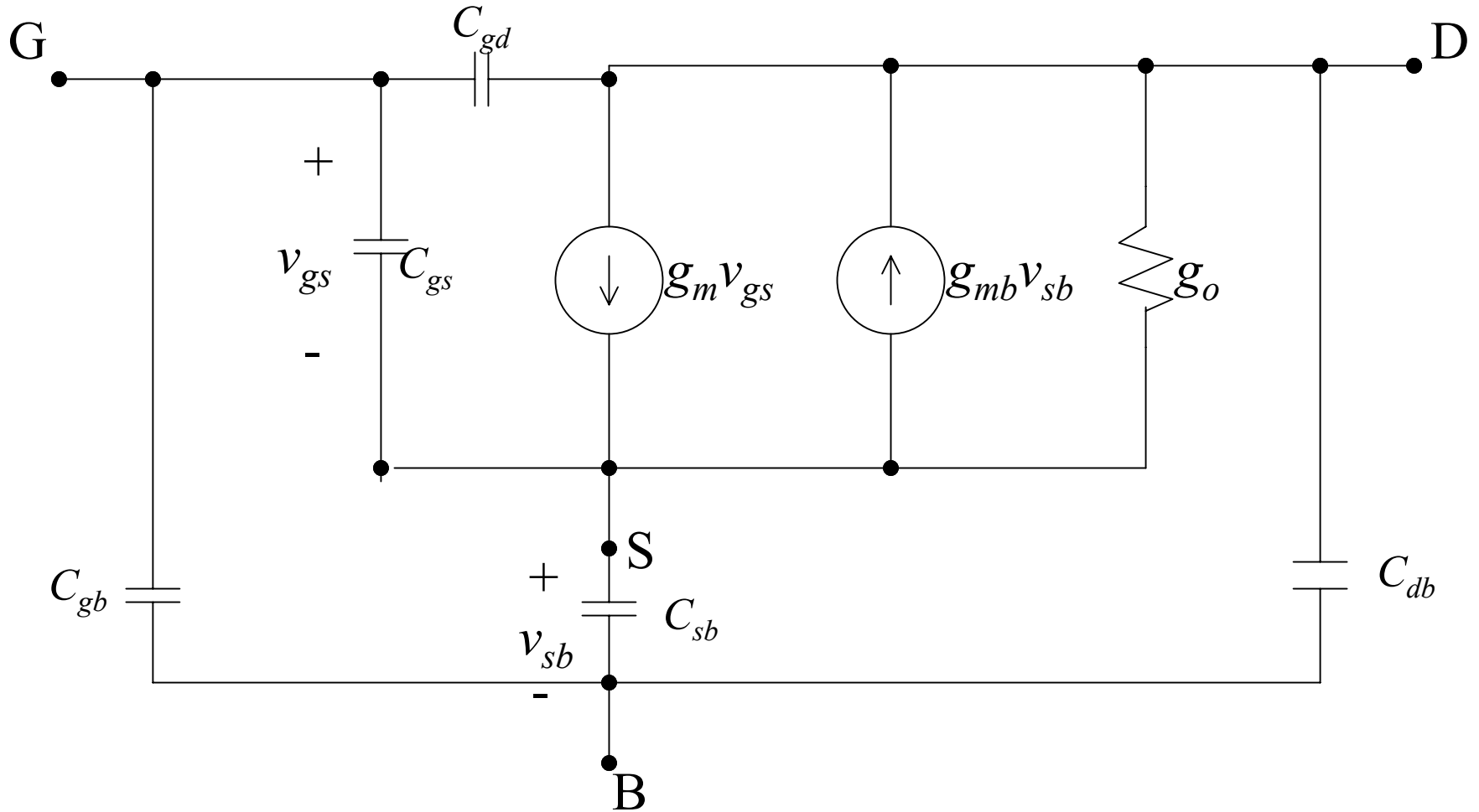

Gate to bulk capacitance C_{gb} is insignificant and hence neglected


Cut-off frequency

Cut off frequency (Transition frequency)

$$f_t = f \Big|_{i_{out}=i_{in}} \quad , \text{ with } Z_L=0$$

At f_t , the out put short circuit current gain is unity

 f_t is the performance metric of transistor for high frequency operation



$$i_{in} = sC_{gs}v_{gs} + sC_{gd}v_{gs}$$

$$i_{out} = g_m v_{gs} - sC_{gd}v_{gs}$$

$$\text{At } s=j\omega_t=2\pi f_t, |i_{out}|=|i_{in}|$$

$$\omega_t = \frac{g_m}{C_{gs} \sqrt{1 + \frac{2C_{gd}}{C_{gs}}}}$$

$$f_t = \frac{1}{2\pi} \omega_t$$

Scaling trend for f_t

$$f_t \cong \frac{1}{2\pi} \frac{g_m}{C_{gs}}$$

Technology scaling factor $k > 1$

Ideally g_m does not scale and C scales as $1/k$
hence f_t increases by a factor k


However, if V_t is not scaled due to leakage constraints then g_m will decrease in DSM regime, thus affecting the scaling trend

In cascaded voltage gain stages f_t forms the upper limit for the *unity gain-bandwidth*

Concept of Poles and Zeros

Poles and Zeros

 The transfer function $H(s)$ of any system can be represented as



$$H(s) = \frac{\left(1 - \frac{s}{z_1}\right)\left(1 - \frac{s}{z_2}\right)\dots}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)\dots}$$

z_1, z_2, \dots are zeros and p_1, p_2, \dots are the poles of the system

Physical Significance of Poles and Zeros


Poles

- Any capacitance which shunts the input-to-output signal path to ground results in a pole for the circuit
- Theoretically every node in the I/O signal path introduces a pole
- The poles degrade the high frequency response of the circuit

Zeros

- Any capacitance which appears in the input-to-output signal path results in a zero for the circuit
- The zeros enhance the high frequency response of the circuit
- The zeros degrade the low frequency response of the circuit

Impact of Pole

 


$$\frac{V_o}{V_i} = \frac{1/sC}{R + 1/sC}$$

$$\frac{V_o}{V_i} = \frac{1}{1 - s/(-1/RC)}$$

The pole is on the left half of s plane (i.e. $s = -1/RC \Rightarrow$ *stable system*)



The pole frequency $\omega_p = 1/RC$

 

Gain and Phase response due to pole

$$G = 20 \log \left| \frac{V_o}{V_i} \right| = -20 \log \left[\sqrt{1 + \left(\omega / \omega_p \right)^2} \right]$$
  
$$\phi = -\tan^{-1} \left[\frac{\omega}{\omega_p} \right]$$



At ω_p the gain is 3dB lower


Beyond ω_p , the gain decreases at a rate of -20dB/decade

At ω_p the the phase shift is -45°

At $0.1\omega_p$ the the phase shift saturates to 0°

At $10\omega_p$ the the phase shift saturates to -90°

Impact of zero

 


$$\frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \frac{1 + sR_1C_1}{1 + \frac{sR_1R_2C_1}{R_1 + R_2}}$$

$$\frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \frac{1 - \frac{s}{(-1/R_1C_1)}}{1 - \frac{s}{-(R_1 + R_2)/R_1R_2C_1}}$$

$$z = -1/R_1C_1 \text{ and } p = -(R_1 + R_2)/R_1R_2C_1$$

The zero frequency $\omega_z = 1/R_1C_1$


 


Gain and Phase response due to zero

$$G = 20 \log \left| \frac{V_o}{V_i} \right| = G_o + 20 \log \left[\sqrt{1 + \left(\omega / \omega_p \right)^2} \right]$$

$$\phi = \tan^{-1} \left[\frac{\omega}{\omega_p} \right]$$
  
$$G_o = 20 \log \left[\frac{R_2}{R_1 + R_2} \right]$$



At ω_z the gain is 3dB higher

At ω_z the the phase shift is 45°


Beyond ω_z , the gain increases at a rate of 20dB/decade

At $0.1\omega_z$ the the phase shift saturates to 0°

At $10\omega_z$ the the phase shift saturates to 90°

Miller Approximation

Miller's Theorem

 

If the circuit in (a) can be converted into that of (b) then


$$Z_1 = \frac{Z}{1 - A_v} \quad \text{and} \quad Z_2 = \frac{Z}{1 - A_v^{-1}}, \quad \text{where} \quad A_v = \frac{V_y}{V_x}$$

Proof: For the two circuits to be equivalent, the current flowing through Z from X to Y in (a) should be same as current flowing through Z1 in (b)


$$\frac{V_x - V_y}{Z} = \frac{V_x}{Z_1} \Rightarrow Z_1 = \frac{Z}{1 - \frac{V_y}{V_x}} \quad \text{Similarly,} \quad Z_2 = \frac{Z}{1 - \frac{V_x}{V_y}}$$

Caveats of Miller's Theorem

 If the impedance Z forms the only signal path between X and Y ,
Then the conversion is not valid




$$A_v = \frac{R_2}{R_1 + R_2}$$

 

The output gain is no longer preserved in the modified circuit

The zeros in the transfer functions are discarded by Miller's transformation

 
The theorem proves useful when the impedance is in parallel with main signal path



Single stage amplifier

- Common Source
 - Resistive load
 - Diode connected load
 - PMOS current source load
 - Source degeneration
- Source Follower
- Common Gate
- Cascode
- Folded Cascode

Common Source with Resistive load

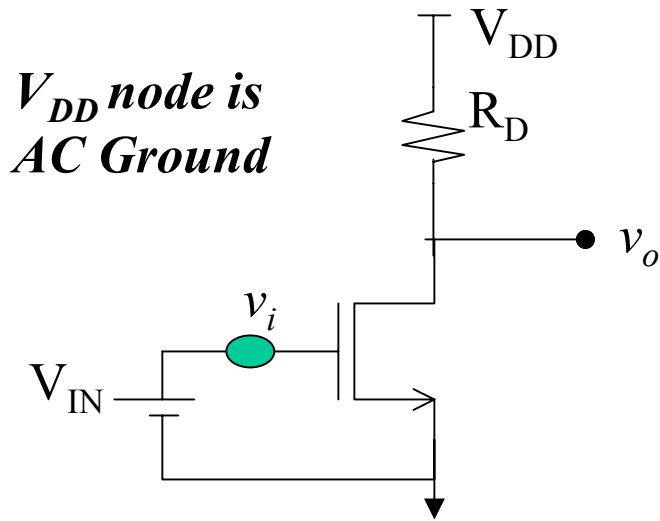


DC bias point

Transistor is kept in saturation in order to maximise g_m and r_o and hence the gain

$$V_{in} = V_{gs}$$

$$I_{ds} = \frac{\mu\epsilon_{ox}W}{T_{ox}L} \frac{(V_{gs} - V_t)^2}{2} (1 + \lambda V_{ds})$$

$$V_{DD} = I_{ds}R_D + V_{ds}$$

 

If there is any output load capacitance, that should be added with C_{db}

AC analysis

Applying KCL at the output node:

$$(v_o - v_i)sC_{gd} + g_m v_i + (g_o + G_D + sC_{db})v_o = 0$$

DC gain at $s=0$:

$$A_v(0) = -\frac{g_m}{g_o + G_D} = -g_m \frac{r_o R_D}{r_o + R_D}$$

The gain at high frequency:

$$A_v(0) = -\frac{g_m}{g_o + G_D} \frac{1 - sC_{gd} / g_m}{1 + s(C_{db} + C_{gd}) / (g_o + g_L)}$$

$$z_1 = g_m / C_{gd} \quad \text{and} \quad p_1 = -(g_o + G_L) / (C_{db} + C_{gd})$$

NOTE: Miller's theorem also gives the same pole frequency

Important Trade-offs

The maximum DC gain can never exceed the intrinsic gain of the transistor which is given by $g_m r_o$ (For sub micron transistor, the typical intrinsic gain is around 30)

In the limit $R_D < r_o$, The gain increases with increasing R_D and is Approximately equal to $g_m R_D$




High R_D also results in lower pole frequency and hence the band width

High R_D also results in smaller allowable output voltage swings because Transistor come out of saturation when $V_{DD} - V_{RD} < V_i - V_t$

If attempt to decrease V_{RD} by decreasing $V_{gs} - V_t$ and increasing W/L (thereby keeping g_m constant and decreasing I_d), the input pole can become Dominant, the input swing decreases, large area overhead on Silicon

The gain is a strong function of g_m , which in turn depends on V_{gs} . This results is large non linearity when the input swings are large

Trade-off

   

WISHLIST

Need to make gain insensitive to the input swings

Need to decouple the DC bias point from the AC requirements

Diode connected load



Very inefficient to implement a large resistance in CMOS technology

Hence CS with resistive load is never implemented on CMOS



Diode connected transistor can act as a resistance

This configuration can make the gain a little more insensitive to input

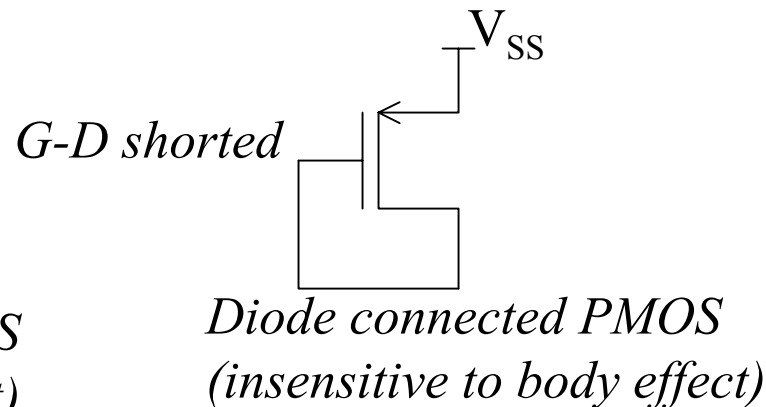 NMOS or PMOS diode connected load can be used



CS with diode connected load

  

Region 1: M1 linear, M2 saturation

Region 2: M1 saturation, M2 saturation


Region 3: M1 saturation, M2 cutoff

Region 1: M1 cutoff, M2 saturation

Region 2: M1 saturation, M2 saturation

Region 3: M1 linear, M2 saturation


Region 2 is useful operating region

 


AC analysis

For M2, C_{DB2} is shorted. $V_{gs2} = -V_o$ and $V_{sb} = V_o$

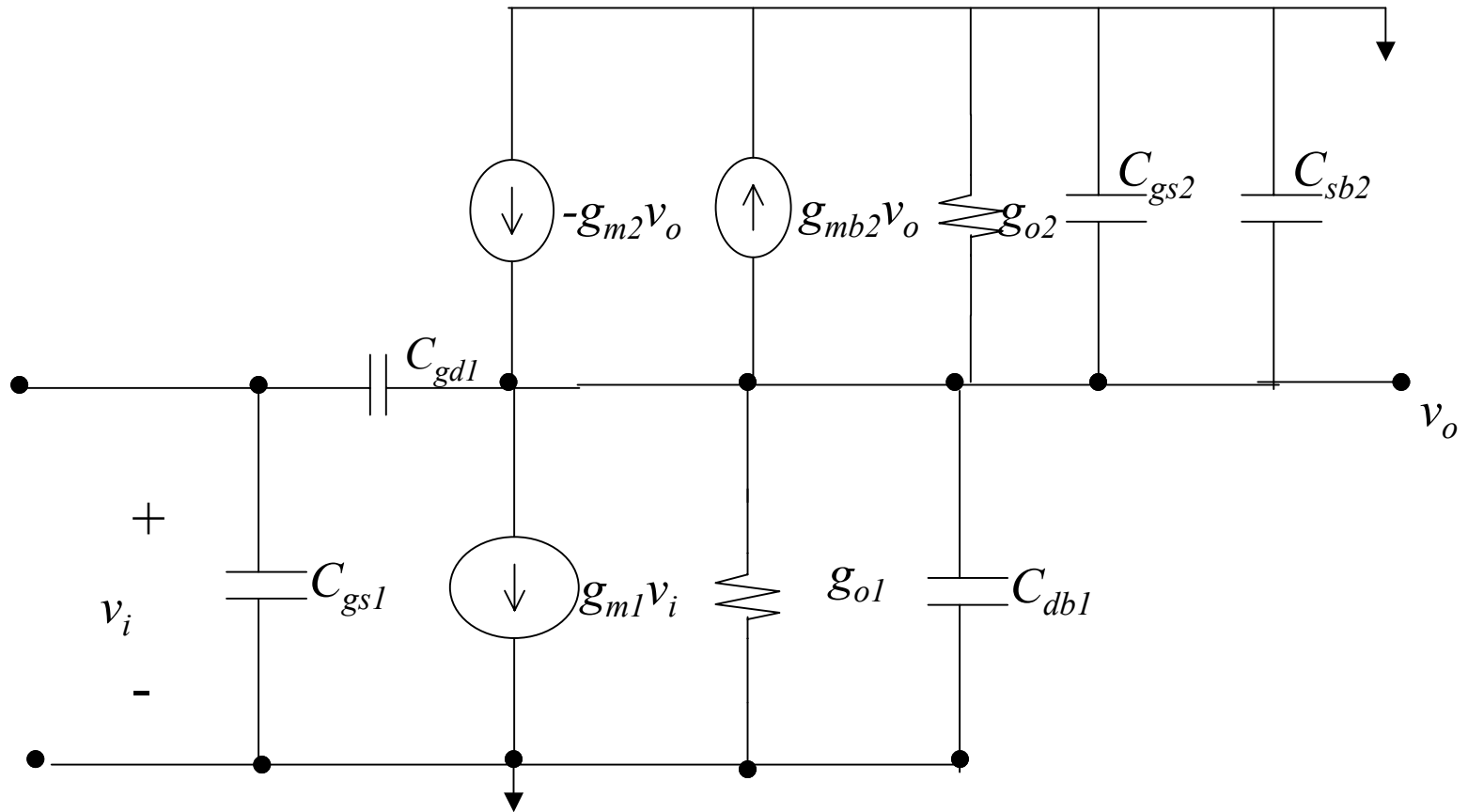If the controlling voltage for a voltage controlled current source, is the voltage across the VCS itself, then it reduces to a conductance



Low frequency gain

 

Applying KCL at the output node:

$$(v_o - v_i)sC_{gd1} + g_{m1}v_i + (g_T + sC_T)v_o = 0$$

DC gain at $s=0$:

$$A_v(0) = -\frac{g_{m1}}{g_T} = -\frac{g_{m1}}{g_{m2} + g_{mb2} + g_{o1} + g_{o2}} \approx -\frac{g_{m1}}{g_{m2}(1 + \eta_2)}$$

The impedance seen looking into the source of the diode connected MOS transistor is $\sim 1/g_m$

Insensitivity of gain to input swing

The DC bias current $I_{ds1} = I_{ds2}$,

$$\frac{g_{m1}}{g_{m2}} = \frac{V_{gs2} - V_{t2}}{V_{gs1} - V_{t1}}, \quad \text{since} \quad g_m = \frac{2I_{ds}}{V_{gs} - V_t}$$

Replacing $V_{gs} - V_t$ in terms of g_m and W/L


$$\frac{g_{m1}}{g_{m2}} = \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

$$A_v(0) = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{(1 + \eta_2)}$$

The gain is essentially controlled by device dimension which are the design parameters under the control of the designer

There is some sensitivity on body bias

Body bias insensitivity using PMOS load

 

Since the body and the source of PMOS are connected to V_{DD} node, $V_{sb}=0$ and hence the body bias trans-conductance term becomes zero

$$A_v(0) = -\sqrt{\frac{(W/L)_1 \mu_n}{(W/L)_2 \mu_p}}$$

Where μ_n/μ_p is the ratio of electron and hole mobility
 $\mu_n/\mu_p \sim 2$ to 3

Trade off between gain and output swing

This trade off is not eliminated even in diode connected load


$$A_v(0) \approx \frac{V_{gs2} - V_{t2}}{V_{gs1} - V_{t1}}$$

Suppose $V_{DD}=3.5V$, $V_{t1} = V_{t2}=0.4V$, and gain is required to be 30

Let $V_{gs1}-V_t=0.1V$ in order to maximise output swing (i.e. $V_{IN}=0.5V$)

Then, $V_{gs2}-V_t=3V$ i.e. $V_{gs2}=V_{ds2}=3.4V$

 Hence $V_o=V_{ds2}=0.1V$ which is just at the verge of saturation.



The necessity for higher gain makes the bias point unfavourable to output swing

High Frequency gain

$$A_v(s) = - \frac{g_{m1}}{g_{m2} + g_{mb2} + g_{o1} + g_{o2}} \frac{1 - \frac{sC_{gd1}}{g_{m1}}}{1 + \frac{s(C_{gd1} + C_{db1} + C_{gs2} + C_{sb2})}{g_{m2} + g_{mb2} + g_{o1} + g_{o2}}}$$

$$z = \frac{g_{m1}}{C_{gd1}}$$

$$p = - \frac{g_{m2} + g_{mb2} + g_{o1} + g_{o2}}{C_{gd1} + C_{db1} + C_{gs2} + C_{sb2}}$$

Gain bandwidth product:


$$\frac{1}{2\pi} |A_v(0)| \omega_p = \frac{1}{2\pi} \frac{g_{m1}}{C_{gd1} + C_{db1} + C_{gs2} + C_{sb2}}$$

The relative location of pole and zero


$$\left| \frac{p}{z} \right| = \frac{C_{gd1} (g_{m2} + g_{mb2} + g_{o1} + g_{o2})}{g_{m1} (C_{gd1} + C_{db1} + C_{gs2} + C_{sb2})}$$

$$\left| \frac{p}{z} \right| = \frac{1}{A_v(0)} \frac{1}{1 + \frac{C_{db1} + C_{gs2} + C_{sb2}}{C_{gd1}}} \ll 1$$

 i.e. The amplifier works as a single pole transfer function with the dominant pole and insignificant zero location



CS amplifier with current source load

 

In order to remove the trade-off between the gain versus the output swing, the DC resistance should be decoupled from AC impedance of the load!

i.e. use a constant current source load

Remove the trans-conductance contribution to AC resistance by fixing G & S voltage

M2 in the above circuit acts as a constant current source as long as it is in saturation condition $|V_{ds}| > |V_{gs} - V_t|$

$$I_{ds} = \frac{\mu\epsilon_{ox}W}{T_{ox}L_{eff}} \frac{(V_{DD} - V_{GB} - V_t)^2}{2}$$


$$R_{ac} = \frac{1}{g_{o2}}$$

Small signal equivalent circuit


For M2,

C_{gs} and C_{sb} are shorted

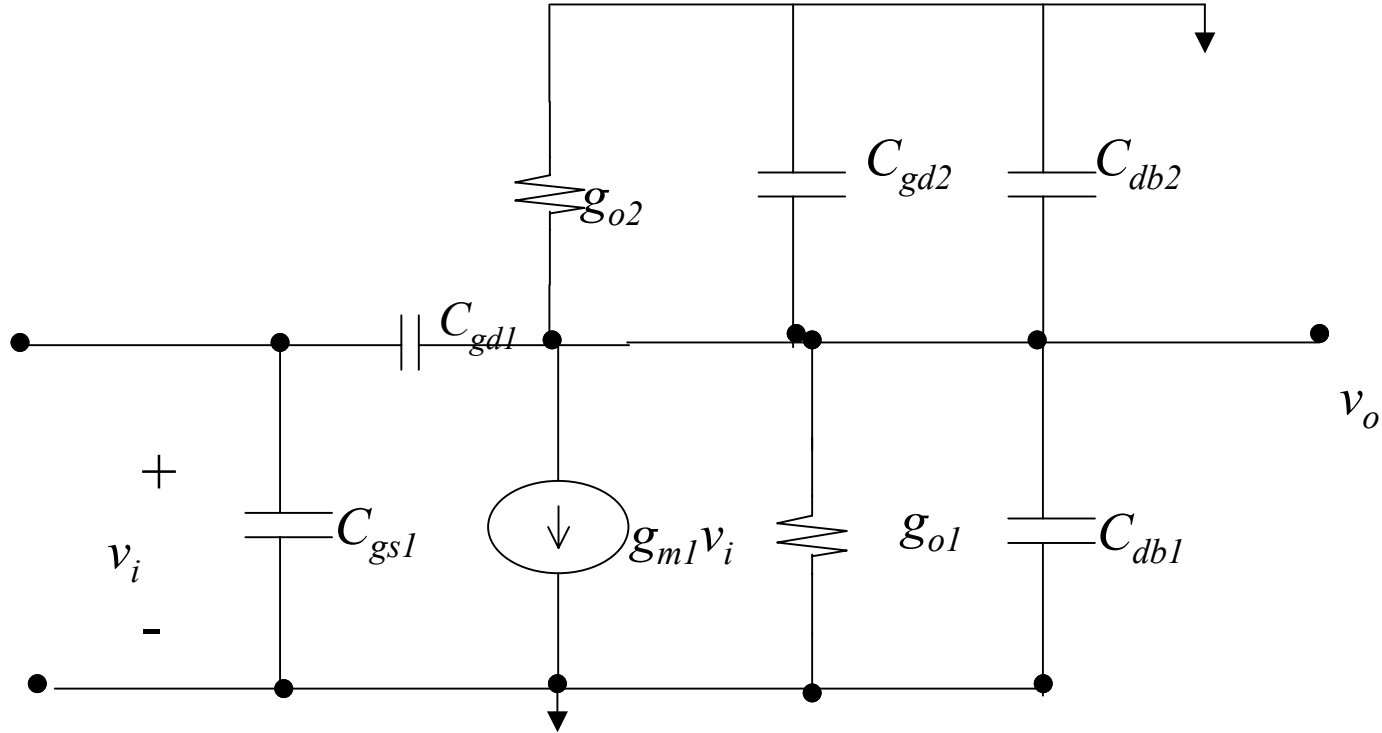v_{gs2} and v_{sb2} are zero and hence the corresponding g_m terms are absent



Low frequency gain

 

Applying KCL at the output node:

$$(v_o - v_i)sC_{gd1} + g_{m1}v_i + (g_T + sC_T)v_o = 0$$

DC gain at $s=0$:

$$A_v(0) = -\frac{g_{m1}}{g_T} = -\frac{g_{m1}}{g_{o1} + g_{o2}}$$

The impedance seen looking into the current source MOSFET load transistor is $\sim 1/g_o$

High Frequency gain

$$A_v(s) = -\frac{g_{m1}}{g_{o1} + g_{o2}} \frac{1 - \frac{sC_{gd1}}{g_{m1}}}{1 + \frac{s(C_{gd1} + C_{db1} + C_{gd2} + C_{db2})}{g_{o1} + g_{o2}}}$$

$$z = \frac{g_{m1}}{C_{gd1}}$$

$$p = -\frac{g_{o1} + g_{o2}}{C_{gd1} + C_{db1} + C_{gd2} + C_{db2}}$$

Gain bandwidth product:

$$\frac{1}{2\pi} |A_v(0)| \omega_p = \frac{1}{2\pi} \frac{g_{m1}}{C_{gd1} + C_{db1} + C_{gd2} + C_{db2}}$$

Comparison with diode connected load

↑ Low frequency gain $A_v(0)$ is higher

↑ 3 dB bandwidth is lower

↑ Gain-bandwidth product may be slightly higher

↑ Larger output swing without sacrificing gain



— Dominant pole transfer function similar to diode connected load

↓ Gain is dependent on DC bias condition (g_m)

CS with source degeneration

The low frequency behaviour is affected

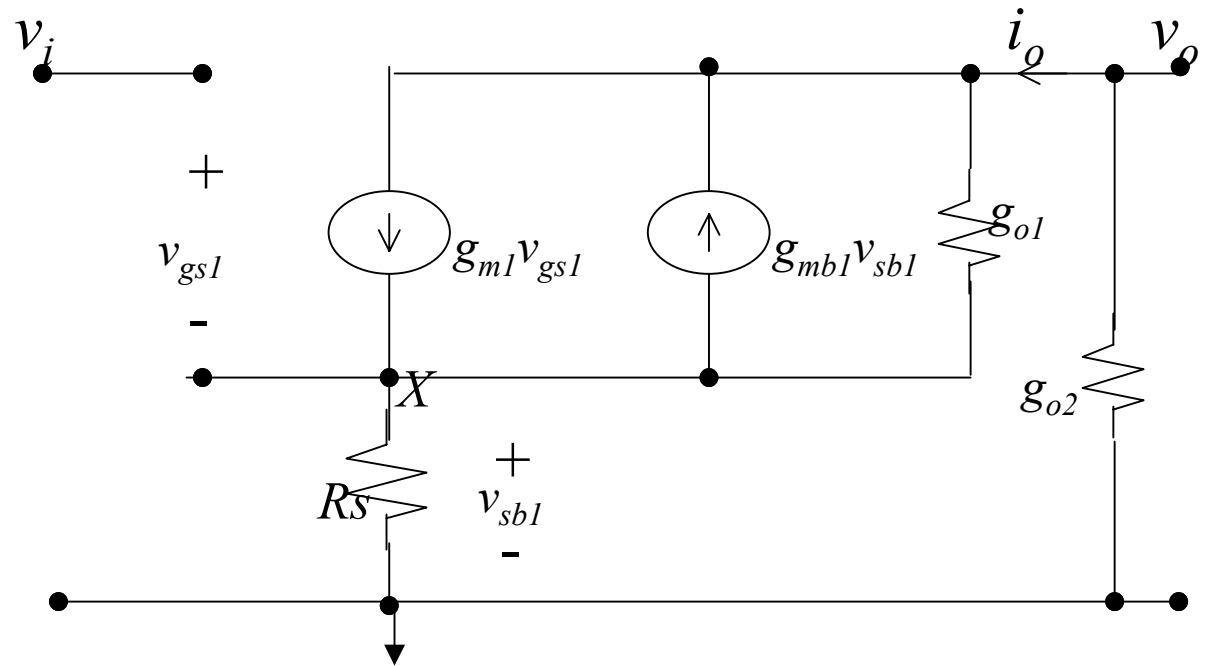 The small signal equivalent at low frequency:



Low Frequency gain

$$i_o = -v_o g_{o2}$$

$$v_{sb} = i_o R_s$$

$$v_{gs1} = v_i - i_o R_s$$

Applying KCL at node X

$$i_o = g_{m1}(v_i - i_o R_s) - g_{mb1} i_o R_s + (v_o - i_o R_s) g_{o1}$$

$$A_v(0) = -\frac{g_{m1}}{g_{o1} + g_{o2} [1 + R_s (g_{m1} + g_{mb1} + g_{o1})]}$$

$$A_v(0) \approx -\frac{g_{m1}}{g_{o1} + g_{o2} g_{m1} R_s} = -\frac{1}{g_{o2} R_s}$$

Effect of source degeneration

The transconductance of M1 is de-rated from g_{m1} to $1/R_s$

The gain becomes insensitive to bias and input swing

The output resistance of M1 is increased by a factor $g_{m1}R_s$


This concept is used in several analog circuits to enhance the out put impedance

$$A_v(0) \approx - \frac{g_{m1}}{g_{m1}R_s \left(g_{o2} + \frac{g_{o1}}{g_{m1}R_s} \right)}$$

$$A_v(0) \approx - \frac{1}{R_s} \frac{1}{\left(\frac{1}{r_{o2}} + \frac{1}{r_{o1}g_{m1}R_s} \right)}$$

The pole frequency (high frequency response) is not affected

Source Follower (Common Drain)

 


Used as buffer device or level shifter

Provides current gain

Provides low output impedance

Voltage gain is almost unity

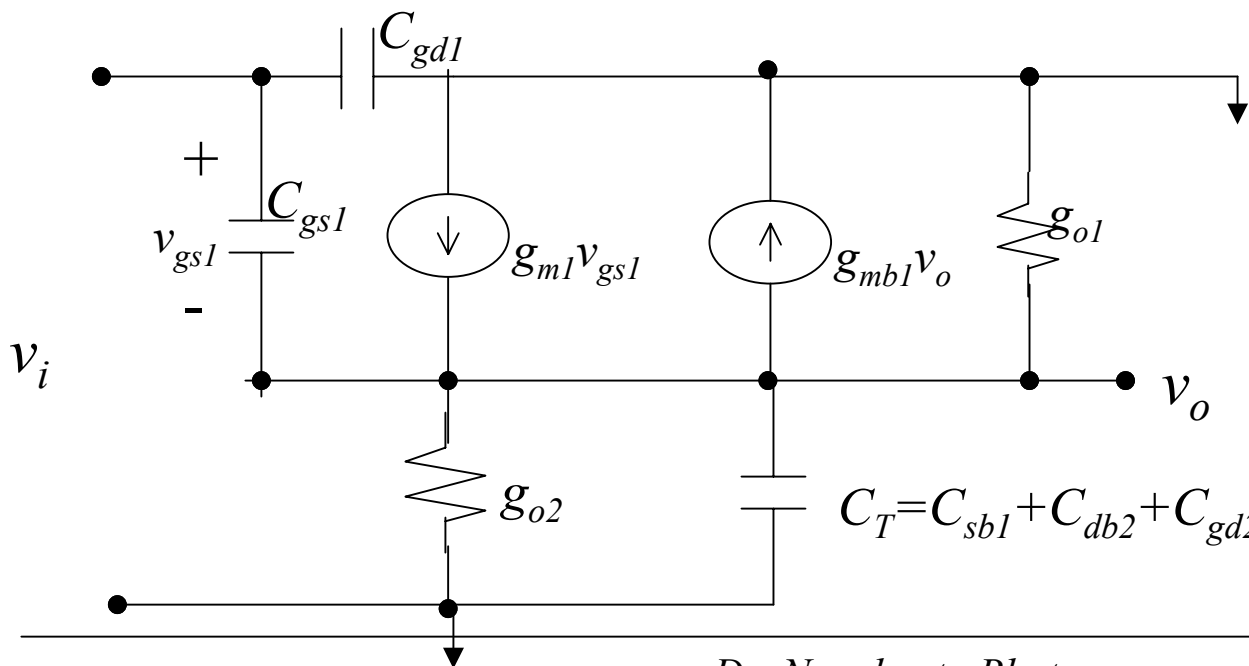

$$v_{gs1} = v_i - v_o$$

*g_{m2} and g_{mb2} do not appear since $v_{gs2} = v_{sb2} = 0$
 C_{gs2} and C_{sb2} are shorted*

Low frequency gain

Applying KCL at the output node

$$(g_{mb1} + g_{o1} + g_{o2} + sC_T)v_o = g_{m1}(v_i - v_o) + sC_{gs1}(v_i - v_o)$$

$$Av(0) = \frac{g_{m1}}{g_{m1} + g_{mb1} + g_{o1} + g_{o2}}$$

$$Av(0) \approx \frac{g_{m1}}{g_{m1} + g_{mb1}} = \frac{1}{1 + \eta}$$

Transistor M1 suffers from body effect, I.e. $V_t = f(V_o)$, which results in significant non linearity in gain

In a twin well technology the gain can be made independent of η by connecting the body of M1 to the source of M1 and putting M1 in an isolated p-well

High frequency response

$$Av(0) = \frac{g_{m1}}{g_{m1} + g_{mb1} + g_{o1} + g_{o2}} \frac{1 + \frac{sC_{gs1}}{g_{m1}}}{1 + \frac{s(C_{gs1} + C_{sb1} + C_{gd2} + C_{db2})}{g_{m1} + g_{mb1} + g_{o1} + g_{o2}}}$$

$$z = -\frac{g_{m1}}{C_{gs1}} \quad p = -\frac{g_{m1} + g_{mb1} + g_{o1} + g_{o2}}{C_{gs1} + C_{sb1} + C_{gd2} + C_{db2}}$$

Both pole and zero are on the left half of S plane


The relative location depends on the values of different parameters

Broadband condition

$$|p|=|z|$$

$$\frac{g_{m1} + g_{mb1} + g_{o1} + g_{o2}}{C_{gs1} + C_{sb1} + C_{gd2} + C_{db2}} = \frac{g_{m1}}{C_{gs1}}$$
 
$$\frac{C_{gs1}}{C_{gs1} + C_{sb1} + C_{gd2} + C_{db2}} = A_v(0)$$




Relative location of pole and zero


In most of the cases $p < z$

since
 
$$C_{gs1} + C_{sb1} + C_{gd2} + C_{db2} > \frac{C_{gs1}}{A_v(0)}$$




Low frequency output resistance

 

Input source is shorted for output Resistance computation

A test voltage source V_x is applied at output node

$$R_o = V_x / I_x$$

 


$$I_x = V_x g_{m1} + V_x g_{mb1} + V_x g_{o1}$$

$$R_o = \frac{V_x}{I_x} = \frac{1}{g_{m1} + g_{mb1} + g_{o1}}$$


$$R_o \approx \frac{1}{g_{m1} + g_{mb1}}$$

Thevenin equivalent

 

$$A_v = \frac{v_o}{v_i} = \frac{1/g_{mb1}}{1/g_{m1} + 1/g_{mb1}} = \frac{g_m}{g_m + g_{mb}}$$

 
If the source follower is loaded by R_L such that $R_L < 1/g_{mb1}$



$$A_v = \frac{R_L}{1/g_{m1} + R_L}$$


Limitation of SF on previous stage

CS with current source load

 

$$V_{x_{min}} = V_i - V_t$$

CS with current source load, driving SF

 


$$V_{x_{min}} = V_{gs2} + V_{gs3} - V_t$$

Otherwise $M3$ comes out of saturation

The voltage swing at node X is reduced

Output impedance in presence of R_s

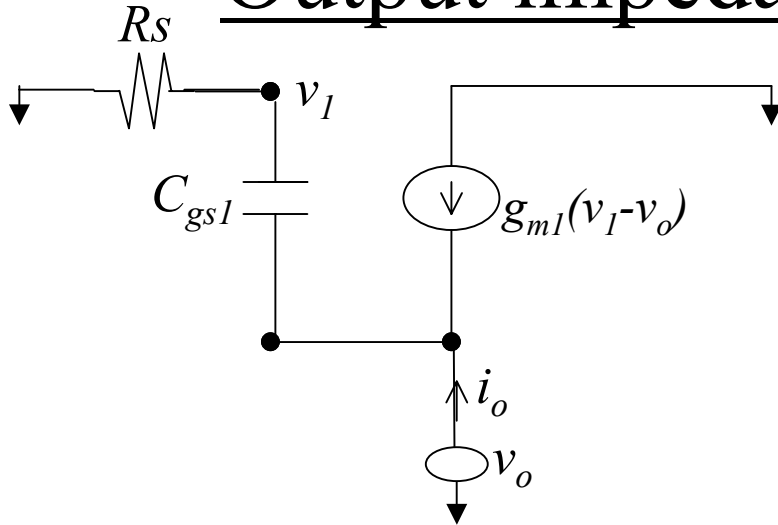

Assumptions:

$$g_{mb1} + g_{o1} + g_{o2} \ll g_{m1}$$

R_s is small compared to $1/sC_{gd1}$

Output shunt capacitance excluded

Applying KCL at output node

$$i_o + g_{m1}(v_1 - v_o) + sC_{gs1}(v_1 - v_o) = 0$$


using
$$\frac{v_1}{v_o} = \frac{R_s}{R_s + \frac{1}{sC_{gs1}}}$$

$$Z_o = \frac{v_o}{i_o} = \frac{1}{g_{m1}} \frac{1 + sR_s C_{gs1}}{1 + s \frac{C_{gs1}}{g_{m1}}}$$


$$Z_o(0) = 1/g_{m1} \text{ and } Z_o(\infty) = R_s$$

Variation of Z_o with ω
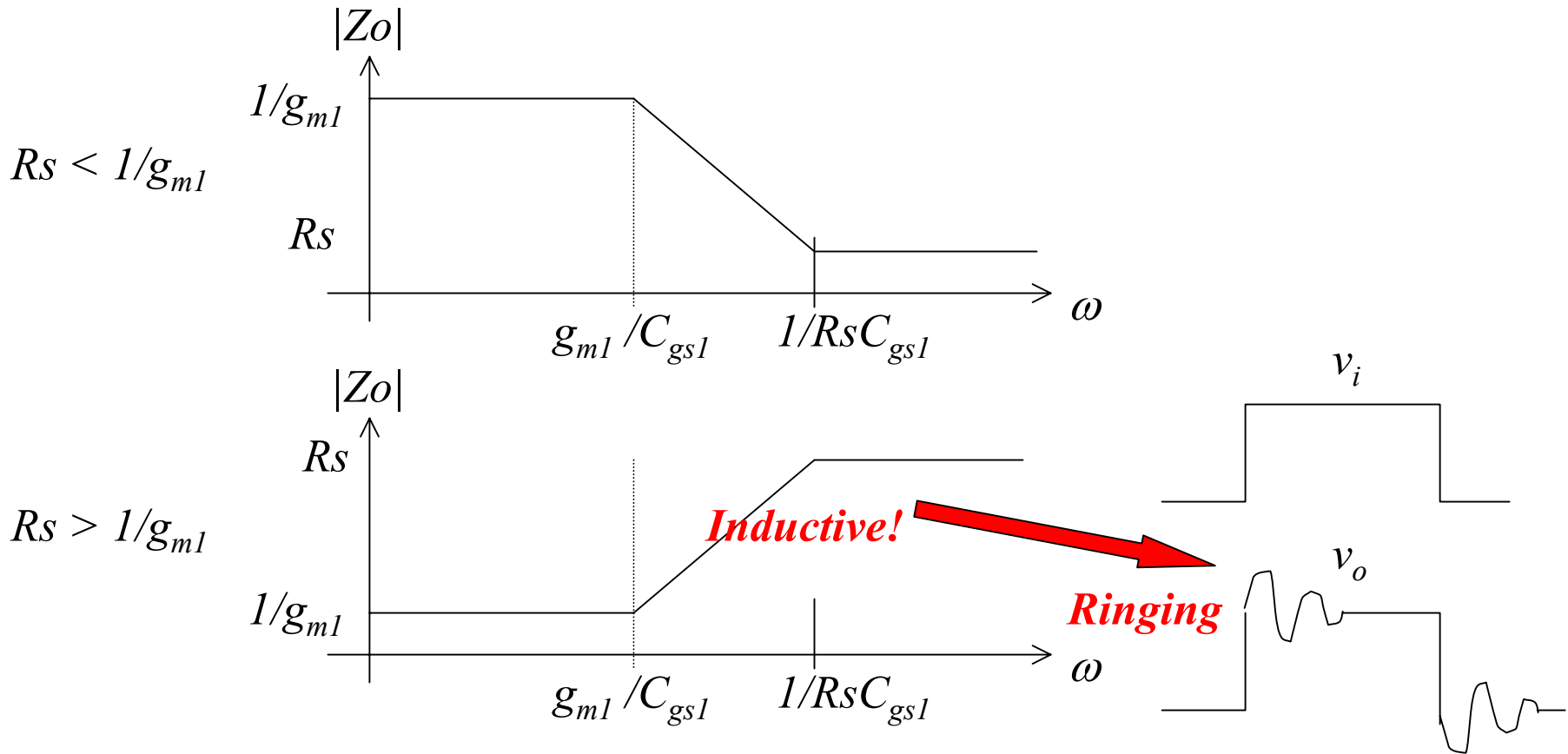
$$Z_o = \frac{v_o}{i_o} = \frac{1}{g_{m1}} \frac{1 + sR_s C_{gs1}}{1 + s \frac{C_{gs1}}{g_{m1}}}$$



Input Impedance Z_{in}

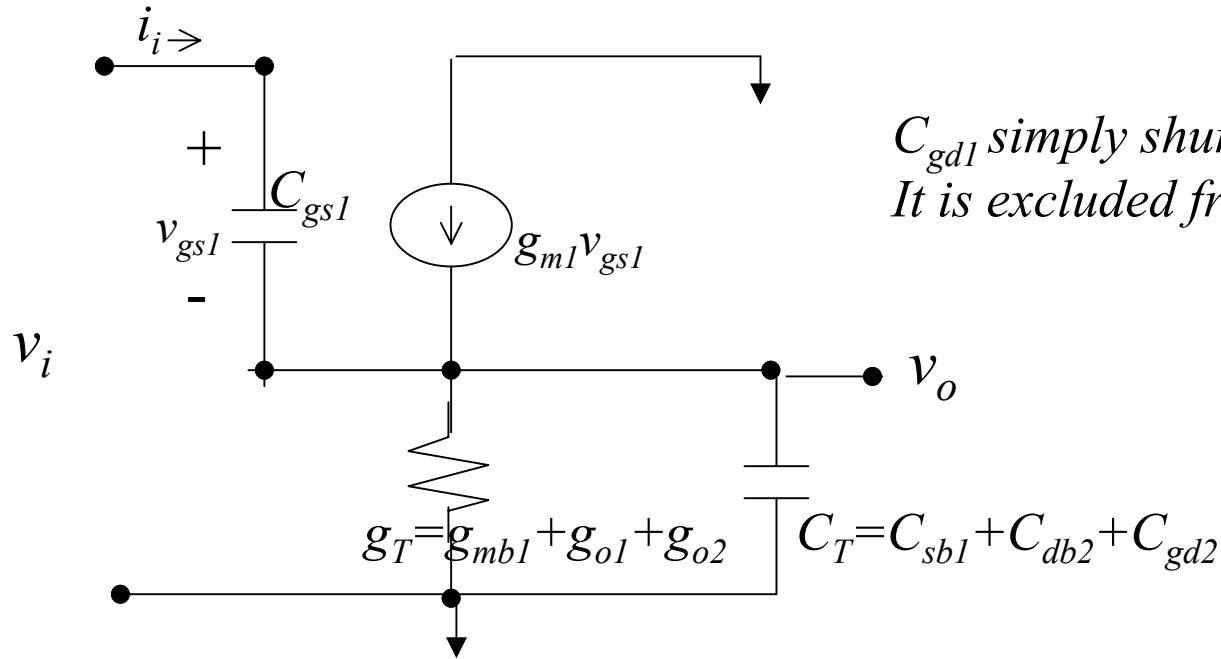

$$v_i = \frac{i_i}{sC_{gs1}} + \left(i_i + \frac{g_{m1}i_i}{sC_{gs1}} \right) \frac{1}{(g_T + sC_T)}$$

$$Z_{in} = \frac{v_i}{i_i} = \frac{1}{sC_{gs1}} + \left(1 + \frac{g_{m1}}{sC_{gs1}} \right) \frac{1}{(g_T + sC_T)}$$

Low Frequency dependence of Zi

For relatively low frequency, $sC_T \ll g_T$

$$Z_{in} = \frac{v_i}{i_i} = \frac{1}{sC_{gs1}} + \left(1 + \frac{g_{m1}}{sC_{gs1}}\right) \frac{1}{g_T}$$

$$Z_{in} = \frac{1}{g_T} + \frac{1}{sC_{gs1}} \left(1 + \frac{g_{m1}}{g_T}\right)$$

$$Z_{in} \approx \frac{1}{g_{mb1}} + \frac{1}{sC_{gs1}} \left(\frac{g_{m1} + g_{mb1}}{g_{mb1}}\right)$$

i.e. a fraction of C_{gs1} is felt at the input along with $1/g_{mb1}$


High Frequency dependence of Zi

For relatively low frequency, $sC_T \gg g_T$

$$Z_{in} = \frac{v_i}{i_i} = \frac{1}{sC_{gs1}} + \left(1 + \frac{g_{m1}}{sC_{gs1}}\right) \frac{1}{sC_T}$$

$$Z_{in} = \frac{1}{sC_{gs1}} + \frac{1}{sC_T} - \frac{g_{m1}}{\omega^2 C_{gs1} C_T}$$

**Negative
Resistance!**

 

At the input a series combination of C_{gs1} , C_T and a negative resistance is seen

This negative resistance could be exploited to build oscillators

Common Gate Amplifier



Provides large voltage gain

Current gain is about unity

Provides low input impedance

Provides high output impedance

Often used for impedance transformation

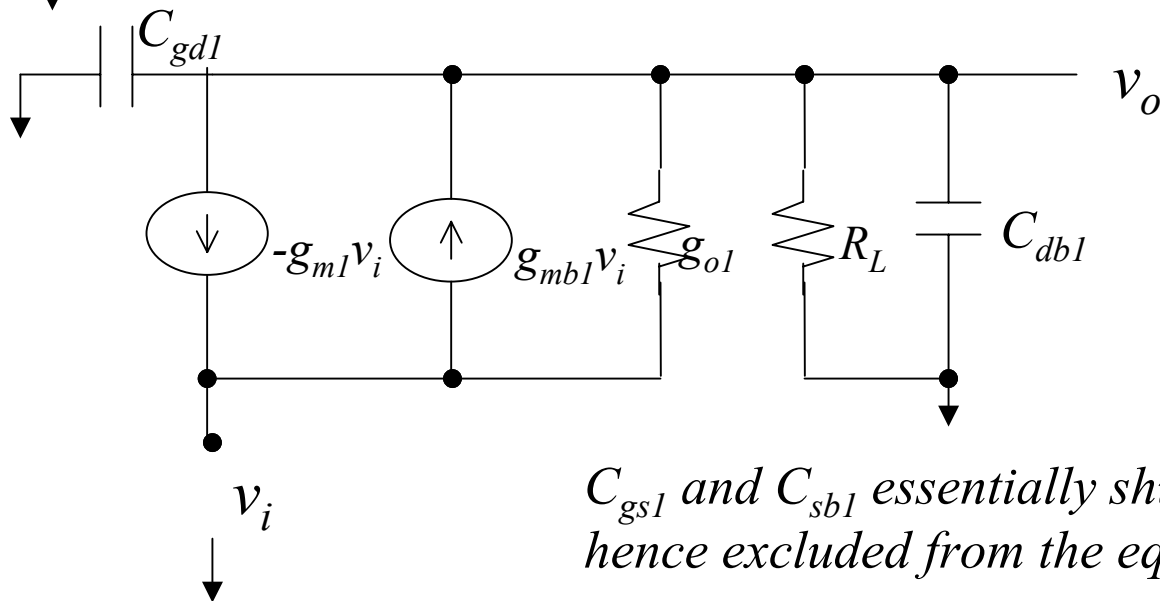 

C_{gs1} and C_{sb1} essentially shunt input and hence excluded from the equivalent ckt

Gain Expression

Applying KCL at the output node

$$(g_{m1} + g_{mb1})v_i + (v_i - v_o)g_{o1} = (G_L + sC_{db1} + sC_{gd1})v_o$$

$$A_v = \frac{v_o}{v_i} = \frac{g_{m1} + g_{mb1} + g_{o1}}{g_{o1} + G_L} \frac{1}{1 + \frac{s(C_{db1} + C_{gd1})}{g_{o1} + G_L}}$$

$$A_v(0) = \frac{g_{m1} + g_{mb1} + g_{o1}}{g_{o1} + G_L}$$

$$p = -\frac{g_{o1} + G_L}{C_{db1} + C_{gd1}}$$

The transfer function has single pole and no zero

Low frequency Input impedance


$$Z_{in} = \frac{v_i}{i_i} = \frac{1 + g_{o1}R_L}{g_{m1} + g_{mb1} + g_{o1}}$$

$$Z_{in} = \frac{1 + \frac{R_L}{r_{o1}}}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}}}$$

If $r_{o1} \gg R_L$ and $1/r_{o1} \ll g_{m1} + g_{mb1}$, then

$$Z_{in} = \frac{1}{g_{m1} + g_{mb1}}$$

Impedance Transformation

 


The impedance R_L can be transformed into $50\ \Omega$ at the input by making $1/(g_{m1} + g_{mb1}) = 50\ \Omega$

Cascode Amplifier

The term “cascode” is believed to be abbreviation of “cascaded triodes”

 Cascode is a combination of common source and common gate stage



M1 : Input Device

M2 : Cascode Device

Features of Cascode Amplifier

Output impedance increases

Intrinsic gain is squared

Shielding property :

Node X is desensitized w.r.t. o/p


Input pole, in presence of R_s , is pushed away

Output swing impacted due to stacking

$$V_{O_{min}} = V_{ds2} + V_{ds1}$$

Low frequency gain for low R_L

$$R_L \ll r_{o2\text{eff}}$$

 

The current flowing through the node X due to an input voltage v_i is $i_x = g_{m1}v_i$

The current through output node is same as i_x

$$i_o = i_x \quad v_o = i_x R_L$$

$$v_o = g_{m1}v_i R_L$$



$$Av(0) = g_{m1}R_L$$

This result is identical to common source stage

Low frequency gain for larger R_L

For an ideal current source load, the gain is dependent on the output resistance seen looking into drain of M2

  For computation of r_{o2} , M2 can be viewed as common source stage with source degeneration of r_{o1}



$$r_{o2eff} = (g_{m2}r_{o1})r_{o2}$$

The output impedance enhanced!


$$A_v(0) = g_{m1}g_{m2}r_{o1}r_{o2}$$

The intrinsic gain of cascode is the square of the CS stage

The increased output impedance is exploited in current mirror design

Input pole desensitisation

 The small signal equivalent, neglecting g_{o1} , g_{o2} and neglecting zero due to C_{gd1}



$$C_{T1} = C_{gs1} + C_{gd1}(1 + v_1/v_x) \quad , \quad \text{using Miller's theorem}$$

$$C_{T2} = C_{gs2} + C_{gd1} + C_{db1} + C_{sb2}$$

$$C_{T3} = C_{db2} + C_{gd2} + C_L$$

Gain Expression

$$A_v = -g_{m1} R_L \frac{1}{1 + sR_s C_{T1}} \frac{1}{1 + \frac{sC_{T2}}{(g_{m2} + g_{mb2})}} \frac{1}{1 + sR_L C_{T3}}$$

$$A_v(0) = -g_{m1} R_L$$

$$p_1 = -\frac{1}{R_s C_{T1}}$$

$$p_2 = -\frac{g_{m2} + g_{mb2}}{C_{T2}}$$

$$p_3 = -\frac{1}{R_L C_{T3}}$$

$C_{T1} = C_{gs1} + 2C_{gd1}$ since $v_1/v_x = 1$,


i.e. Miller capacitance at I/p is drastically reduced

Folded Cascode


Input and Cascode devices are complementary

Hence the current is either folded up or down

Avoids stacking of transistors

 

Current is folded down

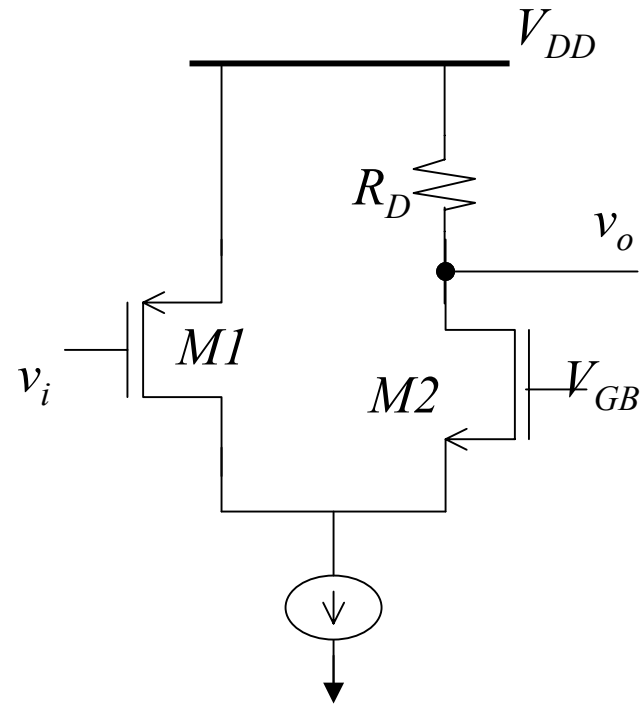

Current is folded up

Current Mirror

Basic configuration


Cascode Current Mirror

Wilson Current Mirror


Regulated Cascode

Basic Definitions



Current Source

 


Current Sink

 

Current Mirror

  


Current Lens

 

Often times, the term current mirror is used to include current lens

Simplest current source/sink

NMOS/PMOS transistor in saturation

 


$$I_o = \frac{\mu\epsilon_{ox}W}{T_{ox}L} \frac{(V_{GB} - V_t)^2}{2} (1 + \lambda V_o)$$

- Sensitive to variation in V_o (I.e. R_o is not infinity)
- Sensitive to variation in V_{GB}
- Sensitive to temperature variation (V_t , μ_n , μ_p)
- Sensitive to process variation (V_t , W , L , T_{ox})

Strategy: Create one very well defined current reference using complex temperature compensation and V_{DD} insensitivity. Then use current mirrors (copy) to generate others

Basic Current Mirror

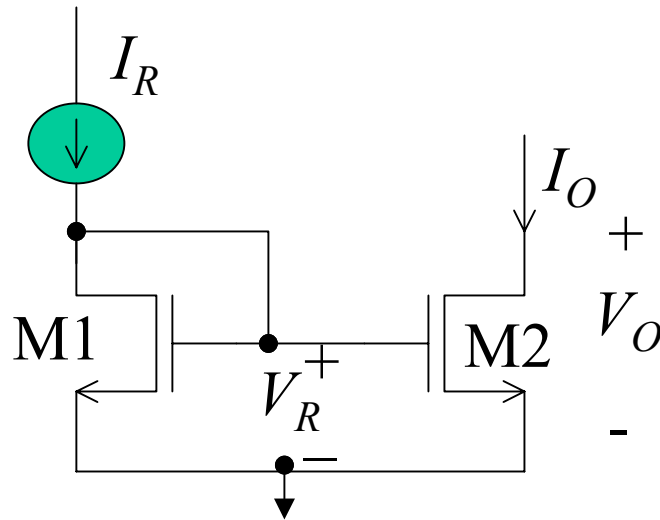


M1 is diode connected and is always in saturation

I_R sets a unique bias voltage V_R

$$I_R = \frac{\mu\epsilon_{ox}W_1}{T_{ox}L_1} \frac{(V_R - V_t)^2}{2} (1 + \lambda V_R)$$

M2 will mirror this current provided $V_O > V_R - V_t$

 Since $V_R = V_t + \Delta V$ where ΔV is gate over drive ; $V_O > \Delta V$



Current ratio

Neglecting channel length modulation effect,

$$I_O = \frac{(W/L)_2}{(W/L)_1} I_R$$

However it is advisable to choose constant L for Both M1 and M2 and ratio based on Ws only

$$L = L_g - 2L_D$$

L_D is constant for all $L_g \Rightarrow$ Ratio in L_g does not translate to ratio in L

$$I_O = \frac{W_2}{W_1} I_R$$

Channel width effect

Strictly speaking



$$W = W_g - 2\Delta W$$

where ΔW is due to field oxide encroachment


Ratio in W_g does not translate to ratio in W

Parallel transistor layout can be used to overcome this problem

Ex: $I_o = 2I_R$, then $W_2 = 2W_1$

  
 
$$I_o = \frac{2W_{g1} - 2\Delta W}{W_{g1} - 2\Delta W} I_R$$



$$I_o = \frac{2W_{g1} - 4\Delta W}{W_{g1} - 2\Delta W} I_R = 2I_R$$

Issues with basic current mirror

V_{ds} effect results in incorrect mirroring

$$\frac{I_O}{I_R} = \frac{W_2}{W_1} \frac{1 + \lambda V_o}{1 + \lambda V_R} \quad \text{For } L_1=L_2, \lambda_1=\lambda_2=\lambda$$


For $\lambda V_R \ll 1$, and neglecting λ^2 term:

$$\frac{I_O}{I_R} = \frac{W_2}{W_1} [1 + \lambda(V_o - V_R)]$$

The output resistance is finite

$$R_o = r_{o2}$$

Cascode current mirror

 

M3 is in common gate configuration

Hence M2 and M3 form cascode pair

M3 *shields* node Y from variations in V_o

$$\frac{\Delta v_o}{\Delta v_y} = \frac{g_{m3} + g_{mb3}}{g_{o3}}$$


$$\Delta v_y = \frac{\Delta v_o}{A_v(0)}$$

In order for $I_o = I_R$, V_{GB} should be chosen such that $V_x = V_y$

$$V_{GB} = V_x + V_{GS3}$$

This is achieved by introducing another diode connected transistor in series with M1

Cascode current mirror with matching

 

$$V_{GB} = V_x + V_{gs0}$$

For $V_{gs0} = V_{gs3}$, we need

$$\frac{(W/L)_3}{(W/L)_0} = \frac{(W/L)_2}{(W/L)_1}$$

Then $V_x = V_y$ and $I_O = I_R W_2 / W_1$


The minimum allowed V_O :

$V_{GB} = V_{gs0} + V_{gs1} = 2\Delta V + 2V_t$
 assuming similar overdrive and V_t

$$\therefore V_{Omin} = 2\Delta V + V_t$$

Beyond V_{Omin} , M3 comes out of saturation

Output resistance of cascode mirror

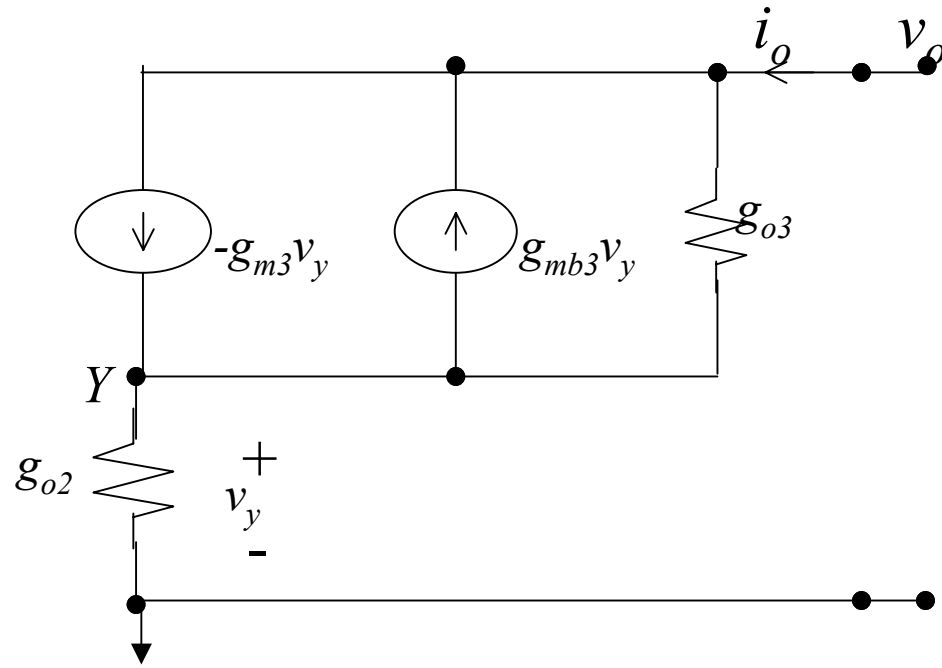

Applying KCL at output node

$$i_o = -(g_{m3} + g_{mb3})v_y + g_{o3}(v_o - v_y)$$


$$i_o = v_y g_{o2}$$

$$R_o = v_o / i_o$$

$$R_o = r_{o3} \bullet g_{m3} r_{o2} (1 + \eta) \approx r_{o3} \bullet g_{m3} r_{o2}$$

The output resistance of M3 (r_{o3}) is enhanced by a factor $g_{m3} r_{o2}$

Cascode mirror with improved o/p swing

 

The voltage at G_o is $V_{G0} = 2\Delta V + 2V_t$

Hence the voltage at G3 is

$$V_{G3} = 2\Delta V + V_t$$


$$\therefore V_{Omin} = 2\Delta V$$

Although output swing is increased, it should be noted that $V_x \neq V_y$

Hence the improvement has come at the expense of current matching

Cascode mirror with improved o/p swing

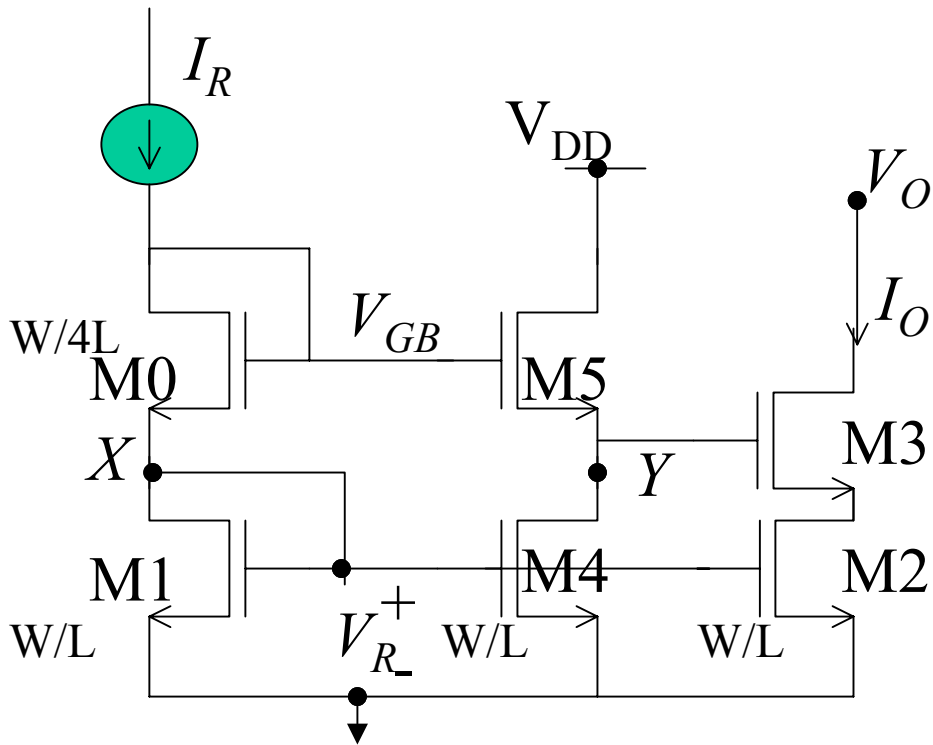Vt can be implemented using following configuration



The size of M0 is 4 times smaller than that of M1


For the currents to be identical the gate overdrive of M0 be twice that of M1 ($2\Delta V$ and ΔV)

$$V_{gs0} = 3\Delta V + 2V_t$$

$$V_{gs3} = 2\Delta V + V_t$$

$$V_{Omin} = 2\Delta V$$

Wilson Current source

 

Negative feedback arrangement through M1, M2 and M3.


- If V_O increase, then I_O tends to increase I_{d2} and hence V_y increase
- Since I_R is constant, V_x decreases thus decreasing the gate drive for M1
- This will restore I_O to its initial value

i.e. any change in V_O is absorbed as an appropriate change in V_x

$$\frac{I_O}{I_R} = \frac{W_2}{W_3} [1 + \lambda_2 V_x - \lambda_3 V_y]$$

$$V_{omin} = 2\Delta V + V_t$$

Output resistance

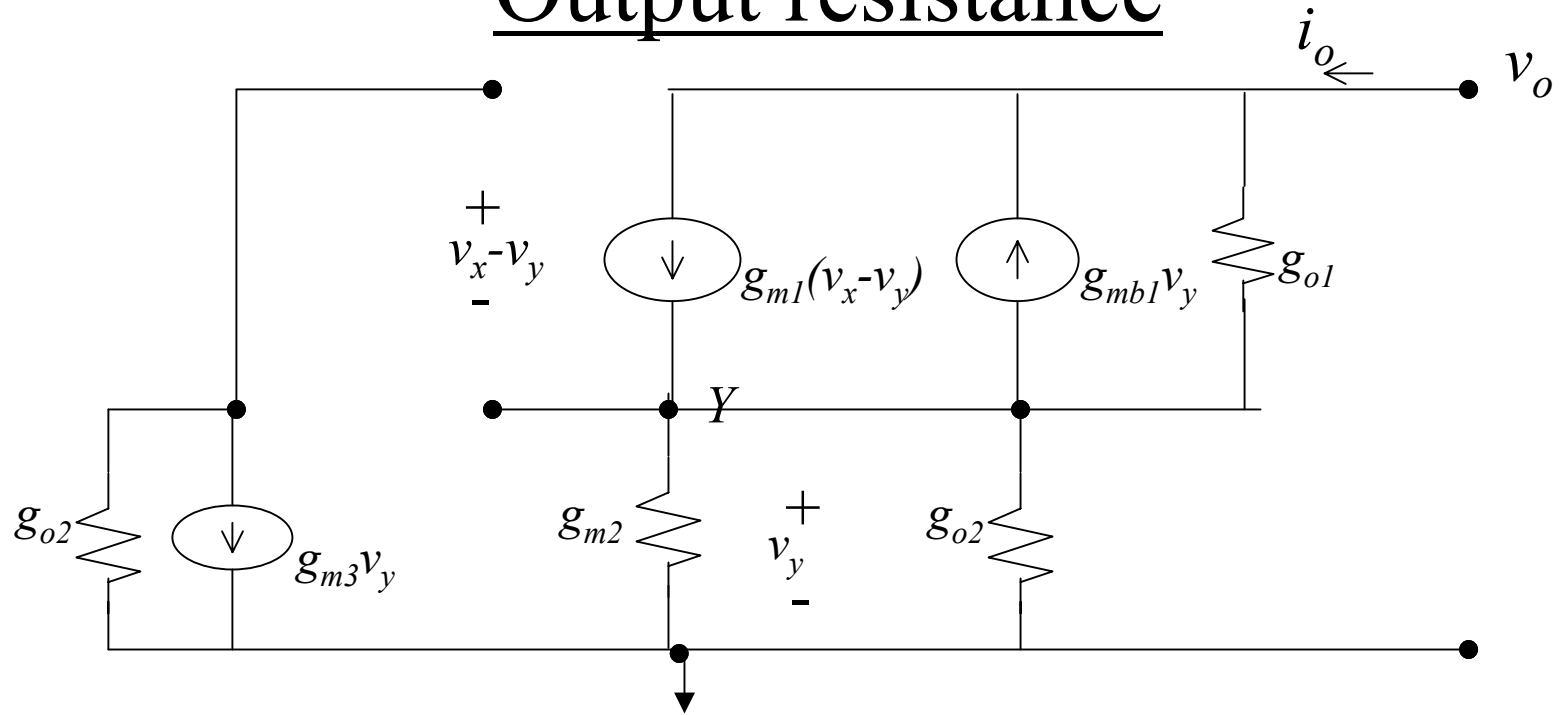


$$R_o = v_o / i_o$$

$$R_o = r_{o1} \left[1 + \frac{g_{m1} g_{m3}}{g_{m2} g_{o3}} \right]$$

$$R_o \approx r_{o1} (g_{m1} r_{o3})$$

Modified Wilson

 

The current matching is improved

$V_x = V_y$ can be ensured if

$$\frac{(W/L)_1}{(W/L)_4} = \frac{W_2}{W_3}$$


Under this condition,

$$I_O = I_R W_2 / W_3$$

The output resistance is similar to Wilson

$$R_o = r_{o1}(g_{m1}r_{o3})$$

Regulated Cascode

 

The gate of M3 is connected to drain of M2

The gate of M2 is connected to fixed V_{G2}

The negative feedback is provided through M1 and M3

Change in V_O is absorbed at V_X

No explicit conventional mirror connection of transistors


The mirroring is entirely due to the negative feedback

The output resistance is enhanced significantly

The minimum allowed output voltage is lowered $V_{omin} = 2\Delta V$

*The circuit works reasonably well even if V_{omin} drops to ΔV

Output resistance

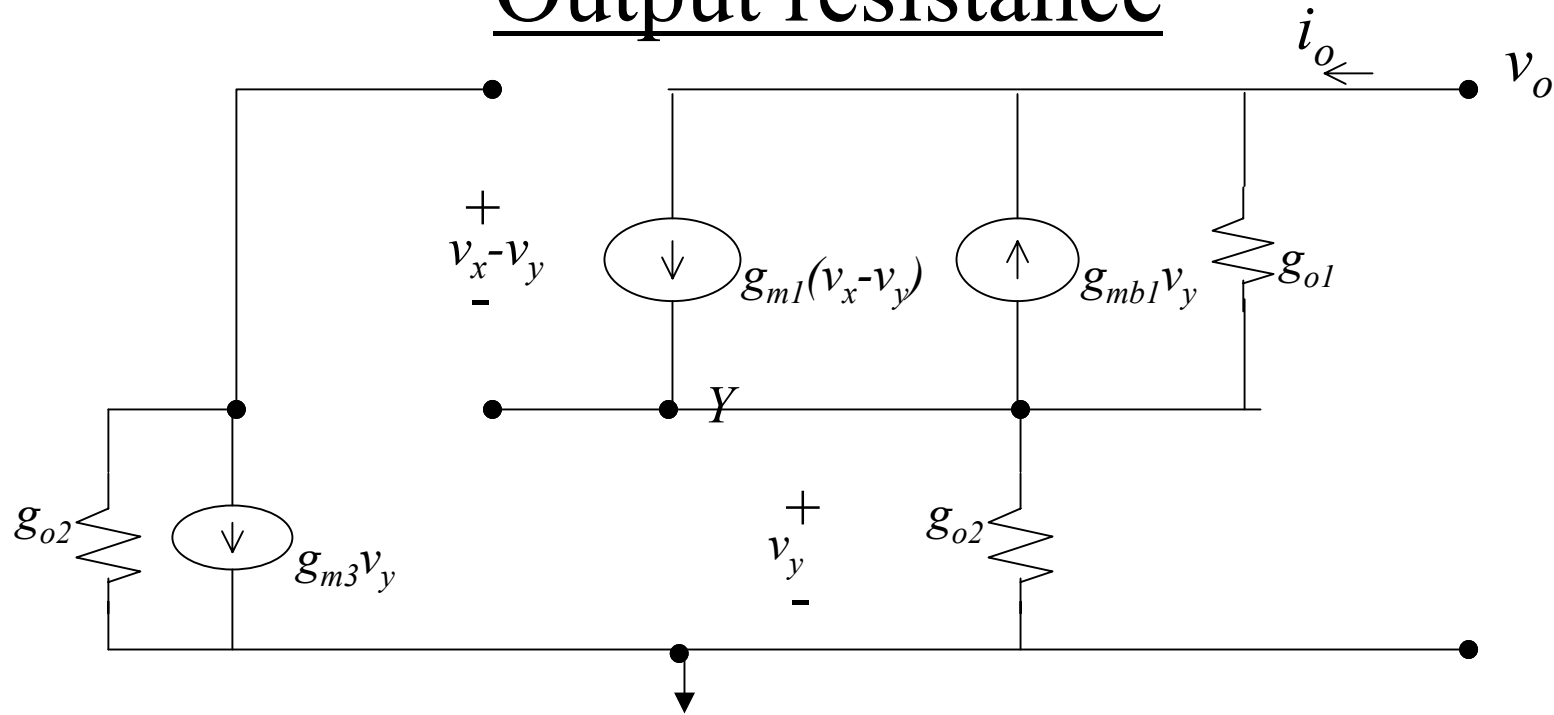


$$R_o = r_{o1} \left[1 + \frac{g_{m1} g_{m3}}{g_{o2} g_{o3}} \right]$$

$$R_o \approx r_{o1} (g_m r_o)^2$$

Very high output impedance

Regulated cascode with bias generation

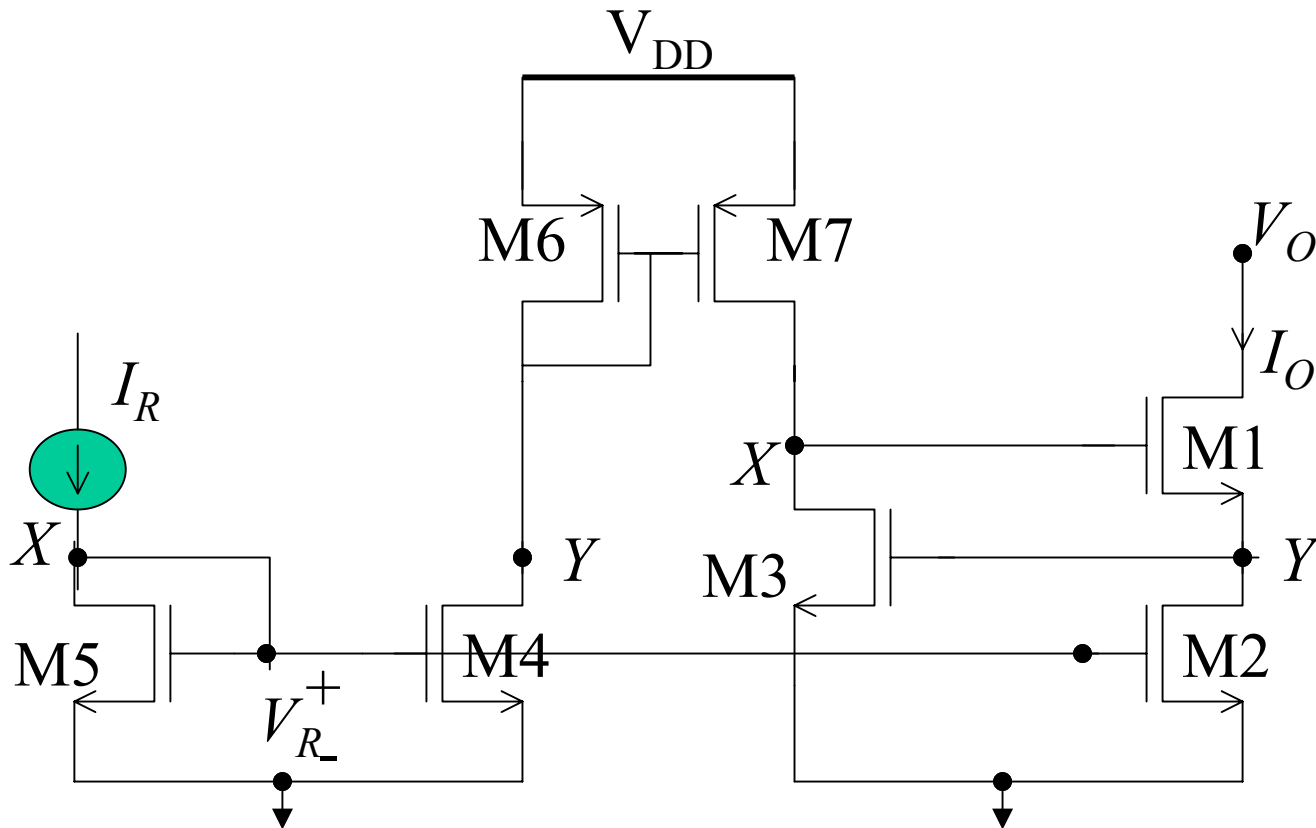

I_R generates fixed bias for VG2

I_R is mirrored on to M3 through the NMOS (M4-M5) and the PMOS (M6-M7) current mirrors

Layout Issues

Orientation

Symmetry

Adding dummy layers


Unit cell repetition

Common centroid

Avoiding interconnect resistance

Orientation

 
Matched transistors should be oriented in same direction




Photolithography process has different biases in different axes, hence the requirement

Symmetry

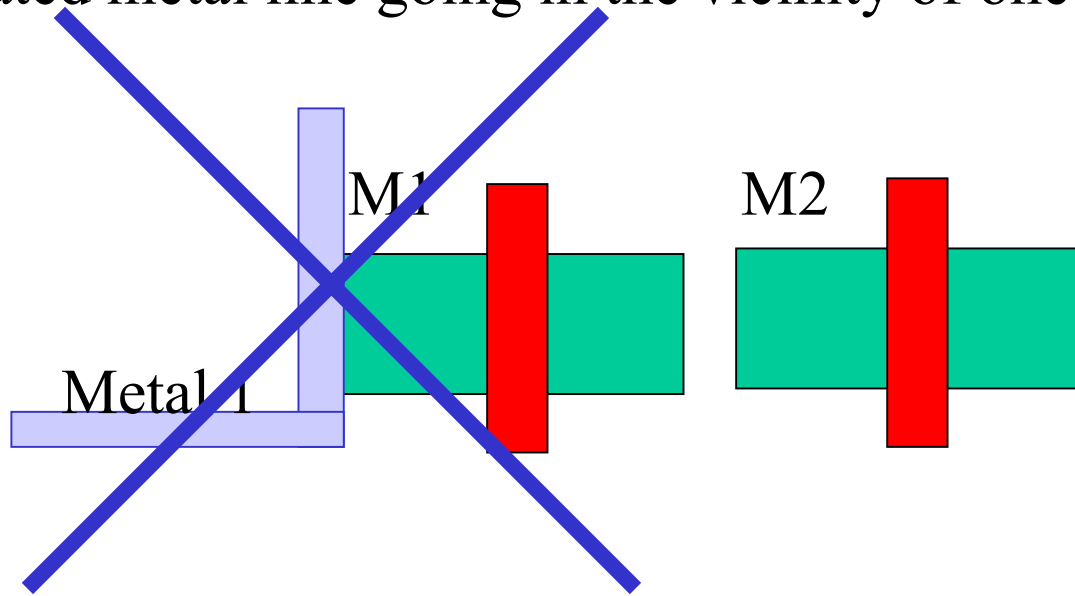An unrelated metal line going in the vicinity of one of the transistor



 
Symmetry should be preserved by adding another similar line




Unit cell repetition

Wide transistor should be laid out as parallel transistors of unit width to decrease gate resistance, s/d area capacitance as well as to counter ΔW effect

 Disproportionate aspect ratio can be managed as below:




Interdigitation and dummy layer

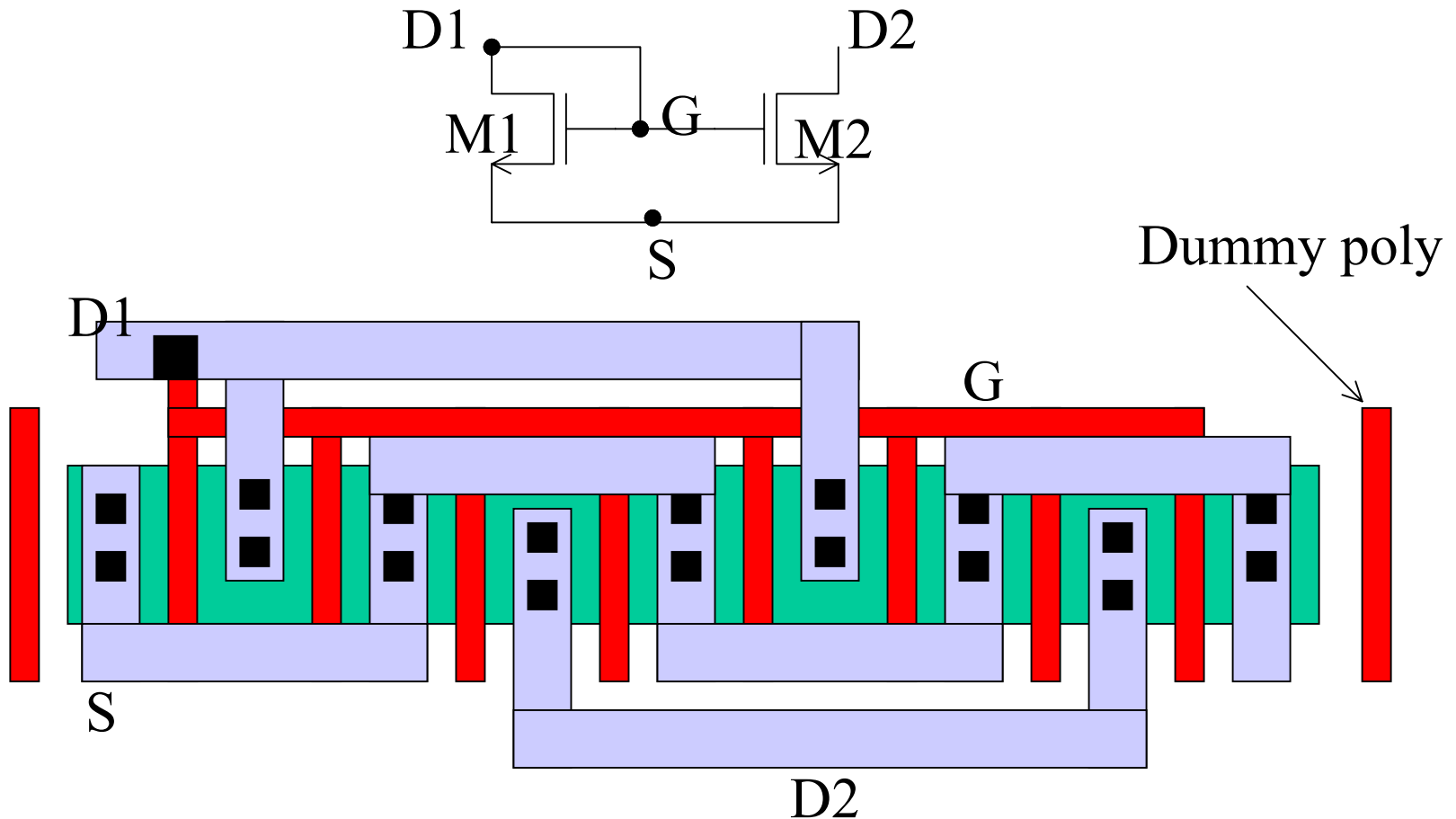

Interdigitation distributes the transistors uniformly


Dummy poly line eliminates loading effect in photo and etch

Common centroid

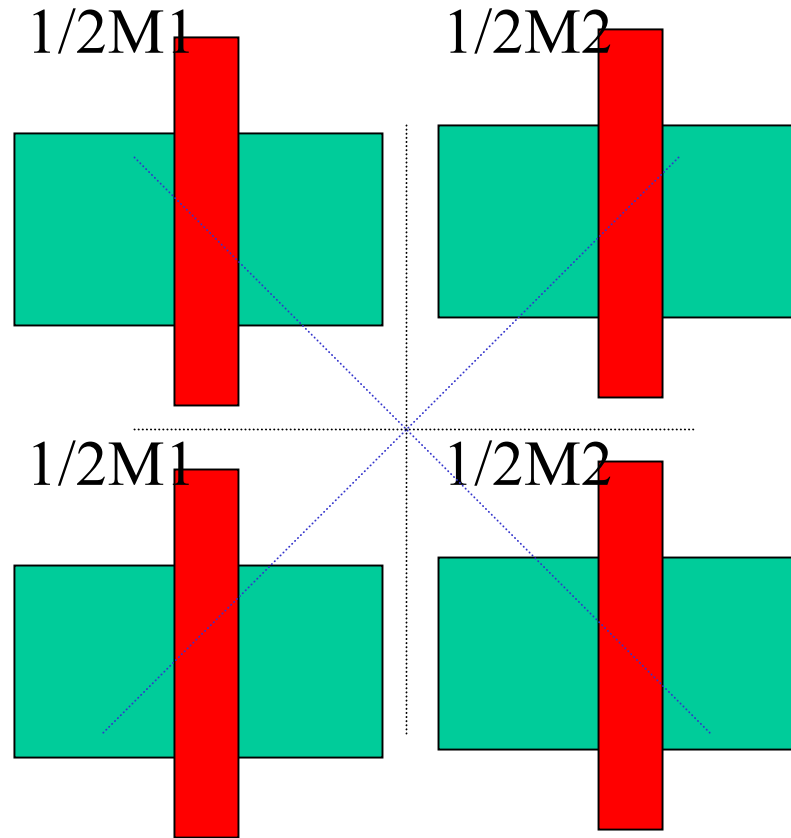

Common centroid configuration eliminates the first order gradient effects of parameters along both the axes

Interconnect routing

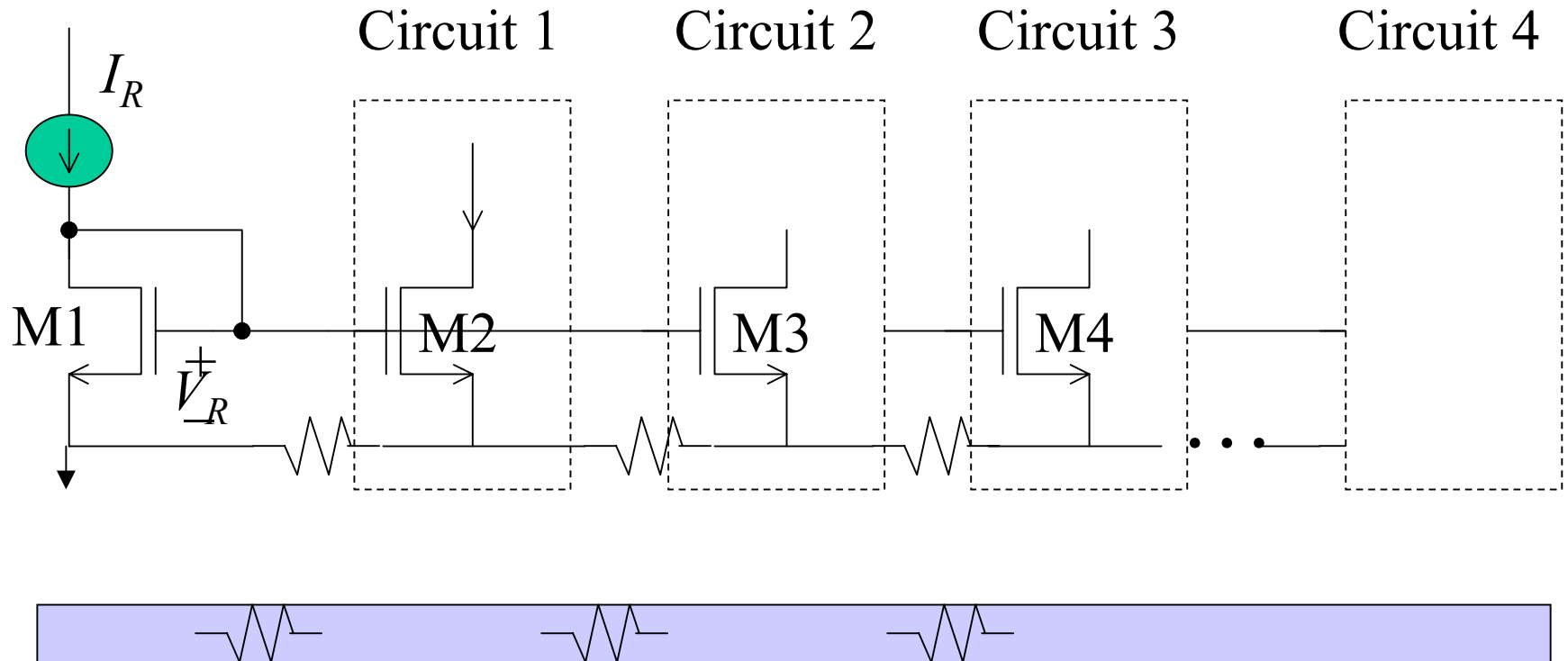

To distribute I_R in a large circuit, the resistance of ground bus makes $V_{gsn} \neq V_{gs1}$, thus affecting the current mirroring significantly

Interconnect routing

Decrease the ground bus resistance

Provide multiple ground node connections if possible
And use short span ground bus

Keep several reference distributed in a large circuit
and mirror the reference locally


Bandgap Voltage Reference

Bandgap Voltage reference

Design Task to set the DC bias of any circuits

1. Power Supply Independent Biasing
2. Temperature Independent Biasing
Bandgap Voltage Reference

Resistance biasing

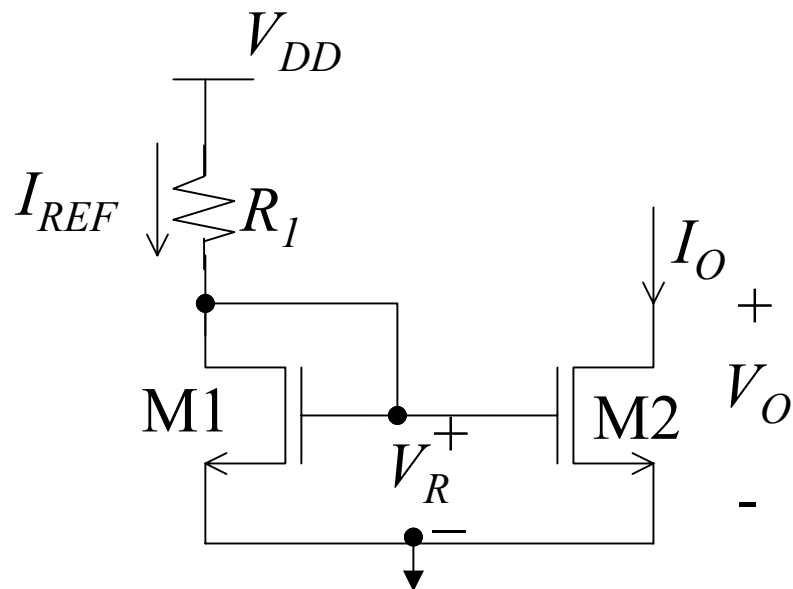


$$I_o = \frac{V_{DD}}{R_1 + \frac{1}{g_{m1}}} \frac{W_2}{W_1}$$

$$\Delta I_o = \frac{\Delta V_{DD}}{R_1 + \frac{1}{g_{m1}}} \frac{W_2}{W_1}$$

I_o is very sensitive to variation in V_{DD}

*In order to have low sensitivity, the circuit must bias itself
i.e. self biasing*

Self Biasing circuit

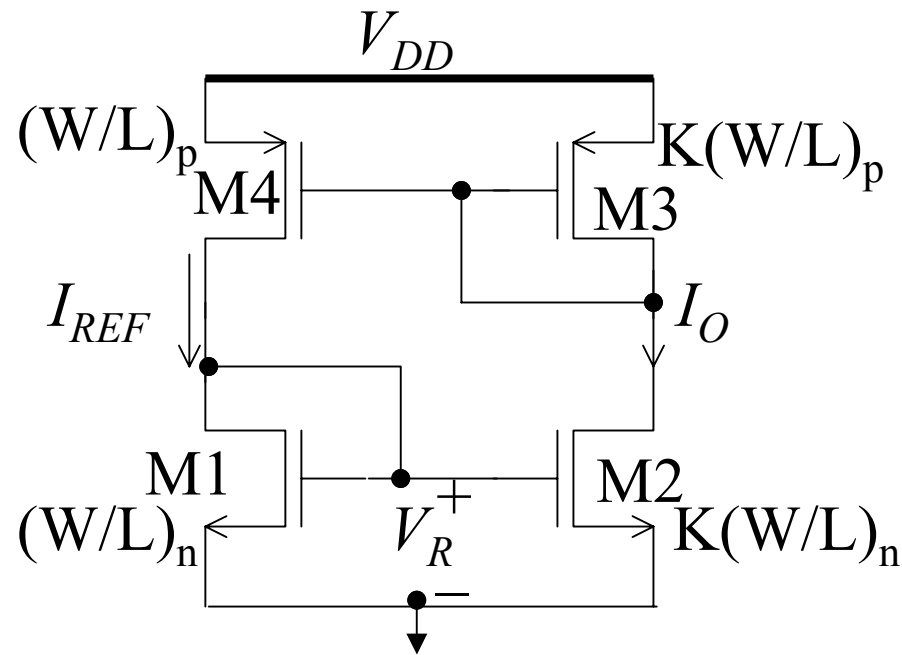

I_O is bootstrapped to I_{REF}

$$I_O = K I_{REF}$$

But how do we fix I_O

Because as long as all transistors are saturated, any current is a valid solution for the circuit!

In order to uniquely define the current another constraint should be added to the circuit

Self Biasing


$$V_{gs1} = V_{gs2} + I_O R_S$$

$$\sqrt{\frac{2I_O}{\mu C_{OX}(W/L)_n}} + V_t = \sqrt{\frac{2I_O}{\mu C_{OX}(W/L)_n}} + I_O R_S$$

$$I_O = \frac{2}{\mu C_{OX}(W/L)_n R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

The current is uniquely defined and it is independent of supply voltage

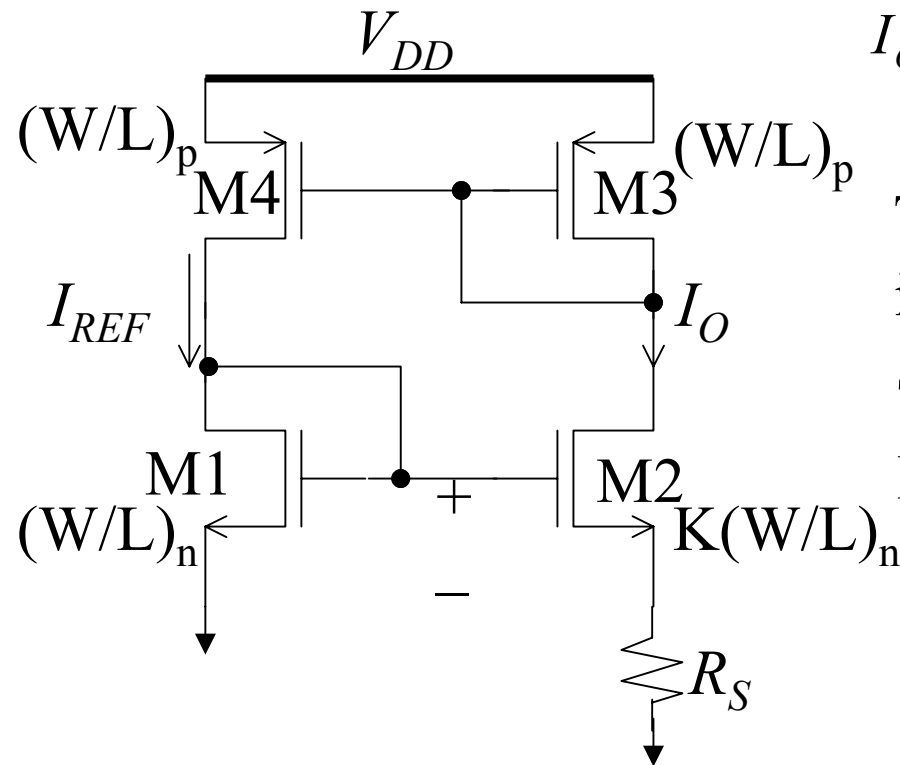The current is still a function of Process parameters and temperature



The Start-up problem

The previous circuit can support zero current as well!

At the start up it should be ensured that the circuit does not enter this degenerate situation


At the start up the 3 diode connected transistors M1, M5 and M3 provide a path to the ground give non zero I_O

$$V_{t1} + V_{t5} + |V_{t3}| < V_{DD}$$

$$3V_t < V_{DD}$$

After start up, M2, M4 should turn on and M5 should be turned off

$$V_{gs1} + V_{t5} + |V_{gs3}| > V_{DD}$$

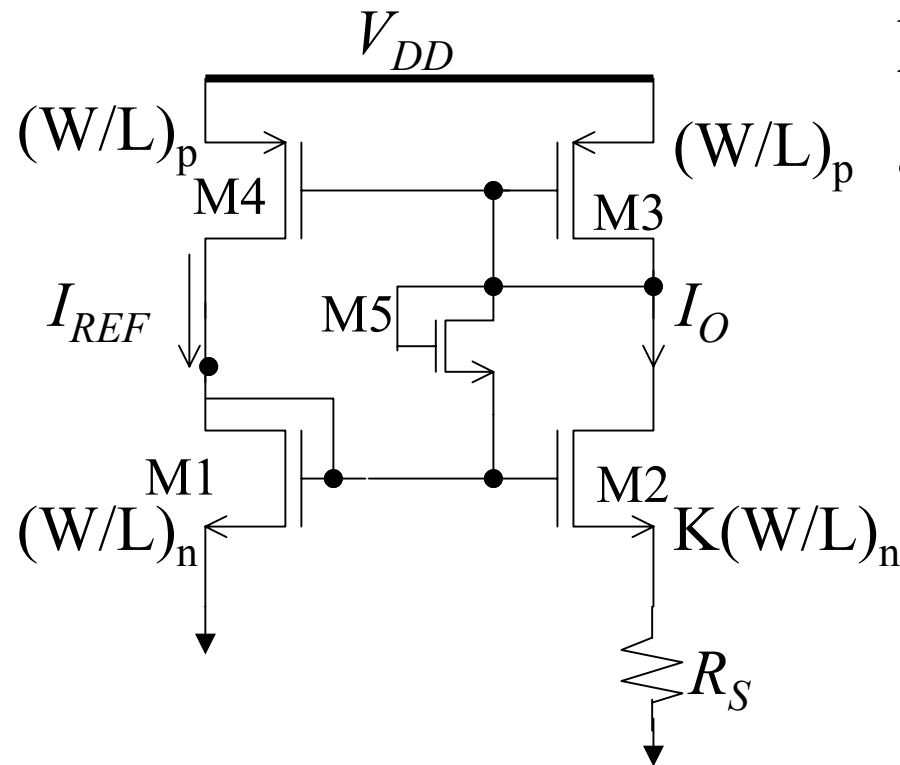

Temperature Independent Reference

The concept:

Generate the reference by combining two voltages of which one has negative temperature coefficient and the other one has a positive temperature coefficient

$$V_{REF} = \alpha_1 V_1 + \alpha_2 V_2$$

$$\frac{\partial V_1}{\partial T} = -ve$$

$$\frac{\partial V_2}{\partial T} = +ve$$

$$\alpha_1 \frac{\partial V_1}{\partial T} + \alpha_2 \frac{\partial V_2}{\partial T} = 0$$

V_{BE} of a BJT (diode) is a good candidate for negative TC

Difference between 2 different V_{BE} s is a good candidate for +ve TC

Other candidates such as resistor etc. also exist

Negative TC

The BJT collector current is given by

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \rightarrow V_{BE} = V_T \ln \frac{I_C}{I_S} \quad \text{where } V_T = kT/q, \text{ is thermal voltage}$$

$$I_S = C \mu k T n_i^2 \quad C \text{ is proportionality constant}$$

$$\mu \propto \mu_0 T^m \text{ where } m \approx 3/2$$

$$n_i^2 \propto T^3 \exp(-E_g/kT) \text{ where } E_g \text{ is bandgap of Si, } E_g \approx 1.12 \text{ eV}$$


At constant collector current, using above equations,

$$\frac{\partial V_{BE}}{\partial V_T} = \frac{V_{BE} - (4 + m)V_T - E_g / q}{T}$$

Note that the TC is a function of V_{BE} and T itself

$$\text{For } V_{BE} = 0.75 \text{ V and } T = 300^\circ \text{K, } \frac{\partial V_{BE}}{\partial V_T} = -1.5 \text{ mV}/^\circ \text{K}$$

Positive TC

 

Suppose that the two collector currents are nI_O and I_O (typically done by adjusting the device dimensions/layout)

$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$\Delta V_{BE} = V_T \ln \frac{nI_O}{I_S} - V_T \ln \frac{I_O}{I_S}$$

$$\Delta V_{BE} = V_T \ln n$$

$$\frac{\partial \Delta V_{BE}}{\partial T} = \frac{k}{q} \ln n$$

Note that the TC is independent of I_c and Temperature

Bandgap Reference

$$V_{REF} = \alpha_1 V_1 + \alpha_2 V_2$$

Choose $V_1 = V_{BE}$ and $V_2 = \Delta V_{BE}$

Set $\alpha_1 = 1$ and choose α_2 such that the TC is zero at 300°K

Since $dV_1/dT = -1.5\text{mV}/^\circ\text{K}$ and $d\Delta V_{BE}/dT = +0.087\text{mV}/^\circ\text{K}$,

Choose α_2 so that $(\alpha_2 \ln n)(0.087\text{mV}/^\circ\text{K}) = +1.5\text{mV}/^\circ\text{K}$

$$V_{REF} \approx V_{BE} + 17.2V_T$$

$$V_{REF} \approx 1.19V$$


Note: V_{REF} can also be expressed as

$$V_{REF} \approx \frac{E_g}{q} + (4 + m)V_T$$

In the limit as $T \rightarrow 0$, $V_{REF} \rightarrow E_g/q$

Hence the name bandgap voltage reference

The circuit to add V_{BE} and $17.2V_T$

 

$Q1$ is unit transistor with area A
 $Q2$ has n unit transistors in parallel
 The current in one unit of $Q2$ is I_O/n

Suppose that V_{O1} and V_{O2} are made equal by some external means

Then,

$$V_{BE1} = RI_O + V_{BE2}$$

$$RI_O = V_{BE1} - V_{BE2} = V_T \ln n$$


$$V_{O2} = V_{BE2} + V_T \ln n$$

which is the required reference

Need a mechanism for $V_{O1} = V_{O2}$

$\ln n = 17.2$ results in impractical n and hence should some how scaled properly

Circuit Implementation

 

The OPAMP forces $V_X = V_Y$

$$V_{BE1} - V_{BE2} = V_T \ln n$$

This results in a current through the right branch

$$I_{R3} = V_T \ln n / R_3$$

$$V_O = V_{BE2} + \frac{V_T \ln n}{R_3} (R_2 + R_3)$$


$$V_O = V_{BE2} + V_T \ln n \left(1 + \frac{R_2}{R_3} \right)$$

If $R_2/R_3 = 10$, then $n=5$

The output V_O gives the required reference voltage


Compatibility with CMOS Technology

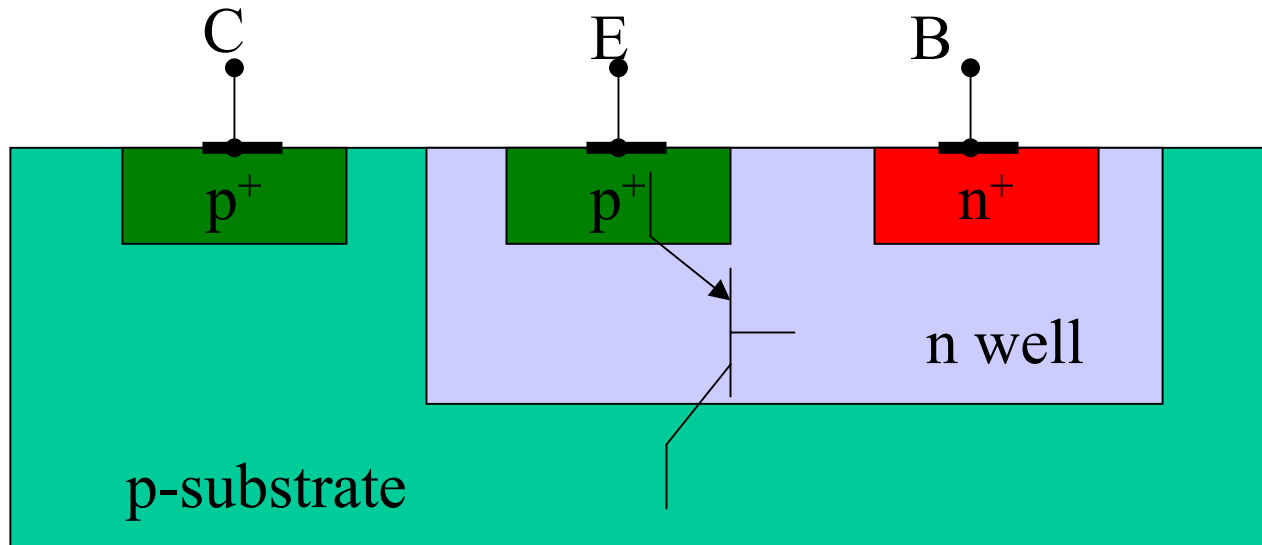In an n-well technology the vertical PNP BJT can be realised




The p-substrate, connected to most negative potential (Gnd) acts as a collector whereas n-well and p⁺ region act as base & emitter

Modified circuit for CMOS Technology

 


 The output voltage V_o is the bandgap voltage reference




Differential Amplifier

Single ended vs. differential signaling

 

 Single ended signal is measured with respect to a fixed potential (gnd)



Differential signal is measured with respect to 2 nodes which make equal and opposite excursion


Differential Voltage $v_d = \Delta v_i = v_{i1} - v_{i2}$

Common mode Voltage $V_c = \frac{v_{i1} + v_{i2}}{2}$

Advantages of differential signaling

High immunity to environmental noise

i.e. common mode noise is rejected

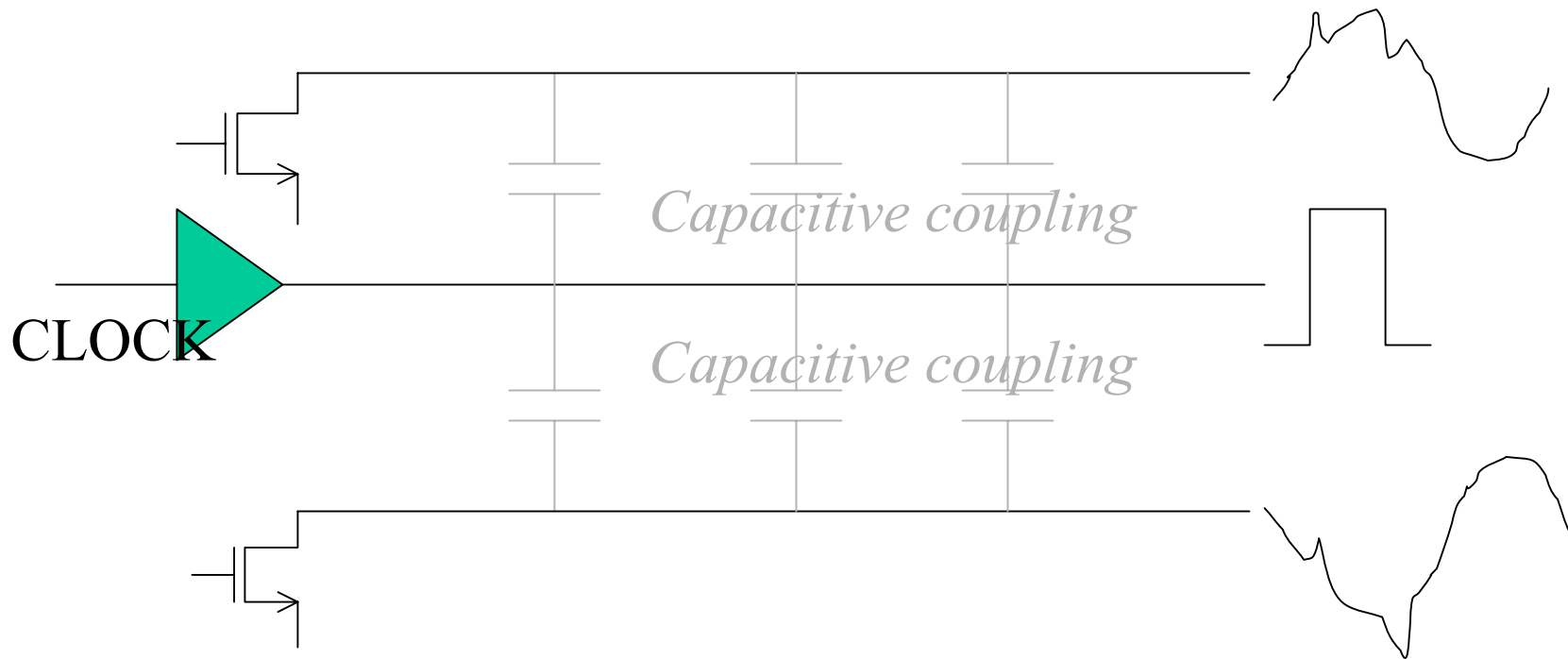


The capacitive coupling noise is cancelled


Advantages of differential signaling

Similar to noise reception, the noise injected by differential signal lines is also very low

 The output swing is doubled in differential signaling



Differential signal amplification

 

Combine two single ended amplifiers to form a differential amplifier


The common mode input level determines the differential gain, which is undesirable

Requirement of an ideal Differential Amplifier:

Differential gain should be independent of common mode input

\Rightarrow A configuration in which bias current is independent of V_c

 Differential Amplifier with current source bias




If I_s is constant then I_{d1} and I_{d2} are independent of V_c

$$I_{d1} = I_{d2} = I_s/2$$

Does it mean V_c can be between 0 to ∞ ?

The lower limit of V_c :

 I_s is typically realised using current mirror transistor



When $V_c=0$, M1 and M2 are off, M3 is in deep triode region and $V_p=0$ and $I_s=0$



Hence the circuit does not act as an amplifier

Lower limit for V_c

When V_c reaches V_t , M1 and M2 start turning on and hence V_p starts following V_c (source follower)

The current I_s starts increasing and hence I_{d1} and I_{d2}

  When V_p reaches ΔV_3 of M3, then M3 comes into saturation I_s remains constant and so do I_{d1} and I_{d2}



$$V_{c\min} \approx V_t + 2\Delta V$$

Upper limit for V_C

As V_C starts approaching V_{DD} at certain value of V_C , M1 and M2 come out of saturation


This happens at
$$V_{c\max} = V_{DD} - \frac{I_S}{2} R_D + V_t$$

Beyond this point circuit is not usable since gm and ro drop

Further after this point, V_p starts lagging behind V_C in order to maintain high gate overdrive to conduct the current $I_S/2$


We will revisit this point when we discuss low voltage wide common mode range OPAMPs

The useful range of operation w.r.t. V_C

 

Useful voltage gain can be obtained for $V_{C_{min}} < V_C < V_{C_{max}}$

Differential Response

 


When $v_{id} = \pm \Delta v_{iM}$

The entire current I_S flows through only one of the two branches of differential pair (i.e. either through M1 or M2)

This limits the maximum input swing for v_{id}

Input range and Transconductance

 

$$I_{d1} = \frac{\mu\epsilon_{ox}W_1}{T_{ox}L_1} \frac{(V_{gs1} - V_t)^2}{2} = \frac{k_1}{2} (V_{gs1} - V_t)^2$$

$$I_{d2} = \frac{\mu\epsilon_{ox}W_2}{T_{ox}L_2} \frac{(V_{gs2} - V_t)^2}{2} = \frac{k_2}{2} (V_{gs2} - V_t)^2$$

$$\Delta V_i = V_{i1} - V_{i2} \text{ and } \Delta I_d = I_{d1} - I_{d2}$$

The objective is to get $\Delta I_d = f(\Delta V_i)$

$$I_{d1} = \frac{I_S}{2} + \frac{\Delta I_d}{2}$$

$$I_{d2} = \frac{I_S}{2} - \frac{\Delta I_d}{2}$$

Let $k_1 = k_2 = k$, then

$$V_{gs1} = V_t + \sqrt{\frac{2I_{d1}}{k}}$$

$$V_{gs2} = V_t + \sqrt{\frac{2I_{d2}}{k}}$$

Input range and Transconductance

$$\Delta V_i = V_{i1} - V_{i2} = V_{gs1} - V_{gs2}$$

$$\Delta V_i = \sqrt{\frac{2}{k}} \left[\sqrt{I_{d1}} - \sqrt{I_{d2}} \right]$$

$$\Delta V_i^2 = \frac{2}{k} \left[I_{d1} + I_{d2} - 2\sqrt{I_{d1}I_{d2}} \right]$$

$$\Delta I_d = \frac{k}{2} \Delta V_i \sqrt{\frac{4I_S}{k} - \Delta V_i^2}$$

This is used to get the input range and transconductance

Input range

$$\Delta I_d = \frac{k}{2} \Delta V_i \sqrt{\frac{4I_S}{k} - \Delta V_i^2}$$

At $\Delta V_i = V_{iM}$, $\Delta I_d = I_{SS}$, Hence

$$\Delta V_{iM} = \sqrt{\frac{2I_S}{k}}$$

Trade-off

ΔV_{iM} can be increased by decreasing k

but lower $k \Rightarrow$ higher $V_{gs} - V_t$

this results in increased V_{cmin}

ΔV_{iM} can be increased by increasing I_S

but higher $I_S \Rightarrow$ lower $V_{DD} - I_S R_D / 2 + V_t$

this results in reduced V_{cmax}

also higher static power

Typical input range

If the bias current $I_S = 100\mu\text{A}$

$$\mu C_{ox} = 50\mu\text{A}/\text{V}^2$$

$$W/L = 100$$

$$\Delta V_{iM} = \sqrt{\frac{2 \times 100}{50 \times 100}} = \sqrt{0.04} = 0.2\text{V}$$

Differential Transconductance

$$G_m = \frac{d\Delta I_d}{d\Delta V_i}$$

$$G_m = \frac{k}{2} \sqrt{\frac{4I_S}{k} - \Delta V_i^2} - \frac{k}{2} \frac{\Delta V_i^2}{\sqrt{4I_S/k - \Delta V_i^2}}$$

G_m is maximum when $\Delta V_i = 0$

$$G_{m0} = \sqrt{kI_S}$$

Trade-off

G_m can be increased by increasing k


but higher $k \Rightarrow$ lower input swing ΔV_{iM}

G_m can be increased by increasing I_S

but higher $I \Rightarrow$ lower V_{cmax}

also higher static power


G_m versus ΔV_i

 

Trade-off between Gain and linearity!

Differential and Common mode response

 Any given inputs v_{i1} and v_{i2} can be decomposed into differential and common mode signals



$$v_{id} = v_{i1} - v_{i2} \quad v_{ic} = \frac{v_{i1} + v_{i2}}{2}$$

$$v_{od} = v_{o1} - v_{o2} \quad v_{oc} = \frac{v_{o1} + v_{o2}}{2}$$


$$v_{i1} = v_{ic} + \frac{v_{id}}{2} \quad v_{i2} = v_{ic} - \frac{v_{id}}{2}$$

$$v_{o1} = v_{oc} + \frac{v_{od}}{2} \quad v_{o2} = v_{oc} - \frac{v_{od}}{2}$$

Differential mode gain $A_d = \frac{v_{od}}{v_{id}}$ with $v_{ic} = 0$

Common mode gain $A_c = \frac{v_{oc}}{v_{ic}}$ with $v_{id} = 0$

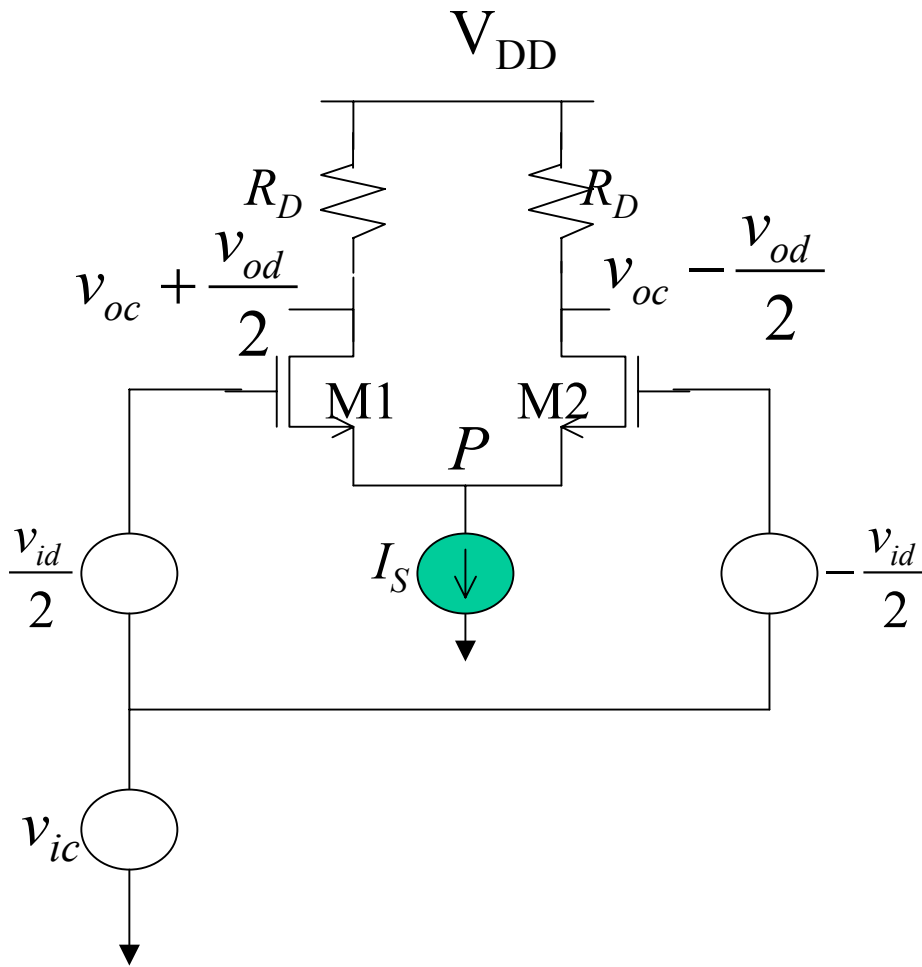Modified circuit in terms v_{id} and v_{ic}



For the symmetric differential pair:

$$g_{m1} = g_{m2},$$

$$r_{o1} = r_{o2},$$

$$R_{D1} = R_{D2}$$

The differential response is obtained by setting $v_{ic} = 0$

The common mode response is obtained by setting $v_{id} = 0$

Differential response

What happens at node P for a pure differential input?

1. If v_{i1} changes by $+\Delta v$ and v_{i2} by $-\Delta v$ and if the circuit is linear then V_p does not change

2. Since the current flowing out of node P is constant (IS), the change in currents in two arms should cancel

i.e. $g_m(\Delta v_{gs1} + \Delta v_{gs2}) = 0$ or $\Delta v_{gs1} = -\Delta v_{gs2} = \Delta v_{gs}$


3. Also $V_{gs1} = V_{i1} - V_p$ and $V_{gs2} = V_{i2} - V_p$

From 1, 2, 3, it follows that V_p can not change and the entire change in input is absorbed by gate overdrive

V_p is at AC ground

Half circuit concept

 A fully differential circuit can be analysed by looking at only one half of the circuit



$$A_d = \frac{v_{od}}{v_{id}} = \frac{v_{od}/2}{v_{id}/2} = -g_m \frac{r_o R_D}{r_o + R_D}$$


$$A_d \approx -g_m R_D \quad \text{If } R_D \ll r_o$$

Note: If a single stage CS amplifier is biased with I_S , then the gain would be twice the differential gain

Common mode equivalent circuit

For a pure common mode signal v_{ic} is translated equally in both branches, thus changing v_{oc}

V_p is NOT at AC ground

 

In a balanced circuit $i_X=0$

Common mode response


The circuit can be broken into two parts

The equivalent circuit looks like common Source amplifier with source degeneration

The degenerated transconductance $-1/2R_S$

$$\therefore A_c = -\frac{R_D}{2R_S}$$

 The common mode gain affects the DC bias point and also affects the output differential mode swing



Common Mode Rejection Ratio

CMRR is a measure of differential amplifier which indicates its ability to suppress common mode gain and enhance the differential mode gain

$$CMRR = \frac{A_d}{A_c}$$

$$CMRR = \frac{-g_m R_D r_o / R_D + r_o}{-R_D / 2R_S}$$

$$CMRR = \frac{2g_m r_o R_S}{r_o + R_D}$$

For high CMRR, R_S should be as large as possible
Hence the need for good current source at source of M1/M2

Common mode to differential conversion

Another important problem is the conversion of CM signal to DM output in presence of device mismatch

We define A_{cd} as $A_{cd} = \frac{v_{od}}{v_{ic}}$ with $v_{id} = 0$


$$CMRR = \frac{A_d}{A_{cd}}$$

For mismatch in R_D , $A_{cd} = -\frac{\Delta R_D}{2R_S}$

For mismatch in gm, $A_{cd} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_S + 1}$

The problem becomes serious at high frequencies, since R_S gets shunted by the capacitances

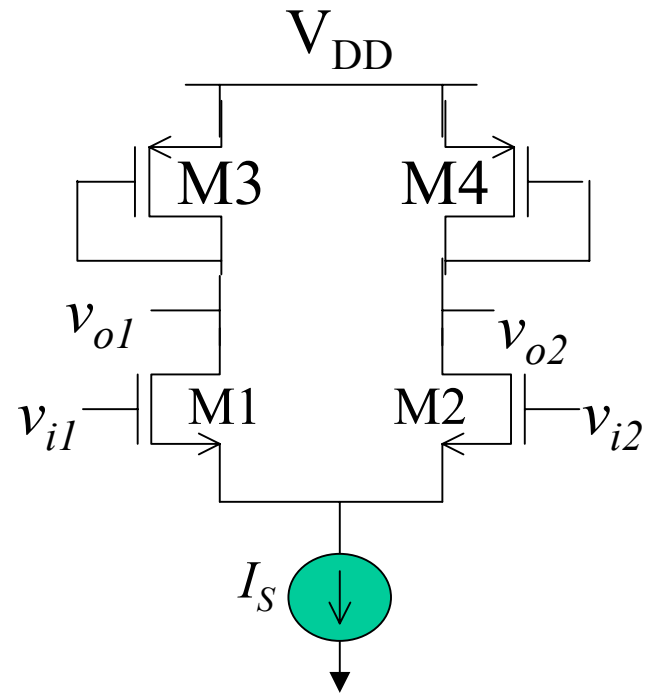Differential pair with diode connected load



Advantages:

Resistance is eliminated

Output common mode voltage is well defined

Disadvantages:


The gain is limited by g_{mp} since

$$A_d = -g_{mn}/g_{mp}$$

Stringent trade off between gain and swing

$$\therefore A_v = -\sqrt{\frac{\mu_n (W/L)_n}{\mu_p (W/L)_p}} = \frac{(V_{gs} - V_t)_p}{(V_{gs} - V_t)_n}$$

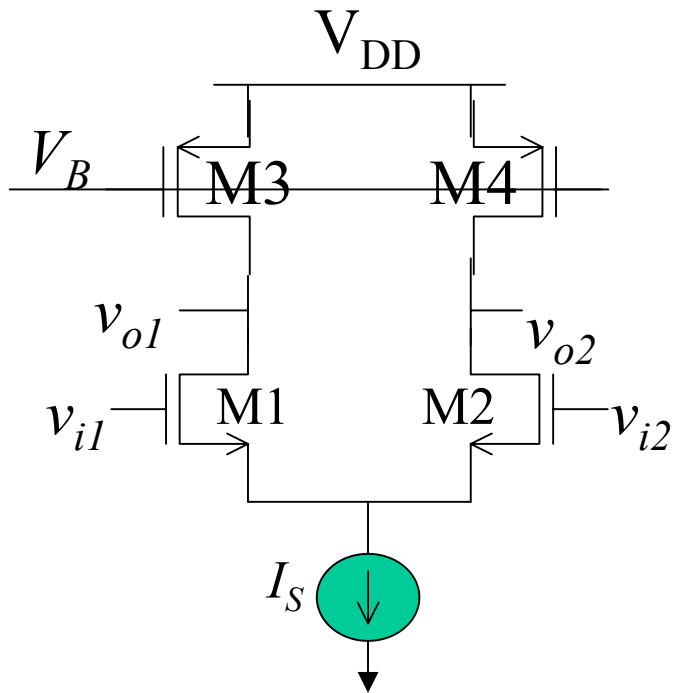Differential pair with current source load



Advantages:


$$A_d = -g_{mn}(r_{on} || r_{op})$$

Gain and swing are not very strongly coupled as in the earlier case

Disadvantages:

The output common mode voltage is not very well defined

Combined load

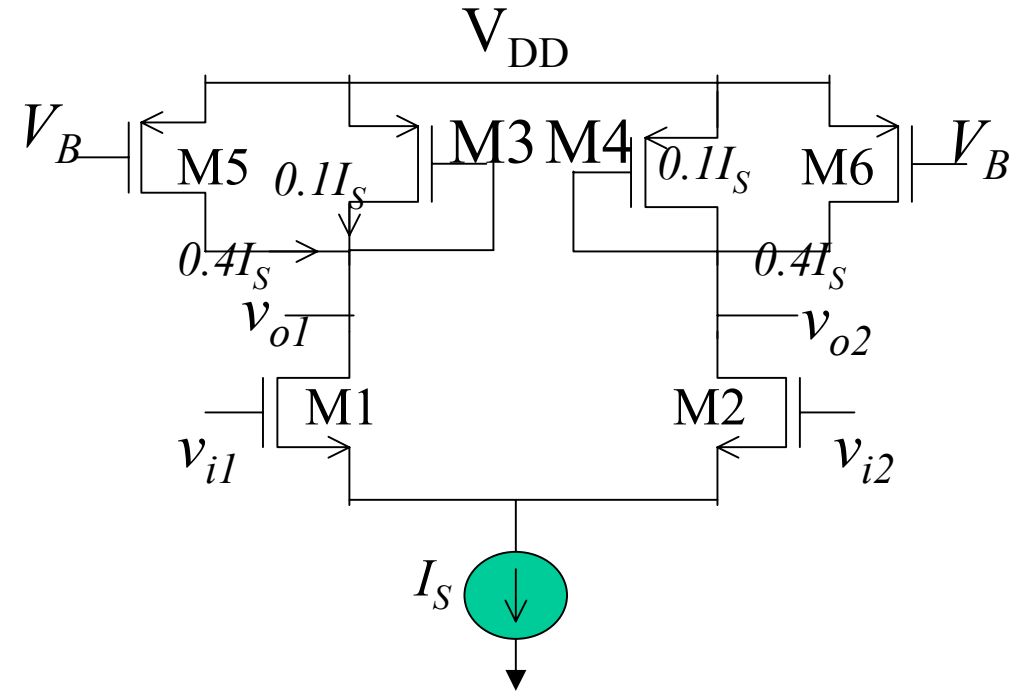


The load consists of diode as well as constant current source to exploit advantages of both the configuration

Only a small fraction of I_S is routed through diode

The output gain is better than diode load

The output common mode voltage is also fixed

Cascode configuration

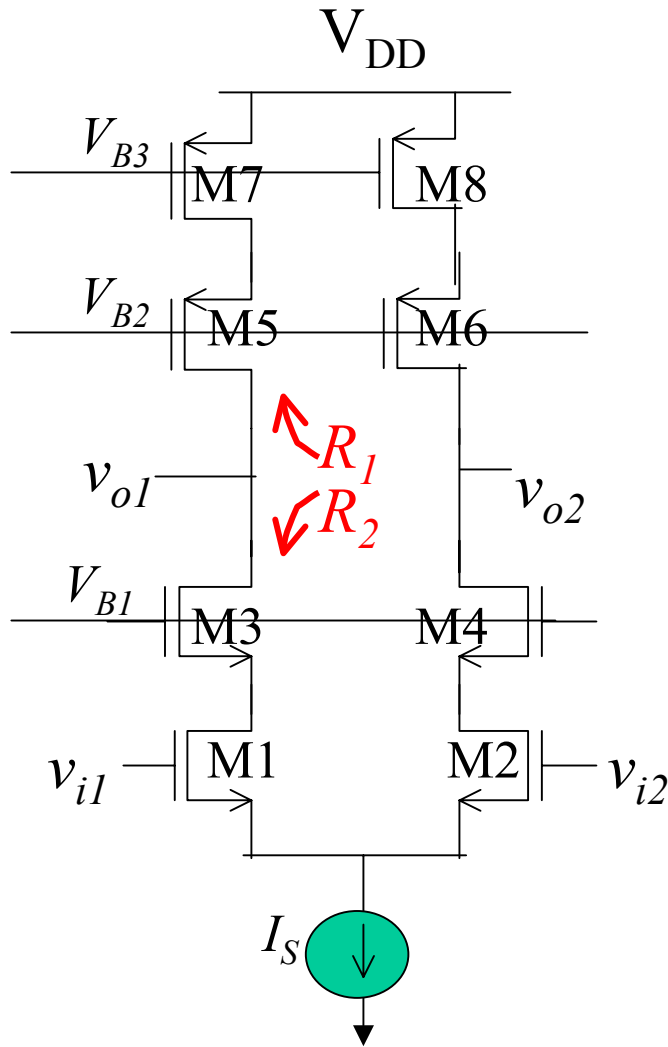

Cascode increases the output resistance significantly

$$R_1 = (g_{m5} r_{o7}) r_{o5}$$

$$R_2 = (g_{m3} r_{o1}) r_{o3}$$


$$A_v = - \frac{g_{m1}}{(g_{m5} r_{o7}) r_{o5} + (g_{m3} r_{o1}) r_{o3}}$$

Stacking transistors reduces the voltage swing

TELESCOPIC CASCODE

Gilbert Cell

2 Quadrant Multiplier

 

$$\frac{v_o}{v_i} = -g_m R_D$$

$$v_o = -g_m R_D v_i$$


$$v_o = -f(V_c) R_D v_i$$

$$v_o = -\alpha V_c R_D v_i$$

Assuming $g_m = \alpha V_c$

Also functions as Variable Gain Amplifier (VGA)

The transfer function

 

$$v_o = -\alpha V_c R_D v_i$$


It is two quadrant multiplier
Because V_c can't be negative

Note that V_c is the DC voltage
and not the AC small signal
voltage

In order to build the 4 quadrant multiplier v_c should be AC voltage

Construct two VGAs and combine the output!

Gilbert Multiplier

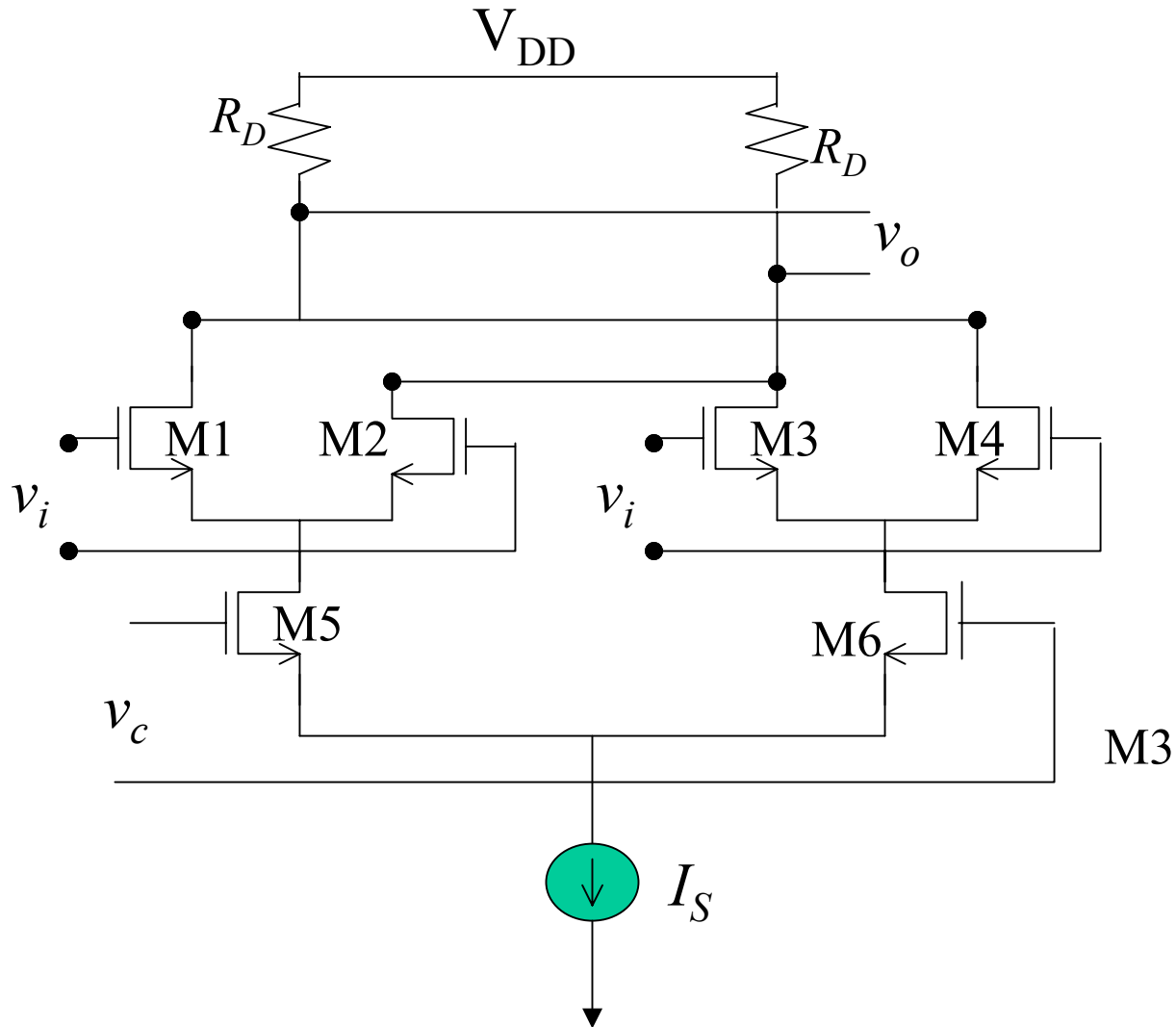

The circuit analysis

$$v_o = R_D(i_{d1} + i_{d4}) - R_D(i_{d2} + i_{d3})$$

Case 1: $v_c = 0$, $v_i \neq 0$; then $i_{d1} = -i_{d4}$ and $i_{d2} = -i_{d3}$ Hence $v_o = 0$

Case 2: $v_i = 0$, $v_c \neq 0$; then $i_{d1} = i_{d2}$ and $i_{d3} = i_{d4}$ Hence $v_o = 0$

Case 3: $v_i \neq 0$, $v_c \neq 0$;

$$\Delta g_{m1} = \Delta g_{m2} = \alpha \frac{v_c}{2} \qquad \Delta g_{m3} = \Delta g_{m4} = -\alpha \frac{v_c}{2}$$


$$i_{d1} + i_{d4} = \frac{v_i}{2} (\Delta g_{m1} - \Delta g_{m4}) = \frac{v_i}{2} \left(\frac{\alpha v_c}{2} + \frac{\alpha v_c}{2} \right) = \frac{\alpha v_i v_c}{2}$$

$$i_{d2} + i_{d3} = -\frac{v_i}{2} (\Delta g_{m2} - \Delta g_{m3}) = -\frac{v_i}{2} \left(\frac{\alpha v_c}{2} + \frac{\alpha v_c}{2} \right) = -\frac{\alpha v_i v_c}{2}$$

$$v_o = \alpha R_D v_i v_c$$


The circuit acts as 4 quadrant multiplier for small signal v_i , v_c

Transfer curves

 


Balanced Modulator

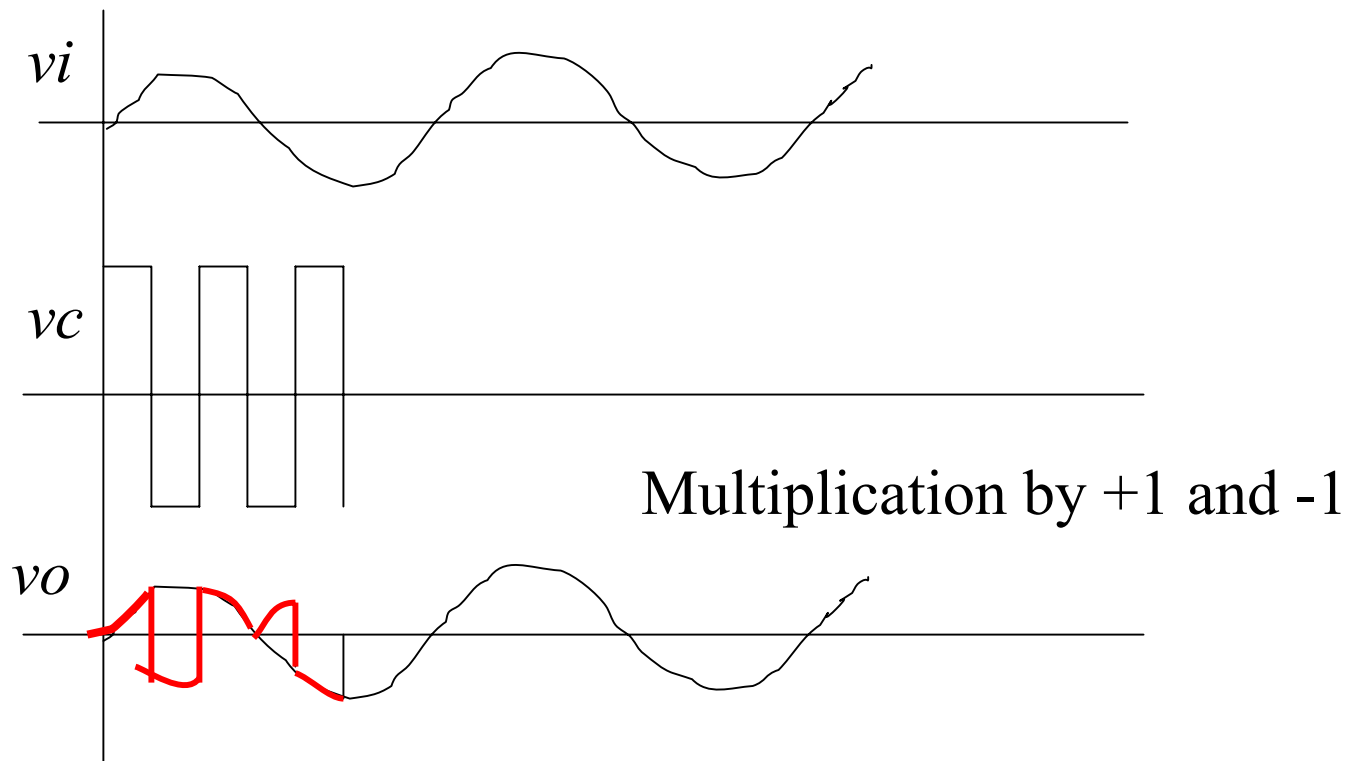Among v_c and v_i , when one of them is small signal and the other is large signal square wave, the circuit acts like a modulator




Phase Detector

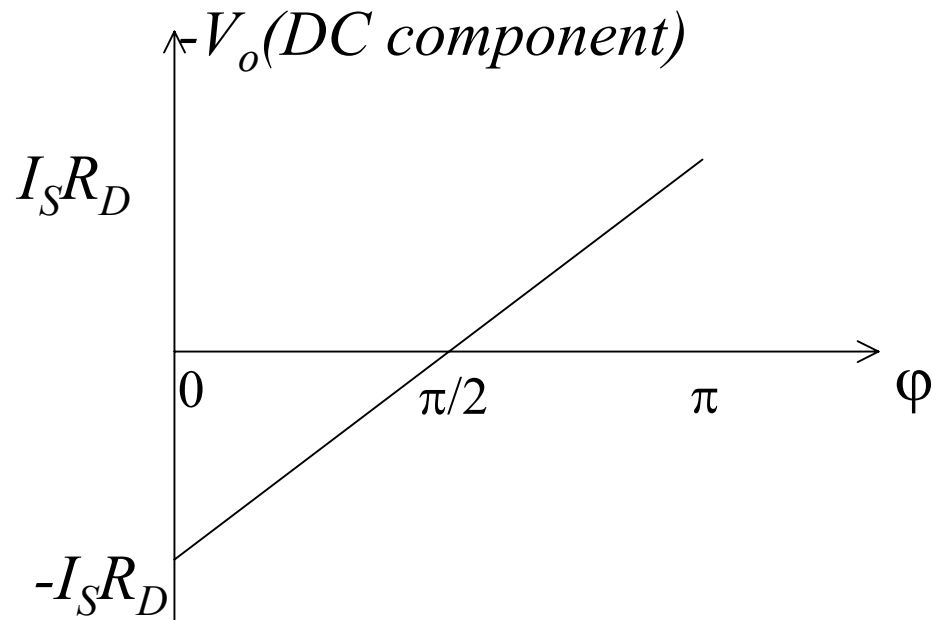When both v_i and v_c are large signal square waves, the circuit functions as phase detector with the DC component of the output voltage proportional to the phase difference



Design of 2 stage OPAMP

Ideal OPAMP

 

Infinite differential gain

Infinite input impedance

Zero output impedance

Zero input current

Zero common mode gain


Unfortunately Ideal OPAMP does not exist in reality!

Further attempts to reach ideality with these parameters will have trade off with respect to speed, power, voltage swings etc

We will treat OPAMP as a “high gain differential amplifier” designed with an adequate performance metrics for a given application at hand

Parameters of interest-Open loop gain

 OPAMPs are invariably used with closed loop negative feedback



For an ideal OPAMP ($A_v = \infty$), the closed loop gain can be set by only resistance ratio


$$\frac{v_o}{v_i} = 1 + \frac{R_2}{R_1}$$

Suppose $R_2/R_1 = 9$ and $A_v \neq \infty$ and it is required to have less than 0.1% error in the gain. Then what is the minimum A_v required?

$$\frac{v_o}{v_i} = 1 + \frac{R_2}{R_1} \left(1 - \frac{R_1 + R_2}{R_1} \frac{1}{A_v} \right)$$

For gain error $< 0.1\%$, the open loop gain $A_v > 10,000$

 Parameters of interest-small signal bandwidth



The open loop gain drops at higher frequency resulting in an increased error for the closed loop feedback system

Also the large signal settling time for the closed loop system depends on the open loop unity gain frequency


$$\tau = \frac{A_{CL}}{A_v(0)\omega_{3dB}} = \frac{A_{CL}}{\omega_U}$$

Parameters of interest-slew rate

Determines the large signal behaviour

It gives the highest rate of change of input beyond which the output does not respond instantaneously

Need very large slew rate for linearity

 

Parameters of interest

Output swing: Trade off between O/P swing, bias current and gain

Linearity:

Differential implementation to suppress even harmonics

Allow significant open loop gain so that closed loop feedback system achieves required linearity

Noise : Thermal noise and $1/f$ noise

Offset : Systematic and Random offset


Output load : Typical on-chip OPAMP applications mostly have very low capacitive load $< 1\text{pF}$

Stand alone OPAMPs may have to drive high capacitive and low resistance loads


Basic 2 stage OPAMP

Most of the OPAMP designs have two gain stages

 Unless absolutely desired, more gain stages should be avoided
Since the frequency compensation becomes complex due to
Multiple dominant poles




2 pole system response

 

$$H(s) = \frac{1}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)}$$

If $Av(0)$ is very large and if ω_{p2} is close to ω_{p1} , Then it is likely that at at some frequency ω_x , the phase shift will be -180° but the gain will still be greater than unity

 Implication in closed loop negative feedback system



At DC and low frequency there is a phase shift -180° between the Input v_i and the output v_o
(This is due to the inversion between Gate and Drain voltage of Transistor)

If $A_v(\omega)$ is a two pole transfer function, the poles introduce and additional phase shift of -180° at ω_x

The negative feedback system gets converted to a positive feedback system!!

The system becomes unstable and oscillatory

Pole splitting

Split the nearby poles far apart by some technique



By the time the second pole is reached the gain has already dropped below unity

The closed loop feedback system becomes a stable system

The phase margin is defined as


$$PM = \phi(\omega_t) + 180^\circ$$

PM should be positive for stability

  

Positive Zero can be more dangerous
 
$$H(s) = \frac{(s - z_1)}{(s + p_1)} \quad \phi = -\tan^{-1}\left[\frac{\omega}{\omega_{z1}}\right] - \tan^{-1}\left[\frac{\omega}{\omega_{p1}}\right]$$




Positive zero can make the system unstable

If the positive zero exists nearby dominant pole, then cancel the zero

Negative zero is good

$$H(s) = \frac{(s + z_1)}{(s + p_1)}$$
 
$$\phi = \tan^{-1} \left[\frac{\omega}{\omega_{z1}} \right] - \tan^{-1} \left[\frac{\omega}{\omega_{p1}} \right]$$



Negative zero can increase PM


First stage for the 2 stage OPAMP

The first stage should do two tasks

Produce reasonably large gain


Perform differential to single ended conversion

 This is done using differential amplifier with active current mirror load to enhance the gain



Active current mirror adds currents in two branches and doubles the gain while performing differential to single ended conversion


Second stage for the 2 stage OPAMP

 

PMOS common source amplifier
with the current source load

C_{comp} performs frequency compensation

Two stage OPAMP circuit

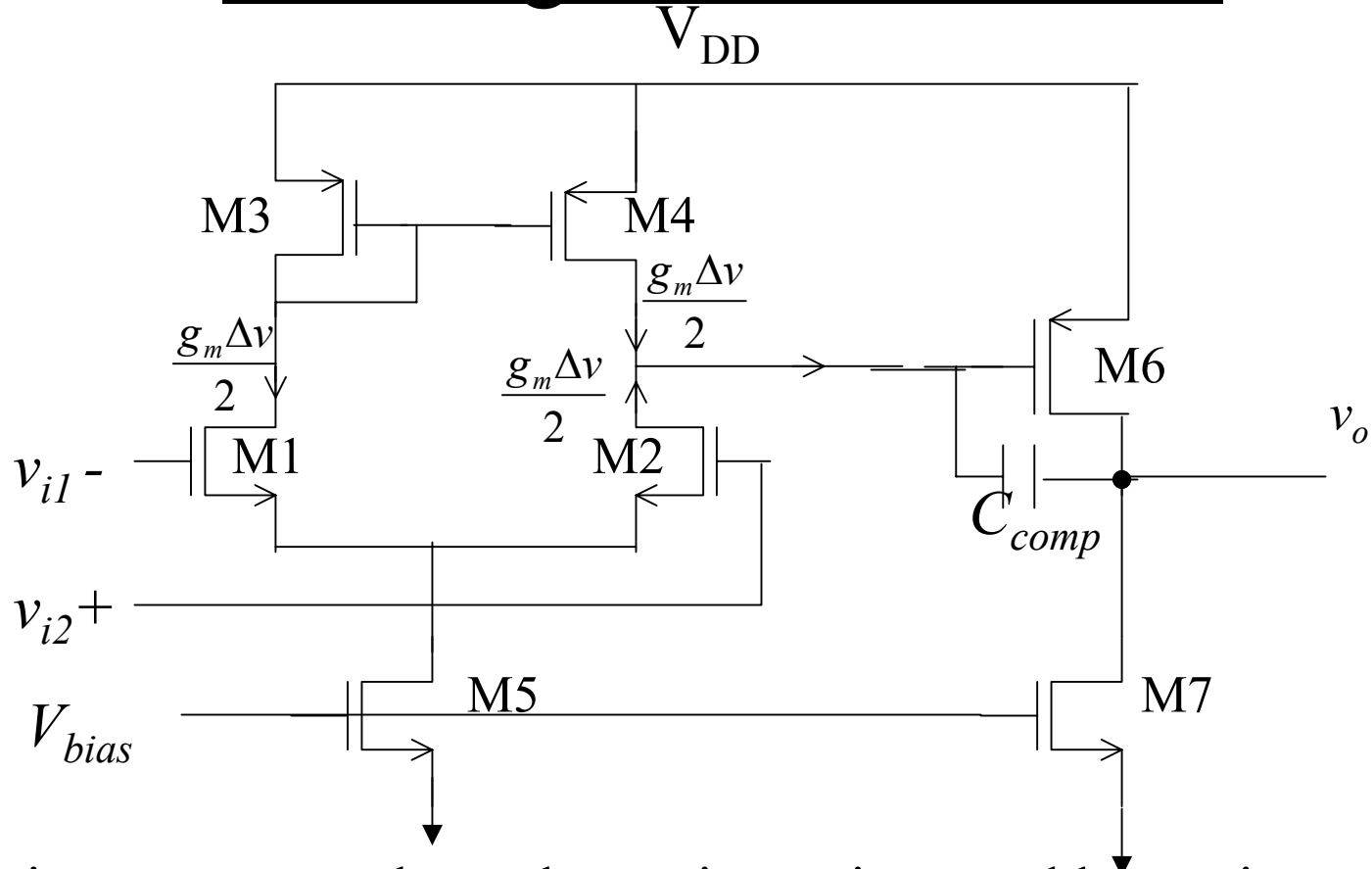


The input v_{i2} goes through two inversions and hence is +ve i/p

The input v_{i1} goes through one inversions and hence is -ve i/p

Note that the AC voltages at drain of M1 and M2 will be quite different

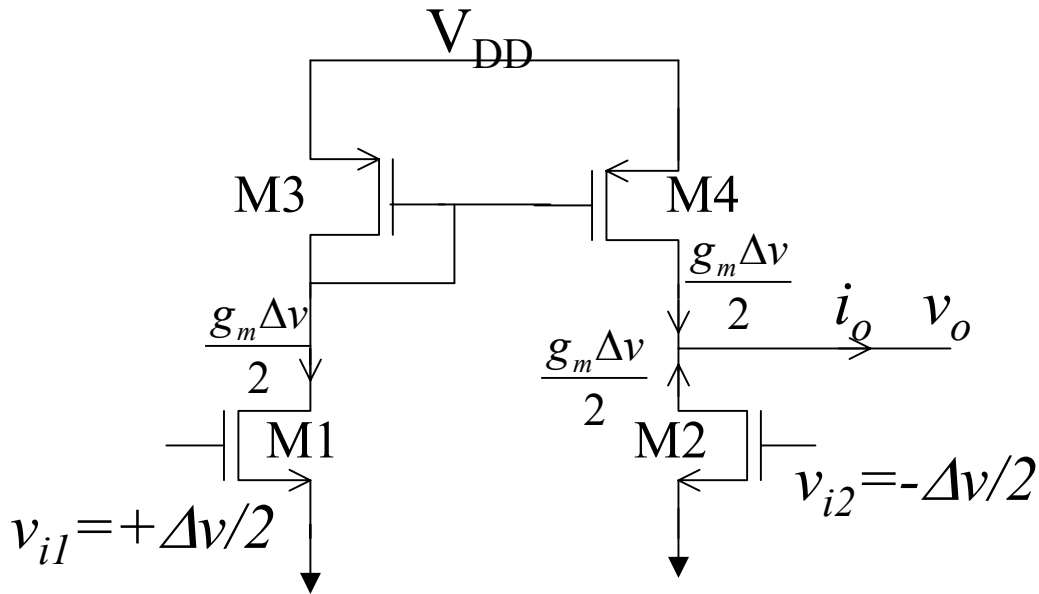First stage Low Frequency Differential Gain



$$g_{m1} = g_{m2} = g_m$$

$$i_o = g_m \Delta v$$


$$R_o = \frac{1}{G_o}$$

$$R_o = \frac{1}{g_{o2} + g_{o4}}$$

$$v_o = i_o R_o = \frac{g_m \Delta v}{g_{o2} + g_{o4}}$$

$$A_1 = \frac{v_o}{\Delta v} = \frac{g_m}{g_{o2} + g_{o4}}$$

 Second stage Low Frequency Differential Gain



Common source PMOS amplifier
with current source load

$$A_2 = \frac{v_o}{v_i} = - \frac{g_{m6}}{g_{o6} + g_{o7}}$$

Combined two stage differential response

$$A_v(0) = -\frac{g_m}{g_{o2} + g_{o4}} \frac{g_{m6}}{g_{o6} + g_{o7}}$$

$$A_v(0) = -\sqrt{\mu_n C_{ox} \frac{W}{L} I_{d1}} \frac{1}{I_{d1}(\lambda_2 + \lambda_4)} \sqrt{\mu_p C_{ox} \frac{W_6}{L_6} I_{d6}} \frac{1}{I_{d6}(\lambda_6 + \lambda_7)}$$

$$A_v(0) = -\frac{1}{I_d} C_{ox} \frac{W}{L} \sqrt{\mu_n \mu_p} \frac{1}{(\lambda_2 + \lambda_4)(\lambda_6 + \lambda_7)} \quad \text{For } I_{d1} = I_{d6}$$


$$A_v(0) = -\frac{2}{(\lambda_2 + \lambda_4)(V_{gsn} - V_{tn})} \frac{2}{(\lambda_6 + \lambda_7)(V_{gsp} - V_{tp})}$$

For high gain either use small I_d or large device dimension


Small I_d impacts slew rate, large W/L impacts area and input capacitance

First stage Common mode Gain

 For matched devices
 $V_x = V_y$, and hence
we can short these




$$g_{m1} = g_{m2} = g_m$$

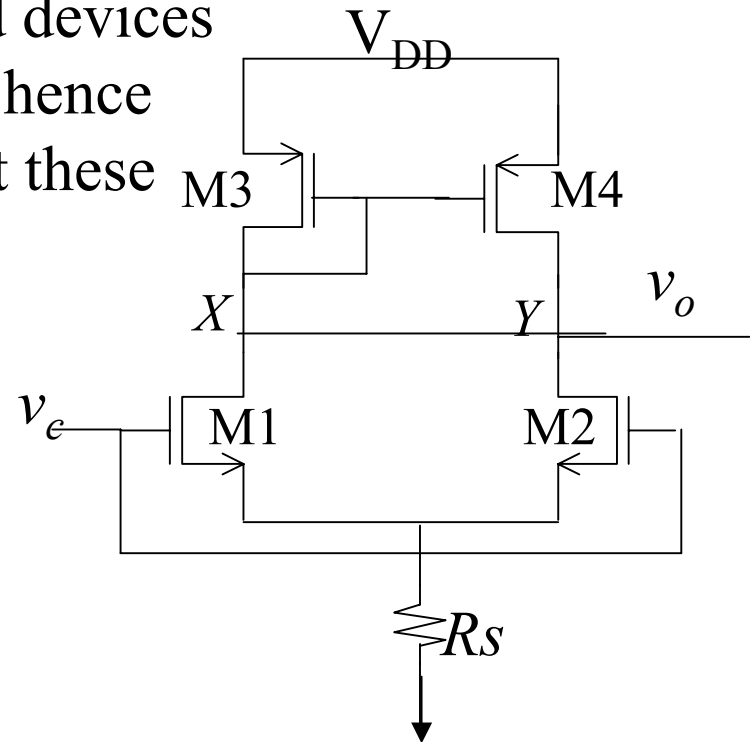

$$g_{m1} = g_{m2} = g_m$$

This brings M1 in parallel M2 and M3 in parallel M4

Equivalent circuit for CM response

 

This configuration now looks like common source amplifier with source degeneration R_S and drain Resistance $R_D = 1/2g_{m3/4}$

$$Ac_1 = -\frac{R_D}{R_S} = -\frac{1}{2g_{m3/4}R_S}$$

The second stage simply amplifies this further

The two stage common mode gain is

$$Ac = Ac_1 Ac_2 = -\frac{1}{2g_{m3/4}R_S} \frac{g_{m6}}{g_{o6} + g_{o6}}$$


Common Mode Rejection Ratio

$$CMRR = \frac{A_d}{A_c} = \frac{g_{m1} / (g_{o1} + g_{o2})}{1 / 2g_{m3/4}R_s}$$

$$CMRR = \frac{2g_{m1}g_{m3}R_s}{g_{o1} + g_{o2}}$$

CMRR is essentially determined by the first stage

High frequency equivalent circuit

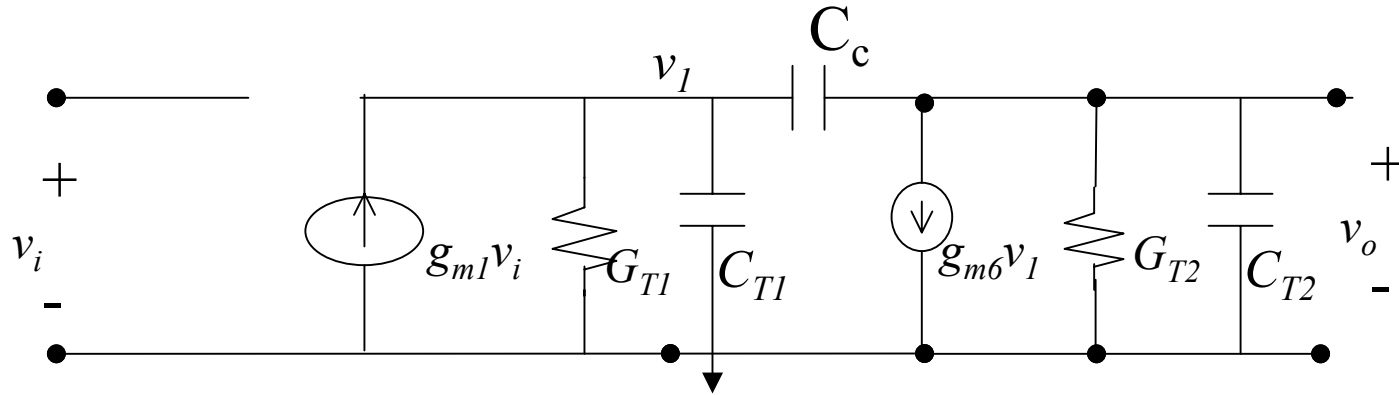

$$G_{T1} = 1/R_{T1} = g_{o2} + g_o$$

$$G_{T2} = 1/R_{T2} = g_{o6} + g_{o7}$$

$$C_{T1} = C_{db2} + C_{db4} + C_{gs6}$$

$$C_{T2} = C_{db6} + C_{db7} + C_L$$

$$C_C = C_{gd6} + C_{comp}$$

High frequency Response

Writing the nodal equations for equivalent circuit and solving for the gain, we obtain poles and one zero

$$p_1 = -\frac{1}{g_{m6} R_{T1} R_{T2} C_c}$$
$$p_1 = -\frac{g_{m6} C_c}{C_{T1} C_c + C_{T2} C_c + C_{T1} C_{T2}} \approx \frac{g_{m6}}{C_{T1} + C_{T2}}$$
$$z_1 = \frac{g_{m6}}{C_c}$$

p_1 needs to be made a dominant pole by appropriately choosing the compensation capacitance

z_1 is a positive zero that can impact stability

Pole splitting and choice of C_c

$$p_1 = -\frac{g_{m1}}{g_{m1}g_{m6}R_{T1}R_{T2}C_c} = -\frac{1}{|Av(0)|} \frac{g_{m1}}{C_c}$$

C_c should be chosen such that the unity gain frequency $\omega_u \ll p_2$ to get adequate Phase Margin

Also for the single pole response (with p_1), the unity gain frequency is given by

$$\omega_u = \frac{g_{m1}}{C_c}$$

$$C_c = \frac{g_{m1}}{\omega_u}$$

Feed forward zero


The positive zero location is very close to ω_u and this will degrade the phase margin

$$z_1 = \frac{g_{m6}}{C_c}$$

If $g_{m6} \leq g_{m1}$ then $z_1 \leq \omega_u$

This zero should be cancelled, otherwise the system becomes unstable

 Zero cancellation with nulling resistance



$$\frac{V_o}{V_i} = \frac{R_2 [1 + sC_c (R_1 + R_z)]}{R_1 + R_2 + sC_c (R_1 R_2 + R_1 R_z + R_2 R_z)}$$

$$z_1 = \frac{1}{C_c (-R_1 - R_z)}$$


$$z_1 = \frac{1}{C_c (1/g_{m6} - R_z)}$$

Qualitatively, adding R_z makes i_2 weaker at any given frequency compared to the value of i_1 , i.e. the effect of feed forward zero is suppressed

When $R_z = 1/g_{m6}$, the zero is at infinity

For $R_z > 1/g_{m6}$, the zero moves to the left half plane improving PM (lead compensation)

Zero cancellation with PMOS

 

The PMOS transistor M_z is biased such that it is in linear region
 $V_{gs} - V_t > V_{ds}$

The linear region R_z is

$$R_z = \frac{1}{\mu_n C_{ox} \frac{W_z}{L_z} (V_{gsz} - V_{tz})}$$


For M_6 ,

$$\frac{1}{g_{m6}} = \frac{1}{\mu_n C_{ox} \frac{W_6}{L_6} (V_{gs6} - V_{t6})}$$


The R_z is able track $1/g_{m6}$ very well in spite of through process variations

OPAMP Performance Metrics

Slew rate

 

 When a step input is applied, in order for the output to follow the input the capacitance C_c should be charged to the new value



The maximum current that is available to charge this capacitor is the bias current I_s

Hence the slew rate, i.e. the maximum rate of change of output is $= I_s/C_c$

Random Input offset

Random offset arises due to transistor mismatch in the supposedly matched differential pair (first stage)

The effect of offset is modeled as an input referred offset voltage in series with the input terminal of ideal OPAMP

$$V_{OS} = \Delta V_{t1,2} + \Delta V_{t3,4} \frac{g_{m3}}{g_{m1}} + \frac{(V_{gs} - V_t)_{1,2}}{2} \left(-\frac{\Delta W/L_{1,2}}{W/L_{1,2}} - \frac{\Delta W/L_{3,4}}{W/L_{3,4}} \right)$$

$$\Delta V_{t1,2} = V_{t1} - V_{t2}$$


$$V_t = \frac{V_{t1} + V_{t2}}{2}$$

$$\Delta(W/L) = (W/L)_1 - (W/L)_2$$

$$W/L = \frac{W/L_1 + W/L_2}{2}$$

Offset voltage in series with the gate of M1

Thermal and $1/f$ noise

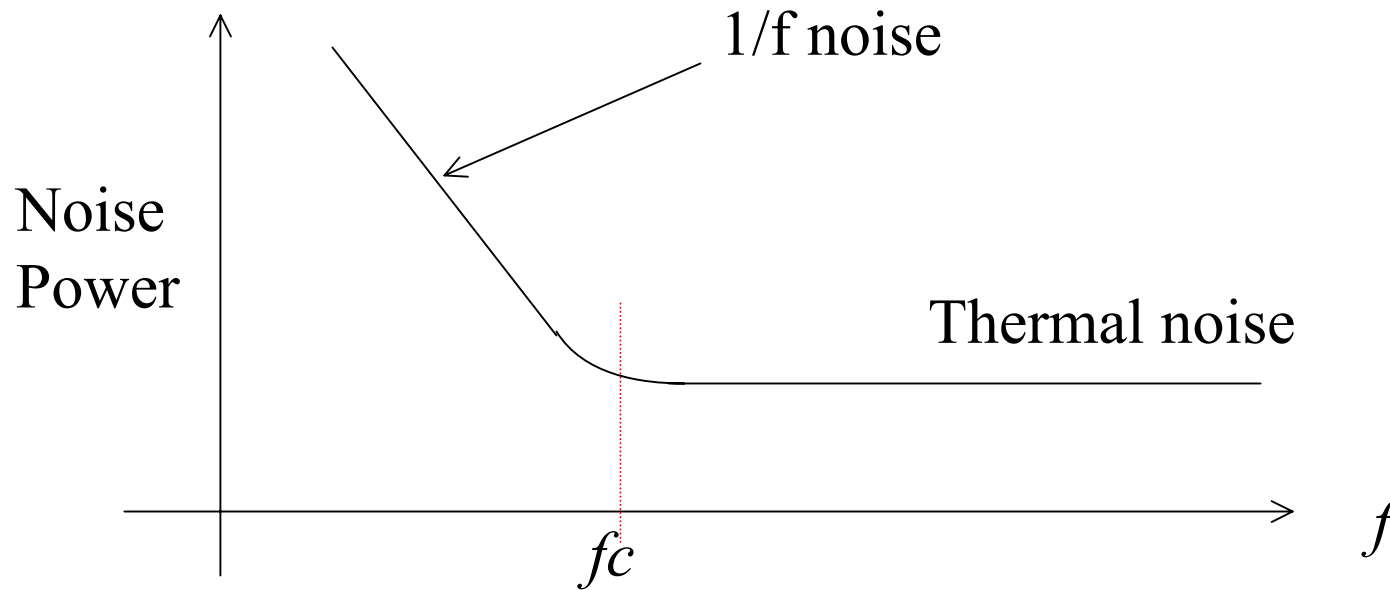


Thermal noise is due to random fluctuation of carriers in a resistor
Higher bias current helps decrease thermal noise

The $1/f$ noise or flicker noise is due to interface states in MOSFET
 f_c is $1/f$ corner frequency in the range of 500KHz

Flicker ($1/f$) noise due to interface states

 Flicker noise is due to trapping and detrapping of carriers from the interface states



The random trapping and detrapping of carriers from the channel creates fluctuations in drain current

$$\overline{v_n^2} = \frac{K}{C_{ox}WL} \frac{1}{f}$$


Noise varies as $1/A$ due to averaging effect

Noise varies as $1/C_{ox}$ since the fraction of charge is less


Noise varies as $1/f$ since traps have certain time constant

MOSFET versus BJT

 The BJT circuits are not affected by flicker noise!



 The current flow path does not encounter any kinds of defects since the current flow is entirely in the bulk of Silicon



The current flow path is abutting the interface defects region

Dual gate vs Single gate technology

- Historically CMOS technology had a single gate type
- Both NMOS and PMOS had n^+ poly-Si gate
- This was because the poly thickness was fairly large (more than $0.5\mu\text{m}$) and it was difficult to activate such poly using implant and annealing
- Hence in-situ doping (i.e. doping during deposition process itself) was invariably used
- As a result both NMOSFET and PMOSFET had n^+ gate
- Almost all the recent technologies use dual poly gate i.e. n^+ gate for NMOS and p^+ PMOS
- The poly is fairly thin ($0.2\mu\text{m}$ or less) and hence the activation is done during s/d implant and anneal step itself

The problem of PMOS V_t setting

$$V_t = V_{fb} + 2\phi_b + \frac{T_{ox} \sqrt{4\epsilon_s q N_a \phi_b}}{\epsilon_{ox}}$$

The V_{fb} term depends on gate material

For NMOS with n^+ gate, $V_{fb} \sim -0.9V$, $2\phi_b = 0.7V$, the third term is positive for p-well And hence V_t can be set to low value


For PMOS with p^+ gate, $V_{fb} \sim +0.9V$, $2\phi_b = -0.7V$, the third term is negative for n-well And hence V_t can be set to low value

For PMOS with n^+ gate, $V_{fb} \sim -0.1V$, $2\phi_b = -0.7V$
hence V_t setting on n-well becomes very difficult

Hence in a single gate technologies the PMOS well was typically counter doped to bring V_t to manageable levels. This process in turn pushes the inversion layer away from interface


Buried vs Surface Channel PMOSFET

Buried channel PMOSFET

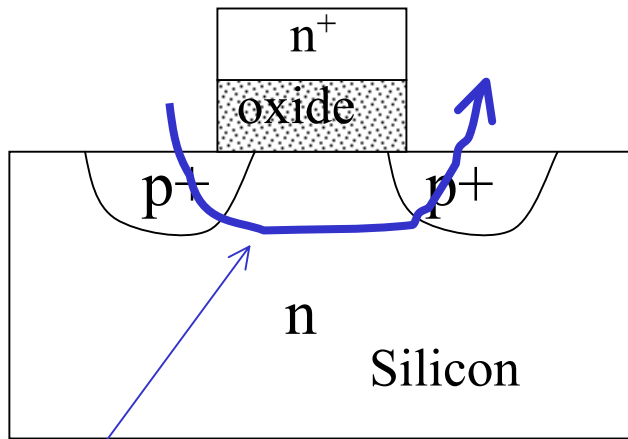

Current flows away from interface

Surface channel PMOSFET

 

Current flows at the interface

The flicker noise performance of buried channel PMOS is similar to BJT with *almost* zero flicker noise

However the surface channel PMOS is no better than the surface channel NMOSFET

Output Stage

Output stage requirement

Capable of providing high output current to drive large loads


However, the DC bias current should be low to avoid Static power dissipation

The output impedance should be very low


Source follower can serve the purpose

Class AB NMOS and PMOS source follower (push-pull) stage is a preferred configuration


Output stage class AB

 

 V_{GG1} and V_{GG2} are set such that M1B and M2B are biased just above V_t to avoid cross over distortion



Biasing the output stage

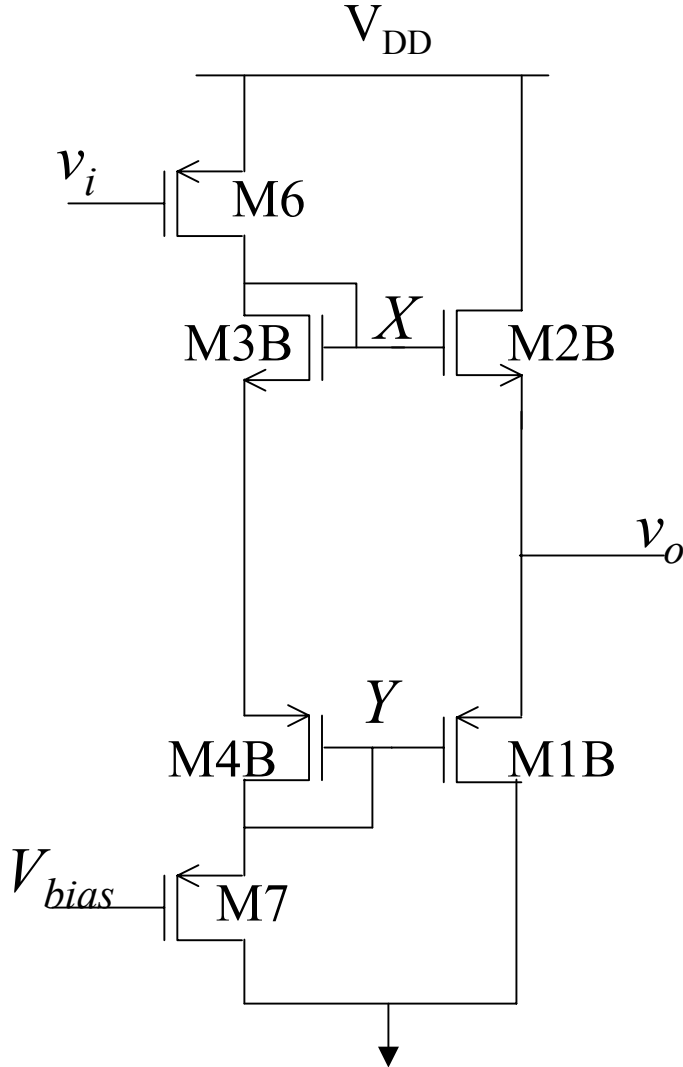

M3B and M4B are diode connected NMOS and PMOS respectively

$$V_{xy} = V_{gs3b} + V_{gs4b}$$

$$V_{xy} = V_{tn3b} + V_{tp4b} + 2\Delta V$$

Choose the sizes of M3B and M4B such that V_{xy} is just above the two V_t s of M1B and M2B to avoid cross over distortion

Folded cascode gain

$$A_v(0) = \frac{g_m}{\frac{g_{o2} + g_{o9}}{g_{m4}r_{o4}} + \frac{g_{o5}}{g_{m7}r_{o7}}}$$

$$A_v(0) = \frac{(g_m r_o)^2}{3} \quad \text{Assuming all } gm \text{ and } ro \text{ are identical}$$

The dominant pole is associated with the output

C_L provides frequency compensation

Increasing C_L improves phase margin

OTA and OPAMP Circuits

Operational Transconductance Amplifier

OTA is essentially an OPAMP without an output buffer


An OTA without output buffer can drive only capacitive loads

OTA is an amplifier where all nodes except I/O are low impedance nodes. Hence the two stage OPAMP configuration minus buffer is NOT an OTA since the drain of M4 is high impedance node

As the name suggests, the quantity of interest in OTA is not the voltage gain, but it is

$$G_m = \frac{i_{out}}{v_{i2} - v_{i1}} = \frac{i_{out}}{v_i}$$

The basic OTA circuit configuration

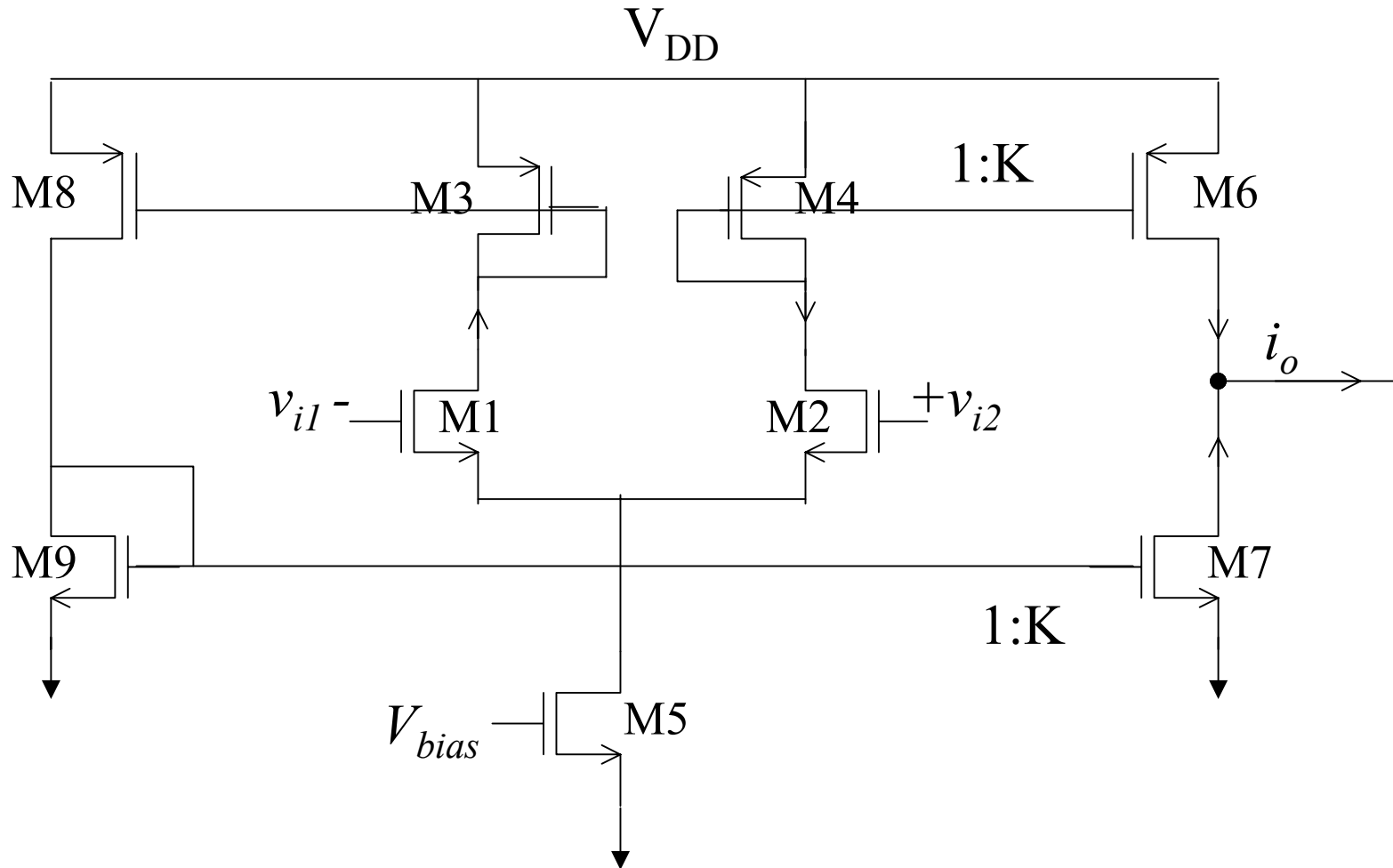

Gm expression

Assumptions

$$g_{m1} = g_{m2} \text{ and } (W/L)_3 = (W/L)_4 = (W/L)_8$$

$$(W/L)_6 = K(W/L)_4 \text{ and } (W/L)_7 = K(W/L)_9$$

Then

$$i_o = i_{d6} - i_{d7} = K(i_{d4} - i_{d9}) = K(i_{d2} - i_{d1})$$

$$i_o = K \left(g_m \frac{v_i}{2} + g_m \frac{v_i}{2} \right) = K g_m v_i$$

$$G_m = \frac{i_o}{v_i} = K g_m$$

Transconductance G_m

G_m can be set by appropriate K


For a given K (i.e. after design) G_m can still be varied by setting an appropriate bias current, I_S

i.e. Filters made using OTA can be tuned by changing I_S


Output pole is the only dominant pole!

i.e. capacitive loads improve the phase margin

The symbol for OTA

 

Simple Low pass filter

 

$$v_o = i_o \frac{1}{j\omega C}$$

$$v_o = G_m (v_i - v_o) \frac{1}{j\omega C}$$


$$\frac{v_o}{v_i} = \frac{G_m / j\omega C}{1 + G_m / j\omega C}$$

$$\frac{v_o}{v_i} = \frac{1}{1 + j\omega \left(\frac{C}{G_m} \right)}$$

Single pole low pass filter with a cut off frequency of

$$\omega_p = G_m / C$$

Simple High pass filter

 

$$v_o - v_i = \frac{i_o}{j\omega C} = \frac{-G_m v_o}{j\omega C}$$


$$\frac{v_o}{v_i} = \frac{1}{1 + \frac{G_m}{j\omega C}}$$

$$\frac{v_o}{v_i} = \frac{j\omega \left(\frac{C}{G_m} \right)}{1 + j\omega \left(\frac{C}{G_m} \right)}$$

High pass filter with cut off frequency of

$$\omega_p = G_m / C$$

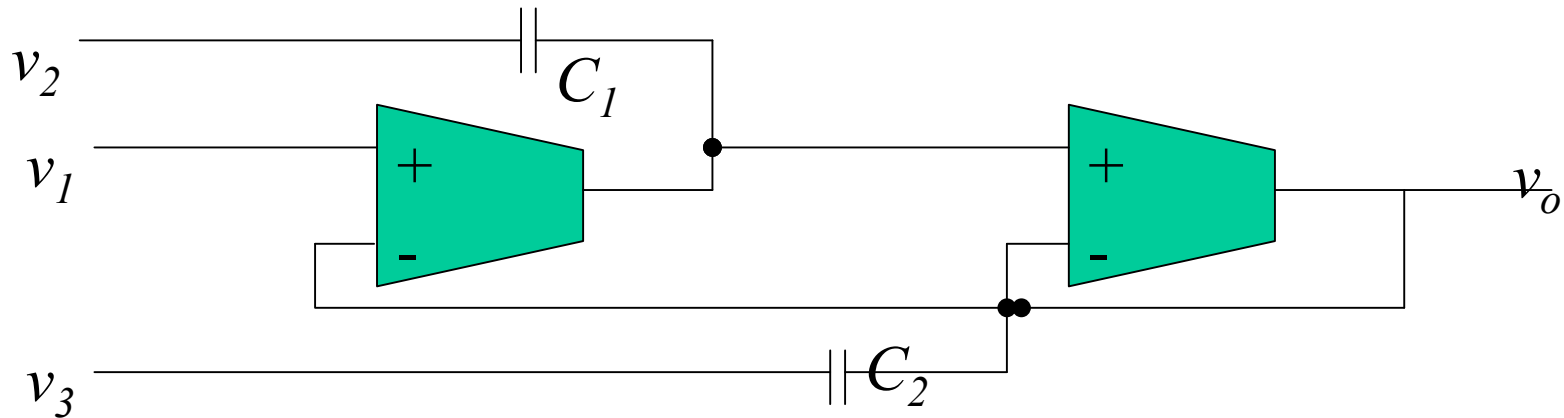
General biquadratic (biquad) configuration



Filter	Input Condition	Transfer function
Low-pass	$v_1 = v_i, v_2 = 0, v_3 = 0$	$\frac{g_m^2}{s^2 C_1 C_2 + s C_1 g_m + g_m^2}$
High-pass	$v_1 = 0, v_2 = 0, v_3 = v_i$	$\frac{s^2 C_1 C_2}{s^2 C_1 C_2 + s C_1 g_m + g_m^2}$
Band-pass	$v_1 = 0, v_2 = v_i, v_3 = 0$	$\frac{s C_1 g_m}{s^2 C_1 C_2 + s C_1 g_m + g_m^2}$
Band-reject	$v_1 = v_i, v_2 = 0, v_3 = v_i$	$\frac{s^2 C_1 C_2 + g_m^2}{s^2 C_1 C_2 + s C_1 g_m + g_m^2}$


Inverting and Noninverting amplifier

Inverting

 

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1}$$


Non inverting

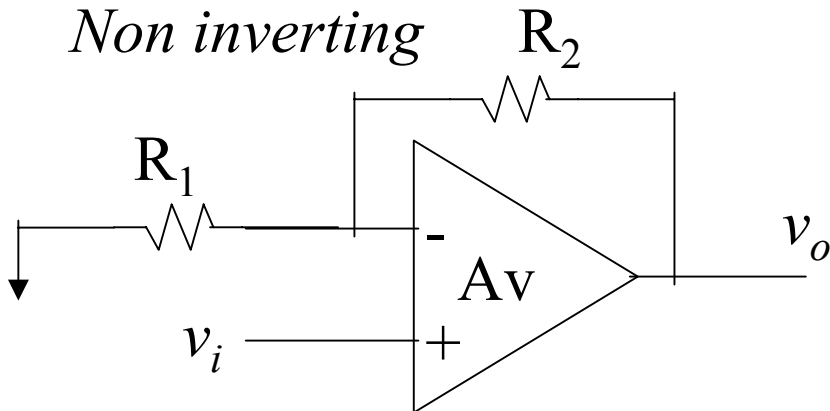

$$\frac{v_o}{v_i} = 1 + \frac{R_2}{R_1}$$


Integrator and Differentiator

Integrator

 

$$v_o = -\frac{1}{R_1 C_2} \int v_i dt$$


Differentiator

 

$$v_o = -R_2 C_1 \frac{dv_i}{dt}$$


Log and Antilog Amplifier

Log

 

$$v_o = -V_T \ln \frac{v_i}{R_1 I_o}$$

Antilog

 

$$v_o = -I_o R_1 e^{\frac{v_i}{V_T}}$$

Sample and Hold Circuit

Sample and Hold Circuit

This is an essential requirement for discrete time systems (sampled data systems)

Applications:

ADCs,


Switched capacitor filters

Comparators etc.

Requirement of discrete time operation:

1. Switches to perform sampling
2. High input impedance to sense the charge without corrupting (ideally suited for CMOS and not for BJT)


Requirements for S/H circuit

 

Advantages of MOSFET over BJT as a switch

 1. ON but zero current
2. S/D voltages are not pinned to gate voltage
3. Conducts well in both the directions

But it still does NOT perform Ideal Sampling function!



MOSFET switch issues

Finite acquisition time

Finite bandwidth in sample mode

DC offset in sample mode (V_{os1})

Finite aperture delay (Δt)



Pedestal error (V_{os2}) : (Charge injection and Clock feed through)

Droop in Hold mode

For $t > t_H + \Delta T$

$$V_o(t) = V_i(t_H + \Delta t) + V_{os1} + V_{os2} + \Delta V(t)$$

MOSFET sampling

  


Acquisition time $\tau = R_{on} C_H$ (RC time constant of channel)

$$R_{on} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{gs} - V_t)} \quad \text{In linear region}$$

Bandwidth in sample mode = $1/\tau$

$V_{os1} = 0$ provided MOSFET is in linear region (i.e. $V_{in} < \phi_H - V_t$)
 Otherwise $V_O \neq V_{in}$ instead $V_O = \phi_H - V_t$

Channel charge injection

 

When switch is ON, channel charge is

$$Q_c = WLC_{ox}(\phi_H - V_i - V_t)$$

When ϕ goes low, the switch turns off and the channel charge must exit out

An approximation is, 50% of this charge Goes to the out put node

The fraction that goes to output node is a complex function of parameters such as impedance seen at each node to the ground, clock transition time etc.
(ex: if clock makes slow transition all the charge could be absorbed at input)

$$\Delta V = -\frac{Q_c}{2C_H}$$

$$\Delta V = -\frac{WLC_{ox}(\phi_H - V_i - V_t)}{2C_H}$$

Effect of charge injection

$$V_o = V_i - \frac{WLC_{ox}(\phi_H - V_i - V_t)}{2C_H}$$

V_t is impacted by body effect

$$V_o = V_i \left(1 + \frac{WLC_{ox}}{2C_H} \right) + \gamma \frac{WLC_{ox}}{2C_H} \sqrt{2\phi_b + V_i} - \frac{WLC_{ox}}{2C_H} (\phi_H - V_{t0} + \gamma \sqrt{2\phi_b})$$

\uparrow
Gain error

\uparrow
Nonlinearity

\uparrow
DC offset

Speed-Precision product : $\tau \Delta V$


$$\tau \cdot \Delta V = \frac{L^2}{2\mu}$$

Interesting trade-off!

Depends only on L and is independent of transistor width and the value of the sampling capacitance

Clock feedthrough

 When the switch is being turned off, the clock transition capacitively couples to the output



$$\Delta V = (\phi_H - \phi_L) \frac{C_{ov}}{C_{ov} + C_H}$$

$$C_{ov} = nC_{ox}WL_d$$

Note: If clock makes slow transition (quasi static)
Then the clock feed through error is significantly less

Example for error values

$W=10\mu\text{m}$, $L=2\mu\text{m}$, $V_t=0.7\text{V}$, $C_{ox}=1.38\text{fF}/\mu\text{m}^2$,
 $C_{ov}=3\text{fF}$, $C_H=1\text{pF}$, $\phi_H=5\text{V}$, $\phi_H=0\text{V}$


Gain error = 1.1%

Charge injection offset = 47mV


Clock feed through offset = 15mV

Total offset = 62mV

kT/C noise

 

Equivalent ckt
in sample mode

 

$$\overline{v_n^2} = 4kTR_{on}\Delta f$$

$$H(f) = \frac{1}{1 + j2\pi fR_{on}C_H}$$

$$\overline{v_{oT}^2} = 4kTR_{on} \int_0^{\infty} \frac{1}{|1 + j2\pi fR_{on}C_H|^2} df$$


$$\overline{v_{oT}^2} = \frac{kT}{C_H}$$

$$v_{oT}(rms) = \sqrt{\frac{kT}{C_H}}$$

For $C_H = 1\text{pF}$, $T = 300\text{oK}$,
 $V_{oT}(rms) = 64.3\mu V$

The lowest limit!

Offset cancellation with dummy switch

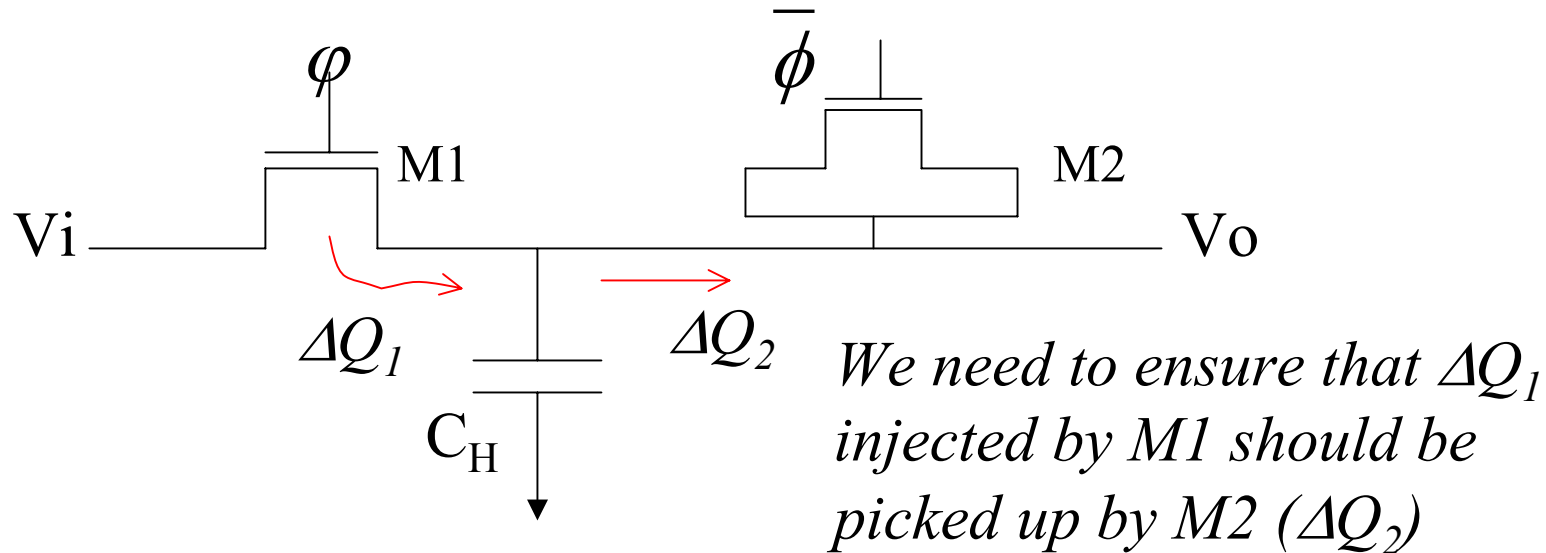

$$\Delta Q_1 = 0.5 W_1 L_1 C_{ox} (V_{DD} - V_i - V_t) \quad \Delta Q_2 = W_2 L_2 C_{ox} (V_{DD} - V_i - V_t)$$


Choose $L_1 = L_2$ and $W_2 = W_1/2$ to cancel the charge injection

Note that the clock feed through error is also cancelled


$$\Delta V_{cft} = -\Delta\phi \frac{C_{ov}}{C_{ov} + C_H} + \Delta\phi \frac{C_{ov}}{C_{ov} + C_H} = 0$$

Switched Capacitor Circuits


Switched capacitor as a resistor

 

 The Resistor takes certain amount of charge per second from node A to B resulting in a current I



S1 and S2 are non overlapping

 

In one cycle a charge $q = V_A C - V_B C$ is transferred from A to B
i.e. charge transferred per second from A to B is

$$I_{avg} = f_{clk} C (V_A - V_B) \quad I_{avg} = \frac{V_A - V_B}{1 / f_{clk} C} \quad R_{eq} = \frac{1}{f_{clk} C}$$

Switched capacitor acts like an equivalent resistance!

Provided f_{clk} is higher than signal bandwidth

Motivation for switched capacitor circuits

It is very easy to build a capacitor compared to a resistor in the CMOS Technology


The value of the capacitance does not depend on temperature

The capacitor connected to the output of an OPAMP does not impact the resistance and hence the open loop gain

Monolithic active RC filters can be built using switched capacitor circuits

In most of the switched capacitor circuits, the poles and zeros are governed by capacitance ratios rather than absolute values. The precision on capacitance ratios is significantly better compared to precision on absolute C and R

Unity gain buffer/Sampler

 


S3 open and S1, S2 closed

One plate of the capacitor is at virtual ground and hence V_i is sampled on the other plate

S1, S2 open and S3 is closed

C_H is connected to V_O and hence V_O is sampled input voltage
Further the circuit enters in holding phase with constant voltage on C_H

Inverting Amplifier

 

Initially S3 open and S1,S2 closed

Negative feedback is enabled and
Hence – input of OPAMP is at
Virtual ground. C_H samples V_i


S1 and S2 open and S3 closed

Capacitance discharges and the
charge will be transferred to C_2

$$V_o = -V_{in} \frac{C_1}{C_2}$$

From conservation of charge

Integrator

 

S1, S2 are non overlapping and are switched at a frequency of f_c


Hence there is an effective Resistance between nodes A and B

$$R_{eq} = \frac{1}{C_1 f_c}$$

$$v_o = -\frac{C_1 f_c}{C_2} \int v_i dt$$

Stray insensitive inverting integrator

ϕ_1 and ϕ_2 are non overlapping

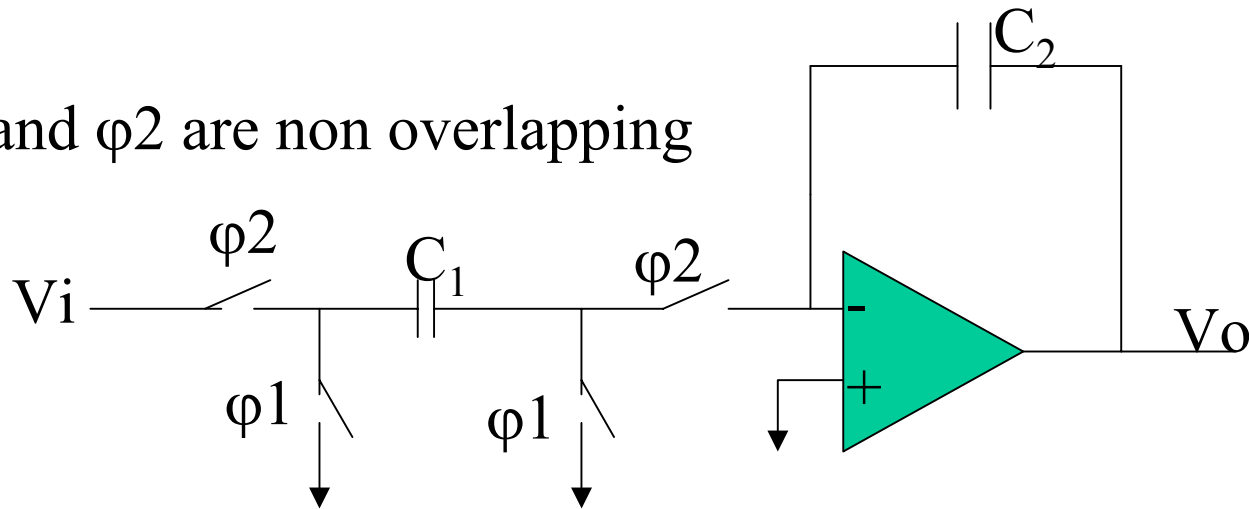

ϕ_1 is closed and ϕ_2 is open , C_1 is discharged to 0V


ϕ_1 is open and ϕ_2 is closed , a charging current flows through C_1 and C_2

At the n^{th} sampling instance

$$v_o(n) = V_o(n-1) - \frac{C_1}{C_2} v_i(n)$$

Stray insensitive noninverting integrator

ϕ_1 and ϕ_2 are non overlapping

 

ϕ_1 is closed and ϕ_2 is open , C_1 is charged to V_i



ϕ_1 is open and ϕ_2 is closed , a charging current flows through C_2 from V_o and the charge is transferred to C_2

At the n^{th} sampling instance

$$v_o(n) = V_o(n-1) + \frac{C_1}{C_2} v_i(n)$$

Integrator as versatile building block

Lossless resonator

  

$$i_L = \frac{1}{L} \int v_o dt$$

$$v_o = \frac{1}{C} \int (i_i - i_L) dt$$

Change variables


$$v_L = \frac{R^*}{L} \int v_o dt \quad v_i = i_i R^*, \quad v_L = i_L R^*$$

$$v_o = \frac{1}{R^* C} \int (v_i - v_L) dt$$

$$\tau_1 = R^* C$$

$$\tau_2 = \frac{L}{R^*}$$

Ladder filter : Low pass

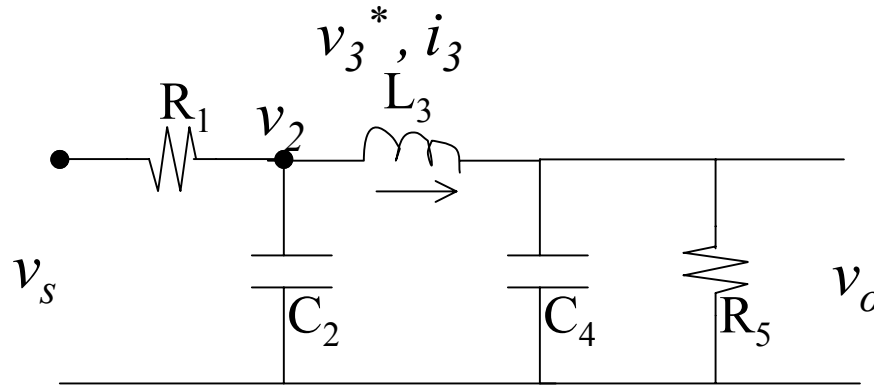

Define $v_3^* = i_3 \times R^*$ where v_3^* is scaled inductor voltage

$$v_2 = \frac{v_s}{j\omega C_2 R_1} - \frac{v_2}{j\omega C_2 R_1} - \frac{v_3^*}{j\omega C_2 R^*}$$

$$v_3^* = \frac{v_2}{j\omega L_3 / R^*} - \frac{v_o}{j\omega L_3 / R^*}$$



$$v_o = \frac{v_3^*}{j\omega C_4 R^*} - \frac{v_o}{j\omega C_4 R_5}$$

These can be realized using summing integrator

Comparator

Characteristics of comparator

  Comparator is a nonlinear circuit which generates rail to rail output for small differential input signal



Configurations:

High gain amplifier without latch

Latched comparator

Selection of A_v

The desired resolution and hence v_{imin} sets up the required gain

Suppose it needs to be used for 12 bit Flash ADC application

Let Full scale I/p=4V , 12 bit ADC \Rightarrow 4K levels


i.e. 1 LSB = 1mV and half LSB=0.5mV

If the output rail voltage is 5V

$$A_v = \frac{5}{0.5 \times 10^{-3}} = 10000$$

High gain realized in a single stage affects speed

 Suppose the gain bandwidth product is 10MHz




$$\text{Then } f_{3dB} = f_u / A_v = 1\text{KHz}$$

$$\tau = 1 / 2\pi f_{3dB}$$

$$\tau = 160 \mu\text{sec}$$

Instead of using a single stage, cascaded stages with lower individual gain but constant overall gain can be used to improve the speed

Time constants of cascaded stage

 

$$A_T(j\omega) = \frac{A_{vn}(0)^N}{\left(1 + \frac{j\omega}{\omega_{oN}}\right)^N}$$


For an n stage cascade, each stage can have significantly lower gain in conjunction with higher bandwidth

The gains get multiplied, whereas the time constants add up

$$\frac{\omega_{oN}}{\omega_{o1}} = A_T(0)^{\frac{N-1}{N}} \sqrt{2^{\frac{1}{N}} - 1} \quad \omega_{oN} \text{ is 3dB bandwidth}$$


For $N=3$, $\omega_{0N}/\omega_{01} = 236$ and $A_v(0)=21.5$

Offset cancellation

 

The offset impacts performance

 If offset is not cancelled then the precision is affected




The concept of cancellation:

Sample the offset voltage

Store the offset voltage either at the input or output

Output series cancellation

 

Offset store: S1, S4 open and S2, S3 closed


$V_c = AV_{os}$, The amplified offset voltage is stored on C

Amplify: S2, S3 open and S1, S4 closed

$$V_o = A(V_i + V_{os}) - V_c = AV_i$$

Note: If the gain is very large the OPAMP may saturate during the offset store phase

Input series cancellation

 

Offset store: S1 open and S2, S3 closed

The OPAMP is in negative feedback mode

$$V_o = V_c = -A(V_c - V_{os})$$

$$V_c = \frac{A}{1+A} V_{os} \approx V_{os}$$

Amplify: S2, S3 open and S1 closed

$$V_o = -A \left(V_i - \frac{V_{os}}{1+A} \right) \quad \text{i.e. input referred offset is reduced by a factor } 1/(1+A)$$

Sense Amplifier

Voltage Sense Amplifier


Current sense Amplifier

Latch type Sense Amplifier

Gain bandwidth analysis


Acknowledge the contributions made by Sugato Mukherjee

SRAM structure

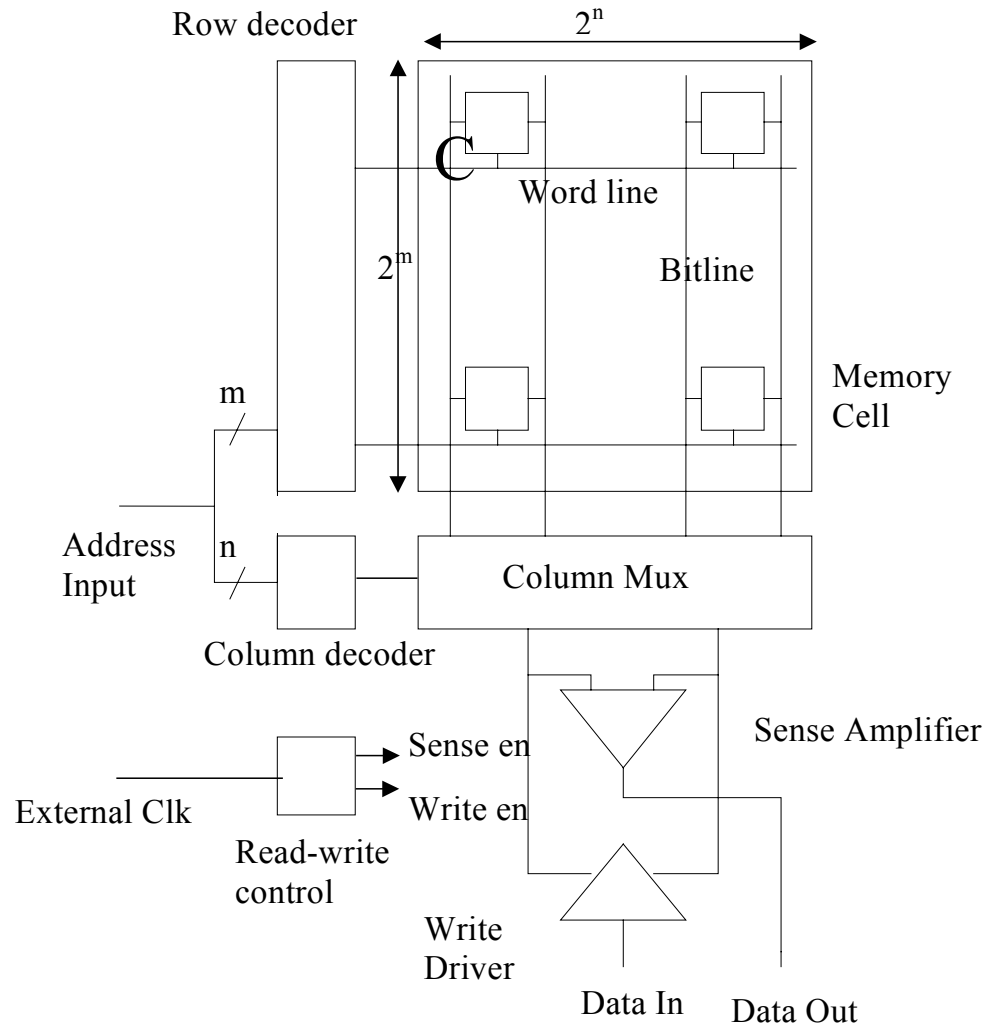

SRAM is 2 dimensional array of memory cells (C)

6T SRAM cell

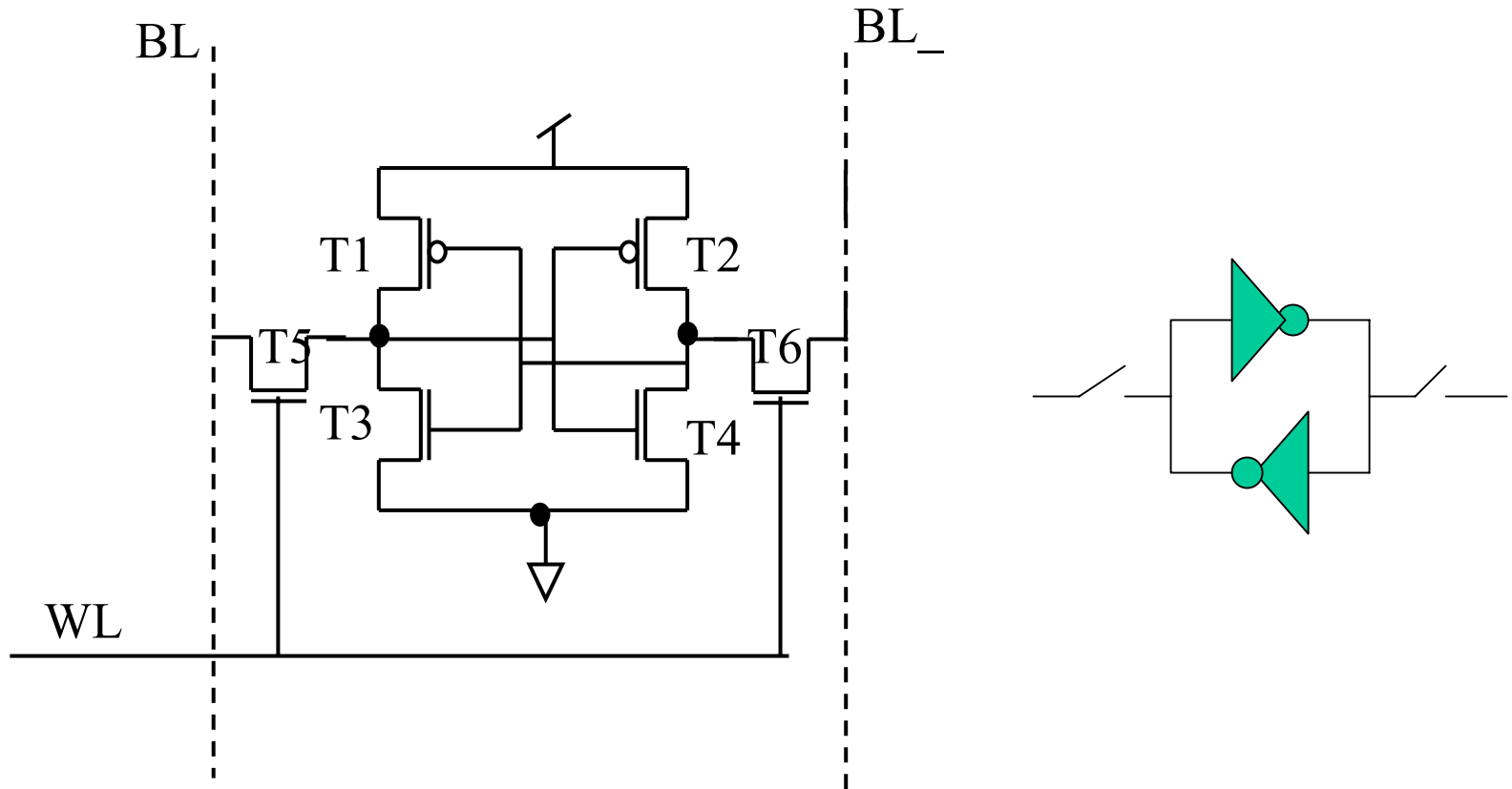

SRAM cell consists of two cross coupled inverters

SRAM Read operation


BL and BL_ are pre-charged and equalized to Vdd

WL selects the memory cell

Either BL or BL_ starts discharging through cell

Differential voltage between BL and BL_ is amplified by the sense amplifier

Role of sense amplifier

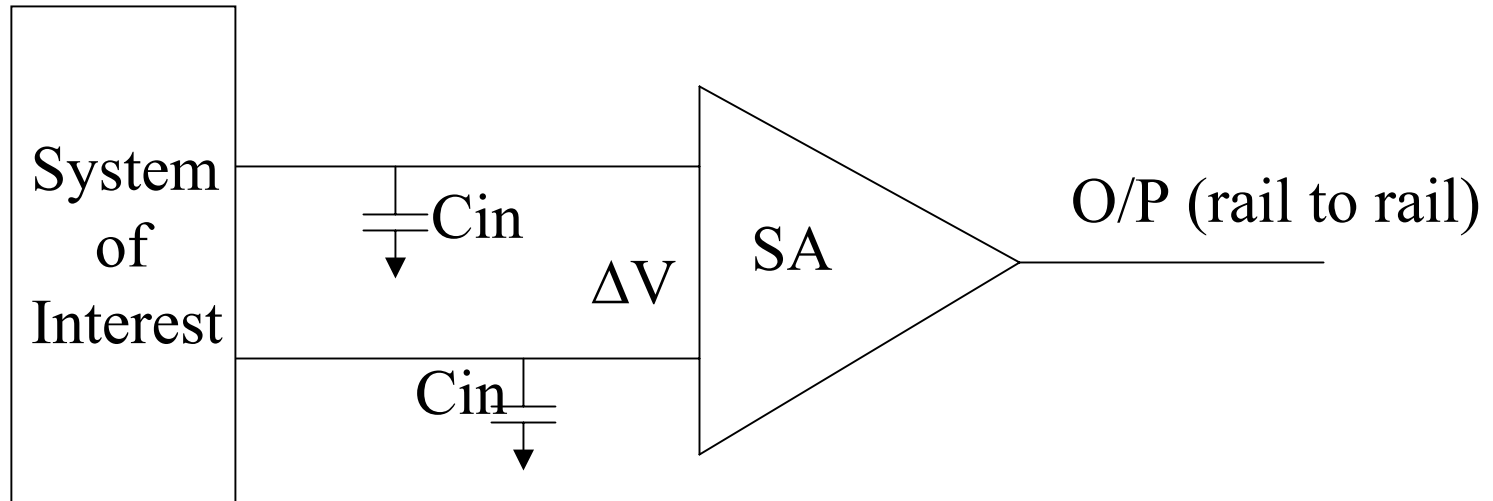

Sluggish inputs (i.e. large input capacitance)

In the absence of SA,

$$\Delta V = I_{in} * \Delta T / C_{in}$$

Sense Amplifier in SRAM

- Sense amplifier is one of the most critical elements in the design of a high speed SRAM
- Sense amplifier is the most important analog block in an otherwise digital memory
- Sense amplifier amplifies small voltage swing on bit-lines to CMOS voltage levels.
- Data sensing delay comprises about 50% of the total access time.

Current Sense and Voltage Sense

Voltage Sense

- Input signal comes to gate of MOS transistors
- Input impedance tends to be very large

Current Sense

- Input signal comes to drain/source of MOS transistors
- Ideally zero input impedance
- Low input differential swing lowers interconnect delay

Current sense vs. Voltage Sense

Current

Cell current is sensed

Speed is independent of C_{BL}

Low input impedance

Low power for small swings

More sensitive to offset voltage

Voltage

Voltage on bit lines is sensed

Speed is a function of C_{BL}

High input impedance

High power for large swings

Less sensitive to offset voltage

SA Implementations

Voltage Sensing

- Current mirror based SA
- PMOS cross-coupled SA


Current Sensing

- Current conveyor based SA

Other Schemes


- Half latch based SA
- Input decoupled latch SA

Current-mirror based SA

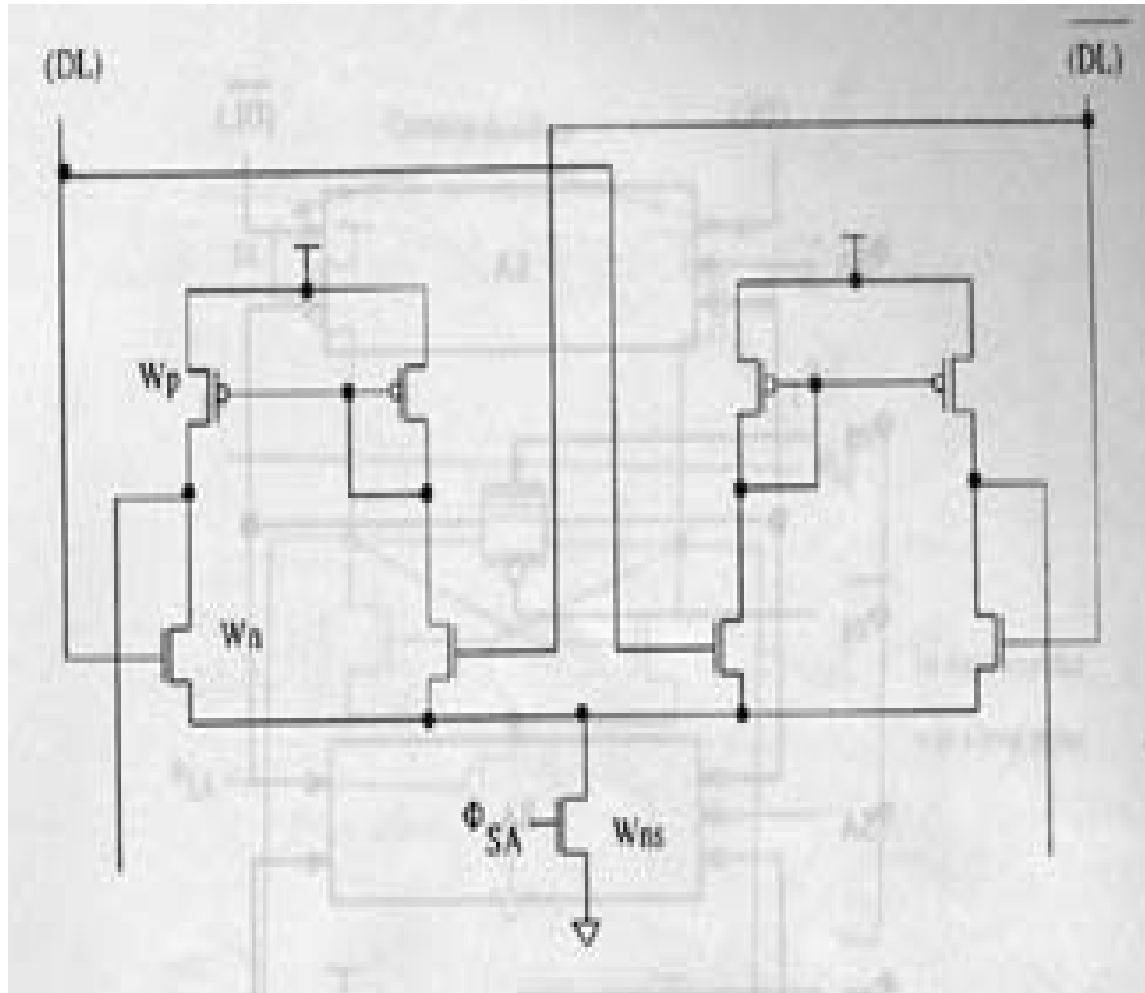

All differential voltages should be equalized before sensing

Current mode vs Voltage mode

 

Voltage mode signaling : $R_L = \infty$


$$\tau = R_B C_T$$

Current mode signaling : $R_L = 0$

$$\tau = \frac{R_T C_T}{2}$$

Ref: IEEE JSSC vol. 26, no. 4, April 1991


Current conveyer

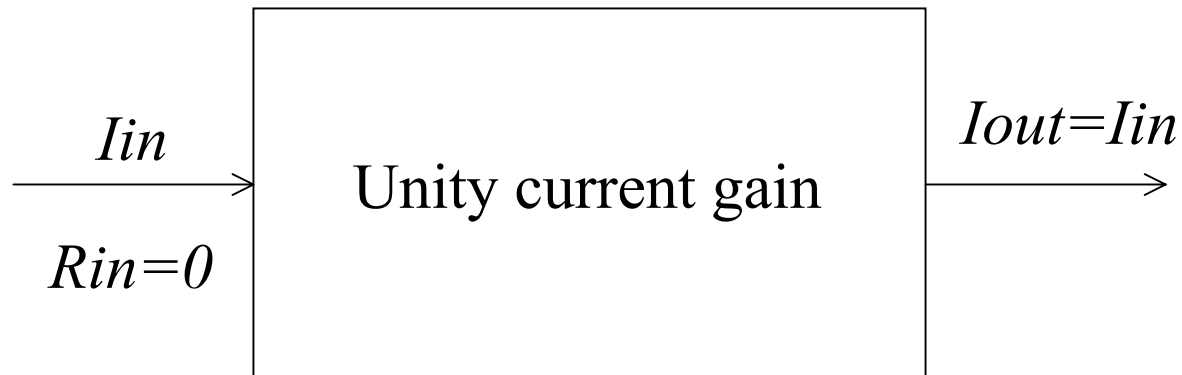

For ideal current conveyer

$R_{in}=0$ and $I_{out}=I_{in}$

Current Conveyor based SA

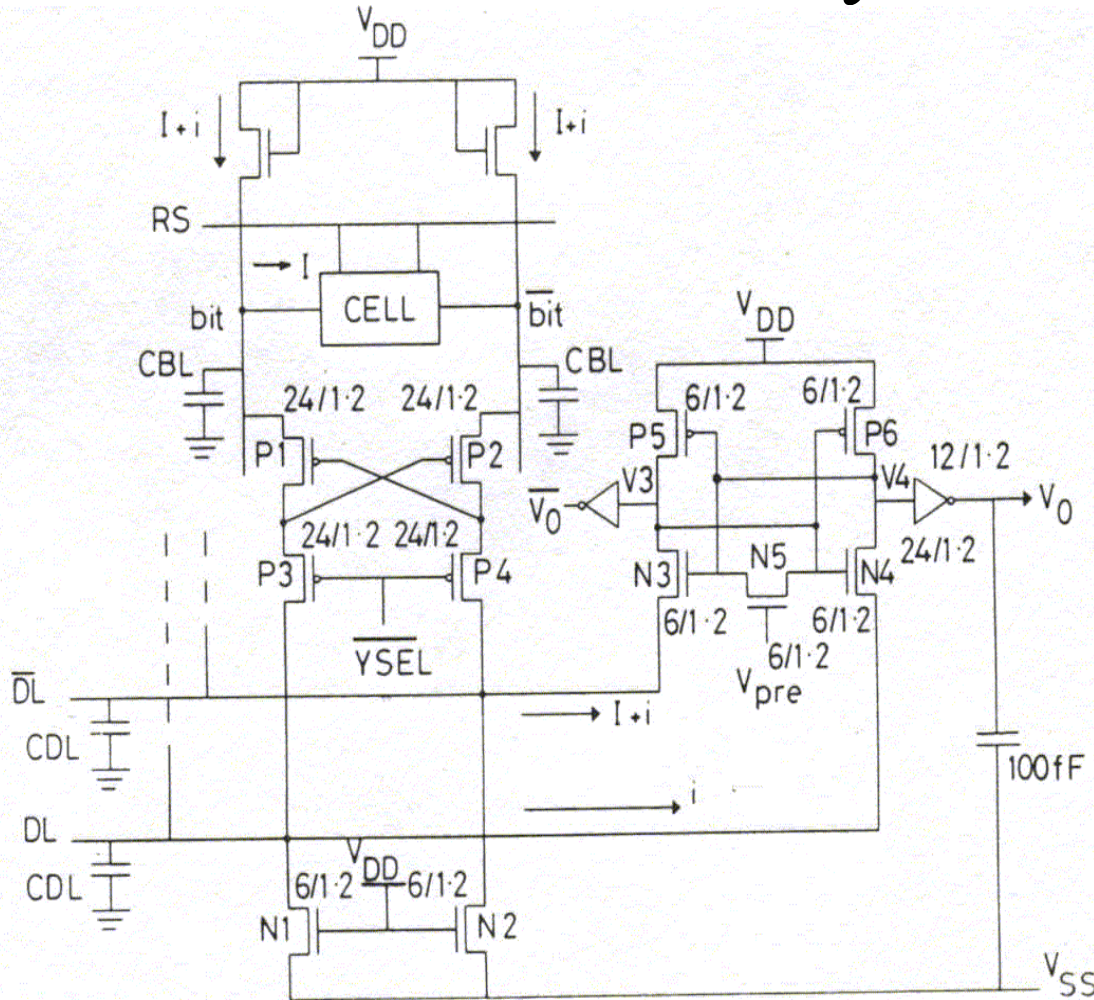


P1 and P2 provide negative feedback

P1 and P2 can be viewed as resistances whose value is modulated to suppress change in input voltage

P1 and P2 are in sat

Latch type sense amplifier

Positive feedback Latch

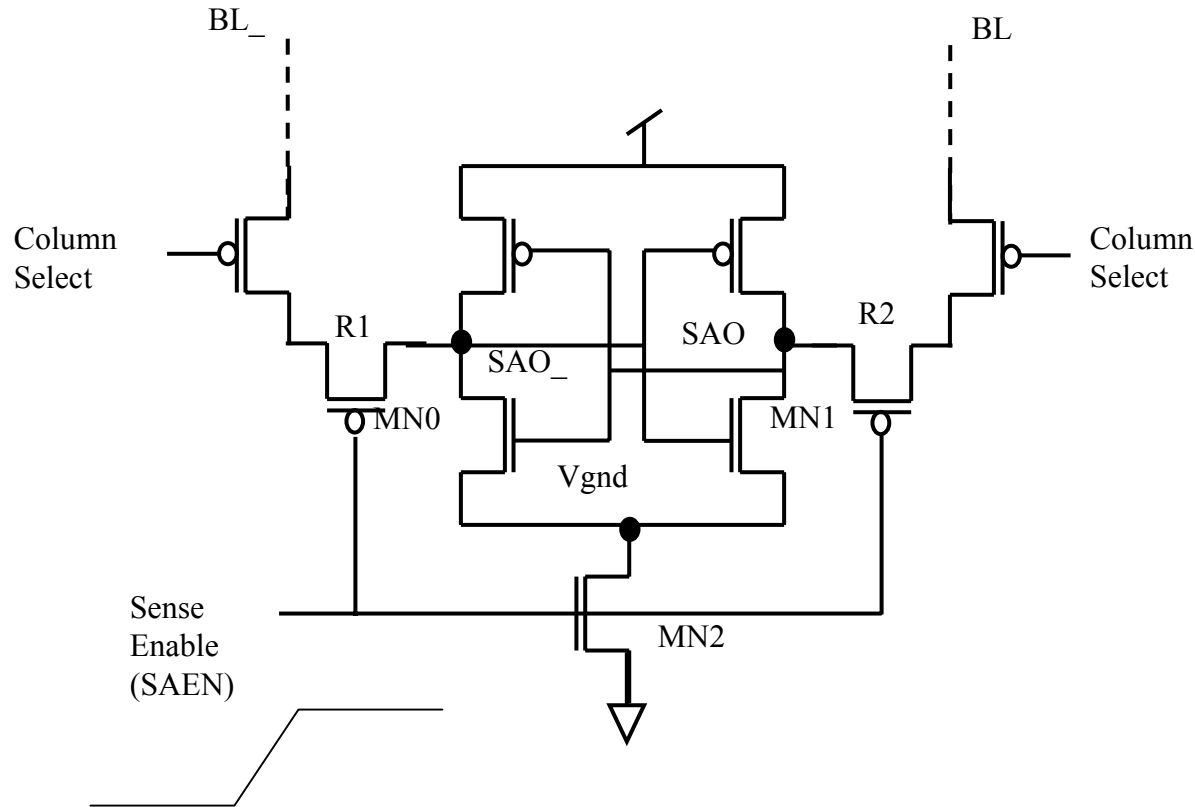

Sense enable controls the latching operation


0.35 μ m Simulation Environment(contd.)

- Cycle time = 1.55 ns
- Supply voltage = 3.0 Volts
- Transistor models = Typical
- Temperature = 25° C
- Rise/fall time for pulsed sources = 200 ps
- Bit-line pre-charge turned OFF during sensing
- Amplifier transistor length = 0.7 μ m

Current Conveyor Simulation

- Circuit nodes do not reach steady state value for high-speed
 - Divergence of cross-coupled nodes for high-speed operation
 - Solved by equalization transistor
 - Second stage activation with memory – wrong operation
 - Second stage activation delayed for correct functioning
 - Memory cell current not transported – attenuation
- *Performance degradation for high operating speed*

Current Attenuation in Current Conveyor

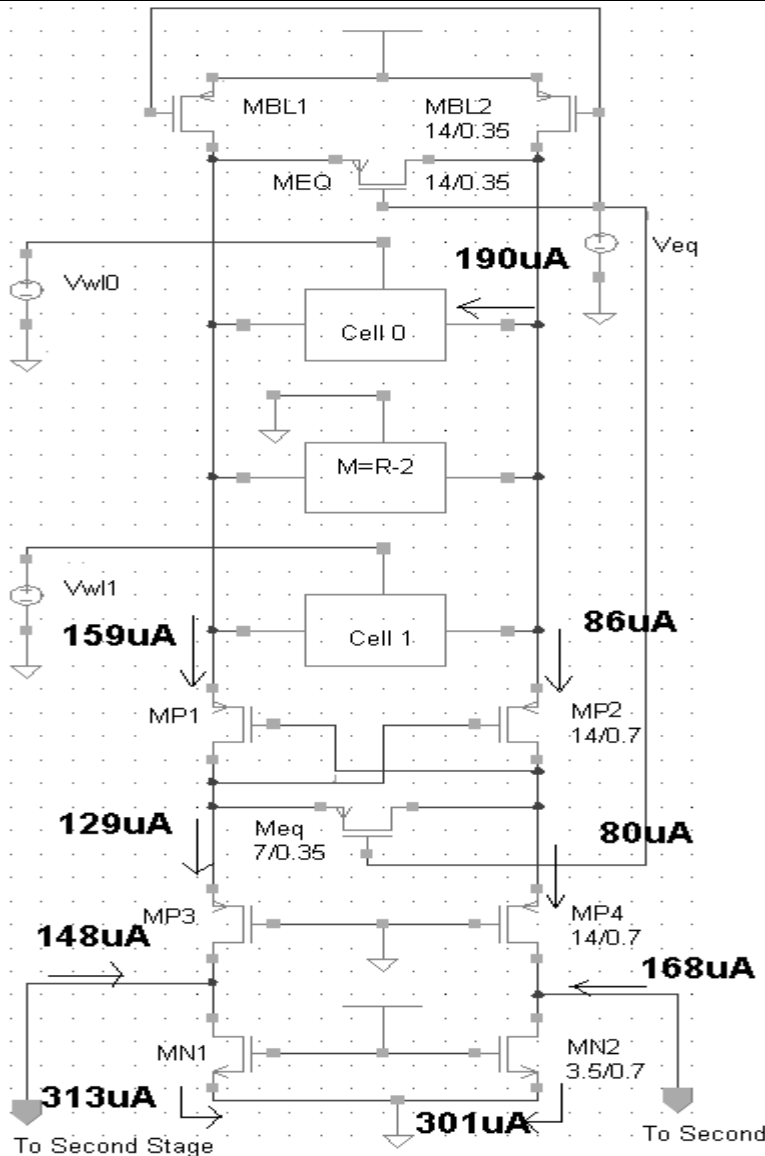

- Measured at end of cycle
- 2nd Stage deactivated

Memory cell differential current is 190 μA


Differential current transported to the second stage is 20 μA

Current attenuation due to capacitive effects at high speed

Current Conveyor Performance

No. of Rows	Sense Delay	Bit-line differential	Power
256	500ps	0.11 Volts	3.52mW
512	605ps	0.07 Volts	3.53mW


Input Decoupled Latch SA Waveforms

 

Initially both the outputs are biased at V_{dd}


During sensing one of the output falls faster than the other output

Half Latch SA

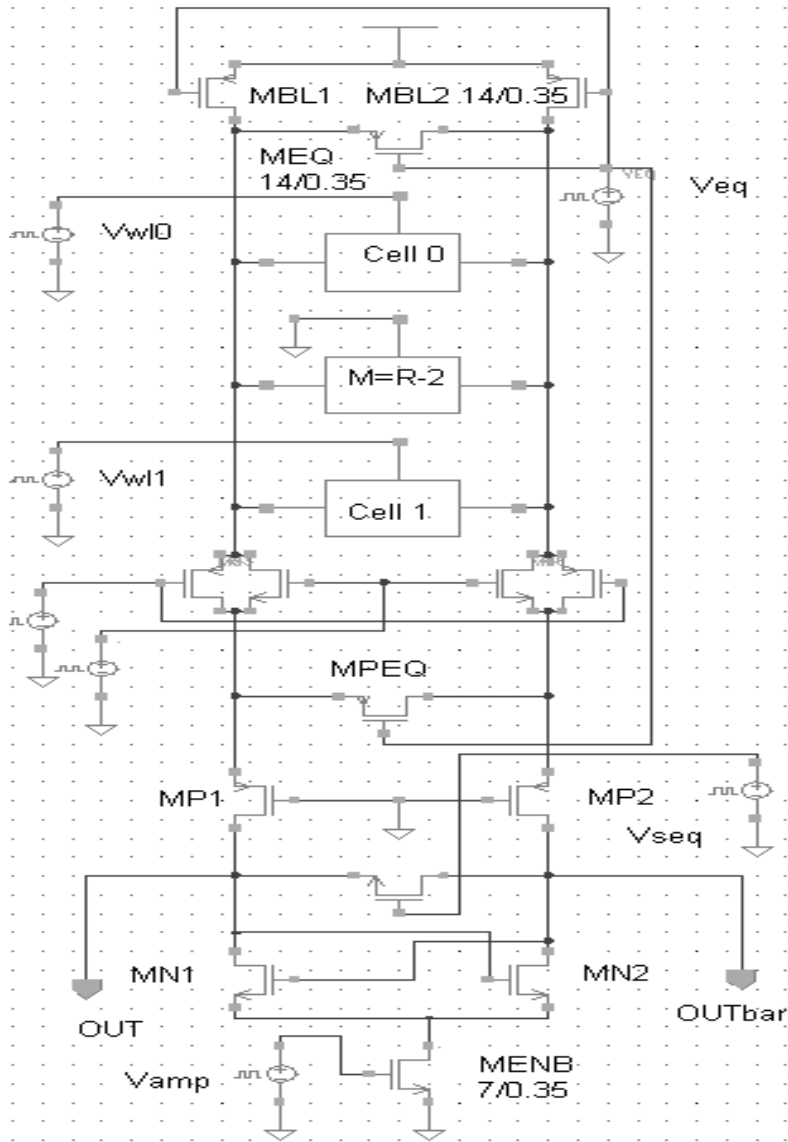


- Single stage
- Powered from the bit-lines
- V_M bias gives best performance
- PMOS transistors operate in linear zone
- NMOS transistors in saturation at start
- MP1,MP2,MN1,MN2: 2.1/0.7 nominal size

Half Latch SA Waveforms (V_M Bias)

 

 Comparison of Single Stage Latch Style SA



SA Comparison for 512 rows

SA Type	Sense Delay	Bit-line Differential	Power
Curr.Conv.	605ps	0.07Volts	3.53mW
PMOS cc	624ps	0.09Volts	3.51mW
Half Latch	355ps	0.09Volts	2.54mW
I/P Dec. Lat.	552ps	0.09Volts	3.00mW

Frequency Domain Analysis

- Open loop gain-bandwidth analysis for single stage positive feedback latch style amplifiers
- Small signal input impedance analysis for “current sensing” schemes


Advantages

- Minimum number of components needed
- Compare different amplifier structures
- Perform a preliminary sizing of amplifier transistors
- AC simulations will be much faster than the transient simulation

Open Loop Gain-Bandwidth Analysis


- Open loop GBW indicator of response speed of positive feedback amplifiers
- Cross-coupled inverter amplifier core of the single stage latch style SA
- Feedback loop opened with appropriate loading
- Input signals mimic the bit-line differential signals
- Frequency analysis done for open loop gain
- GBW studied for various amplifier transistor sizes

Open Loop Circuit for Half Latch

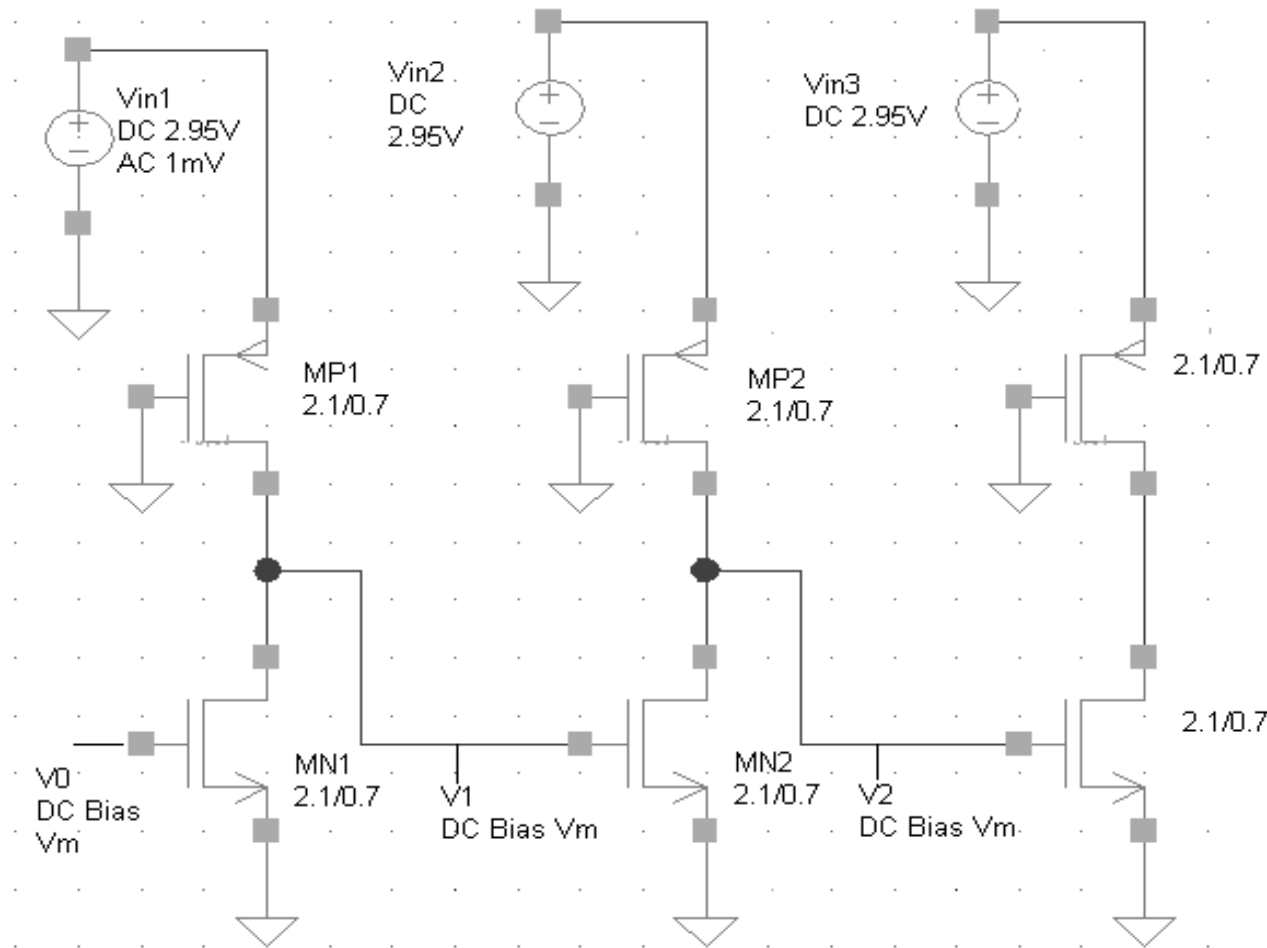

Dummy transistors are added to simulate the loading

Gain Characteristic for Half Latch

 

3-pole 3-zero
response up to 1 THz

For figure shown


Gain=20dB

Bandwidth=802MHz

GBW=8.02GHz


Similar responses for
other two amplifiers

 Time and Frequency Domain Results-Half Latch Amplifier




$(GBW)^{-1}$ compared with time domain sense delay for varying transistor sizes

 Time and Frequency Domain Results: I/P Decoupled Latch Amplifier




Scaled $(GBW)^{-1}$ compared with time domain sense delay for varying transistor sizes

Small Signal Input Impedance Study

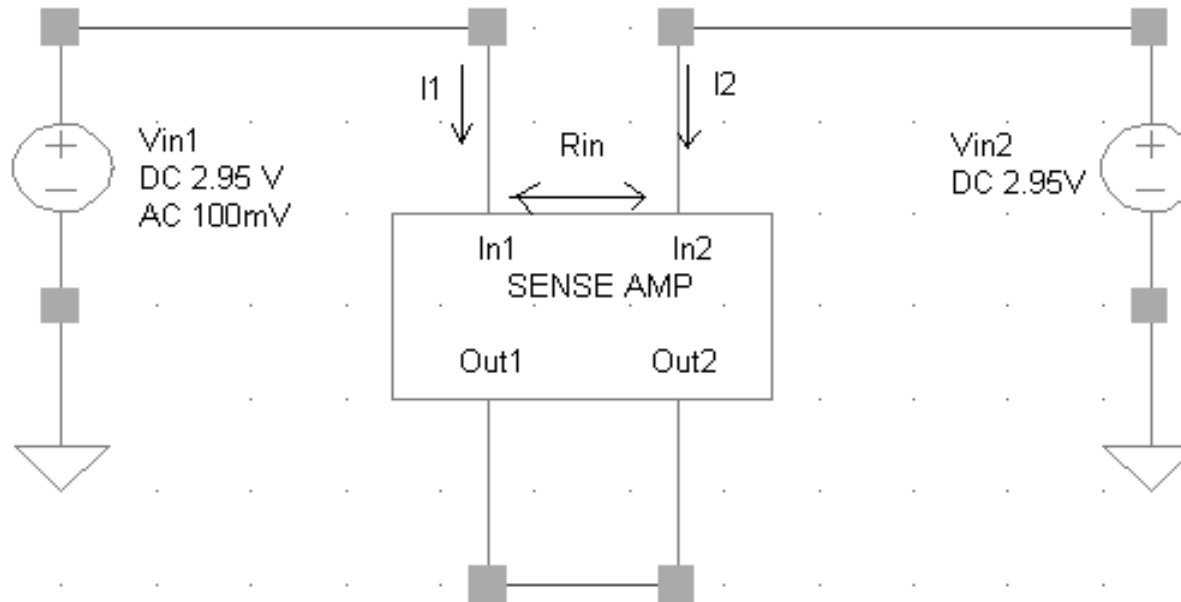

- Circuit to measure input impedance
- Differential output = 0
- Differential input impedance measured as a ratio of differential input voltage and current


Input Impedance of Current Conveyor

 

2-pole 1-zero response
up to 1THz

DC value = 302 Ω

Peak value = 1.83k Ω at
1.29 GHz

 

For 1.55 ns cycle time
1.3GHz is twice
fundamental frequency

**INPUT IMPEDANCE
NOT LOW FOR HIGH
SPEED OPERATION.**

Summary of SA architecture

- Half latch and input decoupled latch amplifiers found to give best speed performance
- Current conveyor based schemes are not well suited for high-speed applications
- Frequency domain analysis useful tool to study positive feedback amplifiers
- *Access time limitations expected to increase with increasing densities*

Impact of Mismatch on Analog Design


Acknowledge the contributions made by Ravpreet Singh and Srinivasaiah

Transistor mismatch in deep sub-micron technology


- Factors causing transistor mismatch
- Modeling the transistor mismatch
- Controlling mismatch effect at process/device level
- Impact of transistor mismatch in sense-amplifier design
- Controlling mismatch effect at circuit level

Transistor Mismatch Effects

 3 identical transistors in a chip at the circuit design phase




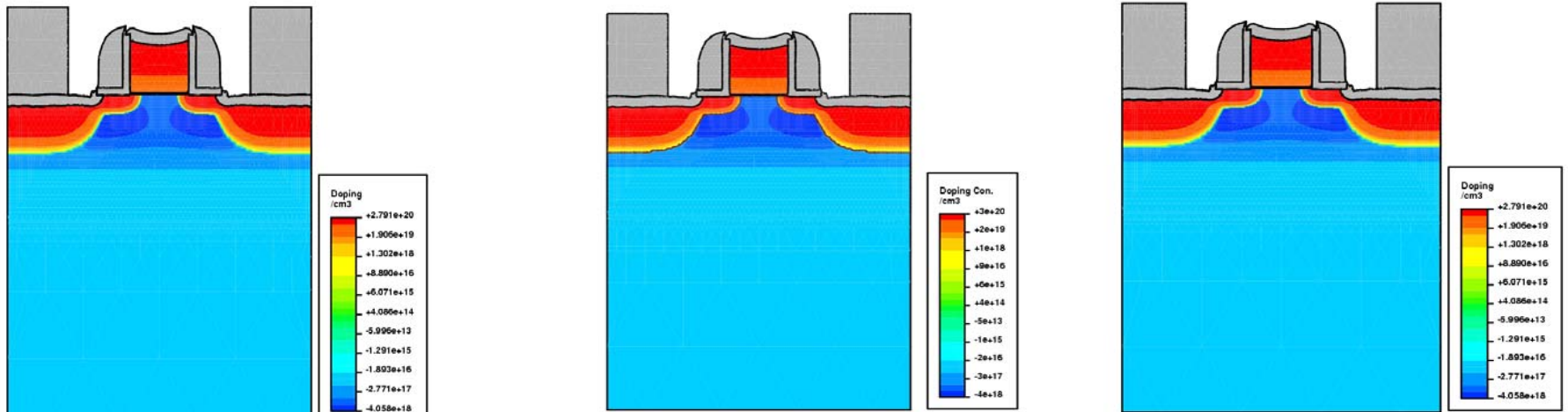The structure of 3 transistors after the completion of IC processing



Simulated devices with $\pm 10\%$ halo variation from nominal value

 Impact of process variation on drain current



Factors Causing Mismatch

1. Intrinsic type

- Discrete dopant effect
- Interface state density fluctuations


2. Extrinsic type due to random variation in:

- Gate length and width
- Oxide thickness
- Implant dose
- Implant energy
- Anneal temperature
- Gate & S/D overlap
- Spacer thickness

Device parameters affected by process parameters

- I_{off} , the leakage current
- I_{on} , the saturation current
- V_t , the threshold voltage
- S , the Sub threshold slope
- g_m , the Transconductance.
- Various R s, C s and parasitics

 Impact of process parameters on circuit parameters



- Circuit performance has a direct relation on process in a complex way.
- The relation between circuit parameter to process parameter is highly nonlinear.
- Some of the Process level parameters are statistically correlated.

Short range and long range order

Inter die, Inter wafer and Inter lot variations have long range order

Intra die variations can be medium and short range

The variation along a clock tree has medium range order

The variation in matched differential pair is short range order

SPICE corner models are derived from long range order and they will be very pessimistic for short range order


Typically the intra die variation of a parameter P between two transistors M1 and M2 is given by

$$\sigma^2(P_1 - P_2) = \frac{a_p}{2W_1L_1} + \frac{a_p}{2W_2L_2} + s_p^2 D_{12}^2$$


σ^2 is variance, D_{12} is distance between M1-M2, a_p and s_p are Process technology dependent

Distinction in variation of a parameter vs. variation in matching of parameter

Variation in V_t
(long range)

 


Variation in ΔV_t
(short range)

 


Mismatch coefficient
 
$$\sigma\Delta V_t = \frac{A_{VT}}{\sqrt{WL}} = \frac{qT_{ox}\sqrt{2NW_d}}{\epsilon_{ox}\sqrt{WL}}$$




The equation is obeyed very well except at the edge of the Process technology

Scaling Trend

 

The parameter matching is becoming difficult with scaling

ADC Yield

 


The higher precision requires very low mismatch

The yield for high precision drops off very fast



Offset Effects

- Mismatch effect modeled by variation in β and V_T
- Sense amplifiers can be activated only after input signal voltage (bit-lines) compensates offset voltage
- Different degrees of mismatch – 10%, 5%, 2.5%
- Worst case offset voltage generated for each sense amp
- Matched pair of transistors – ($\max V_T$, $\min \beta$) and ($\min V_T$, $\max \beta$)

 Comparison of Latch Amplifiers with Offset (contd)





Effect of input offset on SA

 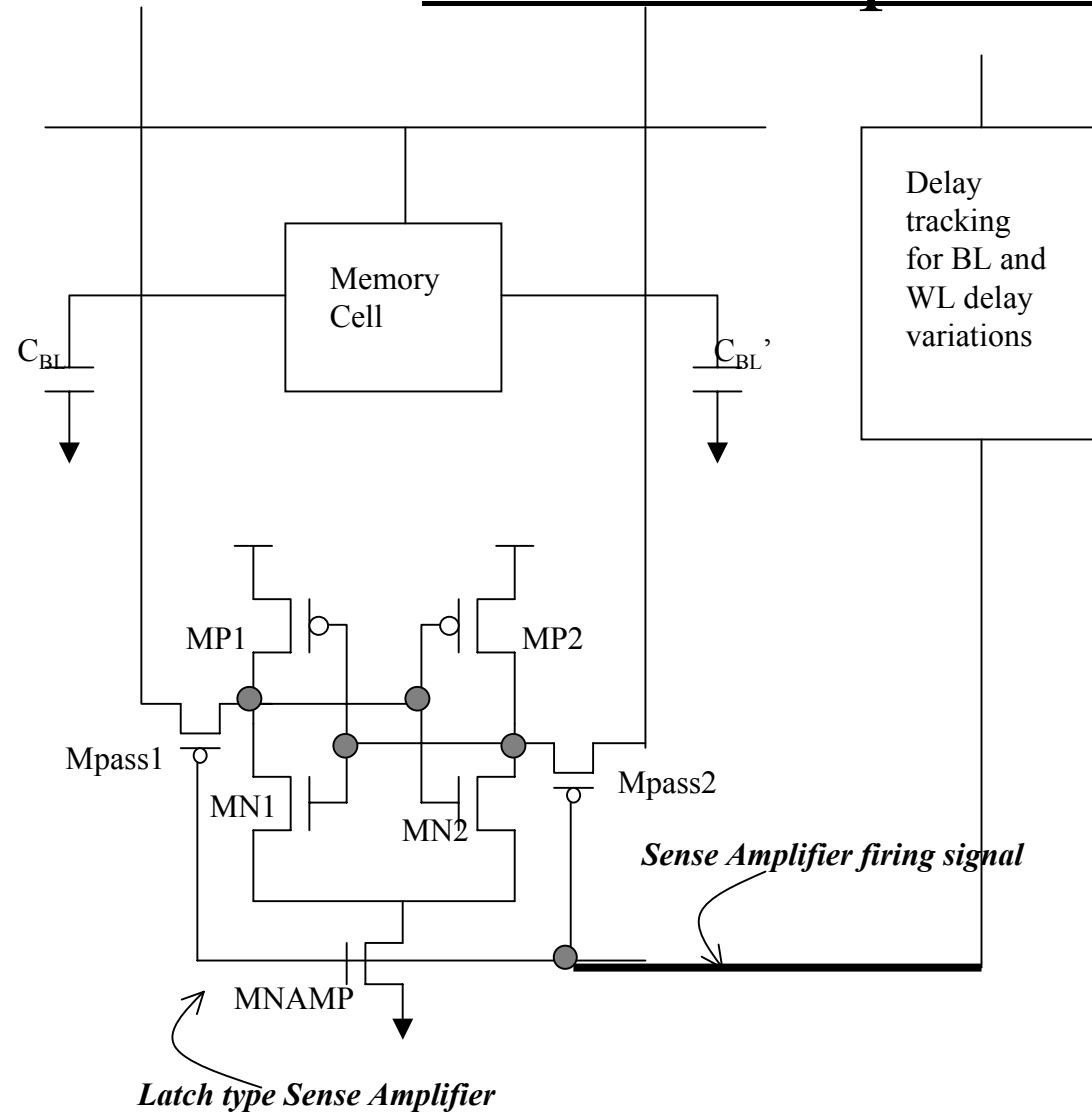

- Higher the offset, longer the delay for proper functionality

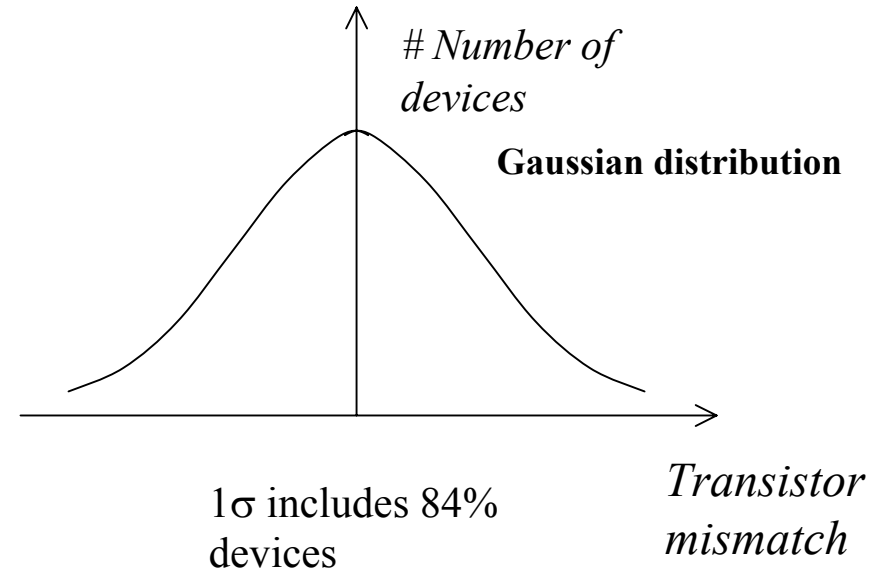 
Impact of transistor mismatch on SA Delay



Design Index (σ)	Percentage of functional devices
1	84.1344740
2	97.7249938
3	99.8650033
4	99.9968314
5	99.9999713
6	99.9999999


- 6σ design index required from circuit yield consideration
- Conservative design compromises the circuit speed (factor of 2 or more!)
- This is a typical speed versus yield trade-off which exists universally

Conventional solution

 


- Adding offset compensation circuit to Sense-Amplifier
- Increased number of transistors connected to SA output
- Added circuitry increases SA output node capacitance
- Intrinsic SA response becomes sluggish

Effect of source-substrate bias

 


Applying body bias increases common mode V_t and hence the difference in drain current decreases


Intrinsic offset vs tail transistor size

 


Extrinsic offset vs pass transistor size

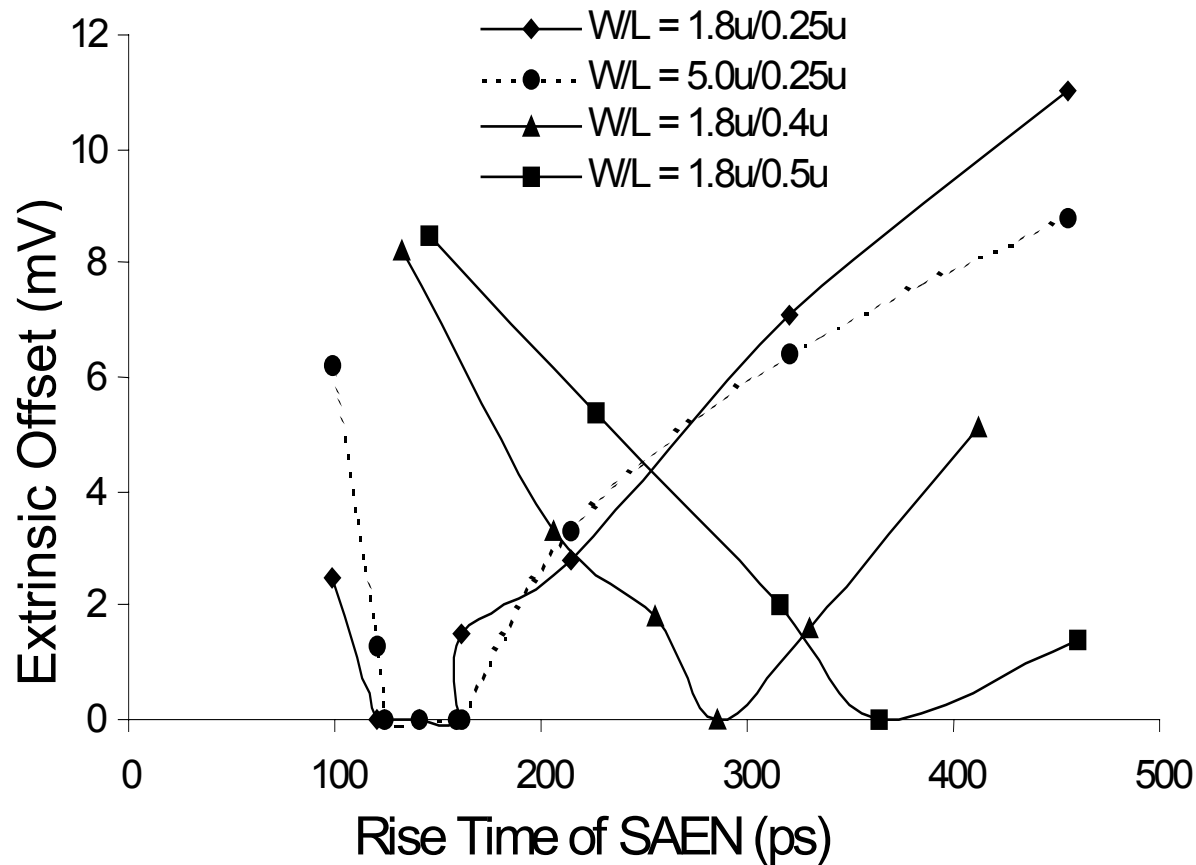


Extrinsic offset vs tail transistor size

 


 
Total latch offset vs pass transistor size



 Total latch offset vs tail transistor size



Speed and Power versus SAEN Rise Time

  

Low power option also corresponds to high speed option!

Effect of rise time on speed and power

Rise Time (ns)	Access time (ns)		
	1024 Rows	2048 Rows	4096 Rows
86	2.66	3.44	5
126	2.5	3.15	4.5
177	2.47	3.07	4.28
230	2.48	3.07	4.23
330	2.53	3.1	4.24
450	2.6	3.18	4.33



Rise Time (ns)	Current consumption (uA/MHz)		
	1024 Rows	2048 Rows	4096 Rows
86	78.2	102	165.3
126	71.6	91.5	145
177	70.2	88	136
230	69	86.7	132
330	69	86.7	132
450	69	86.7	132

Analytical modeling

The input offset voltage is the minimum required input signal
In order to produce correct latching

$$V_{\text{SIG}} > \Delta V_{\text{T}} + \frac{1}{2} \left\{ \left(\frac{\Delta\beta}{\beta} + \frac{\Delta C}{C} \right) + \frac{\Delta C}{C + C_{\text{GS}}} \frac{KC_{\text{GS}}}{\beta} \frac{3a_1}{a_2^2} \right\} (V - V_{\text{S}} - V_{\text{T}})_{\text{max}}$$
$$+ \text{mdec} \frac{\Delta C C_{\text{GS}}}{(C + C_{\text{GS}})^2} (V - V_{\text{S}} - V_{\text{T}})_{\text{max}}$$

Analytical Modeling

  

Excellent matching with simulation results are obtained

Summary of transistor mismatch effects

- Random variations in IC process parameters result in mismatch among identically designed transistors
- Transistor mismatch limits performance and yield of sense amplifiers in memory application
- The mismatch effects will become worse with technology scaling
- Analog and mixed signal circuit design should be able to overcome the transistor mismatch effects

Need for Statistical Design and Simulation

Pessimistic design with Worst Case Process corners SPICE models


If the corner parameters are used to simulate the worst case mismatch effect, the design will be pessimistic

As a designer, in order to do a reliable as well as high performance design, obtain the matching data as well from the fab

It does take quite a bit of effort for the fab to generate mismatch data, but it would be worth the effort from designer's viewpoint

Statistical circuit simulation

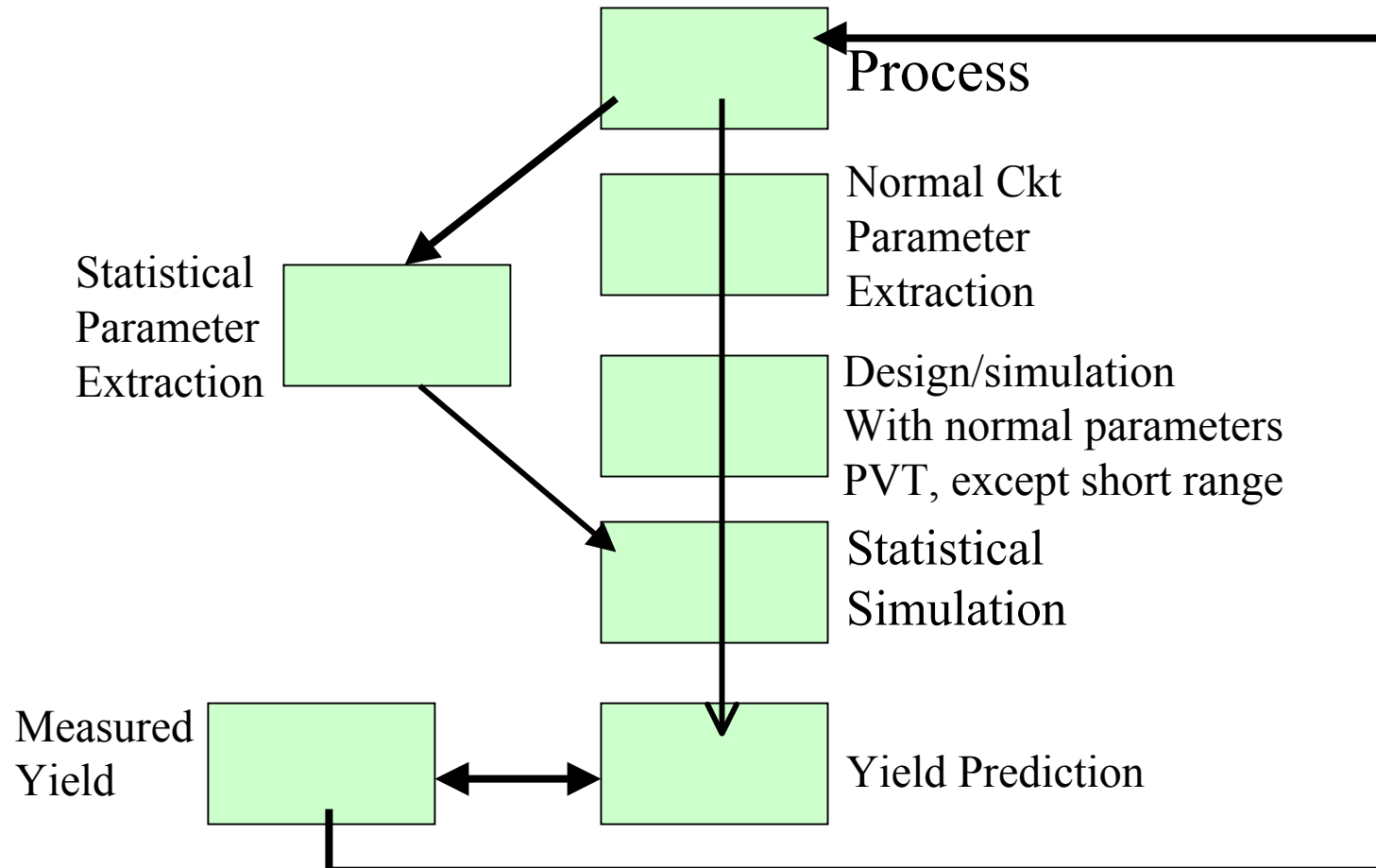Ideally the statistical design/simulation should be part of the design flow for analog circuits



Monte Carlo Technique

Statistical technique used to predict the output distribution when there is no closed form expression relating output distribution to input

Random number generation is used to randomly assign a value to input variables and walk through the input to output transformation

By transforming a large set of inputs to the output the output distribution is obtained

Response surface methodology using DOE

For a complex circuit the SPICE simulations in the Monte Carlo loop become computationally inefficient



By performing very few input to output transformation, a mathematical model could be fit to relate the output quantity to the input (linear, quadratic or some other function)

This model replaces SPICE simulations from MC loop

Computational efficiency is enhanced significantly

Wide Common Range OPAMP

  
Common mode range for differential amplifier





Only the lower limit of V_{ci} is the hard limit and is above negative rail (0V)

We presumed the upper limit also to be much below positive rail (VDD) due to $I_S R_D / 2$ drop

 What if you replace the load R_D with current source load?



 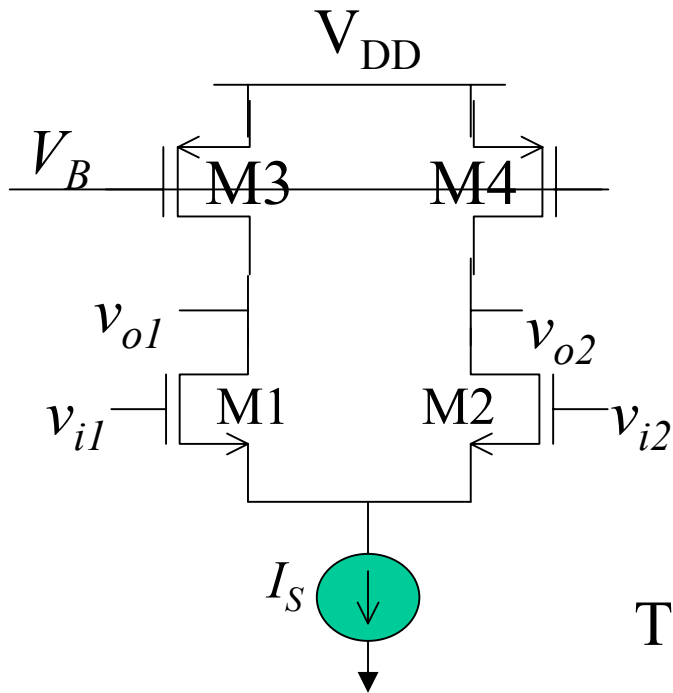
The common mode range with current source load



The $V_{c_{max}}$ will be even greater V_{DD} !


However the $V_{c_{min}}$ is the hard limit

Common Mode Range for NMOS and PMOS

 

Combine NMOS and PMOS input differential pair to obtain rail to rail common mode range, V_{ci} !
 (In fact the CMR Could be even beyond rail to rail)

The rail to rail input stage

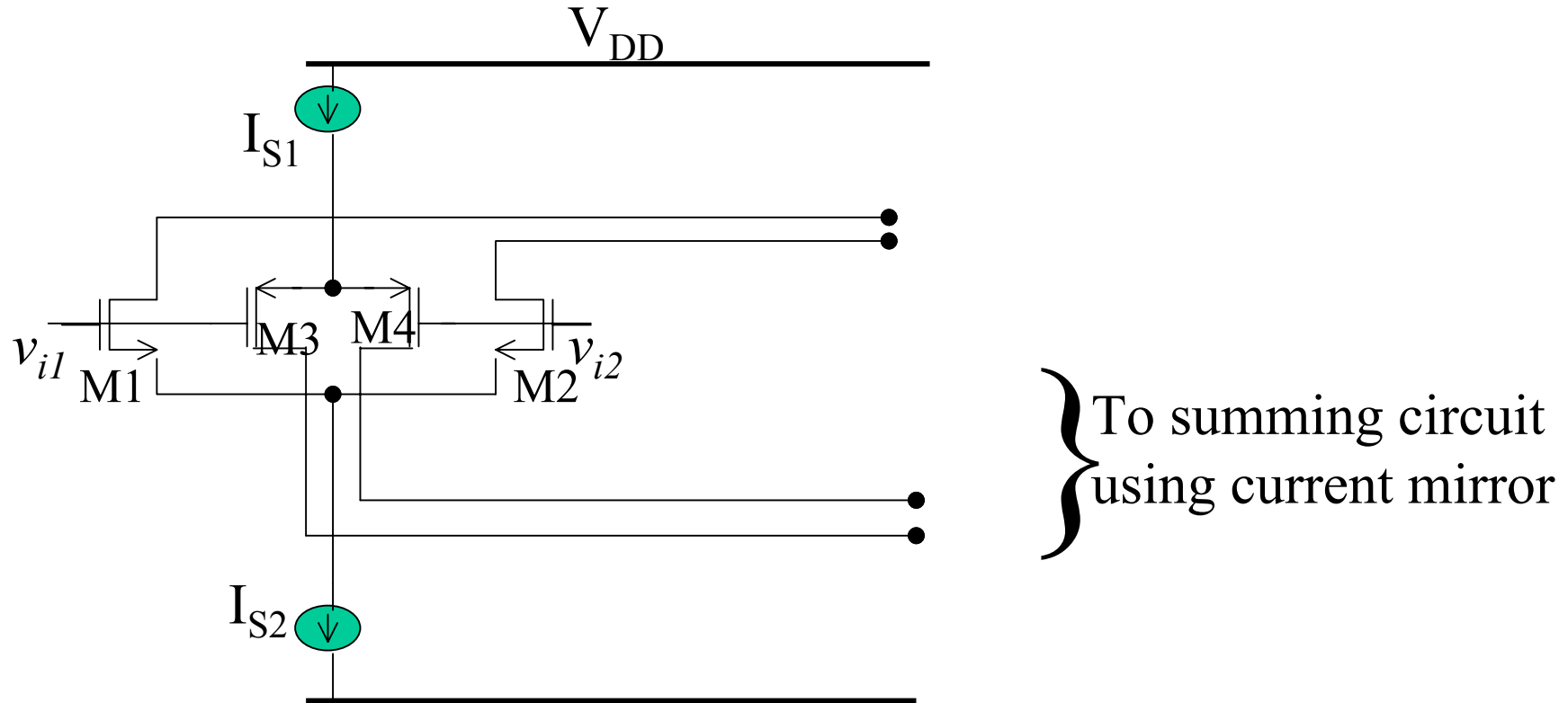


Low common mode input : Only P-type diff pair operates

Intermediate common mode input: Both N and P-type operate

High common mode input : Only N-type diff pair operates

The variation of the first stage gain

 

For the simple circuit, the first stage gain is not constant over the common mode input range

Additional circuit is required to maintain the constant gain

The concept of gain control

Suppose that N and P pair bias current is constant and N and P transistors are sized to match the transconductance

$$\sqrt{k_n I_S} = \sqrt{k_p I_S} = \sqrt{k I_S}$$

When both pairs are active the transconductance gets added

$$G_m = 2\sqrt{k I_S}$$

If we like to maintain the same transconductance when either N or P differential pair is switched off, then we need to change the active pair bias current using some circuitry


$$G_m = \sqrt{k_n 4I_S} = 2\sqrt{k I_S}$$

Increase N bias current by a factor of 4 when only N is active

$$G_m = \sqrt{k_p 4I_S} = 2\sqrt{k I_S}$$

Increase P bias current by a factor of 4 when only P is active

The first stage with gain control

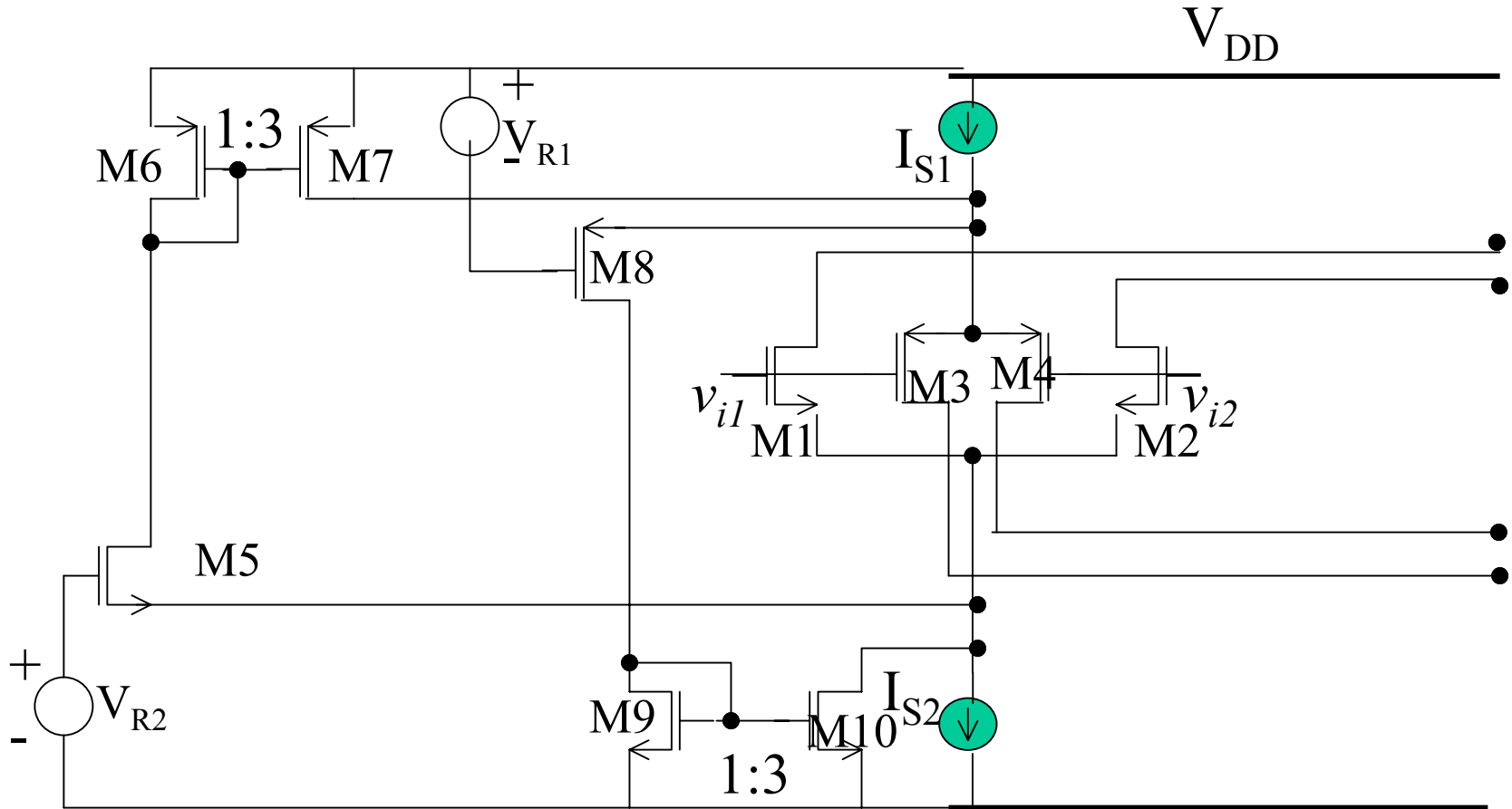

V_{R1} and V_{R2} are chosen slightly above V_t of $M5$ and $M8$

The current switching

For low V_{ci} i.e $V_{ci} < V_t$

M8 is OFF and M5 is ON $\Rightarrow I_{S2}$ flows through M5

The current mirror M6-M7 multiplies I_{S2} by a factor of 3 onto the drain of M7. This is added to I_{S1} , thereby increasing The P bias current by a factor of 4

For high V_{ci} i.e $V_{ci} > V_{DD} - V_t$

M5 is OFF and M8 is ON $\Rightarrow I_{S1}$ flows through M8


The current mirror M9-M10 multiplies I_{S1} by a factor of 3 onto the drain of M10. This is added to I_{S1} , thereby increasing the N bias current by a factor of 4

For intermediate V_{ci} i.e $V_t < V_{ci} < V_{DD} - V_t$

M5 is OFF and M8 is OFF \Rightarrow Current mirrors are disabled

N bias current = P bias current = I_s

The corrected gain

 


Adding current switching makes the differential gain almost flat over the common mode range

Bulk Driven OPAMP

The dead zone problem in complementary input stage

 Suppose that supply voltage is very small $V_{DD} < V_{GSn} + V_{GSp} + 2\Delta V$



Then there is a dead zone in V_c range!

Both the pairs are deactivated and no useful operation

Overcoming the V_t problem in single stage

N and P stages are inherently limited by the fact that the gate voltage should be more than V_t to turn on the transistor



Possible remedy:

Fix the gate voltage above V_t and apply the inputs to the body of the transistor (bulk driven)

Modulating the body voltage results in change in V_t and hence gives rise to body effect transconductance which is used to operate on the input signals

Note: At the higher range of input common mode voltage significant junction leakage may result

The bulk driven NMOS

 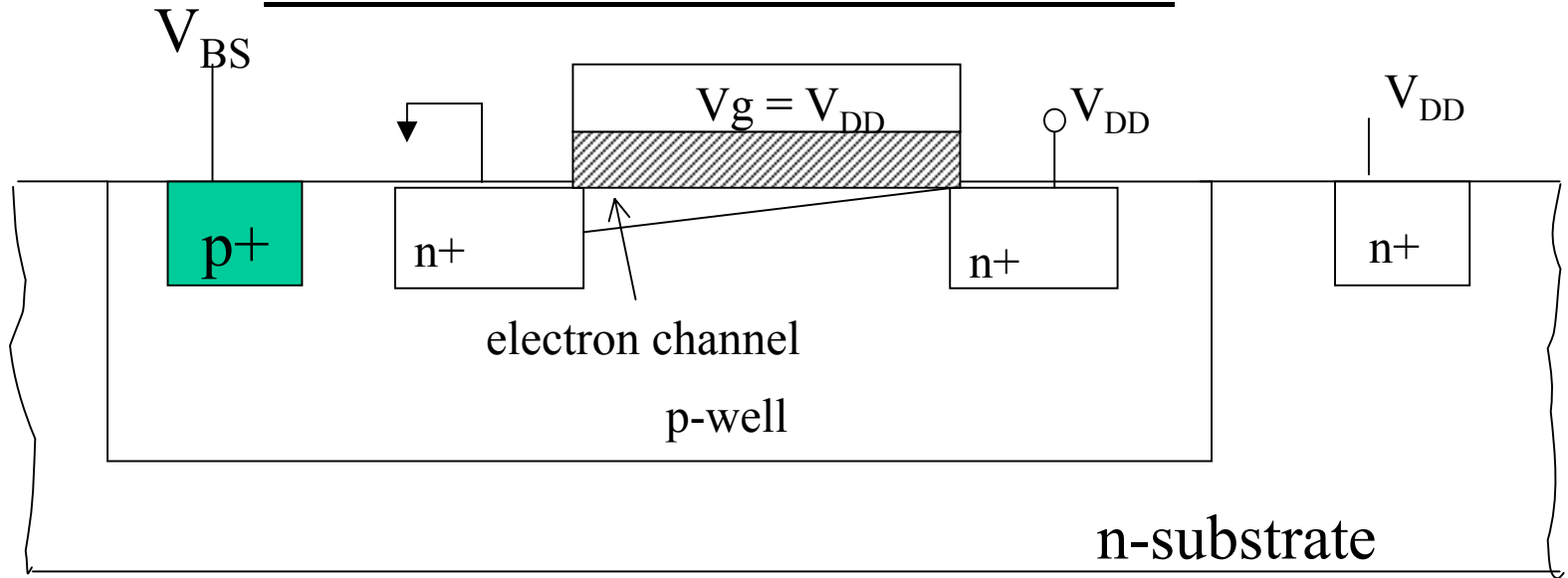


Bulk driven MOSFET can be viewed like a JFET

Parasitic BJTs are not turned on

The transistor is ON even when the input $V_{BS}=0$

Bulk driven NMOS first stage

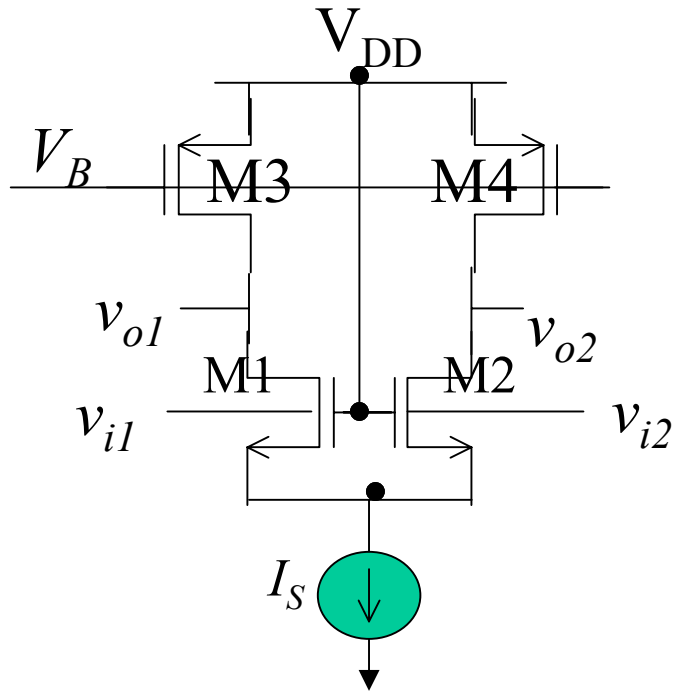

Rail to rail V_{ci} is possible


G_m is not constant over the V_{ci} range

If the supply voltage is less than 1V then the maximum forward bias of junction would be about 0.5V

Note that body effect is active even when body to source voltage is forward biasing the junction

Lateral BJT in CMOS Technology

The Lateral BJT in CMOS

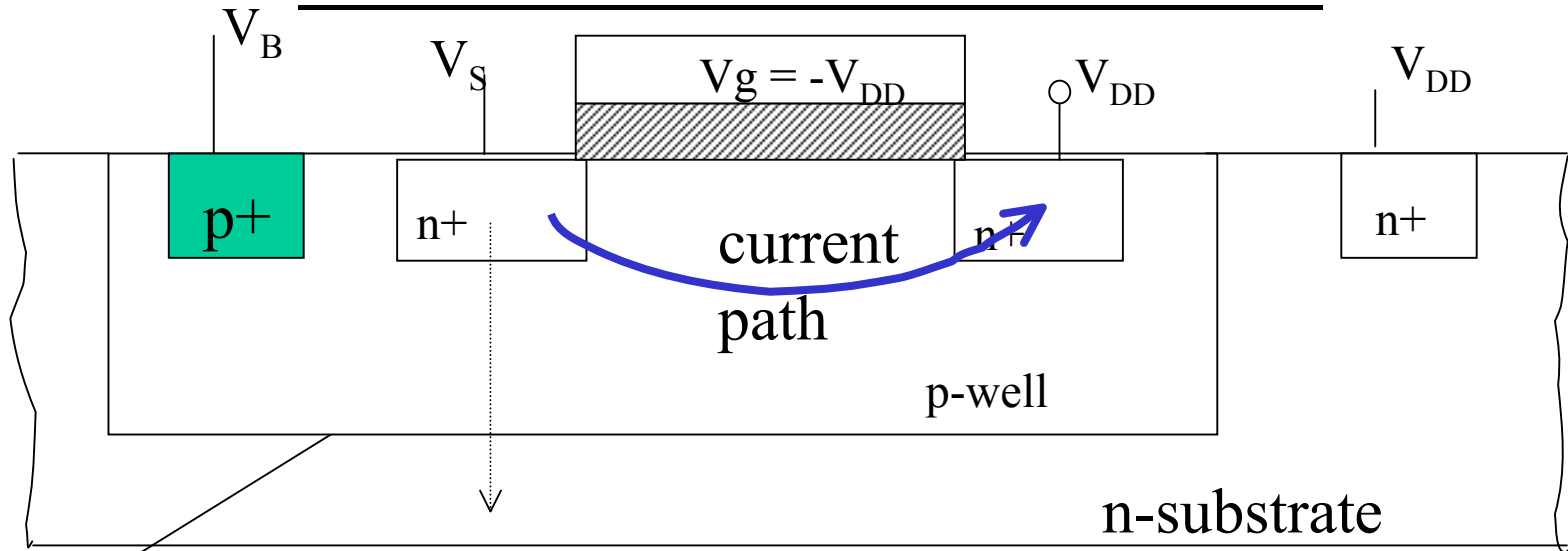

*Suppress vertical component
through layout technique*


Use the lateral BJT between source and drain

Intentionally forward bias well-source (base-emitter) junction

Gate voltage is negative to turn off the MOSFET

For small channel lengths, BJT has reasonable gain

Surround drain layout

 


The edgeless gate layout
Improves the lateral BJT
performance over the
vertical one

The lateral current
collection has increased

Does not require any
modifications to CMOS
technology

1/f noise improves

The device characteristics

 



When the gate voltage is negative,
the I_c - V_s characteristics look like ideal BJT

This device can also overcome the V_t related problem


Subthreshold Operation : Neural Networks

Acknowledge the contributions made by Amit Gupta

Subthreshold Operation

  

Subthreshold Operation

 

Subthreshold Operation

$$I_{DS} = I_0 e^{q\kappa V_{GS} / kT} (1 - e^{-qV_{DS} / kT})$$


Where

$$\kappa = (1 + C_D / C_{OX})^{-1}$$

$$I_0 = k_x \frac{W}{L} e^{q[(1-\kappa)V_{BS} - V_{Th0}] / kT}$$

For $V_{DS} > 50\text{mV}$

$$I_{DS} = I_0 e^{q\kappa V_{GS} / kT}$$

 

$$V_{GS} < V_{Th0}$$

Subthreshold Operation

- Exponential non-linearity
- Extremely low power dissipation
- Highest processing rate per unit power
- Saturation of drain current in few kT/q

V_t limitation is not present to build rail to rail OPAMPs

Motivation for Neuromorphic circuits

- Sequential Processors Vs Neural Networks
- Hardware Implementation
- Analog VLSI
- Low Power Networks

Motivation

- Modern Computer
 - Pre Programmability
 - Repetitive Computation
- Human Brain
 - Speech Recognition
 - Pattern Recognition

Human Brain

- A powerful information processor
- Massively parallel complex network of neurons
- Neuron
 - weak computation unit
 - 7-8 orders of magnitude slower than current Si gates
- Knowledge acquired through learning
- Synaptic weights are used to store the acquired knowledge

NEURAL NETWORKS:
Parallel Distributed Processors

*Machines inspired from the brain's
performance!!!*

Analog VLSI


- Analog systems carry more information per wire and fewer transistors per operation
- Analog computing primitives, multiplication and addition, are much smaller
- Redundant h/w to ensure fault tolerance
- Analog's cost is low
- Real world interfacing: Analog systems eliminates the need of ADC/DAC.

Low Power Networks


- Battery driven portable systems
- High circuit density

SUBTHRESHOLD OPERATION
IS THE NATURAL CHOICE


Model of a Neuron

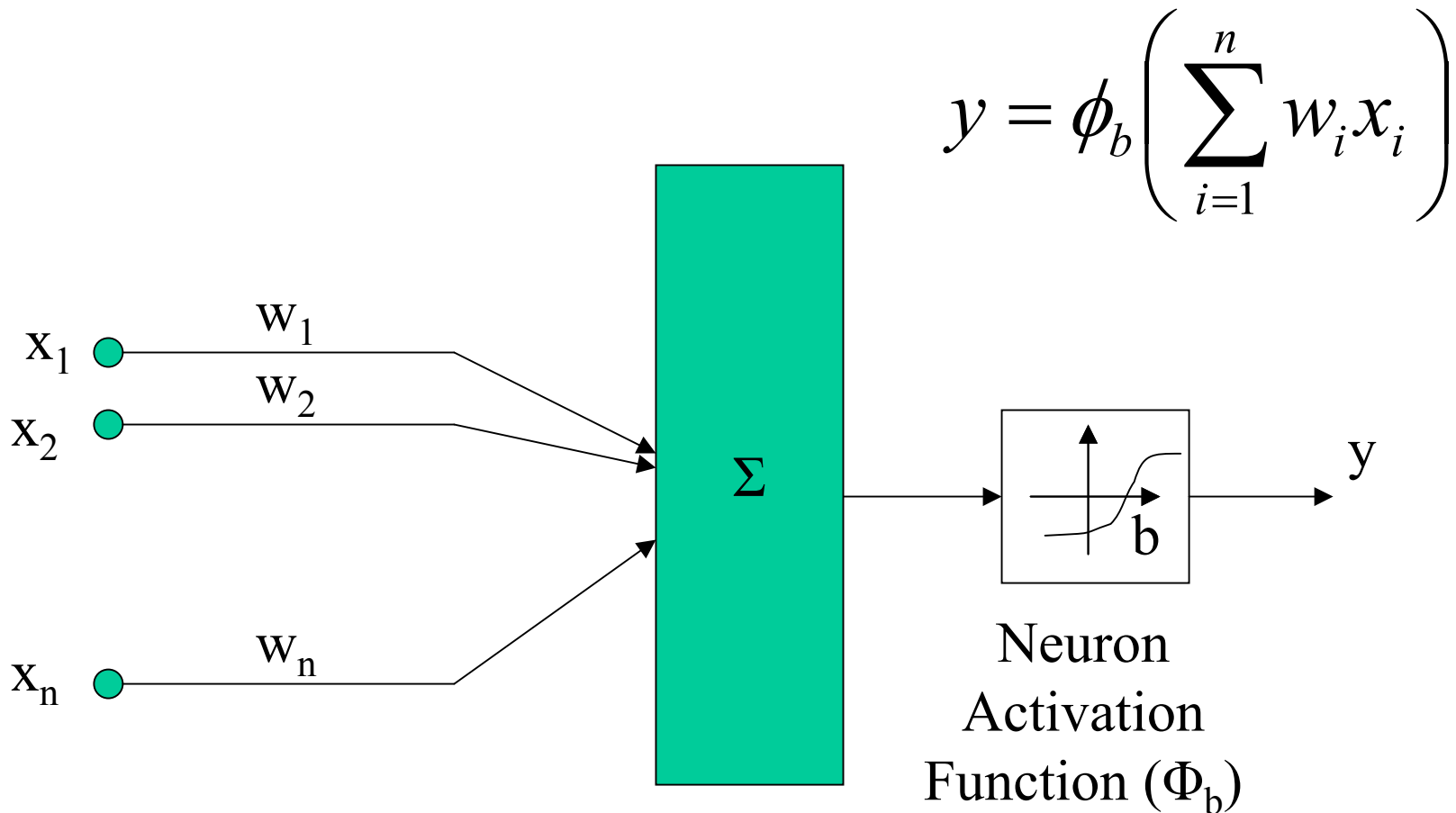


Model of a Neuron

 

Model of a Neuron

 

Feedforward Neural Networks

 

- Back Propagation Algorithms: Highly popular for training
- Perturbation Algorithms: Hardware friendly

Neuron Activation Function (NAF)

- Common choices


- Logsigmoid

$$y_j = \frac{1}{1 + e^{-\lambda s_j}} \quad , y_j \in \{0, 1\}$$

- Tansigmoid

$$y_j = \frac{e^{\lambda s_j} - e^{-\lambda s_j}}{e^{\lambda s_j} + e^{-\lambda s_j}} \quad , y_j \in \{-1, 1\}$$

BP Algorithm

 

• Weight update rule

$$w_{ij}^{(l)}(n+1) = w_{ij}^{(l)}(n) + \eta \delta_i^{(l)}(n) z_j^{(l)}(n)$$

BP Algorithm

- Derivative computation

$$y' = 1 - y^2$$

For tansigmoidal transfer fn

$$y' = y(1 - y)$$

For logsigmoidal transfer fn

- Implementation needs multiplier/squarer and adder/subtractor

$$y' \approx \frac{y(x + \delta x) - y(x)}{\delta x}$$

Forward difference approx

$$y' \approx \frac{y(x + \delta x / 2) - y(x - \delta x / 2)}{\delta x}$$

Central difference approx

- Implementation needs switched capacitor to introduce small voltage.
- Asymmetry eliminates need of switched capacitor and supporting circuitry

Parallel Perturbative Algorithm



- If ($\text{Error}(k) < \text{Error}(k-1)$) then
 - $\text{SmallRandomPerturb}(\text{Weights}(k))$
- Else $\text{Restore}(\text{Weights}(k-1))$ and
 - $\text{SmallRandomPerturb}(\text{Weights}(k-1))$

Low Power Neurons

Differential Transconductance Amplifier

$$I_1 = I_{SS} \frac{1}{1 + e^{-q\kappa V_{diff} / kT}}$$

  
$$I_2 = I_{SS} \frac{1}{1 + e^{q\kappa V_{diff} / kT}}$$



Differentiation



- Central Difference Approximation
 
$$I'(V_{diff}) = \lim_{\Delta V \rightarrow 0} \frac{I(V_{diff} + \Delta V) - I(V_{diff} - \Delta V)}{2\Delta V}$$




Differentiation

$$I = I(V_{diff} + \Delta V)$$

  


$$V_{diff} = V_{in1} - V_{in2}$$

Differentiation

 


$$I = I(V_{diff} - \Delta V)$$


$$V_{diff} = V_{in1} - V_{in2}$$

 


Differentiation

 

 Derivative of Neuron Activation Function (DNAF)




$$I = I(V_{diff} - \Delta V)$$

 


$$I = I(V_{diff} + \Delta V)$$

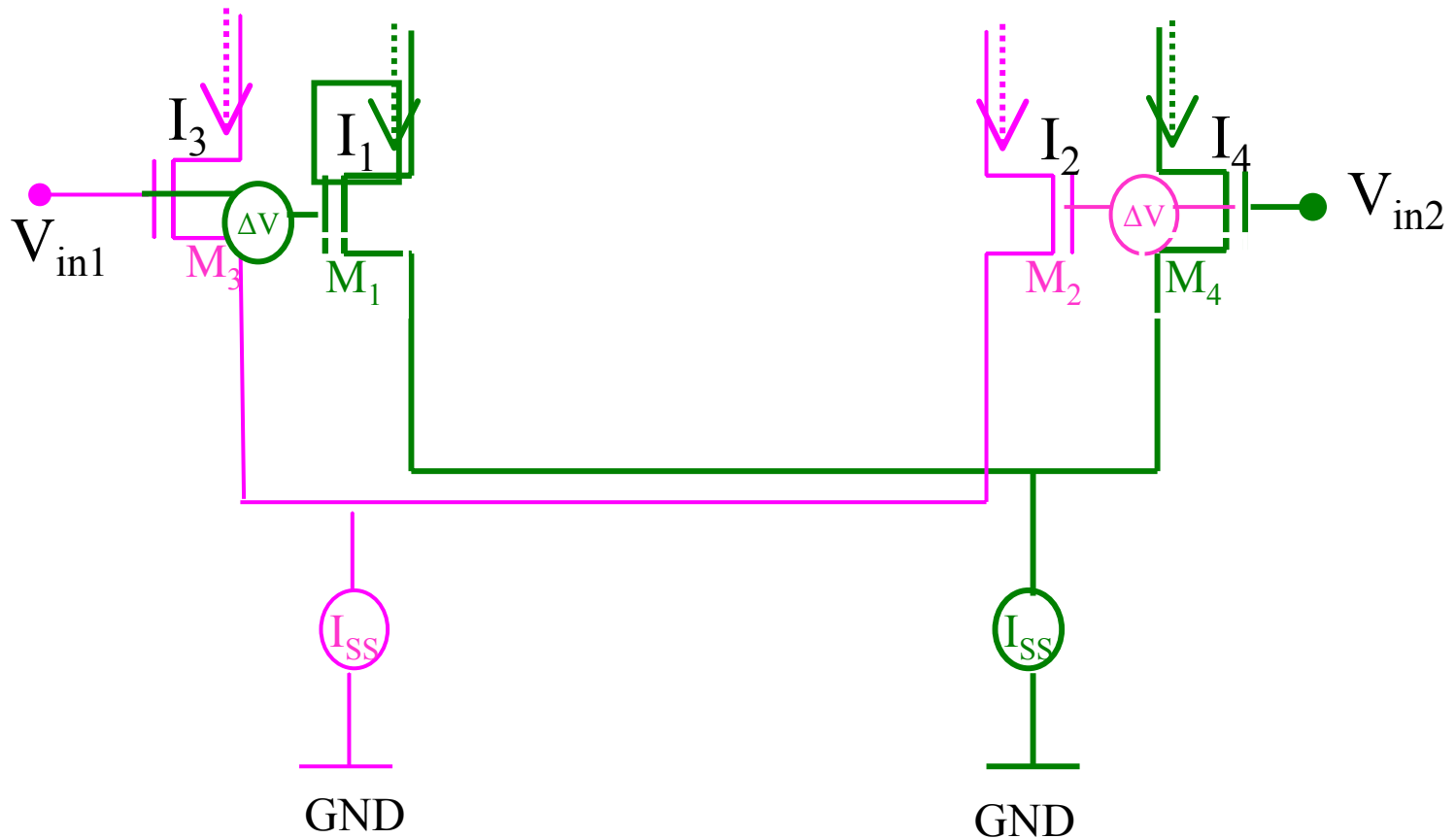
Derivative of Neuron Activation Function (DNAF)



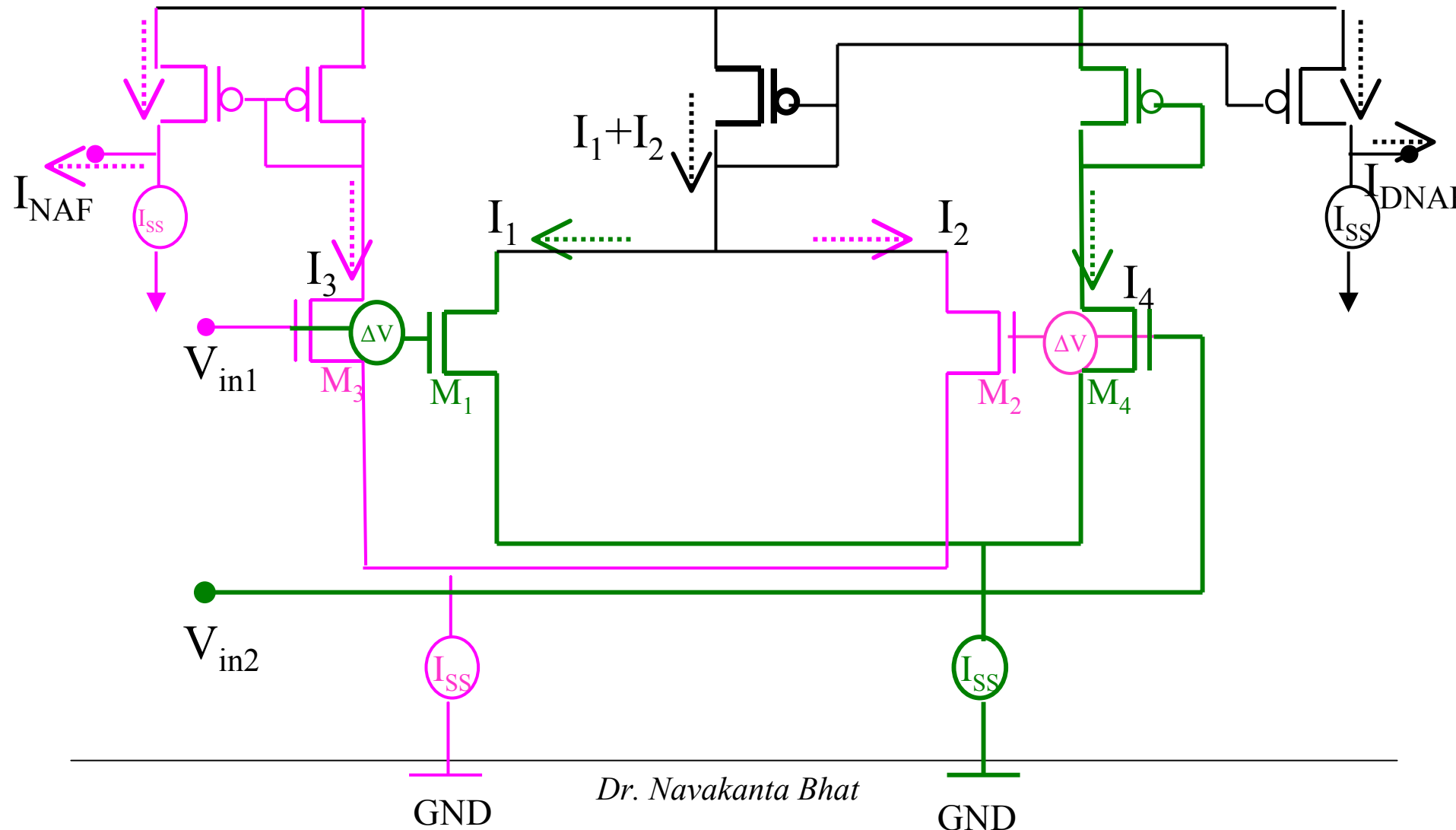Neuron Circuit (with External Offset Voltage)




Source Degeneration

 


- To increase the range of input voltage over which the diff pair behaves approximately as a linear amplifier.
- To increase the input impedance.
- To stabilize the gain (negative feedback)

 
Effect of Source Degeneration on NAF/DNAF




NAF

 


DNAF

 

Offset Voltage

 


Asymmetric differential pair

 

Symmetric differential pair

Offset Voltage

 

$$V_{OS} = V_{GS1} - V_{GS2}$$


$$V_{GS} = \frac{kT}{\kappa q} \ln\left(\frac{I}{I_0}\right)$$

$$I_1 R_{L1} = I_2 R_{L2}$$

$$V_{OS} = \frac{kT}{\kappa q} \ln\left[\frac{R_{L2} (W/L)_2}{R_{L1} (W/L)_1}\right] + \Delta V_{Th0}$$




Symmetric differential pair

Offset Voltage Vs Asymmetry

 


$$\text{Asymmetry} = \frac{\Delta W / L}{W / L}$$

Asymmetry

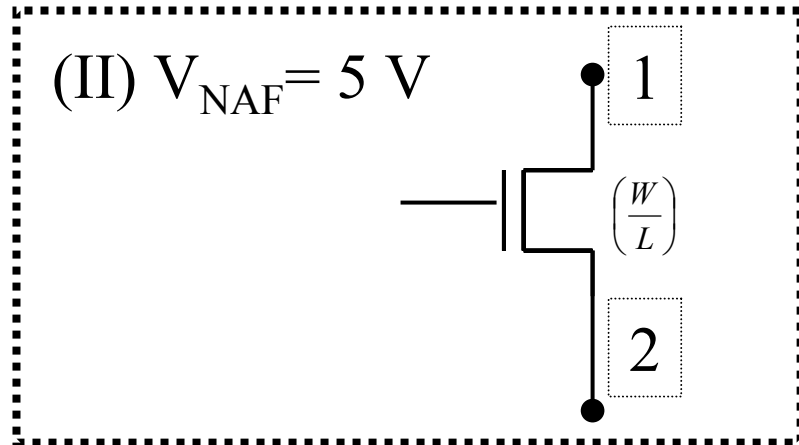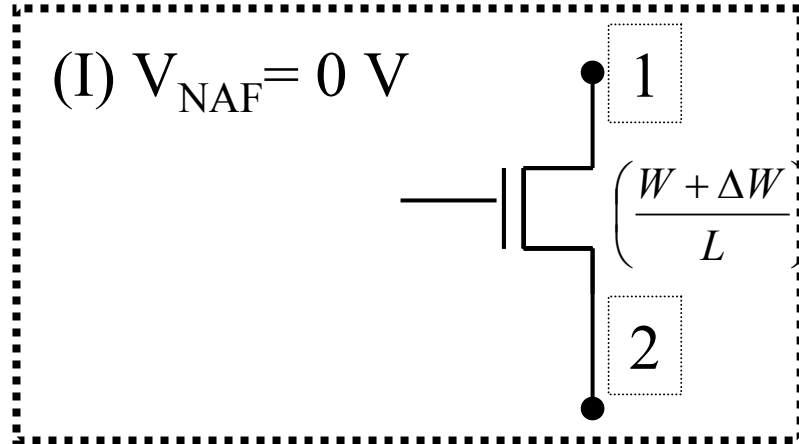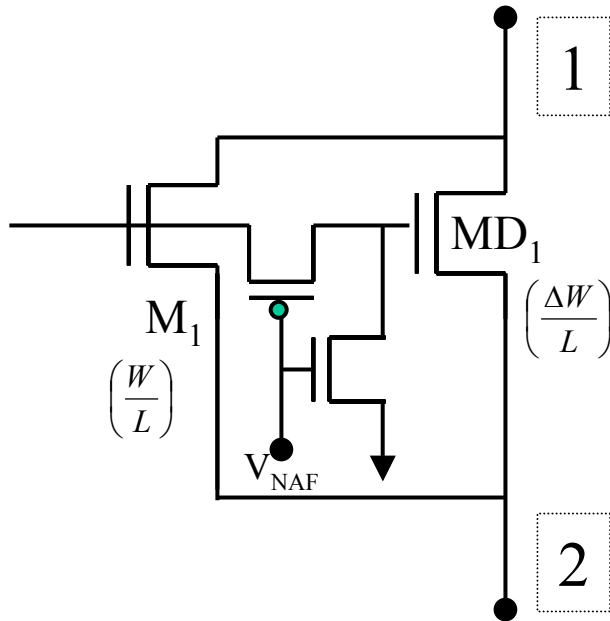


$$\text{Asymmetry} = \frac{\Delta W / L}{W / L}$$

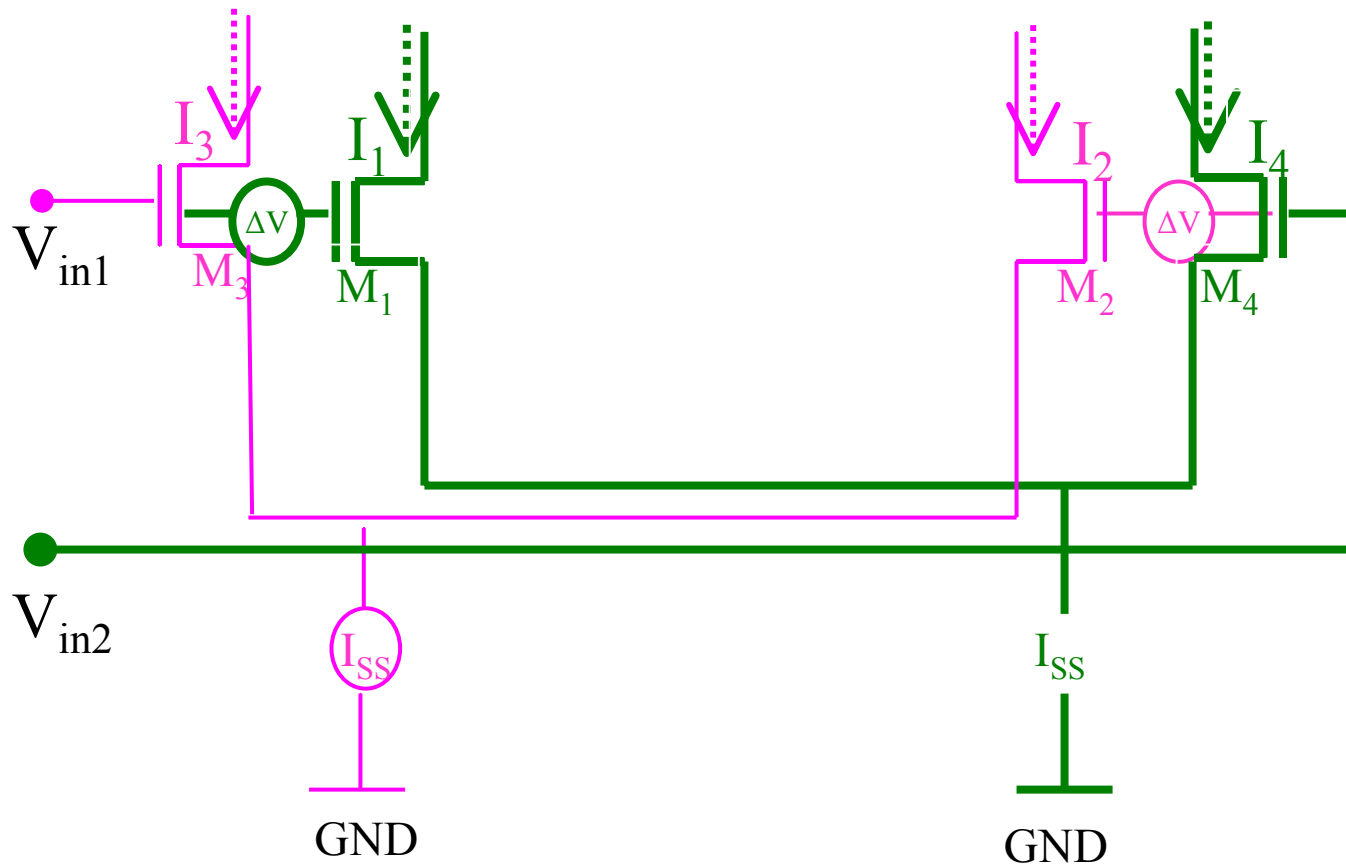
Derivative of Neuron Activation Function (DNAF)




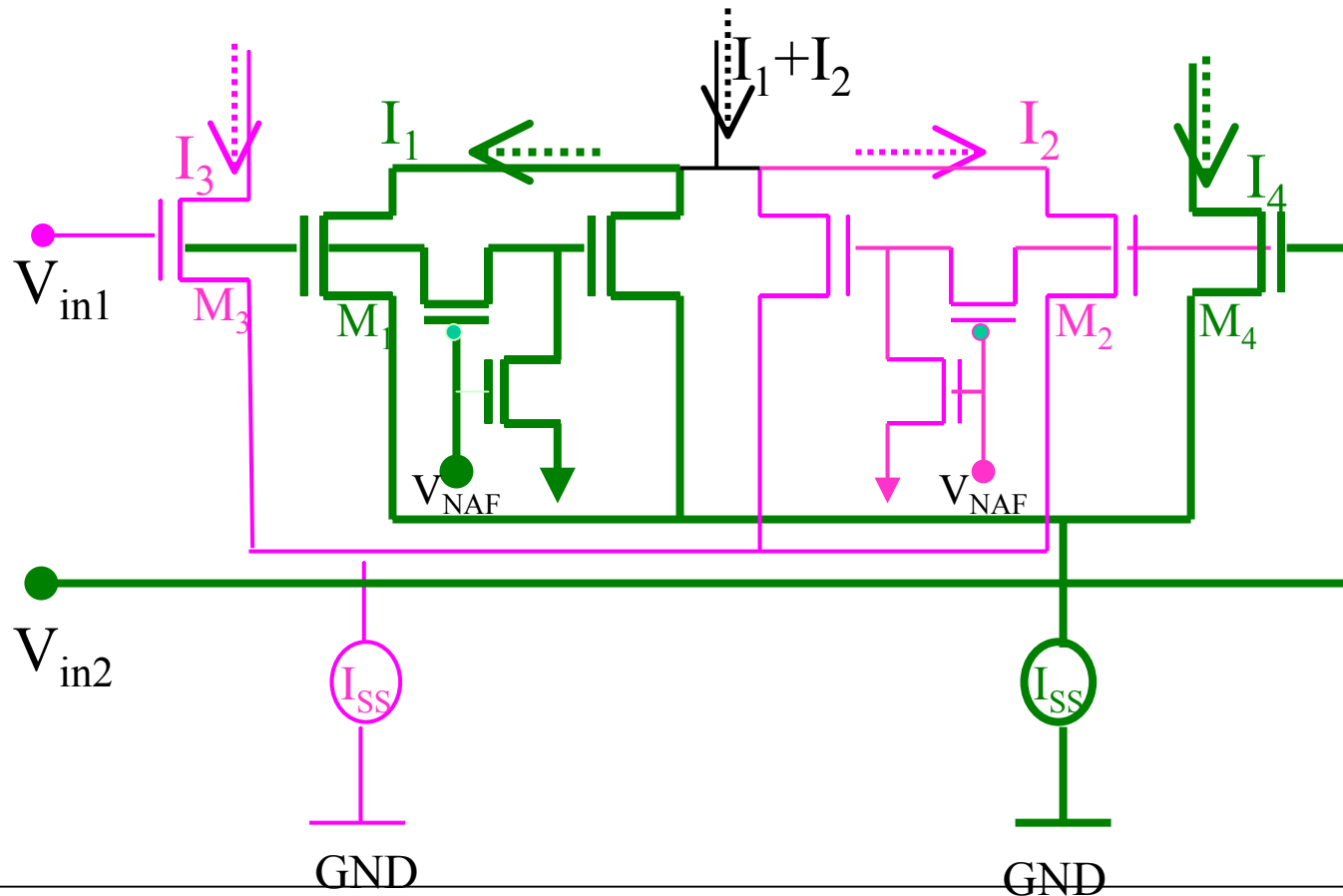
Derivative of Neuron Activation Function (DNAF)




Neuron Circuit (with Asymmetry)

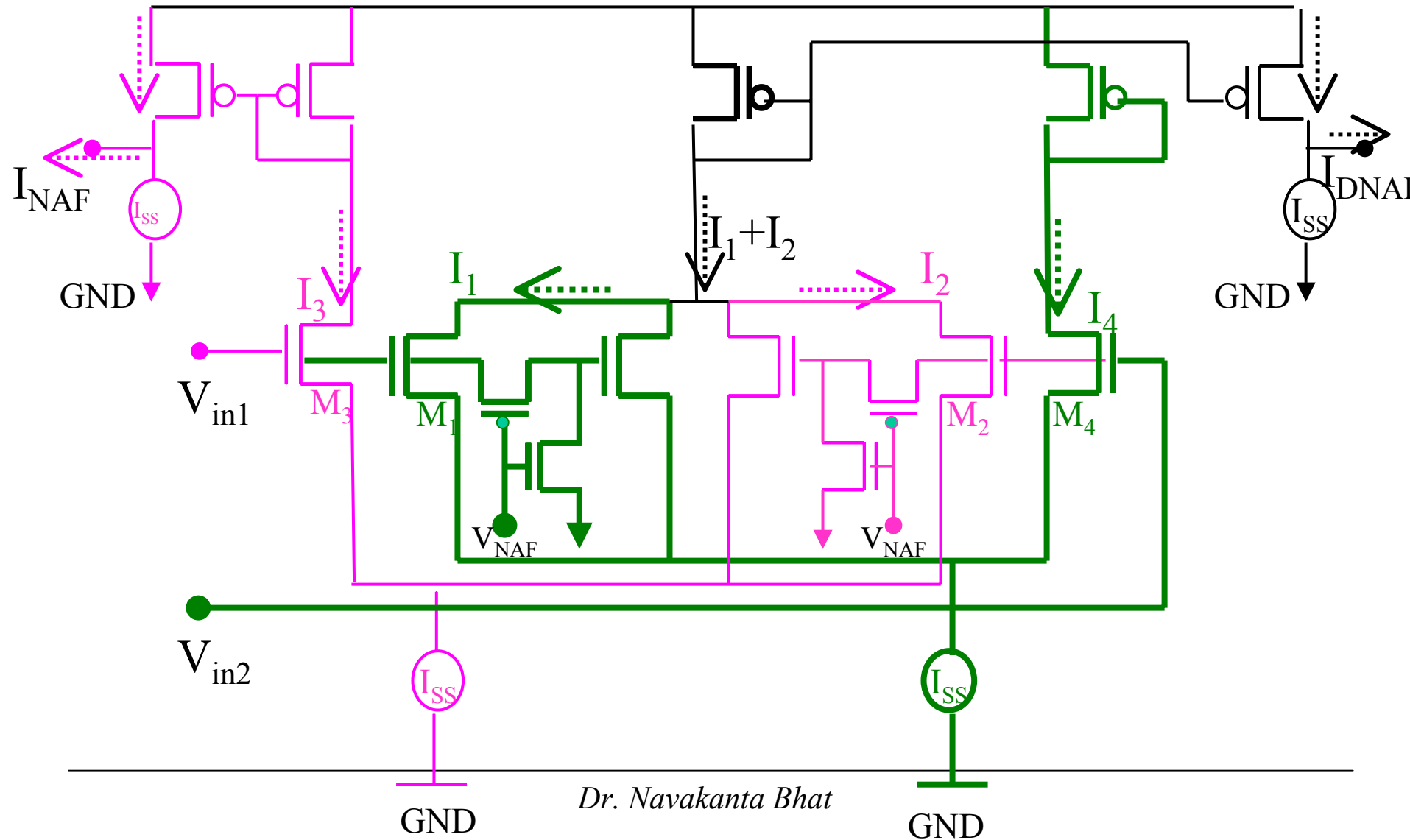


NAF & DNAF

  


Error Curves

 


RMS Error Vs Offset Voltage

 



Peak DNAF Vs Offset Voltage

 



Peak-Error-Ratio Vs Offset Voltage

 

Neuron (with External Offset Voltage)

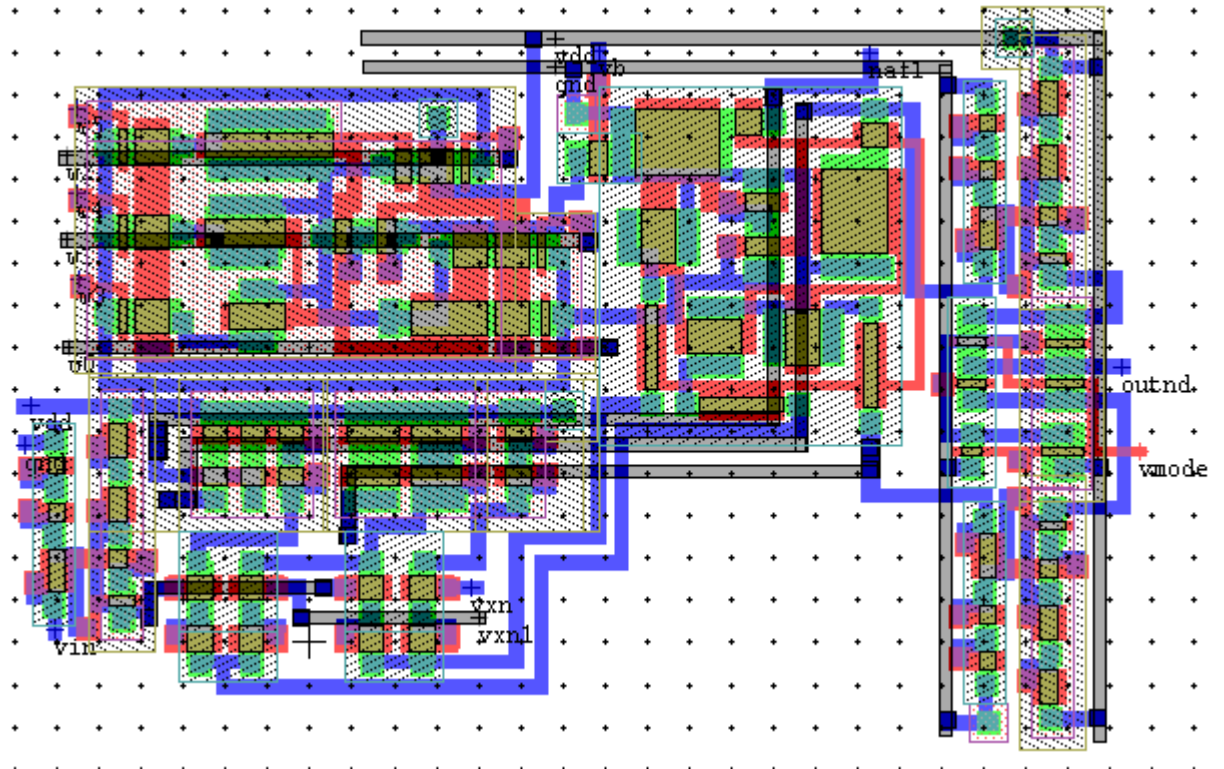 


Neuron (with Asymmetry)

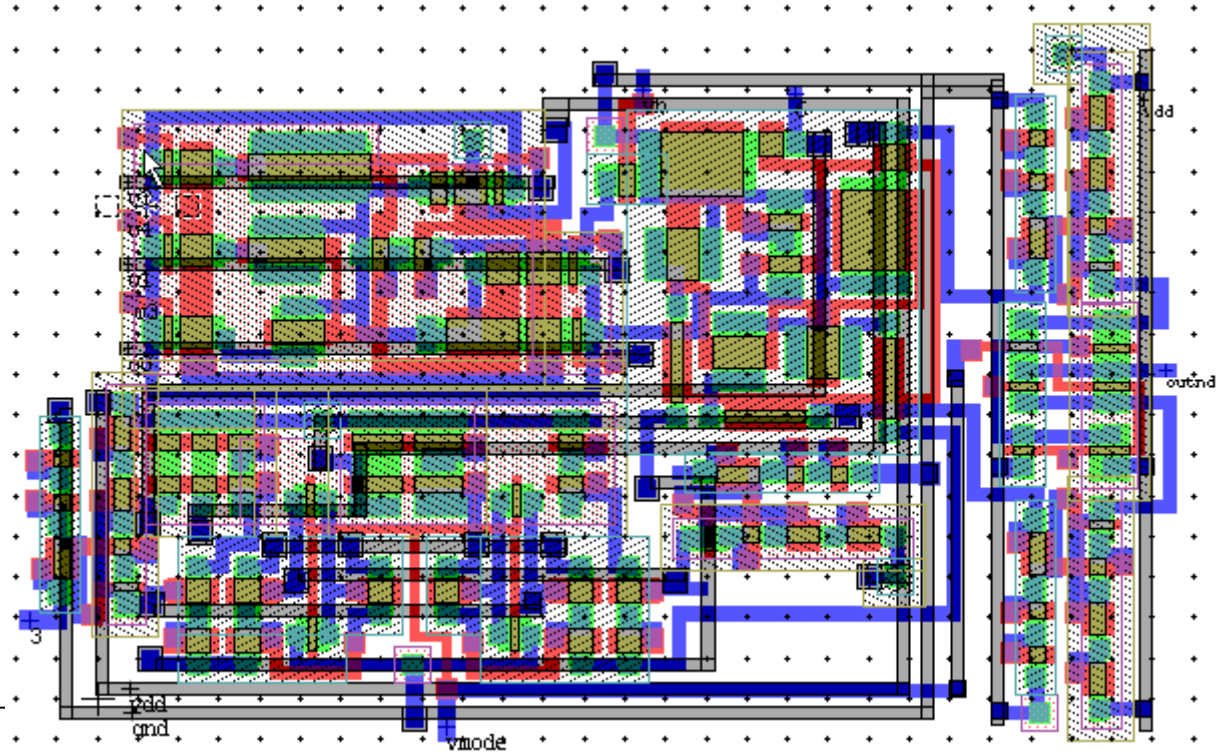 

Low Power Feedforward Neural Network


Training

•Chip-in-the-Loop Training

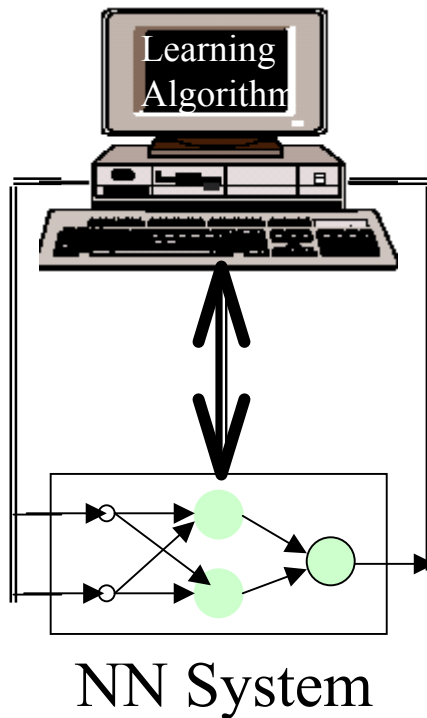

- Learning Algorithm on the host PC
- Weight update from PC
- Can accommodate for offsets & non-idealities
- Programmable Neural Network
- Flexibility in Learning Algorithm
- No learning overhead
- Serial weight update - slow learning
- PC is required for training

Feedforward Neural Network

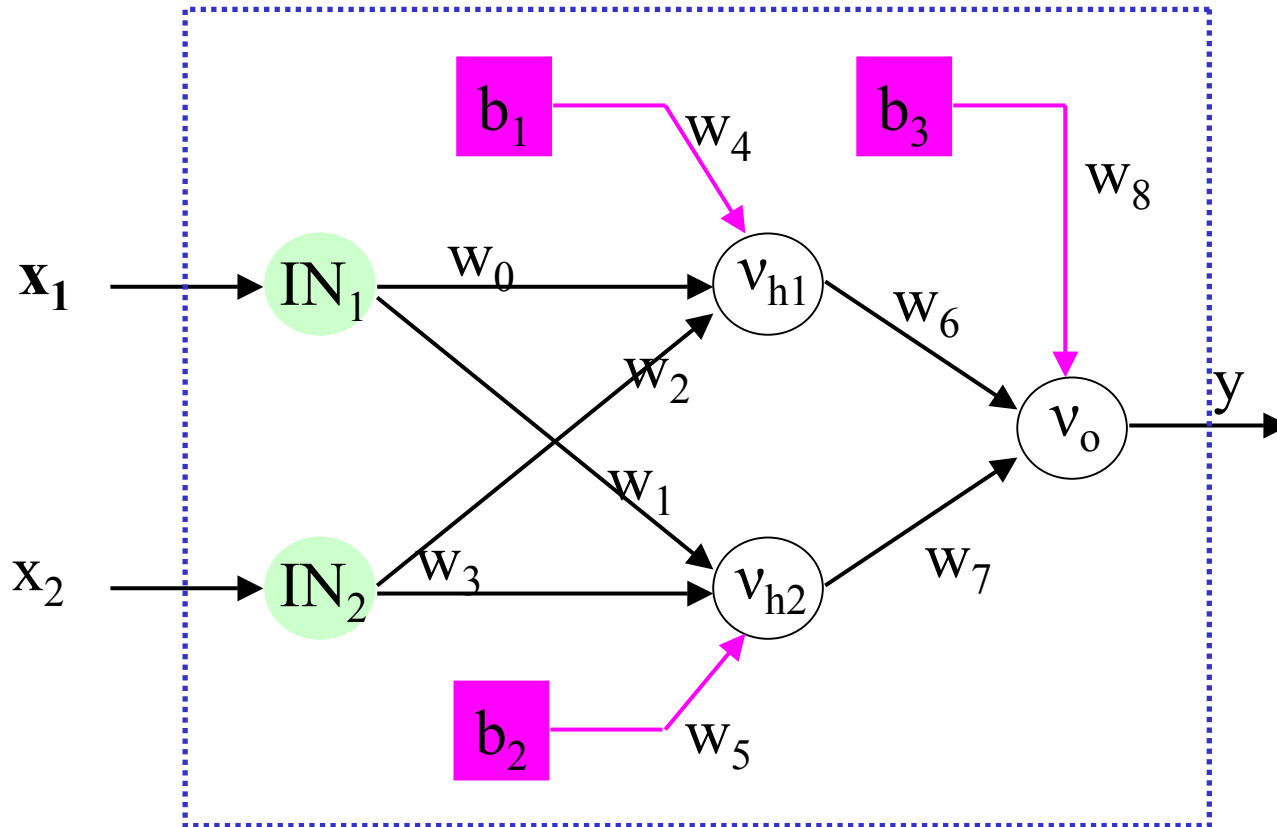


Input
Layer


Hidden
Layer

Output
Layer


Macro-Architecture

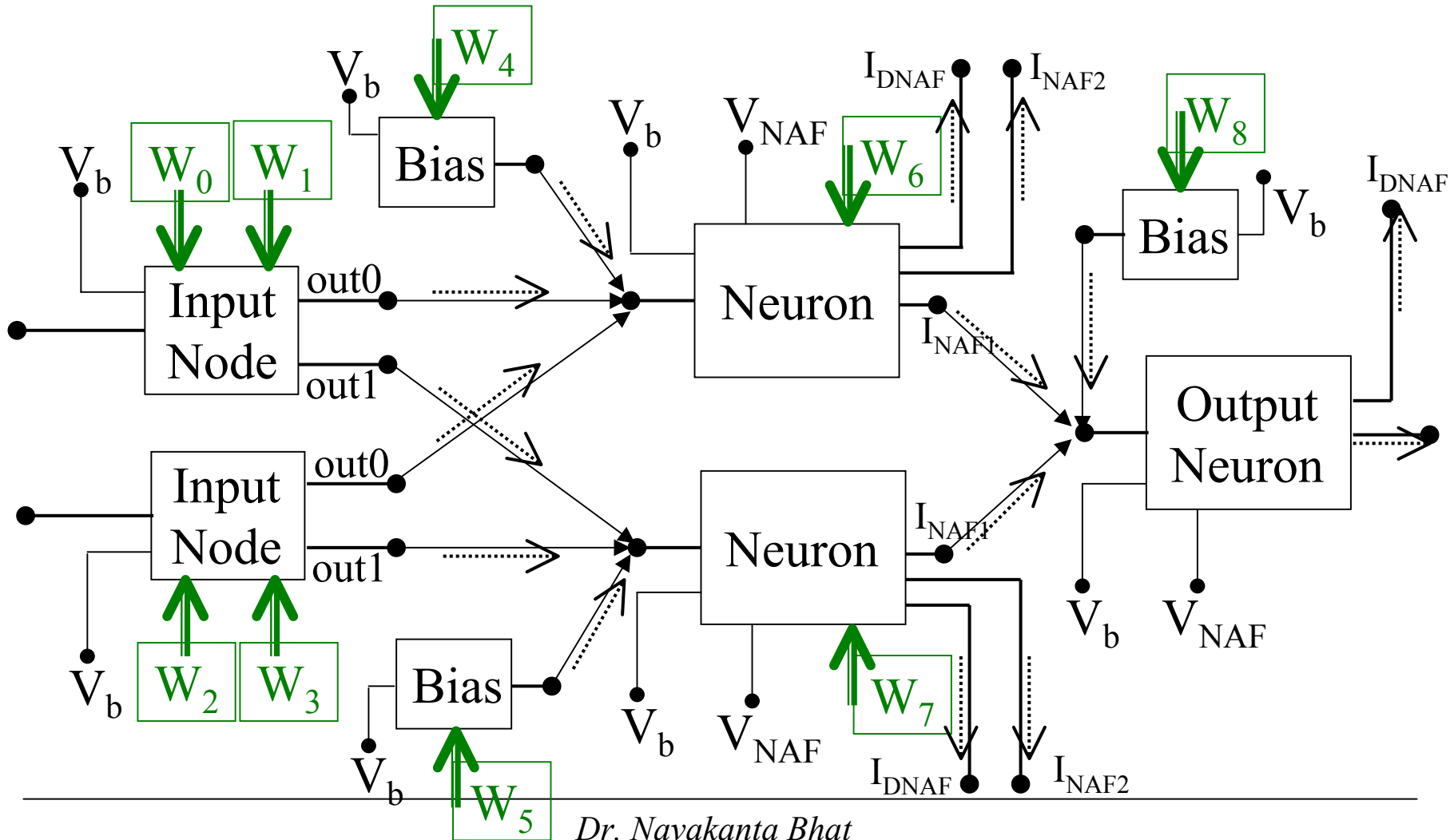


Synaptic Weights: MDAC

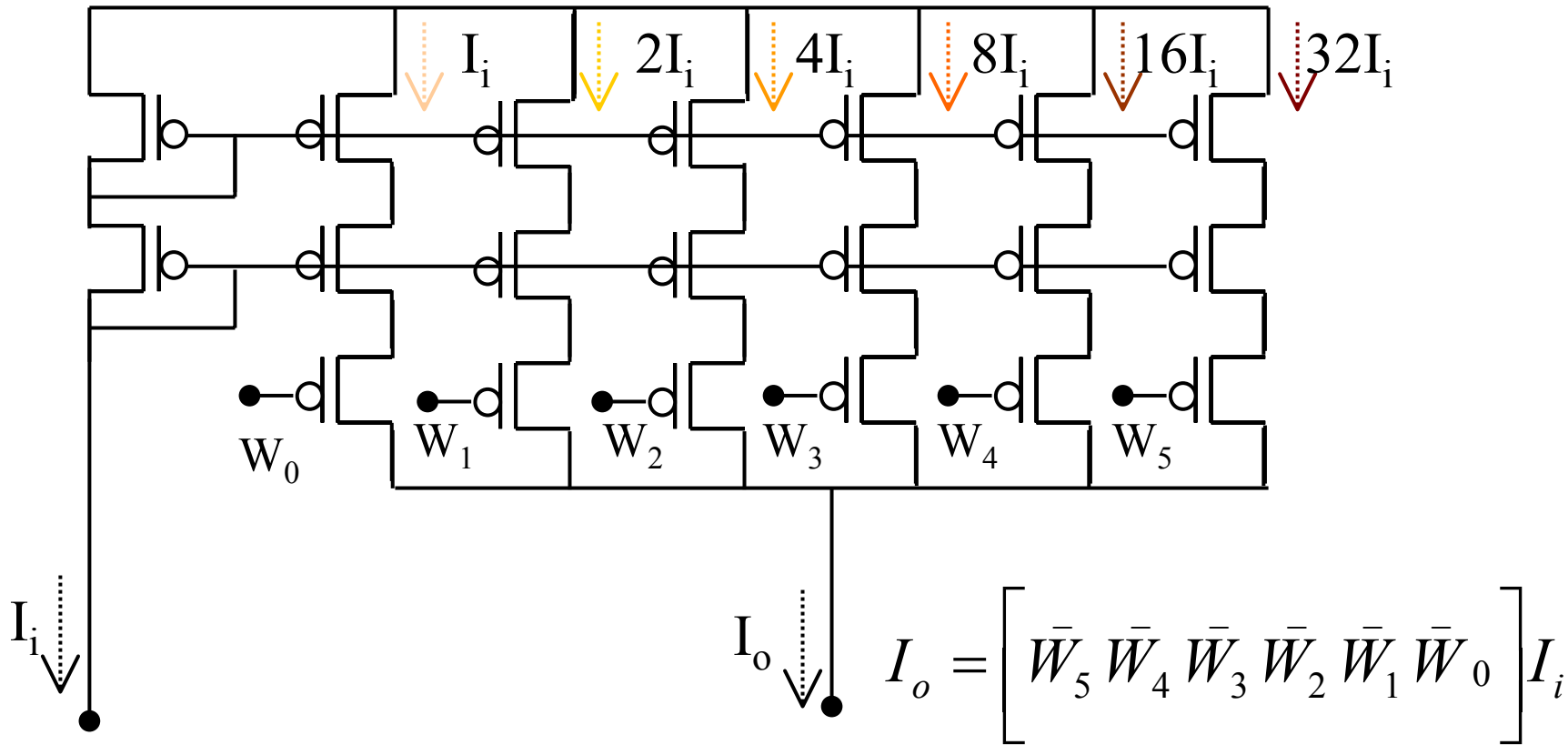


Synaptic Weights: MDAC

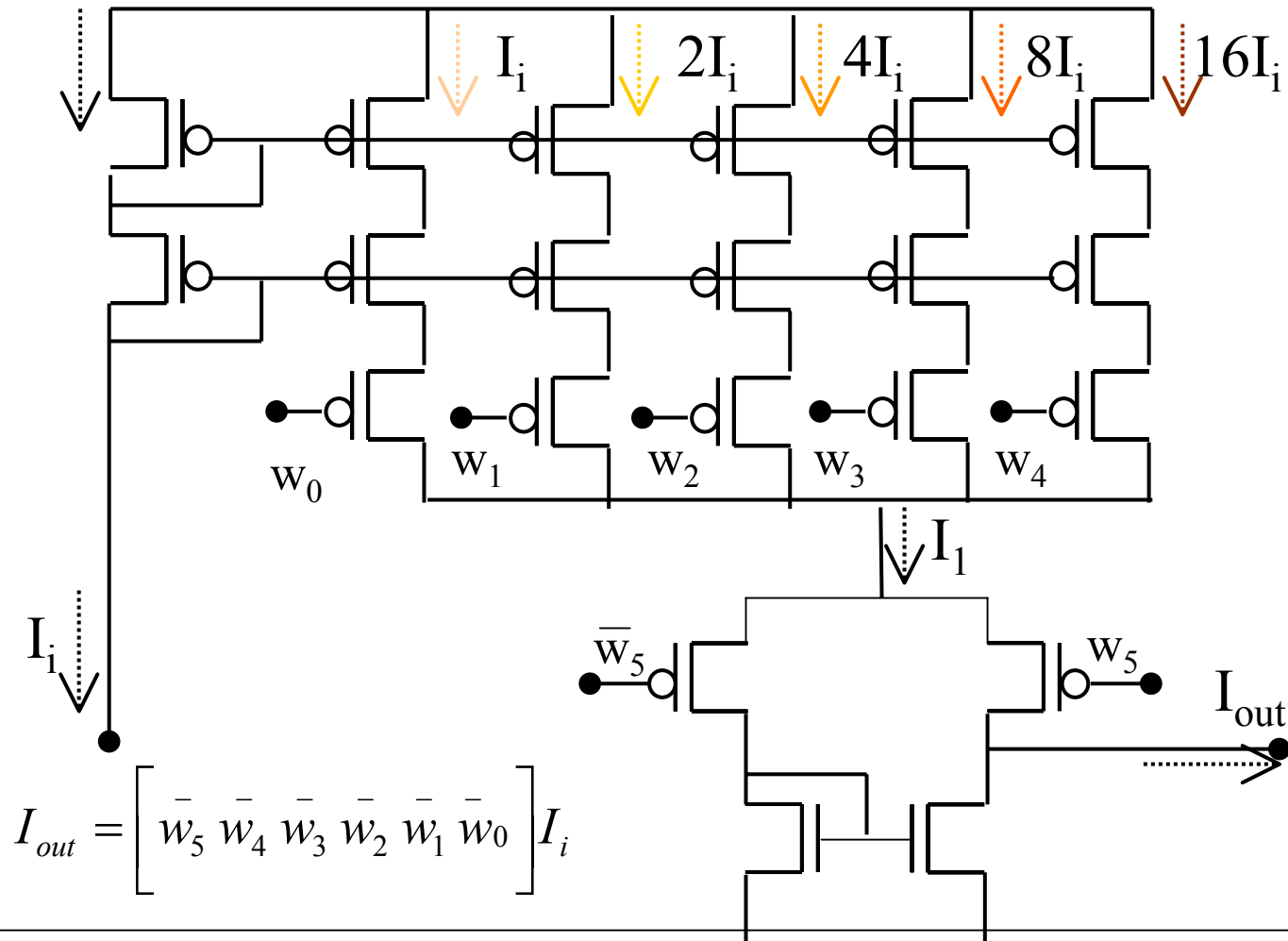

w_5 is used
as sign bit

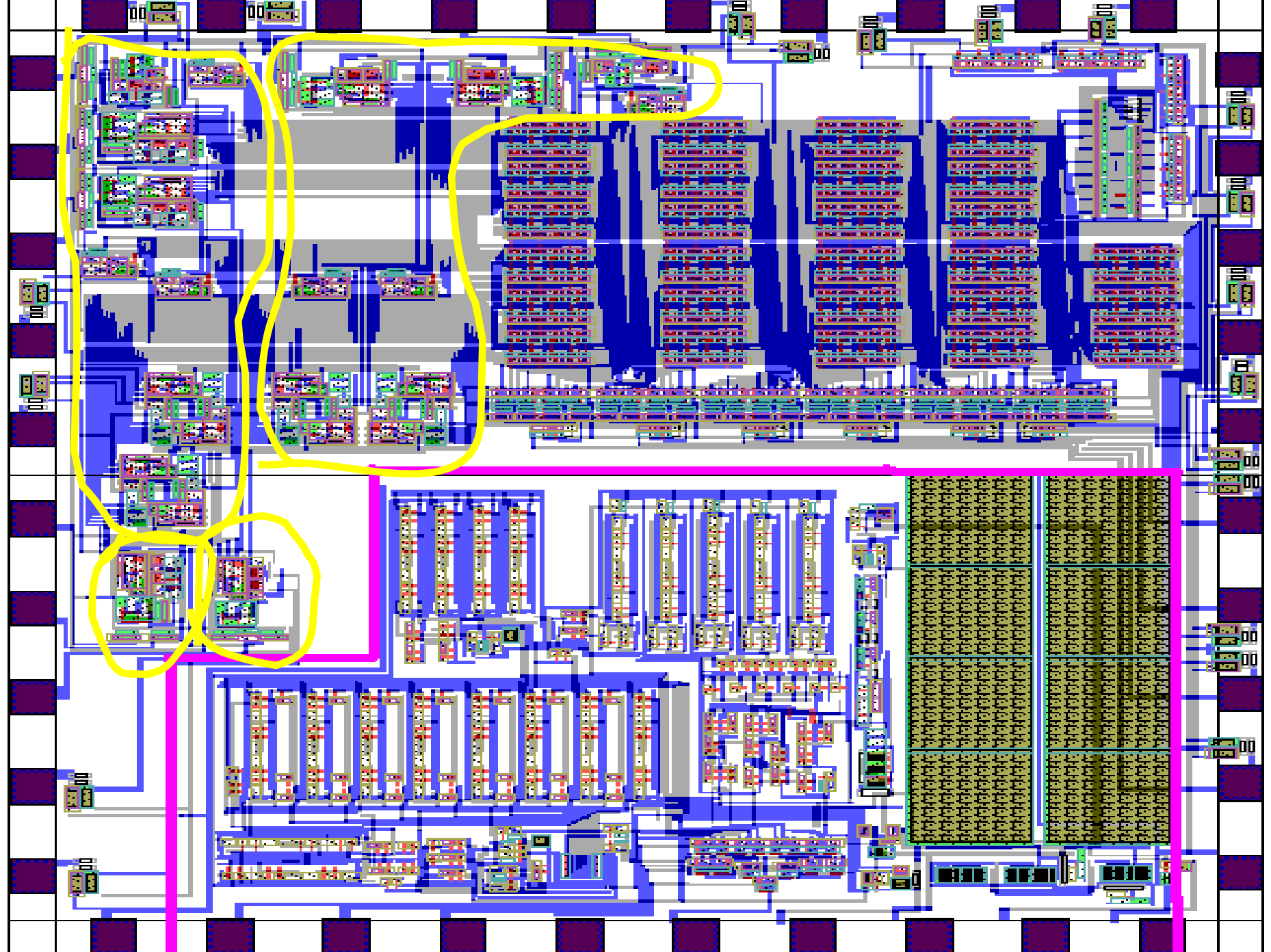


The Chip Micrograph

 


The design was prototyped through MOSIS on AMIS 1.5 μ m technology

Dr. Navakanta Bhat


Neuron (with External Offset Voltage)

 

Neuron (with Asymmetry)

 

DNAF for Neuron with Asymmetry

 


Training


- Parallel Perturbative Algorithm
- Logic OR & Logic AND Functions
- I/P patterns: (0,0), (0,5), (5,0) and (5,5)
- O/P: Logic 0 - 1.9V; Logic 1 - 2.9V

$$Error = \sum_{i=1}^4 |d_i - y_i|$$

Training with OR Function

 

Training with AND Function

 

Floating Gate Transistor as Analog Memory

FGMOS

The floating gate MOSFET can store charge on the FG

This forms a useful block in Neural Networks in order to update the weights in analog fashion


The technology has to support the double poly floating gate device

The floating gate transistor can correct itself for the of process variations

Charge storage on FGNMOS


The electron charge is stored into the FG by hot carrier Injection (program), while the charge is taken out (erase) By tunneling through oxide

 Program and erase are done only under high voltages



FGMOS with single poly?

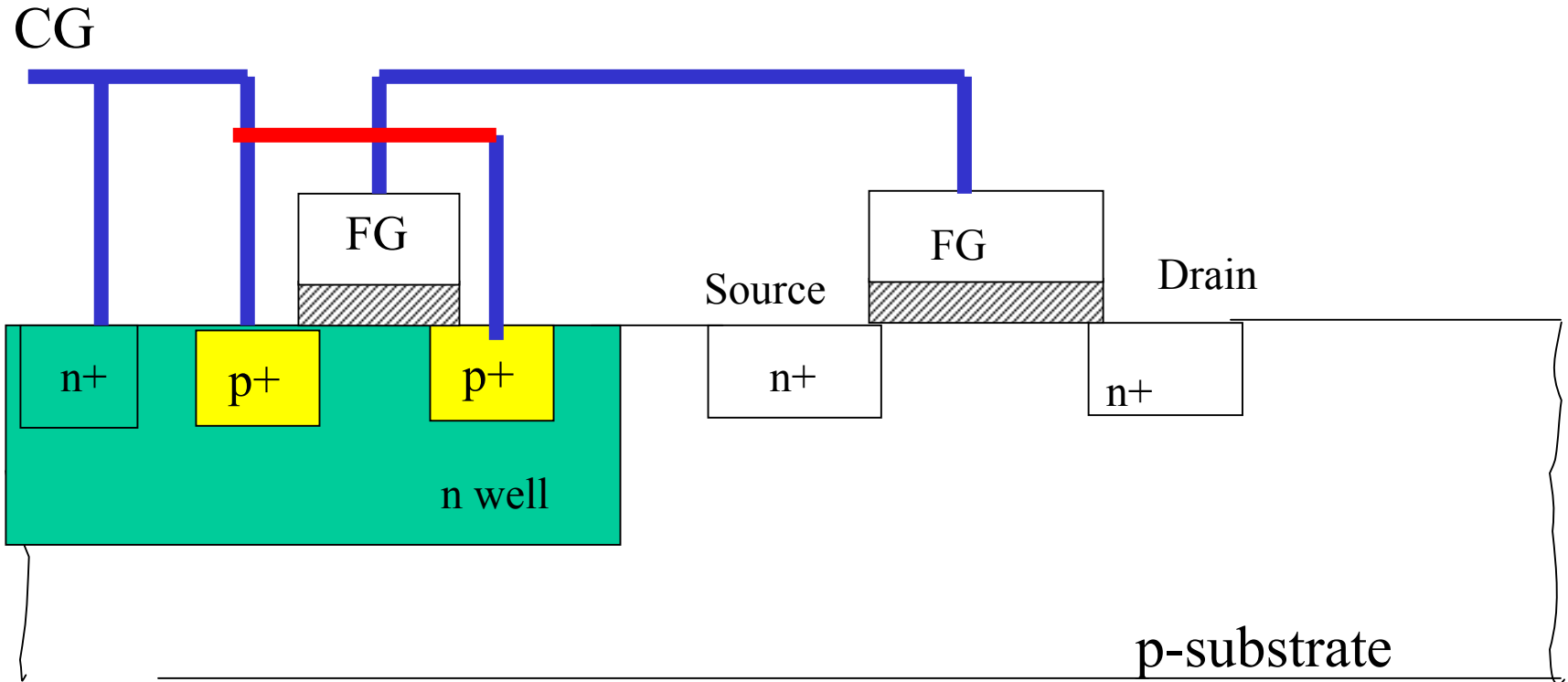There has been attempts to realize FGMOS in the conventional digital technology



This device has been reasonably successful and precision Adaptive analog circuits have been built using this