

Bob Pease
Lab notes 2005



What's All This

- Common

Mode

Rejection

Stuff?

(Anyhow....)

/RAP


PART I: HISTORY....
R.A. PEASE....

PART II -
- How to test Op amps
for CMRR

PART III
DESIGN FOR RAIL-TO-RAIL
CM Range


Part IV CIRCUIT DESIGN
FOR GOOD CMRR

ONCE UPON A TIME....

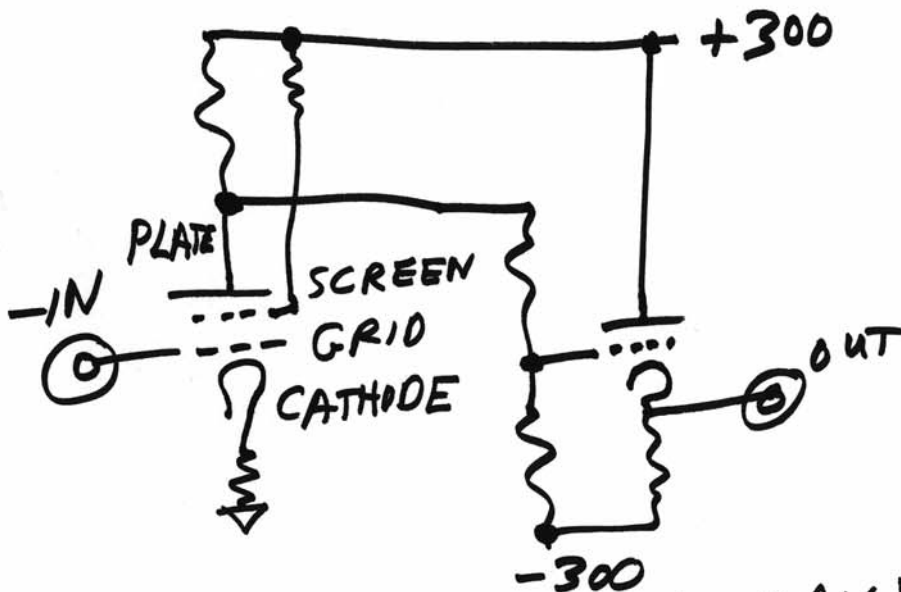


- OP AMPS DIDN'T HAVE
ANY COMMON MODE RANGE....

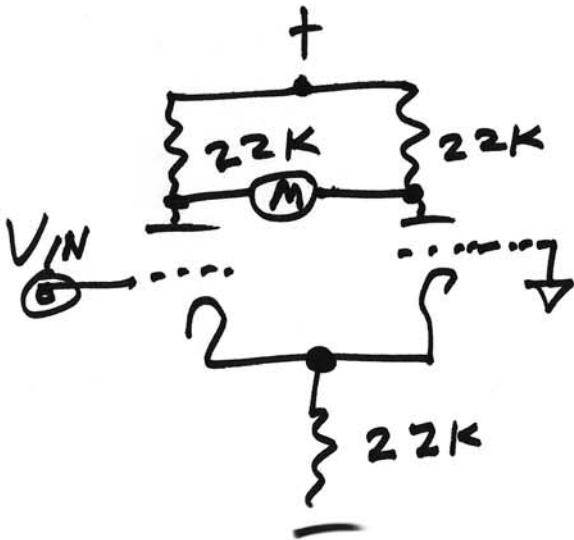YES, DIFFERENTIAL AMPLIFIERS
WERE INVENTED IN THE
1920'S...



RAP


AND THE K2-W CAME
ALONG ~ 1952

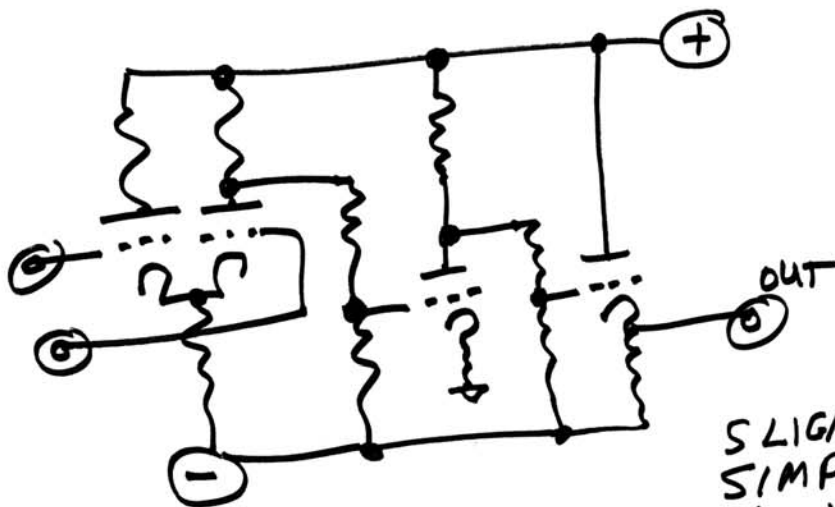

SLIGHTLY
SIMPLIFIED ...
... $\frac{1}{2}$ = 1/2 12AX7


CMRR \approx 300 for $\pm 50V$

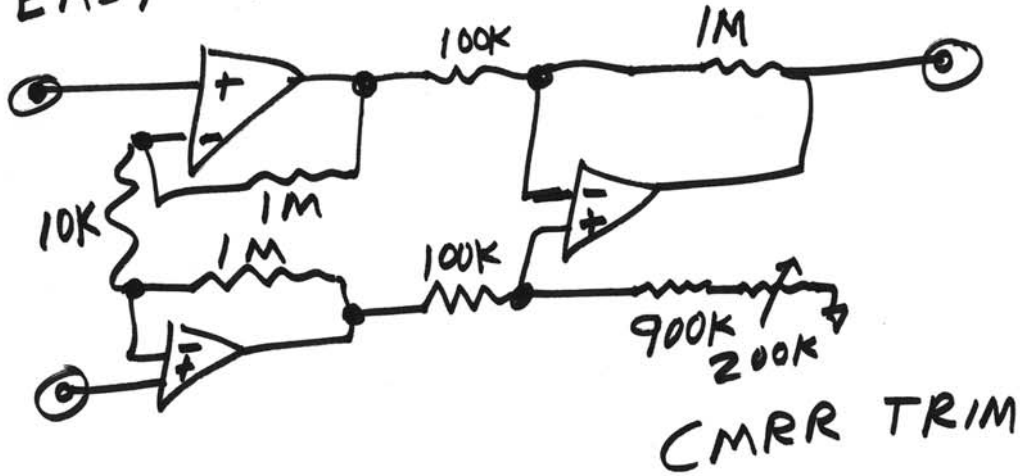STILL - Differential Amplifier
CIRCUITS WERE NOT
EASY TO DESIGN WITH TUBES...



[VOS TRIM NOT SHOWN]

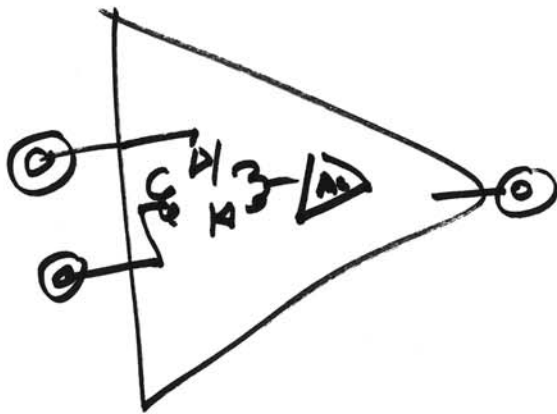
THE PHILBRICK P2 USED
8 GERMANIUM TRANSISTORS TO
PROVIDE A ± 200 VOLT
CM RANGE



THE CMRR WAS $\sim \infty$
- IN 1961....


BOB

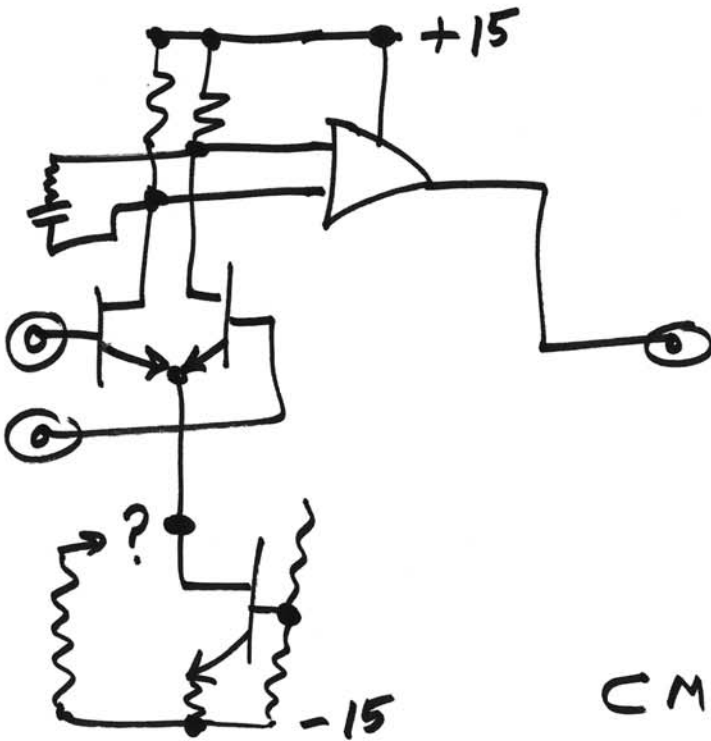SILICON TRANSISTORS
MADE GOOD OP-AMPS
POSSIBLE




CMRR > 10,000 WITH
GOOD MATCHED NPN'S....

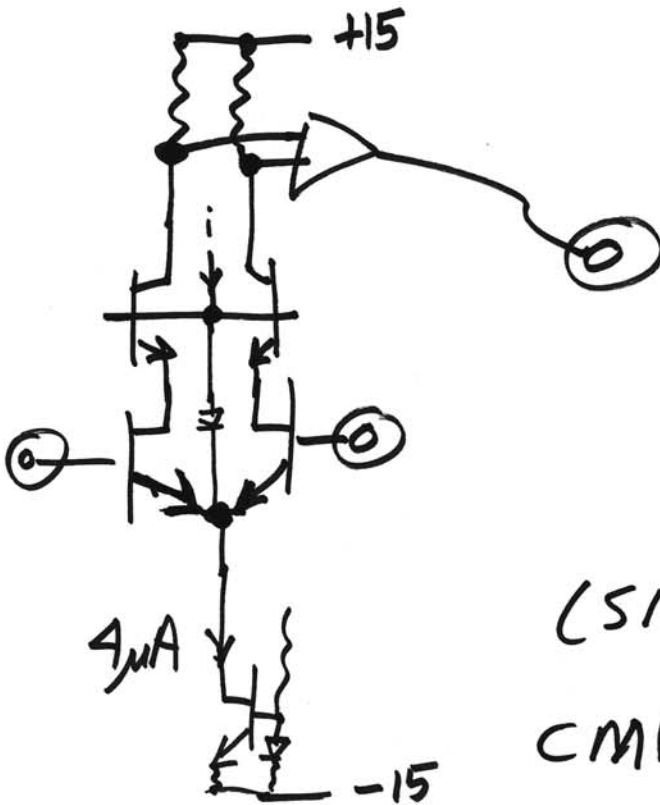BOB WIDLAR'S LM108
MADE HIGH CMRR
FEASIBLE




(SIMPLIFIED CIRCUIT)
CMRR = 100,000
TYP.

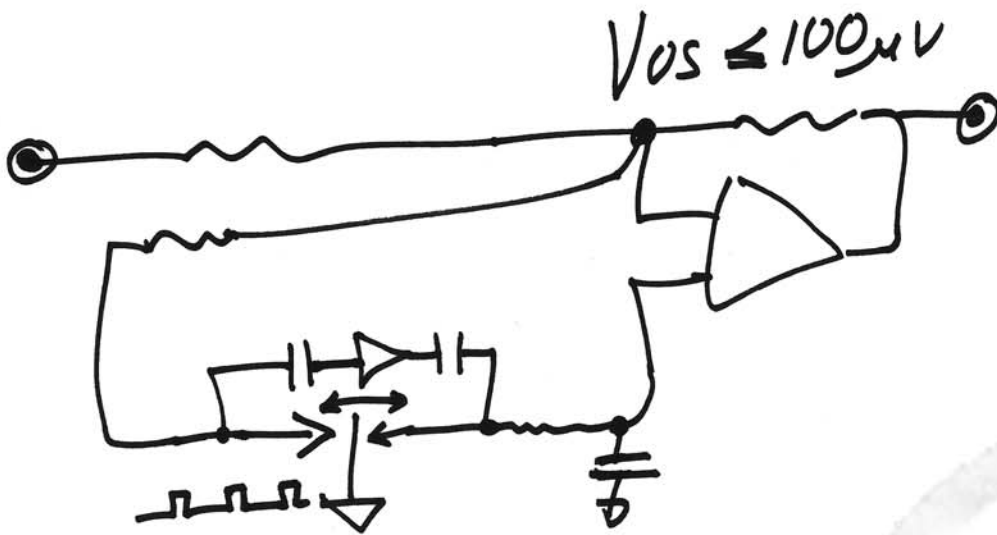CHOPPER-STABILIZED
AMPLIFIERS USED TO GIVE
LOW OFFSET - BUT ONLY AT
GROUND



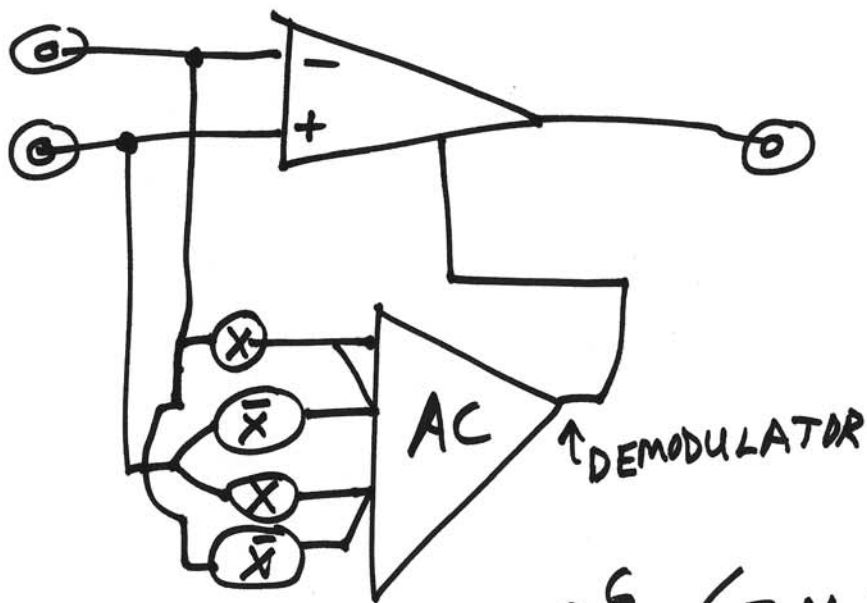CMOS CHOPPERS MAKE
GOOD CMRR FEASIBLE UP TO
+ 2.7V



CMRR > 10^6 (3M typical)

WHAT'S ALL THIS

COMMON

MODE

REJECTION
STUFF?


(ANYHOW.....?)

PART II:

HOW TO MEASURE


OP-AMP CMRR....

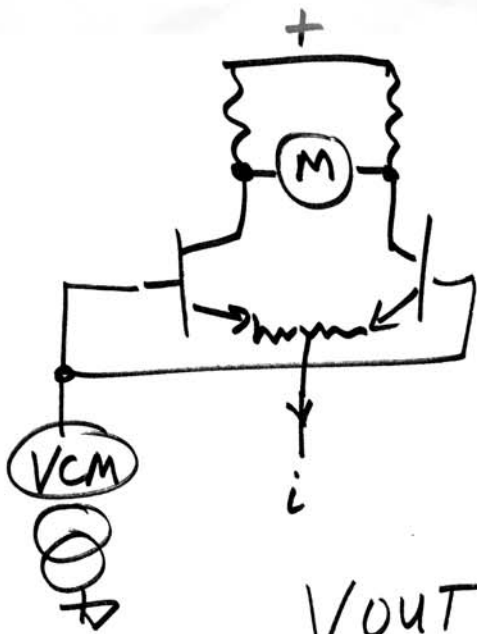OK - NOW WE HAVE GOOD
OP-AMPS - HOW TO MEASURE?




$V_{OUT} = A_V \times V_{CM} / CMRR$
BUT THIS ONLY WORKS FOR
LOW GAIN - NOT FOR
OPAMPS...

IS THIS A GOOD WAY TO
MEASURE CMRR?

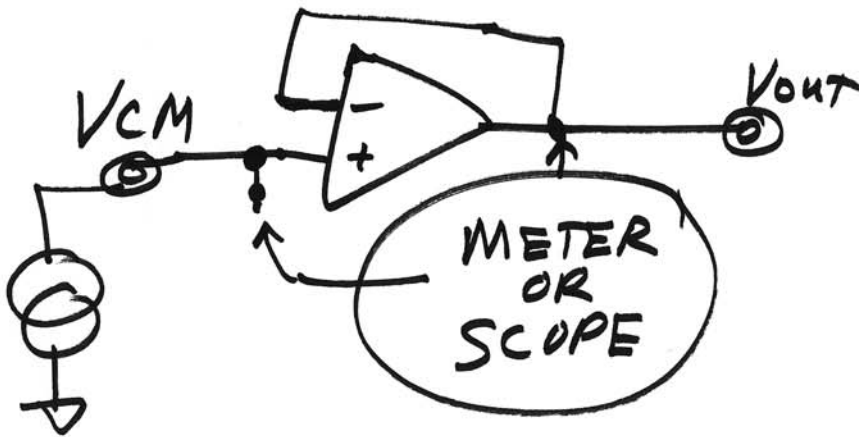


- NO -

RAP

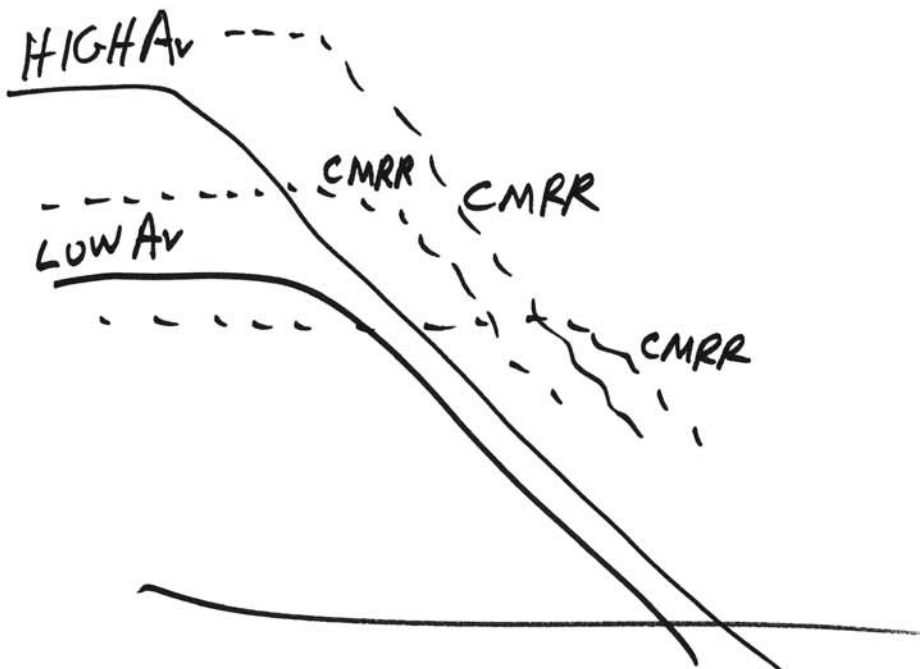


IN GENERAL - YOU CAN'T PREDICT
 HIGH OR LOW DC GAIN OR CMRR,
 HIGH OR LOW AC GAIN OR CMRR.

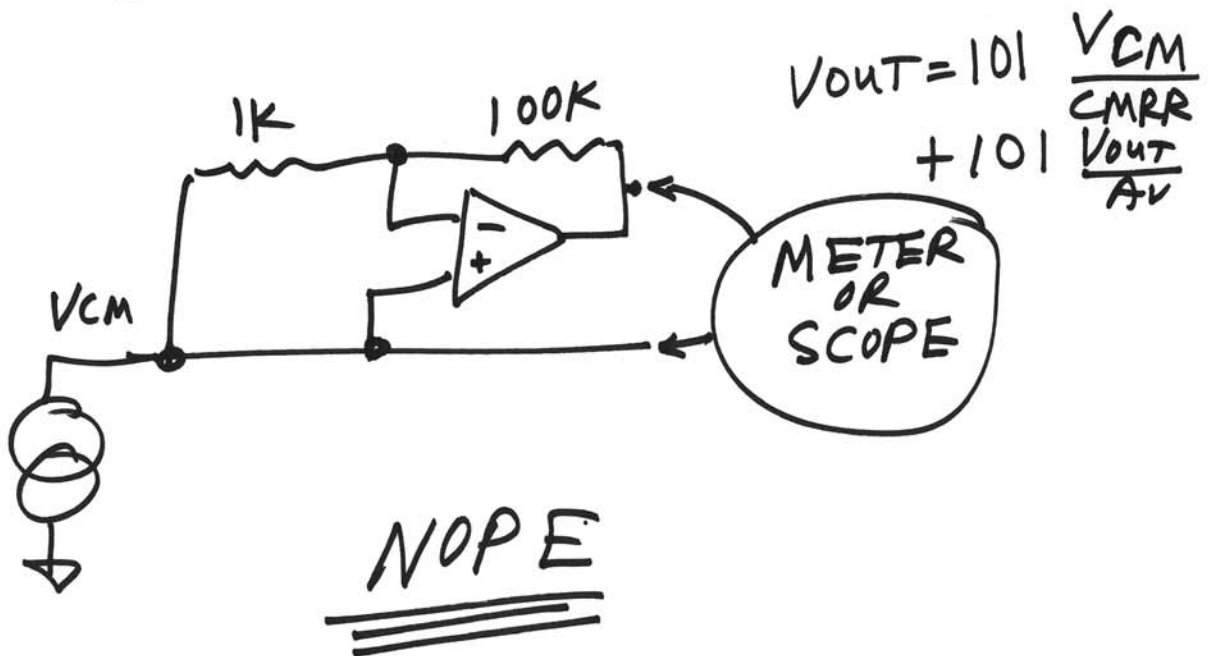AH - THIS MUST BE A
GOOD WAY TO MEASURE CMRR



THIS HAS TO BE GOOD

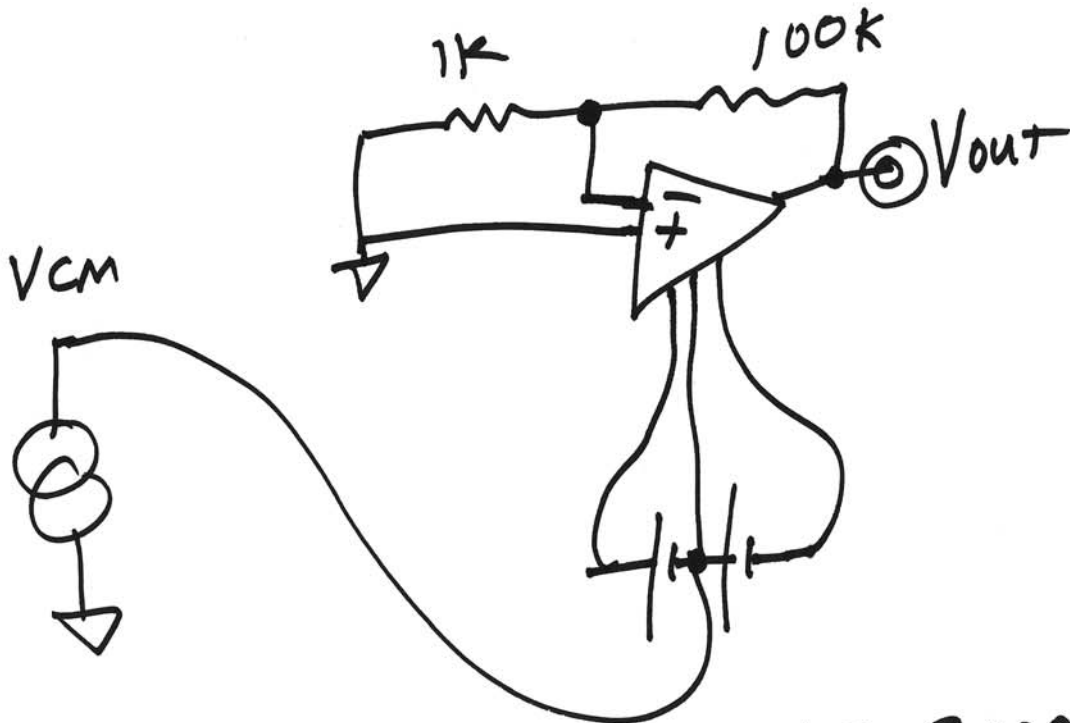


U.H. - U.H. NOT GOOD

$$V_{out} = 101 [V_{cm} / CMRR + V_{out} / A_v]$$


RAP 2005

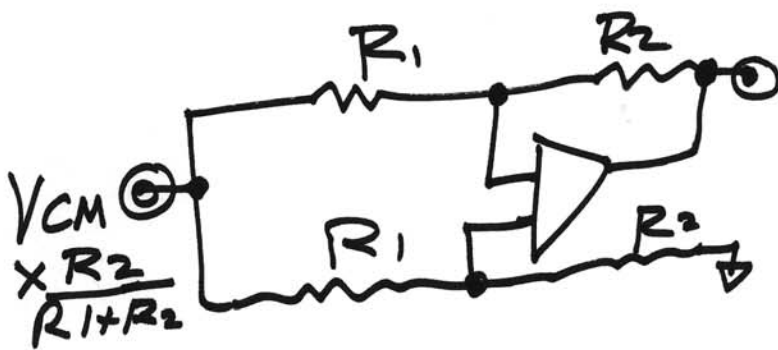OK, HOW ABOUT THIS?
- ASSUME PERFECT RESISTORS



- THIS IS GOOD - NOW -
WHERE DO WE GET THE
"PERFECT R'S"??

AHA - WE'VE GOT IT!!

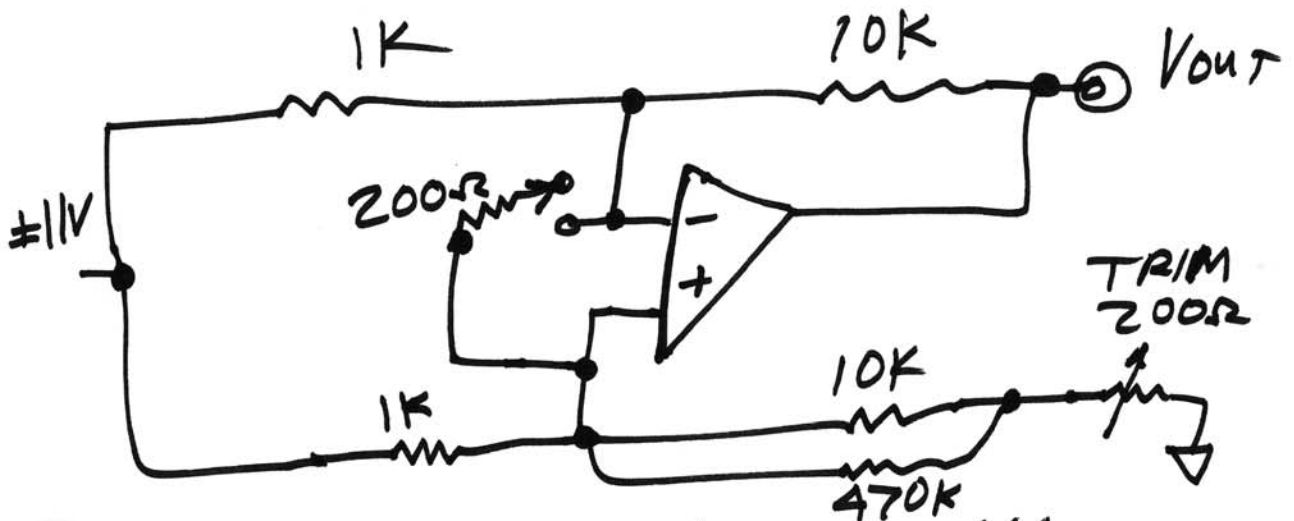


$$\text{NOISE GAIN} = 11 \text{ - or - } 111$$

$$\text{So } V_{\text{out}} (\text{p-p}) = (V_{\text{cm}} / \text{CMRR}) \times 11 \text{ or } 111$$

$$\text{THUS - } V_{\text{cm}} / \text{CMRR} \times 100 = \Delta V_{\text{out}}$$

WHAT IF YOU NEED TO
MEASURE CMRR > 110dB?


EASY!

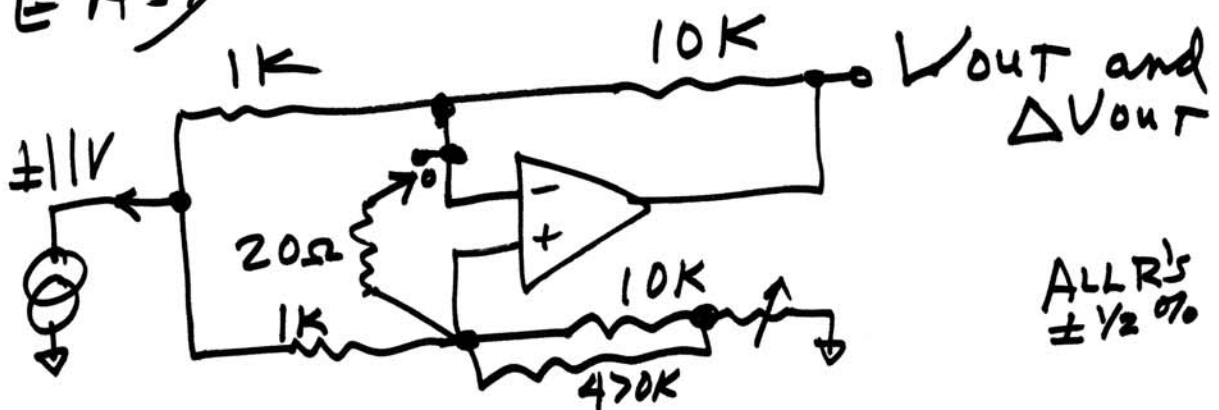

NOISE GAIN = 11 or 1011

SO $\Delta V_{out} = [V_{CM} / CMRR] \times 1000$

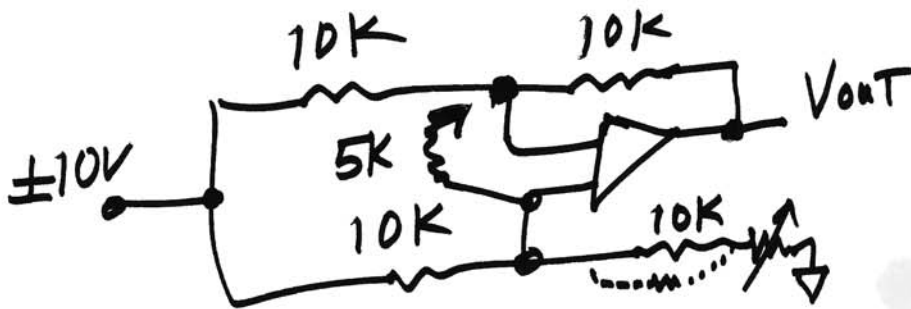WHAT IF YOU NEED
TO MEASURE CMRR
FOR 50KHz?



$$NG = 2 \text{ or } G$$


$$A \times V_{CM} / CMRR = \Delta V_{OUT}$$

$$BW \approx GBW / 10$$


CAUTION!
DC CMRR

Ac CMRR

NONLINEAR
ERROR
DUE TO
CM
SLEW
LIMIT

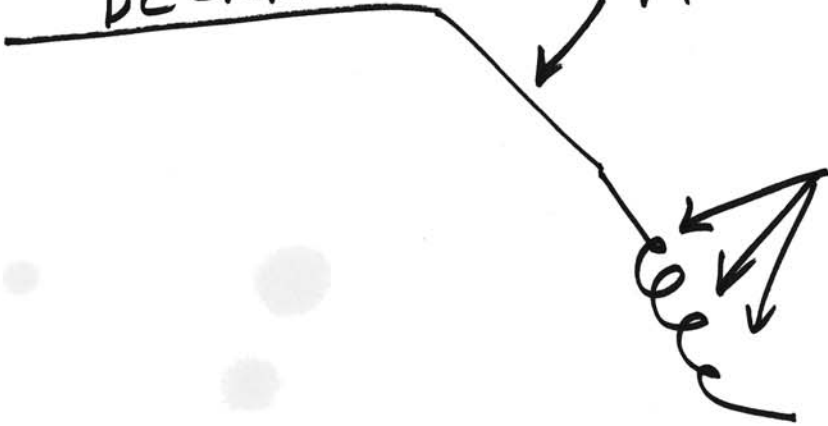

ANOTHER VALID WAY
TO MEASURE CMRR:

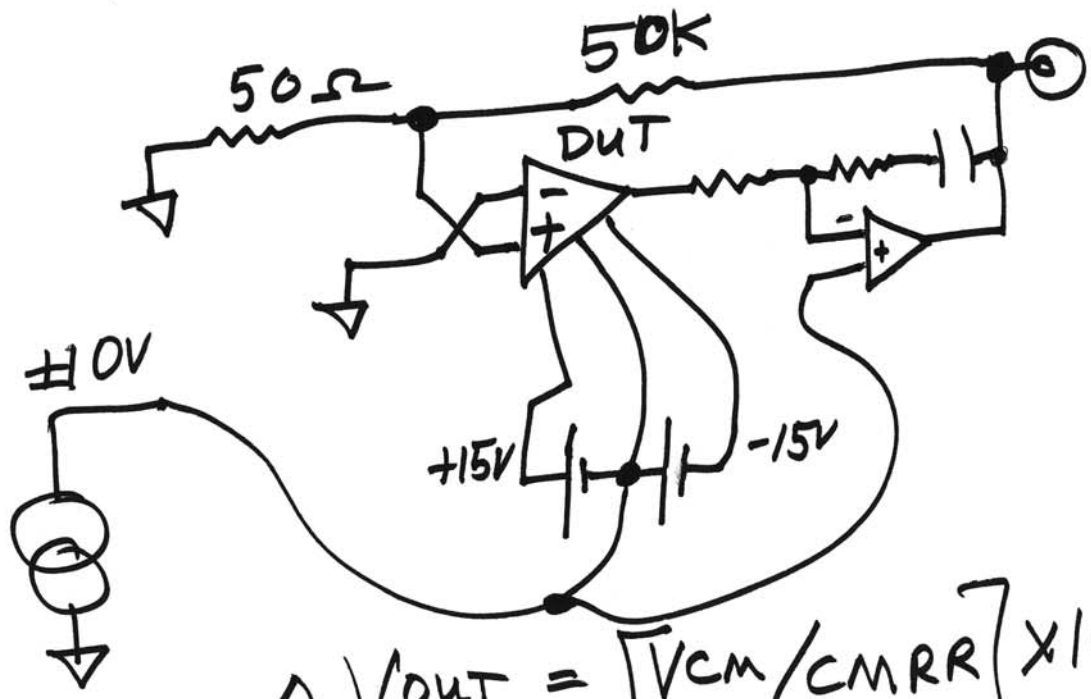

$$\Delta V_{out} = [V_{cm} / CMRR] \times 1000$$

BUT,
BEWARE, THIS WORKS
ONLY AT DC & VERY
LOW FREQUENCIES.

- AC ERRORS ARE -
- UNSPECIFIED.

/RAP

What's All This

COMMON
MODE

REJECTION

STUFF?

(Anyhow.....)

Part III -
Rail-to-Rail
CM Range

RAP

LIST OF TYPICAL
OP-AMPS WITHOUT
+Vs OR -Vs Rail CM Range

- LM741
- LM725
- LM108
- LM709 - and -
- MANY MANY MORE....

LIST OF OPAMPS WITH
CM RANGE TO $-V_S$
[GROUND]

- LM 358 - LM 324
- LMV324 - LMV322 - LMV321
- LMC 660 - (QUAD) LMC 662 (DUAL)
- MANY MORE -
- PLUS - ALL RAIL-TO-RAIL -
INPUT CIRCUITS


LIST OF OP AMPS
WITH CM RANGE TO $+V_S$ -

- LM101A - LM301A
- LF156 - 356
- LF411 - LFA12 (DUAL)
- LF347, LF ~~444~~
- LF351, LF 353

- AND - OF COURSE -
ALL RAIL-TO-RAIL INPUT
AMPLIFIERS


HOW TO MAKE - A - RAIL-TO-RAIL INPUT AMPL

① Pump it up - (+5V)

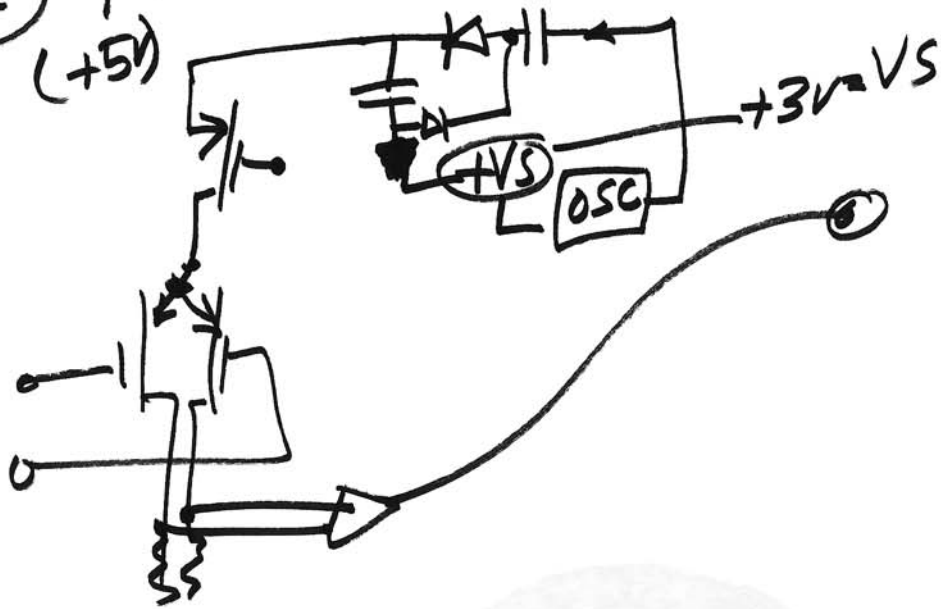


MAKE A R-R INPUT USING

② 2 INPUTS

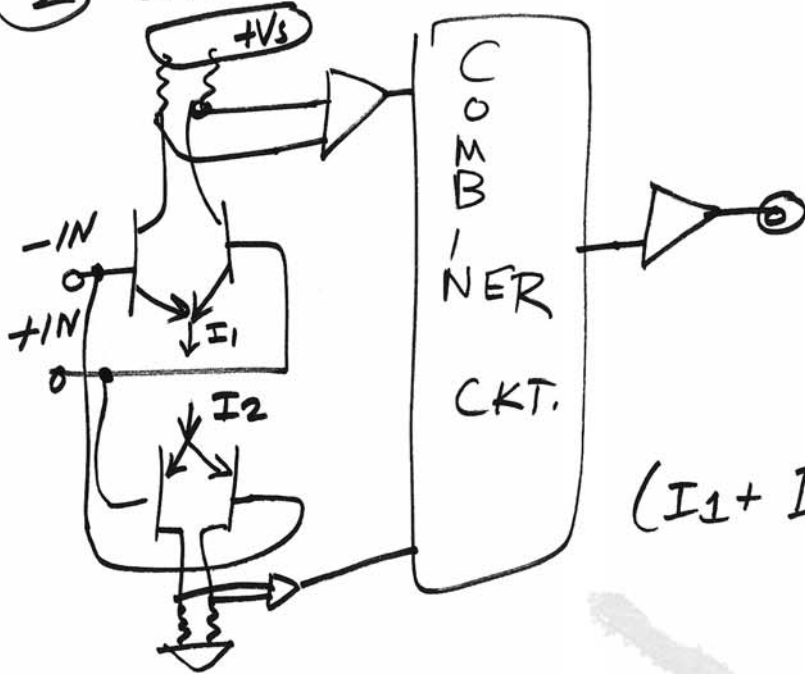

$$(I_1 + I_2 \cong \text{CONSTANT})$$

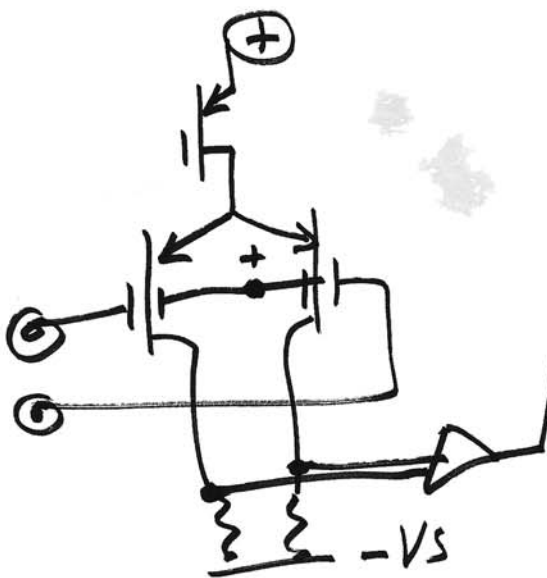
HOW TO MAKE R-R V_{cm} AMPLIFIERS SWEEPING USING MOS-FETS (U.S. PAT. ...)



- ## ADVANTAGES -
- VERY LINEAR
 - LOW NOISE
 - HIGH Z_{in}

HOW TO MAKE HIGH CM Range...

④ USE TRANSFORMERS...

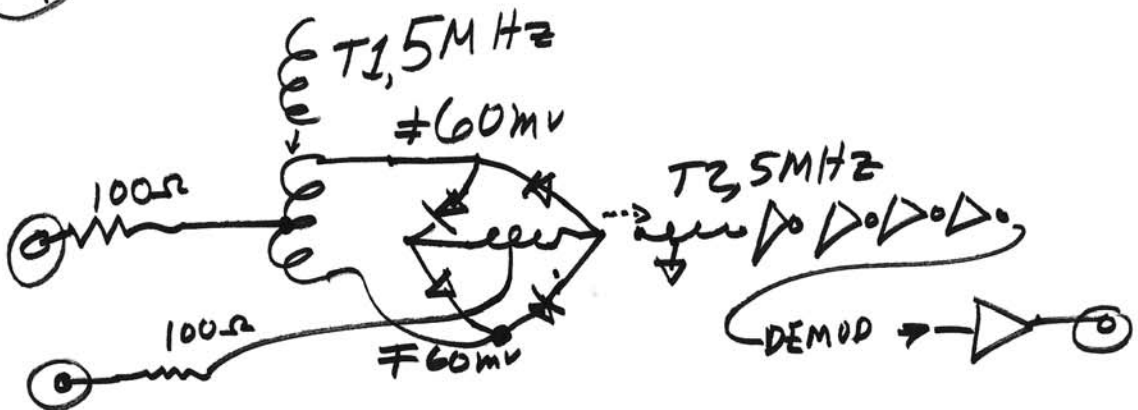

- ADVANTAGES -
- $V_{CM} > 100V$
 - $Z_{IN} > 100M\Omega$
 - $L_{NOISE} - 1\mu V$ for $100Hz$

LATER WE'LL
EXPLAIN WHY
YOU MAY (OR MAY NOT)
NEED RAIL-TO-RAIL
C.M. RANGE

RAP

/more later. RAP

WHAT'S ALL THIS

CMRR
STUFF, ?


(Anyhow?)

(PART III)

RAP 2005

Differential Amplifiers

OR Instrumentation Amplifiers.

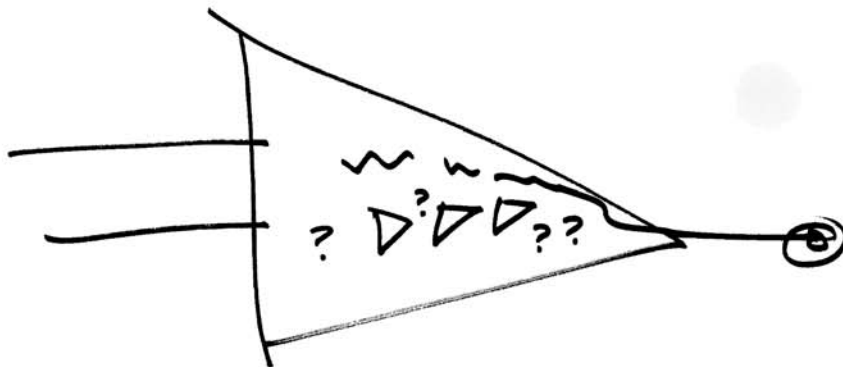

OK - WHAT IS
AN "INSTRUMENTATION
Amplifier"?

RAP

GAIN = K



$Z_{IN} = \text{HIGH}$




NOTE, THE OLD
MA725 data-sheet
SAID IT WAS "AN
INSTRUMENTATION
AMPLIFIER"


It wasn't....

It isn't....

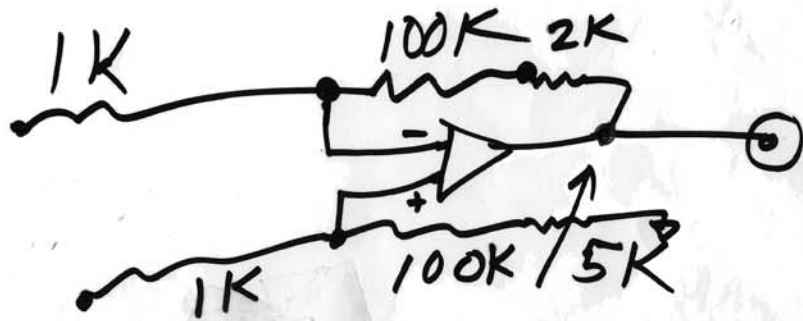
NOTE -
(almost) ALL
Instrumentation Amplifiers
need R TRIMS....



You'll need a TRIM POT.
for CMRR

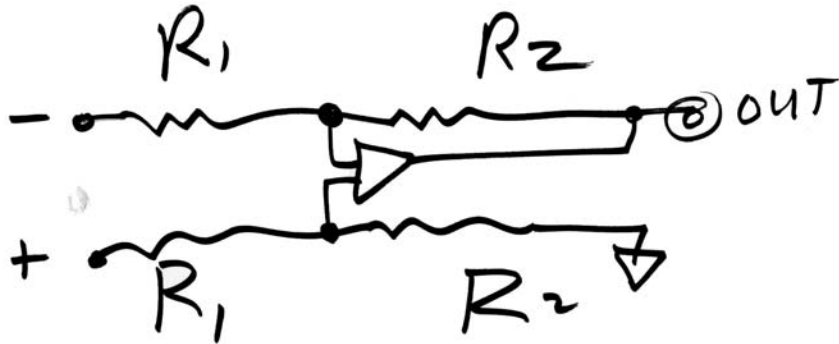

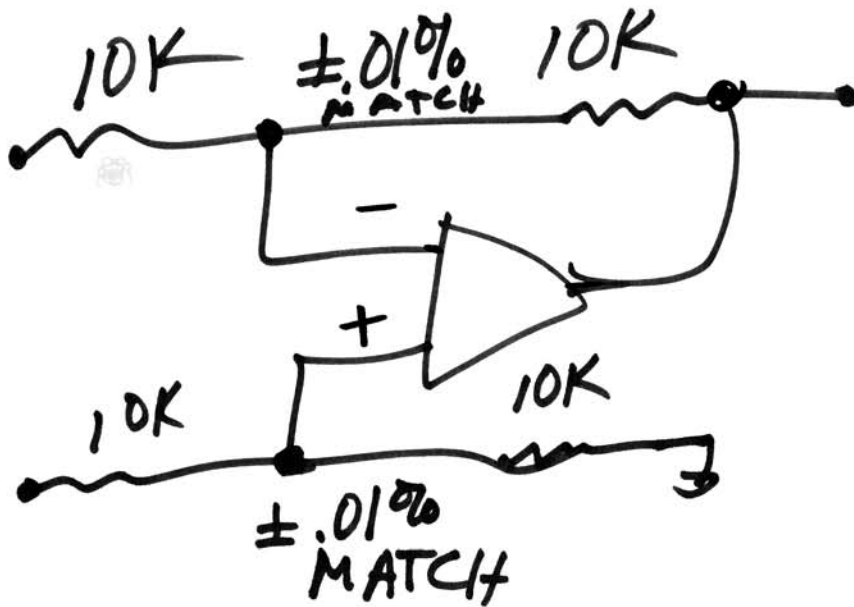- GOOD Differential Amplifier
- Needs TRIMS
- BUT - Z_{IN} ISN'T HIGH.....



YOU WANT
THIN-FILM
NETWORKS WITH
0.01% MATCHING....

NOT JUST FOR
CORRECTING
(CANCELLING OUT)
the OP-amp's CMRR


BUT R-RATIO

1% Resistors? Ha!

0.1% Resistors? (A BIT
BETTER.)

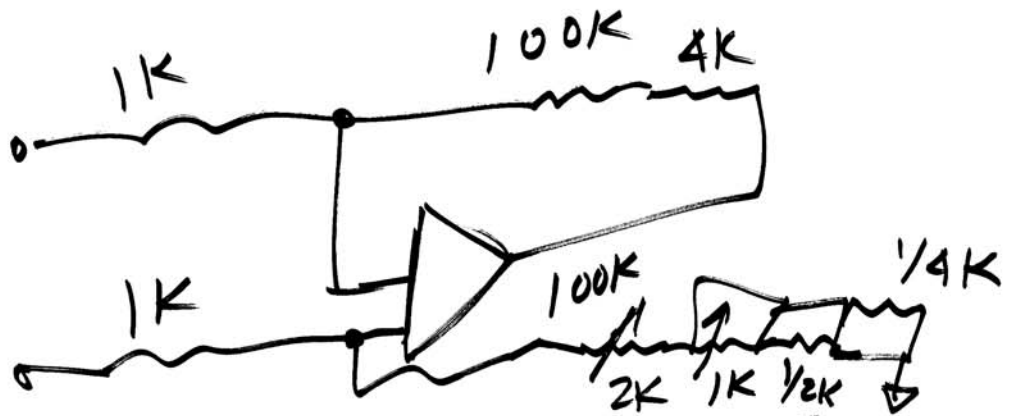
0.01% MATCH?

DO YOU WANT TO TRIM
YOUR CMRR
WITHOUT A POT?




Refer to LB-46...

EXAMPLE ...

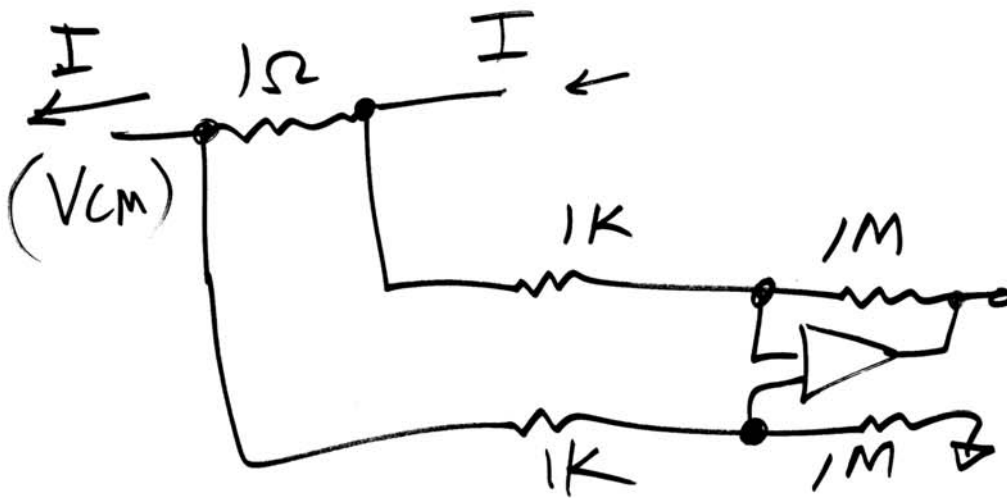


Beware of -
- V_{OS} -
- CMRR

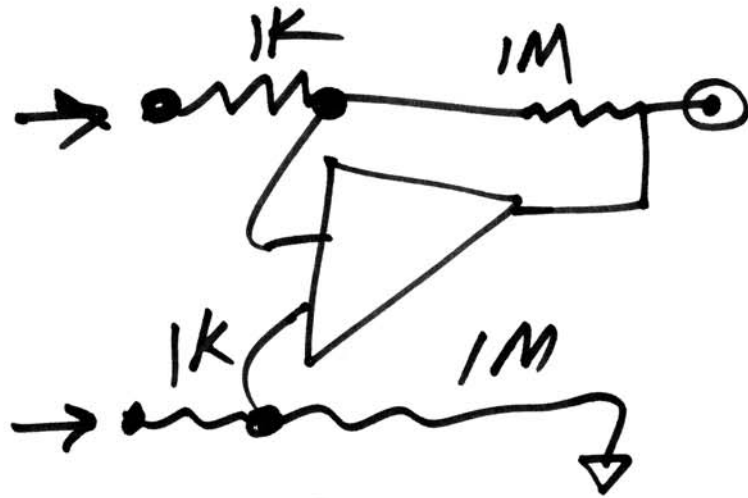


OK —
what is the Z_{IN} ?
1K?
1M?

IMPROVED!!

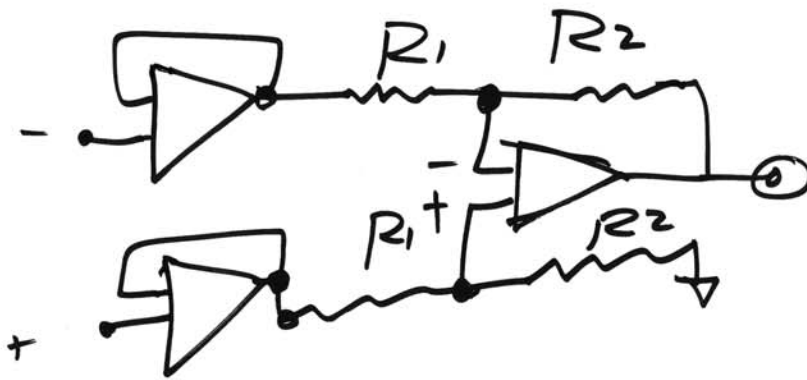

PER THE LM102 Data Sheet....

REALLY GOOD CIRCUIT !!!

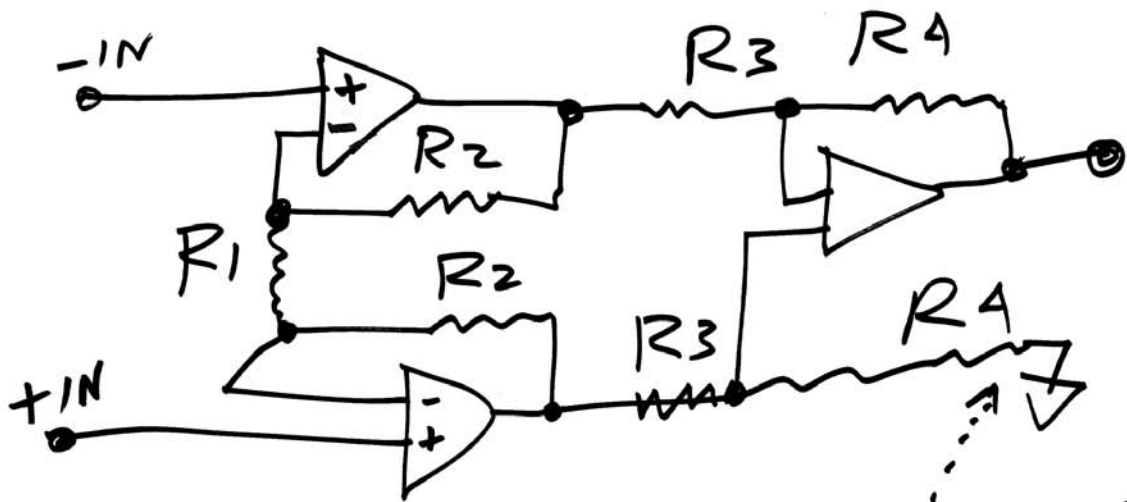

- BETTER GAIN
- BETTER BW.
- BETTER CMRR.....


- $G = (R_2 + R_2/R_1) + 1 \times (R_4/R_3)$

- CMRR is improved

by R_4/R_3

- BW is improved


OTHER TRIM GAMES...

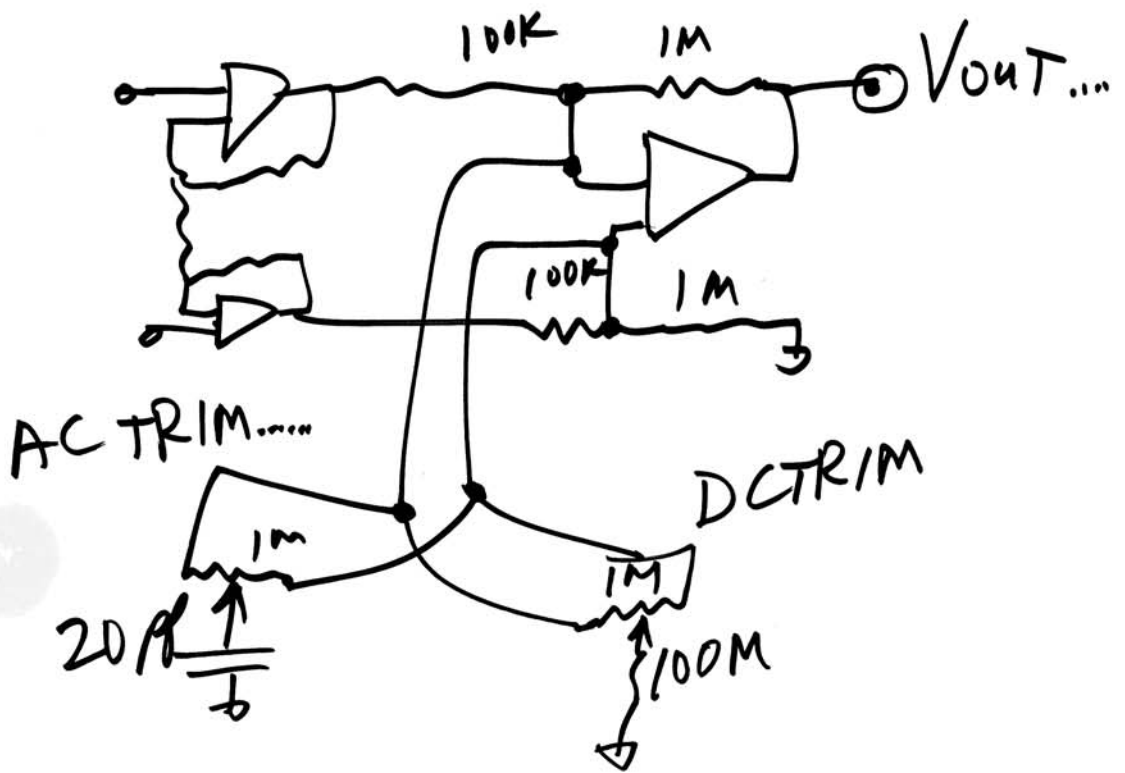

CAUTION ABOUT

C.M. SLEW
RATE


SIMPLER IS BETTER

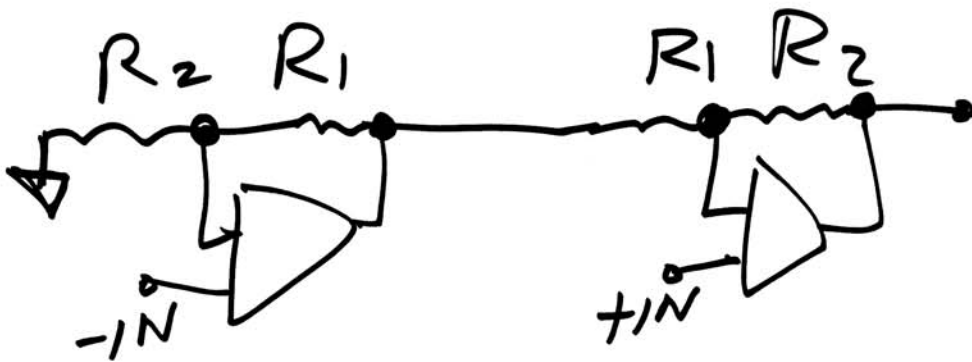

$$G = \frac{R_2}{R_1} + 1 !$$


(well, maybe NOT....)

GOOD NEWS!

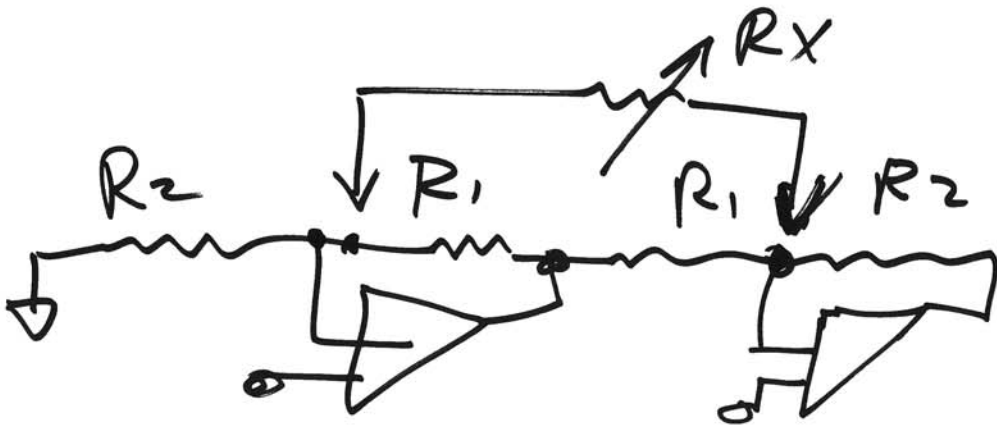


$$G = \left(\frac{R_2}{R_1} + 1 \right) + \left[\frac{2R_2}{R_X} \right]$$

NOT SO GOOD NEWS...

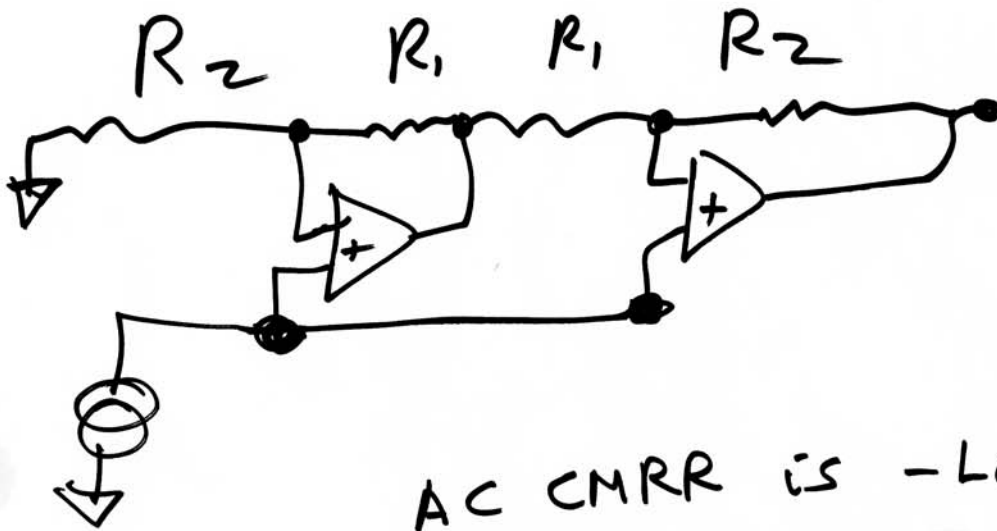


AC CMRR is -LOUSY....


GOOD
BAND-AID
TO
COMPENSATE

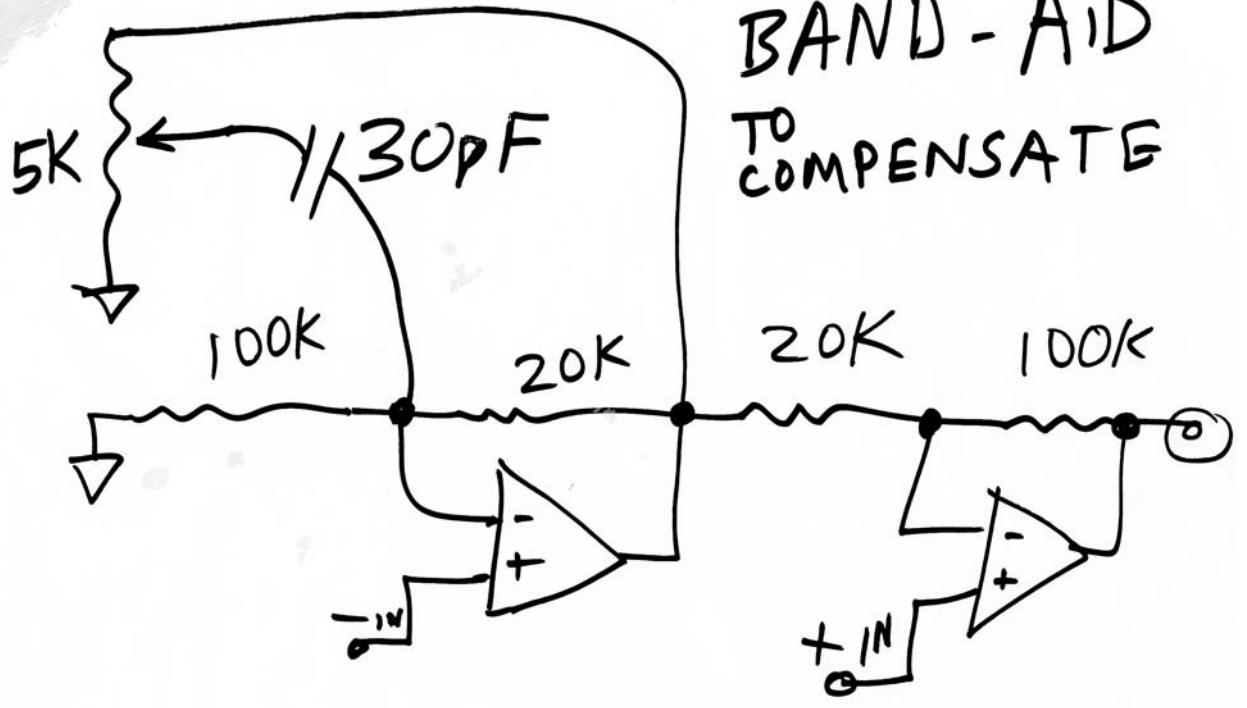

± 200 VOLTS of
CMRANGE
FEATURING
P2/P2A

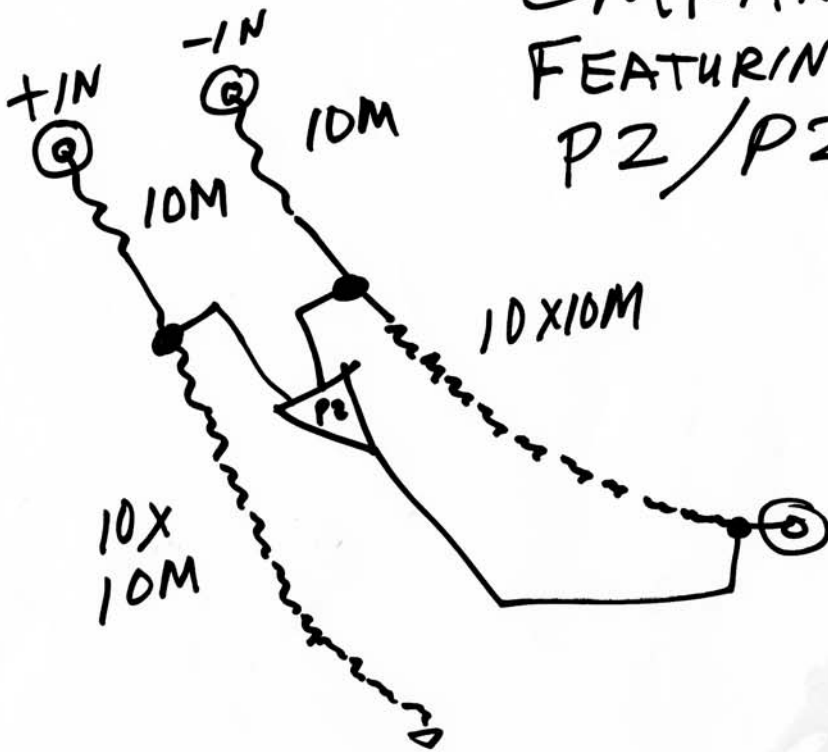

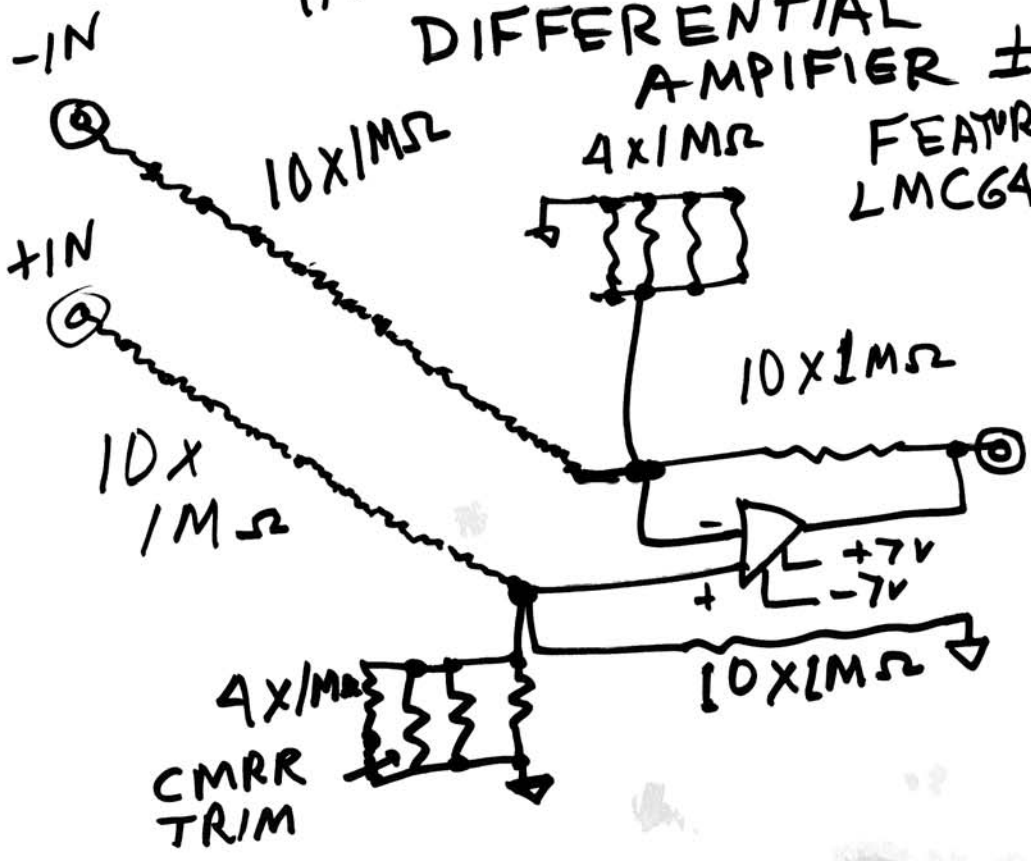HIGH CM-RANGE DIFFERENTIAL AMPLIFIER $\pm 200V$ FEATURING LMC6484



DOUBLE INPUTS

LMH 6645, -46 -47 -(55MHz)
LM 6152, 6154 (75MHz)
LM 7301 (TINY)
LM 6134, LM 6132 (LOW Power)
LM 6142, 44 " "
LM 8261, -62 -(∞ Cap Load)
LM V931, -32, -34 (1.8V Supply)

SMOOTH & SWOOPING

LMC 6482, -84

DUAL/QUAD

LMV 710, -711, -712

LOW PWR.

LMC 6462, -64

LOW POWER

LMC 8101

SINGLE

LMC 6494

QUAD

WHAT'S ALL THIS STUFF, ?

RAP 2005

National Semiconductor provides a comprehensive set of support services. Product information, including sales literature and technical assistance is available through National's Customer Support Centers.

Americas

Email: new.feedback@nsc.com
Phone: 1-800-272-9959

Europe

Fax: +49 (0) 180-530 85 86
Email: europesupport@nsc.com
Phone: Deutsch +49 (0) 69 9508 6208
English +44 (0) 870 24 0 2171
Français +33 (0) 1 41 91 87 90

Asia Pacific

Email: ap.support@nsc.com

Japan

Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Phone: 81-3-5639-7560



The Bob Pease Show

All-analog talk show hosted by Bob Pease and streamed 24/7 from the National website.

www.national.com/bobpeaseshow



Analog University®

Expand your knowledge and understanding of analog with our free online educational training tool.

analogU.national.com