



Edited by Bill Travis

Double DAC rate by using mixers as switches

Randall Carver, Analog Devices, Greensboro, NC

YOU CAN EFFECTIVELY double the sample rate of a DAC by interleaving two DACs into a single unit. Updating each DAC on an alternating basis and switching to the appropriate output dou-

ble the effective throughput of the overall system. It is essential to overall performance that you use a high-quality, high-speed switch in the multiplexing of the DACs' outputs. The current-mode DACs in this Design Idea allow for current-steering implementation of the output switch. Current steering uses two differential-transistor pairs cross-coupled in the form of a four-quadrant multiplier (Figure 1). In this topology, the saturation voltages of the transistors are minimal, voltage swings are small, and switching speeds are high.

The 2.5-GHz AD8343 mixer contains a complete four-quadrant-multiplier structure that you can use as a high-speed, current-mode switch. The bias

Double DAC rate by using mixers as switches	69
DDS IC plus frequency-to-voltage converter make low-cost DAC.....	70
Low-noise ac amplifier has digital control of gain and bandwidth	72
1-kV power supply produces a continuous arc	76
Publish your Design Idea in EDN. See the What's Up section at www.edn.com.	


 


Figure 1 You can use cross-coupled differential transistor pairs as current-mode switches.

circuitry internal to the AD8343 sets the dc voltage at the emitters to approximately 1.2V, which in turn sets the compliance voltage necessary at the DAC

Figure 2

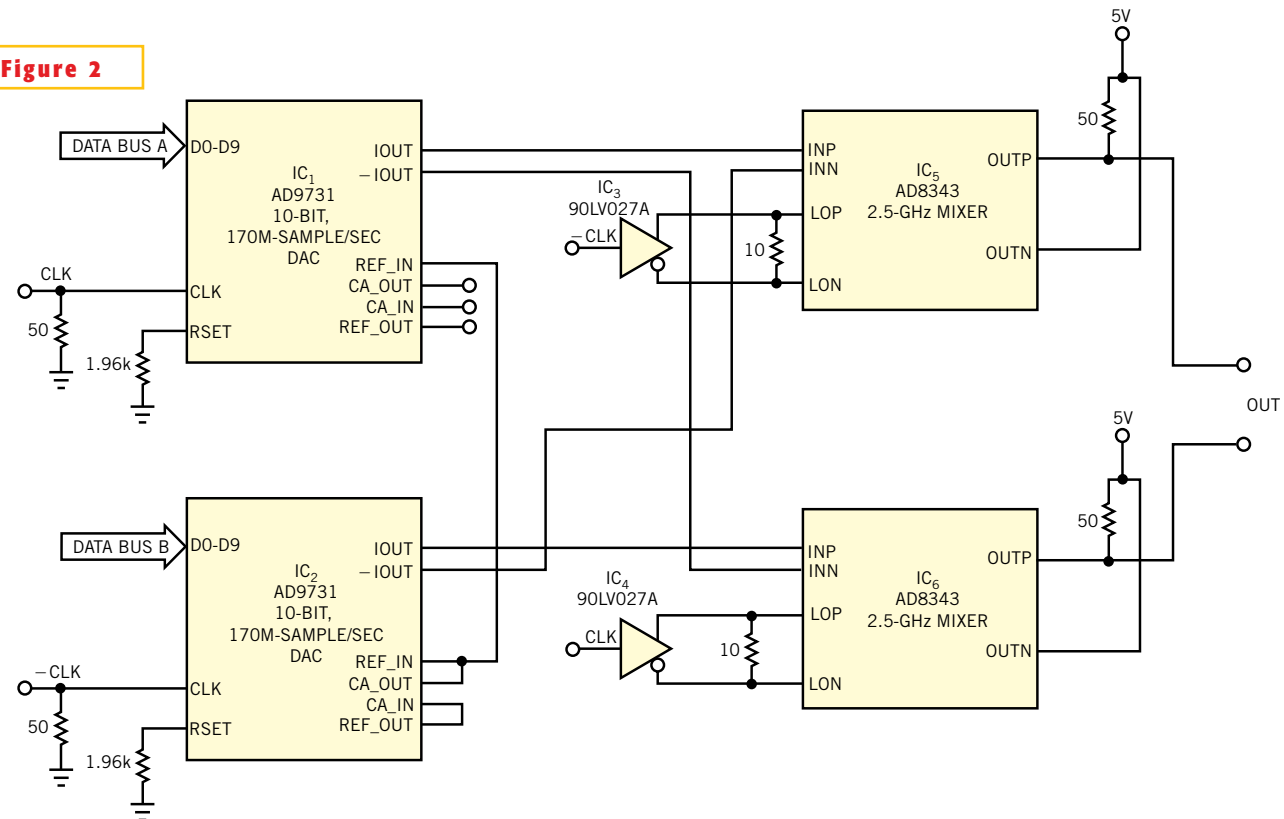

"Ping-ponging" the outputs of two DACs effectively doubles the throughput rate.

outputs. With only a minimal drive signal at the base connections, the emitters appear as a virtual ac ground. The reduced voltage swing at these nodes minimizes the effect of any parasitic capacitances. This Design Idea uses two AD8343 mixers as high-speed switches to multiplex the differential output currents derived from two AD9731 DACs (Figure 2). On the output side of the mixers, the termination resistors allow for a dc path to the supply, provide for the current-to-voltage conversion, and

present a single-ended back-termination impedance of 50Ω. This configuration allows the circuit to drive a remotely located, 100Ω, differential load via two 50Ω coaxial cables. The low-level clock signals at the LO inputs come from high-speed LVDS buffers terminated in resistances of 10Ω. The approximate ±3.5-mA p-p drivers produce roughly 70-mV p-p drive at the LO inputs. Figure 3 shows that the circuit provides output rise and fall times faster than 200 psec. □

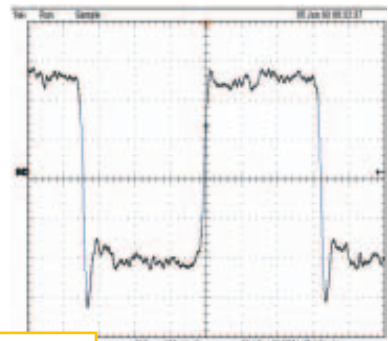


Figure 3

The circuit in Figure 2 produces outputs with less-than-200-psec rise and fall times.

DDS IC plus frequency-to-voltage converter make low-cost DAC

Noel McNamara, Analog Devices, Limerick, Ireland

PRECISION DACs are essential in many consumer, industrial, and military applications, but high-resolution DACs can be costly. Frequency-to-voltage converters have good nonlinearity specifications—typically, 0.002% for the AD650—and are inherently monotonic. This Design Idea shows how you can use a frequency-to-voltage converter and a DDS (direct-digital-synthesizer) chip for precise digital-to-analog conversion. The DDS chip generates a precision frequency proportional to its digital input. This frequency serves as the input to a voltage-to-frequency converter, thereby generating an 18-bit analog voltage proportional to the original digital input. Figure 1

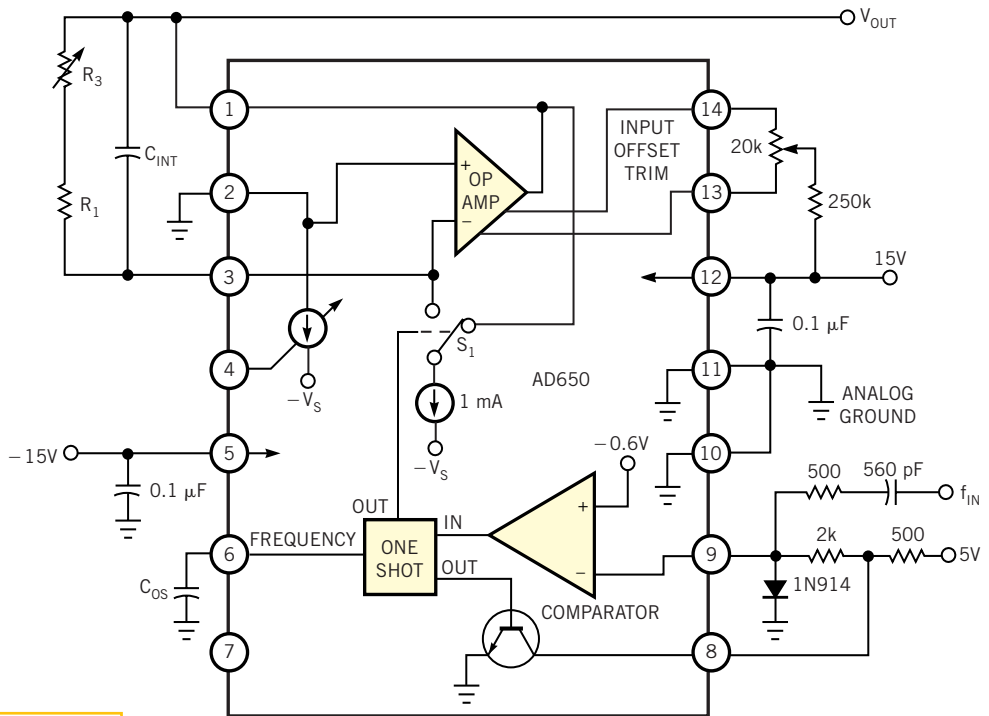


Figure 1

This circuit shows the AD650 in a frequency-to-voltage configuration.

shows how the AD650 is configured for frequency-to-voltage conversion. With $R_1 + R_3 = 20 \text{ k}\Omega$ and $C_{OS} = 620 \text{ pF}$, a full-scale input frequency of 100 kHz produces a full-scale output voltage of 10V. (See Analog Devices (www.analog.com) application note AN-279 for more details on using the AD650 as a frequency-to-voltage converter.)

Resolution of 18 bits requires a programmable clock source with a frequency resolution of 0.38 Hz (100 kHz/262,144). The AD9833 low-power DDS IC with on-chip 10-bit DAC is ideal for this task, because setting the clock frequency requires no external components. The device contains a 28-bit accumula-

tor, which allows it to generate signals with 0.1-Hz resolution when you operate it with a 25-MHz master clock. Figure 2 shows a block diagram of the AD9833 DDS chip. Figure 3 shows the complete system. The most significant bit of the on-chip DAC switches to the V_{OUT} pin of the AD9833, thus generating the 0V-to-

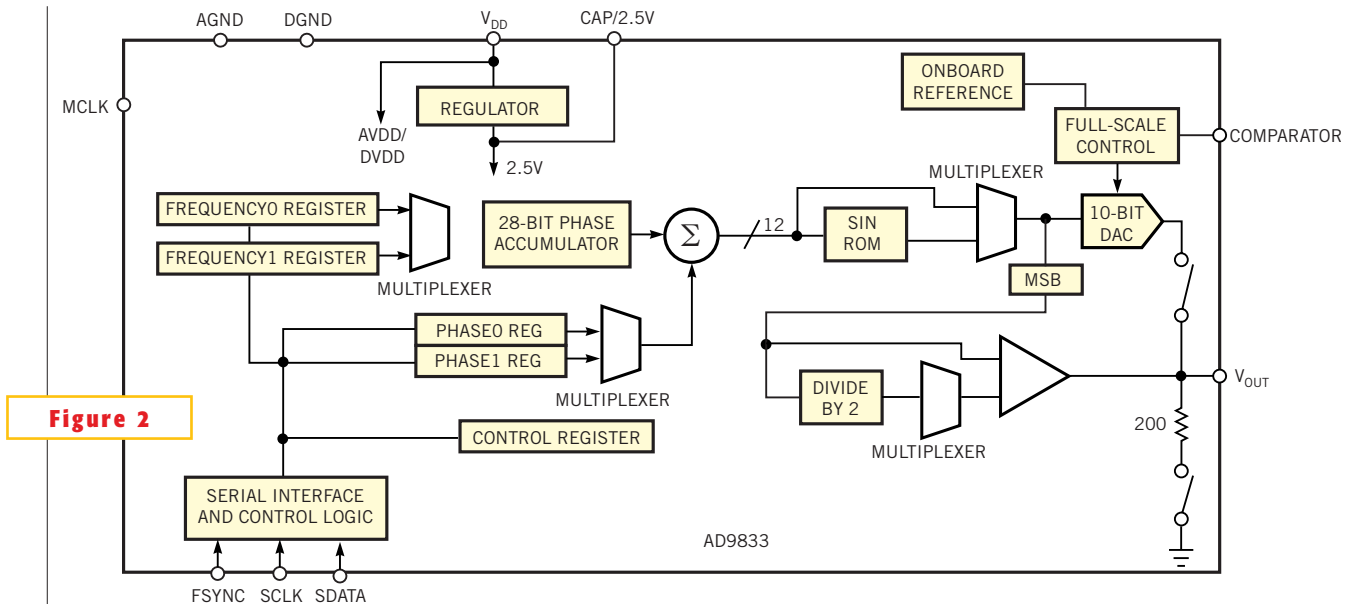


Figure 2

This DDS chip generates signals with 0.1-Hz resolution from a 25-MHz clock.

V_{DD} square wave that serves as the clock input to the AD650 voltage-to-frequency converter. Writing to frequency-control registers via a simple three-wire interface sets the clock frequency, thus programming the voltage output. □

 


Figure 3

This DAC system delivers 0 to 10V output with 18-bit resolution.


Low-noise ac amplifier has digital control of gain and bandwidth

Philip Karantzalis, Linear Technology, Milpitas, CA

IN LOW-NOISE ANALOG circuits, a high-gain amplifier serves at the input to increase the SNR. The input signal level determines the input-stage gain; low-level signals require the highest gain. It is also standard practice in low-noise analog-signal processing to make the circuit's bandwidth


Figure 1

 as narrow as possible to pass only the useful input-signal spectrum. The optimum combination of an amplifier's gain and bandwidth is the goal of a low-noise design. In a data-acquisition system, digital control of gain and bandwidth provides dynamic adjustment to variations in input-signal level and spectrum. **Figure 1** shows a simplified circuit for an ac



NOTES:
 $V_{OUT} = (\text{GAIN A})V_{IN}$
 $\frac{1}{2\pi R_1 C_1} \leq \text{BANDWIDTH} \leq \frac{1}{2\pi \frac{R_2}{(\text{GAIN B})} C_2}$

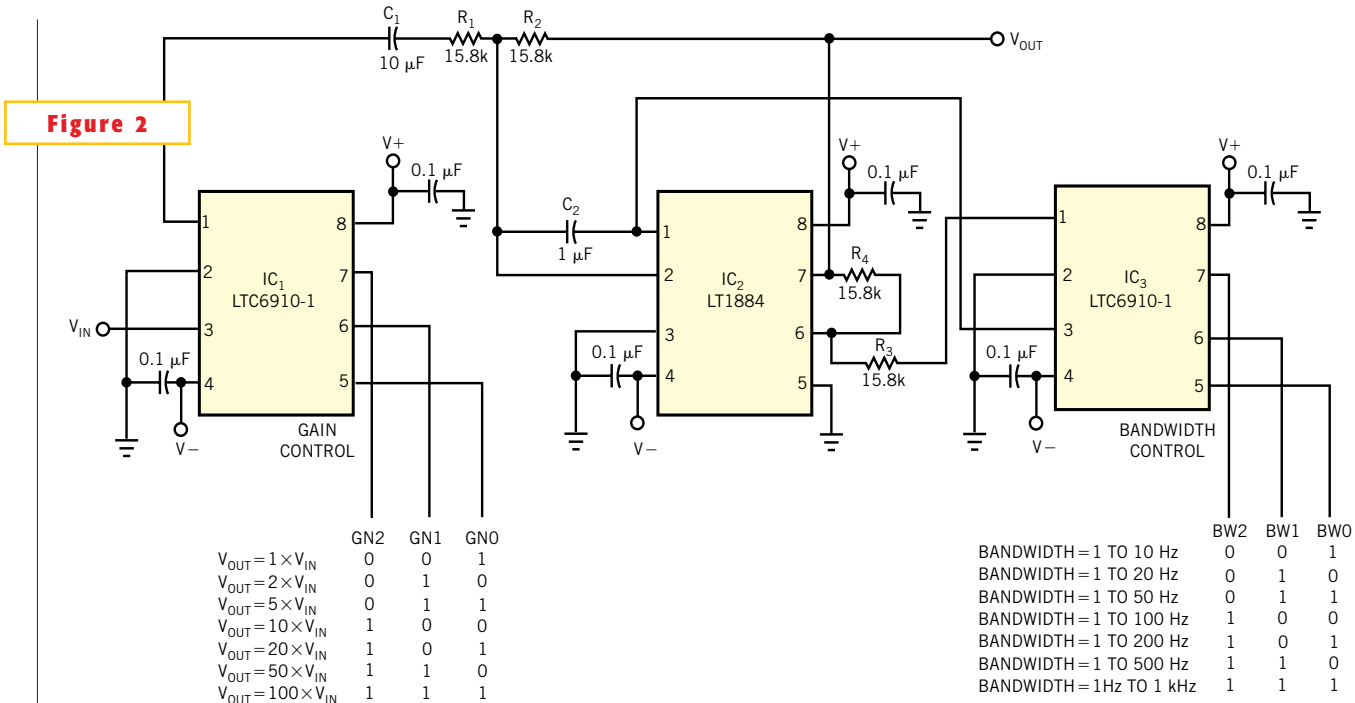This ac-amplifier configuration offers both gain and bandwidth control.



This detailed implementation of the circuit in Figure 1 operates with dual power supplies.

amplifier with control of both gain and bandwidth. The amplifier's input is a PGA (programmable-gain amplifier) providing gain control (Gain A). Following the input PGA is a first-order highpass filter formed with capacitor C_1 and input resistor R_1 of an integrator circuit. Inside the integrator's feedback path, the gain of a second PGA (Gain B) multiplies the integrator's -3 -dB frequency, thus providing bandwidth control.

Figure 2 shows a complete circuit implementation using two LTC6910-1 digitally controlled PGAs and an LT1884 dual op amp. The input LTC6910-1, IC_1 , provides digital gain control from 1 to 100 using a 3-bit digital input to select gains of 1, 2, 5, 10, 20, 50, and 100. The circuit's lower -3 -dB frequency is fixed and set to 1 Hz. A second LTC6910-1, IC_3 , is inside an LT1884-based (IC_2) integrator loop.

 


Figure 3 The frequency response of Figure 2's circuit shows unity gain and three digital bandwidth-control inputs.

The integrator's digital gain control becomes digital bandwidth control, which provides an upper -3 -dB frequency of 10 Hz to 1 kHz. The circuit's low-noise LT1884 op amp and LTC6910-1 ($9 \text{ nV}/\sqrt{\text{Hz}}$ for each device) combine

to provide high SNR. For example, the SNR is 76 dB for a 10-mV peak-to-peak signal with a gain of 100 and 100-Hz bandwidth or 64 dB for a 100-mV peak-to-peak signal with a gain of 10 and 1-kHz bandwidth. With an LT1884 dual op amp (gain-bandwidth product of 1 MHz), the circuit's upper frequency response can increase to 10 kHz by reducing the value of C_2 . (The lower -3 -dB frequency increases by reducing the value of C_1 .) The circuit in Figure 2 operates with ± 5.5 V dual power supplies. You can convert it to a single-supply 2.7 to 10V circuit by grounding Pin 4 of IC_1 , IC_2 , and IC_3 ; connecting a $1\text{-}\mu\text{F}$ capacitor from Pin 2 of IC_1 to ground; and connecting Pin 2 of IC_3 to pins 3 and 5 of IC_2 and Pin 2 of IC_3 . Figure 3 shows the frequency response of the circuit in Figure 2 with unity gain and three digital bandwidth-control inputs. □

1-kV power supply produces a continuous arc

Robert Sheehan, Linear Technology, Milpitas, CA

DESIGNING A HIGH-VOLTAGE switching power supply that can produce a sustained arc can be challenging. This compact and efficient design delivers 1 kV at 20W and can withstand a continuous arcing, or short-circuit, condition (Figure 1). It uses standard, commercially available components. R_1 sets the LTC1871 switching-regulator controller for a nominal operating frequency of 120 kHz. The circuit operates as a discontinuous flyback structure, producing 333V across C_1 . The diode/capacitor charge-pump multiplier triples this voltage to create 1000V at the output. Figure 2 shows the switching waveforms. When the primary switch, Q_1 , is on, the output rectifiers are reverse-biased, and energy is stored in the transformer, T_1 . When Q_1 turns off, energy transfers to the secondary winding, and C_2 and C_3 pump up the output voltage through the rectifiers. The primary voltage goes high and is clamped

through the transformer and rectifier, D_1 , by the voltage across C_1 . The transformer is well-coupled, so the leakage inductance creates little voltage spike. A small RC snubber across the primary winding damps the ringing and reduces EMI (electromagnetic interference).

For current-limit protection, the circuit in Figure 1 contains two active circuits and one passive element. The voltage across the current-sense resistor, R_2 , limits peak primary current to 7.5A. Q_2 provides secondary-side current limit. Notice the bump on the leading edge of the current ramp of Trace


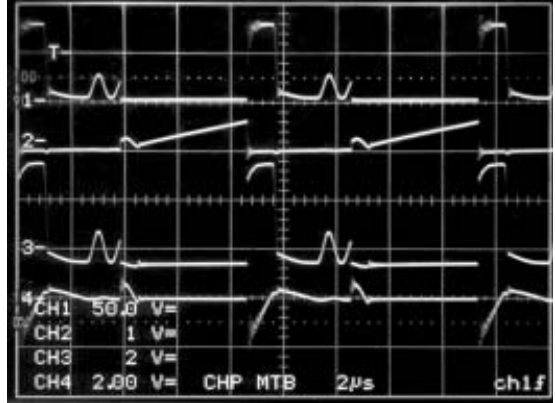


Figure 2 These are the switching waveforms for the circuit in Figure 1. Channel 1 is the primary-switch voltage at T_1 , Pin 12; Channel 2 is the primary-switch current into Q_1 , drain (10A/division); Channel 3 is the secondary-switch voltage at T_1 , Pin 2 (200V/division); Channel 4 is the voltage across R_3 . (Secondary-switch current=2V/1.5Ω=1.33A/division.)

2 in Figure 2. This bump coincides with the positive excursion of the voltage across R_3 in Trace 4, which is the refresh

Figure 1

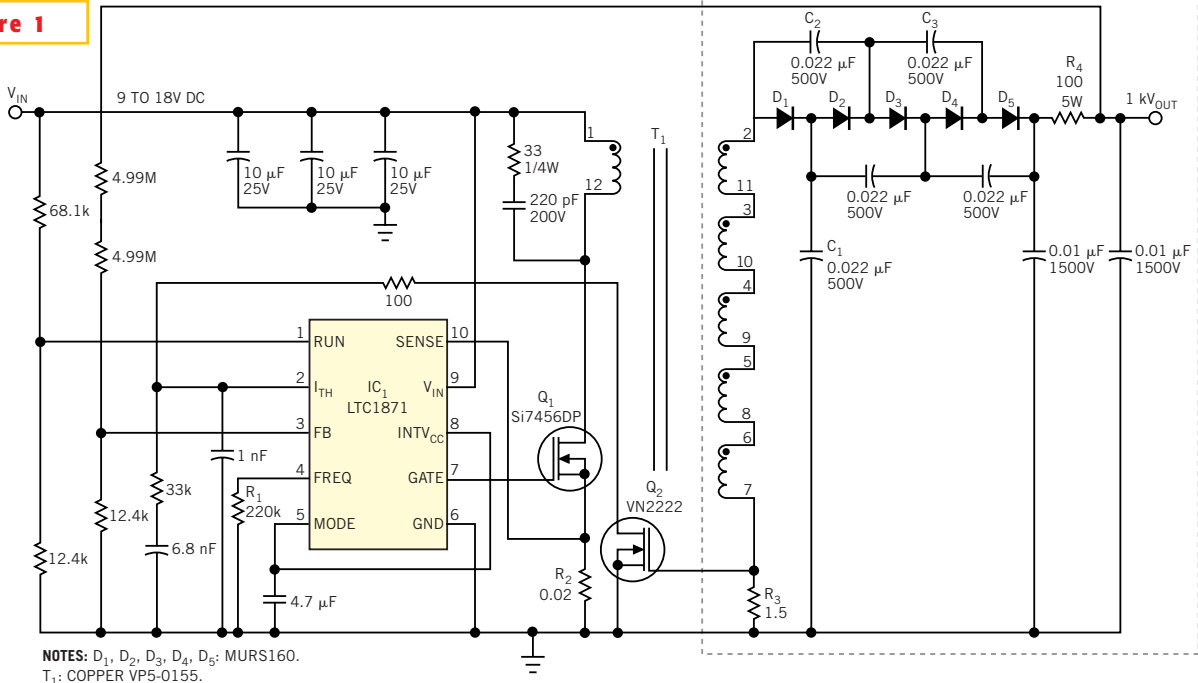

This circuit delivers 1 kV from a low-voltage input and can produce continuous arcing.

current for C_2 and C_3 . When the circuit is overloaded, this slug of current becomes high enough to enhance Q_2 , folding back the load current (**Figure 3**). A hard short circuit results in relatively low power dissipation. Omitting Q_2 for the secondary-side current limit results in substantially increased short-circuit current and internal

power dissipation, resulting in failure of the primary switch Q_1 . R_4 provides a load impedance for the power supply.

This load helps to limit the peak-current stress in the multiplier capacitors and diodes. Don't skimp on the power rating for R_4 , because dissipation during a continuous arc can be substantial. Should R_4 fail open, the feedback circuit forces a full duty cycle with catastrophic results. Too low a value for R_4 can result in charred circuits and hours of debug-

 


Figure 3 The circuit in Figure 1 has a foldback current-limiting characteristic.

ging. (Yes, a hearty explosion elicits a round of applause from the lab crew.) Arcing is the most stressful condition, and the output capacitor constantly charges and discharges (**Figure 4**). As a final figure of merit, the circuit is efficient (**Figure 5**). The efficiency reaches 87.3% at 12V input and a full load of 20W and increases to 87.7% with an overload of 24W.

So what is this circuit good for? A battery-operated bug zapper, perhaps. And, like raking a live wire across a grounded file, this is a great tool for befuddling the AM-radio listeners on the production floor. The circuit probably doesn't deliver enough energy for use as a plasma cutter, though one engineer I knew was willing to give it a try. A previous version of the circuit used a monolithic switcher, and with the right materials for banana jack and plug, created a bright orange glow and enough heat to raise thoughts about the fire extinguisher (plenty of ozone, too). I'd stay away from using this circuit as a cat trainer or an electric fence. The circuit does generate a lethal voltage potential, and lawsuits can be quite costly. Prototype this circuit at your own risk. □

 


Figure 4 These waveforms represent the output voltage of the circuit in Figure 1 when arcing occurs.

 


Figure 5 The conversion efficiency of the circuit in Figure 1 is well over 85%.