#### **Document information**

Information	Content
Keywords	automotive, reverse battery protection, RBP
Abstract	This application note gives details of four methods of reverse battery protection (RBP) that can be used in 12 V automotive systems.



**Nexperia** 

#### Reverse battery protection in automotive applications

### 1. Introduction


This aim of this application note is to help the reader gain an insight into how to protect 12 V automotive systems from being exposed to a reversed biased battery condition e.g. during maintenance where the battery leads may be reconnected in the opposite polarity.

Four methods of reverse battery protection (RBP) are discussed:

- Recovery rectifier (PN diode)
- Schottky rectifier
- P-channel MOSFET
- N-channel MOSFET

The dominant losses in RBP applications are due to conduction. The ordering of the components in the above list is important as it gives an indication of the least capable to most capable methods. In other words for a particular current flow Recovery rectifiers exhibit the greatest loss and N-channel MOSFETs the least loss. Table 1 summarises the key factors of each method.


Table 1. Reverse battery positive rail protection options

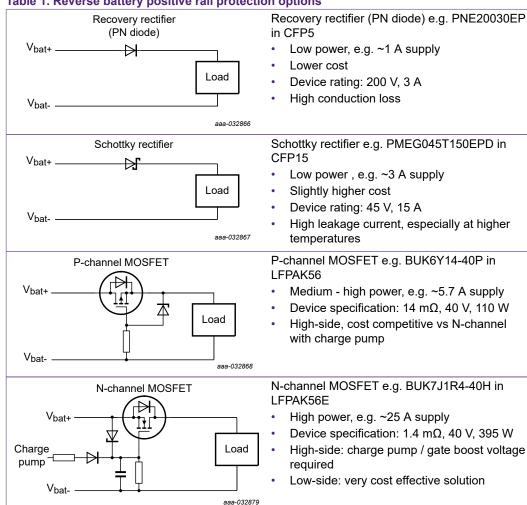

Reverse battery protection in automotive applications
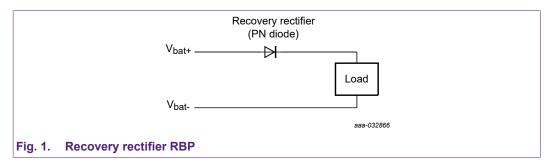
### 2. Recovery rectifier (PN diode) steady state conduction loss

Using a Recovery rectifier as a blocking diode can be considered as the simplest and most cost-effective way to realize a reverse battery protection (RBP) circuit. Inserting a Recovery rectifier in series with the load ensures that current can flow only when the battery is correctly connected. There is no control input needed, resulting in a low complexity and low component count. The usage of a Recovery rectifier for RBP is however compromised by the high forward voltage drop of the PN junction. This is the reason why Recovery rectifiers are only used for low power applications (load currents below ~1 A).



Inrush current through the rectifier must be considered e.g. when the battery is switched into circuit and the bulk capacitance begins to charge. The peak current and duration of the pulse must be checked to ensure it does not exceed specification.


The steady state conduction losses,  $P_{loss}$ , can be calculated by using the forward voltage drop  $V_F$  of the diode given for a steady state temperature of the PN junction and the load current  $I_{load}$ :

$$P_{loss} = I_{load} \times V_F(T) \tag{1}$$

The forward voltage drop of a PN junction decreases by -1.9 mV/K as the device heats up, lowering the losses at higher junction temperatures. Nevertheless the maximum total power dissipation of the Recovery rectifier has to be respected as indicated in the data sheet of the particular diode.

In the option examples above the PNE20030EP Recovery rectifier is identified as being well suited to this type of application. Using close to the example current in a simulation gives an indication of the expected forward voltage drop, junction and PCB temperatures, with the ambient temperature (on the product's case) of  $105\,^{\circ}$ C.
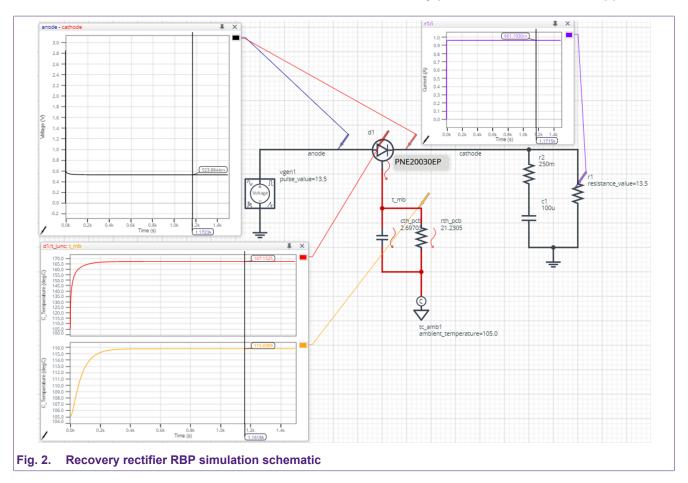
### Reverse battery protection in automotive applications



See graphs of the simulation data results in Fig. 3, Fig. 4 and Fig. 5.

#### Reverse battery protection in automotive applications

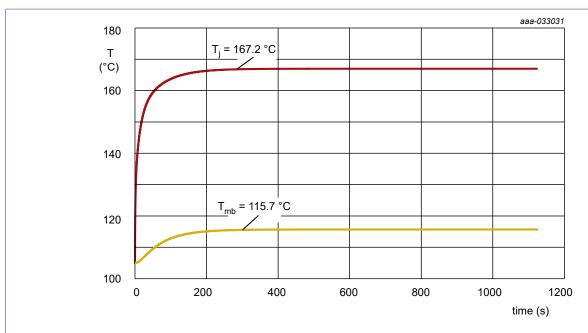


Fig. 3. Recovery rectifier simulation results - junction and mounting base temperatures

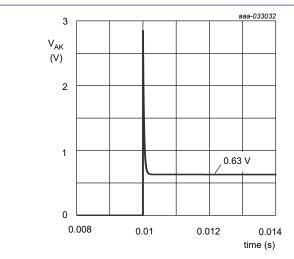


Fig. 4. Recovery rectifier simulation results - D1 anode-to-cathode voltage


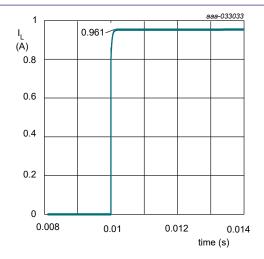


Fig. 5. Recovery rectifier simulation results - load current

#### Reverse battery protection in automotive applications
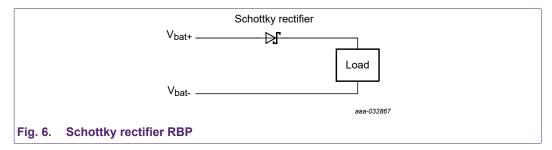
### 3. Schottky rectifier steady state conduction loss

In order to overcome the high conduction losses of a Recovery rectifier, designers could use a Schottky rectifier for RBP. A Schottky device as blocking diode comes with the same advantages as a Recovery rectifier (least complexity). Thanks to its lower forward voltage drop it can be used for higher load currents up to approximately 3 A. However a Schottky rectifier comes with a higher leakage current due to its metal-semiconductor interface. The leakage current of a Schottky rectifier becomes significantly larger at higher junction temperatures, resulting in unwanted effects such as thermal runaway.



Similarly to the Recovery rectifier, inrush current through the diode must be considered e.g. when the battery is switched into circuit and the bulk capacitance begins to charge. The peak current and duration of the pulse must be checked to ensure it does not exceed specifications.


Like in the case of the Recovery rectifier the conduction losses can be calculated by multiplying the temperature-dependent voltage drop with the load current:

Also for Schottky rectifiers the junction temperature must not exceed the specified maximum junction temperature which is 175 °C for automotive types.

In the option examples above the Schottky rectifier PMEG045T150EPD is identified as being well suited to this type of application. Using close to the example current in simulation gives an indication of the expected forward voltage drop, power dissipation, junction and PCB temperatures for an ambient temperature of 105 °C on the product's case

6 / 18

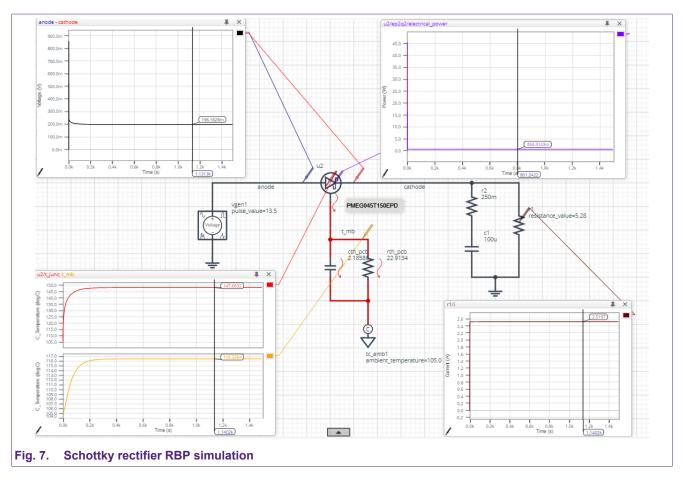
### Reverse battery protection in automotive applications





See graphs of the simulation data results in Fig. 8, Fig. 9 and Fig. 10.

**Nexperia** 

#### Reverse battery protection in automotive applications

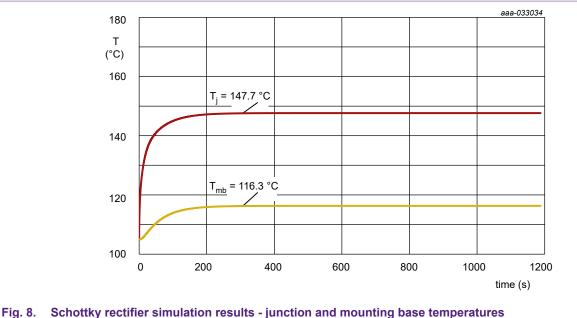

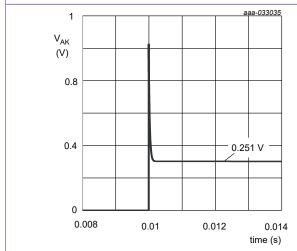

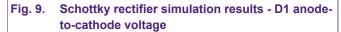


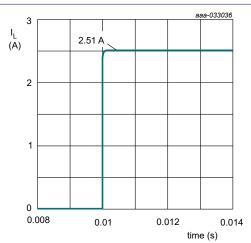


Fig. 10. Schottky rectifier simulation results - load current
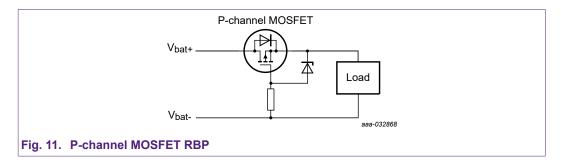
## 4. P-channel MOSFET solution steady state conduction loss

In RBP applications the MOSFET can be considered as operating in two modes: "DIODE" mode and "MOSFET" mode.

During manufacture a parasitic PN junction diode is created within each MOSFET cell, the antiparallel "diode" on the die actually comprises many parallel diodes distributed uniformly across the whole active die area.




#### Reverse battery protection in automotive applications

When the MOSFET is not enhanced i.e. the gate terminal does not have a sufficiently negative voltage below its source to exceed its minimum threshold to turn-on then, with the battery connected correctly, it behaves as a forward biased DIODE. The power loss in the device is the product of the forward diode voltage and current flowing through it. The forward diode voltage decreases with increase in temperature by -1.9 mV/K. Therefore as the die heats the power dissipation reduces for a given current.

Once the gate-source threshold is reached the MOSFET becomes enhanced and switches from "DIODE" to "MOSFET" mode. Current then flows in the drain-source channel. The power loss is then the product of the on-state resistance R<sub>DSon</sub> and square of the current flowing in the channel.

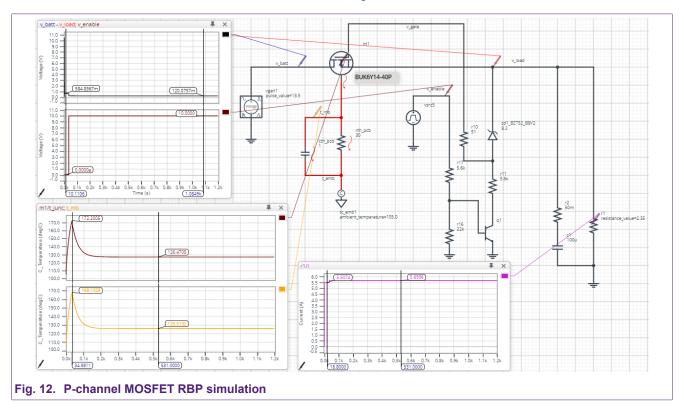To aid illustration a mix of data sheet calculation and simulation is used, the graphical results obtained from simulation are shown in Fig. 12 below:



The P-channel simulation is initially set up with a slightly higher load current to the Schottky rectifier simulation.

To observe the device behaving as a diode look at the first portion of the junction temperature plot where the junction rises significantly above case temperature. Later observe the difference in power dissipation when the MOSFET is enhanced and switches from "DIODE" to "MOSFET" mode. If we consider a battery voltage of 13.5 V and  $V_{SD}$  = 0.7 V typical at 25 °C, (values taken from the BUK6Y14-40P data sheet), driving a load resistance of 2.35  $\Omega$ . The expected power dissipation would be somewhere around 0.7 V × (13.5 V/2.35  $\Omega$ ) = 0.7 V × 5.75 A = ~4.02 W. It will be shown that the effects of temperature soon modify this expected result. This is true because products within vehicles soon rise above this notional outside air ambient of 25 °C and the impact on component behaviour must be considered.

Table 2. BUK6Y14-40P source-drain voltage characteristics

Symbol	Parameter	Conditions	Min	Тур	Max	Unit
Source-drain o	liode					
V <sub>SD</sub>	source-drain voltage	I <sub>S</sub> = -64.4 A; V <sub>GS</sub> = 0 V; T <sub>j</sub> = 25 °C	-	-0.7	-1.2	V

Temperatures above 125 °C are not uncommon dependent on product location within the vehicle and the ambient air temperature. However the focus here is on a product operating with a case temperature representing it being mounted on or near the engine jacket where the coolant temperature is expected to be around 105 °C.


#### Reverse battery protection in automotive applications

Therefore what we see in the simulation is rather more accurate in that it accounts for the impedance presented by the diode and the drop in diode forward voltage as the die temperature rises. The load current is seen reduced to ~5.5 A and diode dissipation to ~3.07 W.

The mounting base temperature is that of the component's location on the PCB. In other words there will be some mounting base offset temperature expected dependent on how good the thermal linkage is between the component's mounting base ( $T_{mb}$ ) and local pedestals connecting the component to the product's external case (local ambient) temperature of 105 °C.

The steady state condition considers the PCB thermal resistance  $R_{th}$  value dominant rather than the transient  $Z_{th}$  value. Simulation uses a  $R_{th(PCB)}$  of 30 K/W and reduced thermal capacitance to allow this dominance. If the device were left in DIODE mode the simulation shows the notional temperature on the PCB would be very close to the maximum junction temperature specification of 175 °C and damage to the PCB surface may result even though a high temperature material may have been chosen for the application.

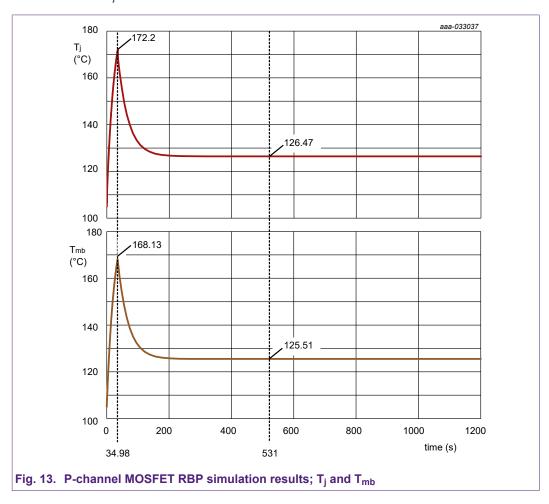To illustrate the effect of DIODE mode self-heating the simulation delays enhancement to MOSFET mode for  $\sim$ 35 s, see Fig. 13. In this time for a dissipation of 3.07 W, simulation shows  $T_{mb}$  has risen to 168.13 °C and  $T_i$  to 172.2 °C.



We can make a calculation based on using the data sheet  $R_{th(j-mb)}$  maximum value of 1.4 K/W, see Table 3. For a power dissipation of 3.07 W we should expect the junction temperature to rise by 3.07 W × 1.4 K/W = 4.29 °C above  $T_{mb}$ . This calculation yields a junction temperature of 172.42 °C which correlates reasonably well with the simulation.

Table 3. BUK6Y14-40P thermal characteristics

Symbol	Parameter	Conditions	Min	Тур	Max	Unit
R <sub>th(j-mb)</sub>	thermal resistance from junction to mounting base		-	1.1	1.4	K/W

10 / 18

#### Reverse battery protection in automotive applications

When the device has sufficient gate bias applied to enhance (turn-on) the MOSFET element the device behaves as having a resistance in parallel with the diode. <u>Table 4</u> gives the typical and maximum values of the on-state resistance with a junction temperature of 25 °C.

Table 4. BUK6Y14-40P drain-source on-state resistance characteristics

Symbol	Parameter	Conditions	Min	Тур	Max	Unit
R <sub>DSon</sub>	drain-source on-state resistance	$V_{GS} = -10 \text{ V}; I_D = -10.8 \text{ A}; T_j = 25 \text{ °C}$	-	11	14	mΩ

Looking at the simulation results shown in Fig. 13, by 531 seconds after enhancement MOSFET power dissipation and  $T_{mb}$  have dropped significantly to near steady state values of 683.77 mW and 125.51 °C respectively. The load current has increased slightly to ~5.69 A indicating a reduction in line impedance presented by the MOSFET to the battery.

If we make a power loss calculation based on 5.69 A load current and  $R_{DSon}$ , the formula changes from DIODE power = V × I to MOSFET power =  $I^2R$  where I is drain current and R is  $R_{DSon}$ , by substitution (5.6942) × 14 m $\Omega$  = 453.9 mW. So why is there such a discrepancy with the 683.78 mW shown in the simulation? The above calculation was made using  $R_{DSon}$  maximum @ 25°C neglecting to factor in temperature.

 $R_{DSon}$  has a positive temperature coefficient, see Fig. 14. The simulation models how  $R_{DSon}$  changes from that 14 m $\Omega$  maximum value at 25 °C to a 1.51 typical multiplier @ 125 °C. Using 1.51 × 14 m $\Omega$  = 21.14 m $\Omega$  we can expect a power dissipation of (5.6942) × 21.14 m $\Omega$  = 685.39 mW which correlates well with simulation.

Now if the power dissipation is multiplied by  $R_{th(j-mb)}$  we see a junction temperature of 685.39 mW × 1.4 K/W = 0.956 °C above the mounting base temperature; 125.51 °C + 0.956 °C = 126.4695 °C which correlates very well with the junction temperature result of 126.4705 °C seen in simulation.

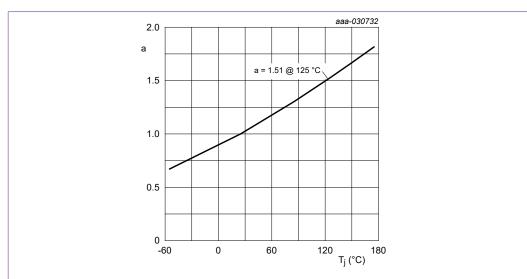


Fig. 14. BUK6Y14-40P normalized drain-source on-state resistance as a function of junction temperature; typical values

The BUK6Y14-40P data sheet specifies the maximum permitted drain current at 25 °C and 100 °C, see <u>Table 5</u>.

#### Table 5. BUK6Y14-40P limiting values

In accordance with the Absolute Maximum Rating System (IEC 60134).

Symbol	Parameter	Conditions	Min	Max	Unit
I <sub>D</sub>	drain current	V <sub>GS</sub> = -10 V; T <sub>mb</sub> = 25 °C	-	-64	Α
		V <sub>GS</sub> = -10 V; T <sub>mb</sub> = 100 °C	-	-46	Α

The maximum drain current derating for temperature is given by the equation below, where maximum junction temperature  $T_i = 175$  °C:


AN50001

#### Reverse battery protection in automotive applications

$$ID(Tmb) = ID(25^{\circ}C) \times \sqrt{\frac{T_j - Tmb}{T_j - 25^{\circ}C}}$$
(2)

Hence the maximum permissible drain current =  $\sqrt{((175-125.51)/(175-25))}$ ] = 0.57 of full rated value @ 25°C. This gives a value of 64 A \* 0.57 = 36.8 A, so we have excellent margin.

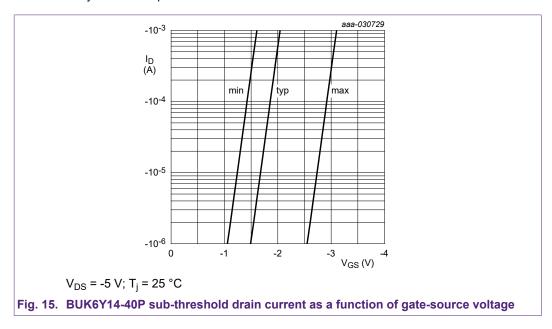If the threshold voltage falls to -1 V the device is guaranteed to be off, see Fig. 15 and the DIODE will be the only conduction path.




Hence losses when the device is in DIODE mode are large compared to when the device is operating in MOSFET mode making the MOSFET ideally suited to larger current, high temperature RBP applications.

Reverse battery protection in automotive applications
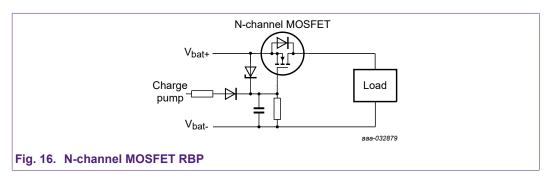
### 5. N-channel MOSFET solution steady state conduction loss

The majority of the description of P-channel behaviour also applies to N-channel devices. The major difference being that to enhance an N-channel device into MOSFET mode its gate must be biased positively with respect to its source.




Importantly the N-channel MOSFET is capable of conducting larger currents as the R<sub>DSon</sub> value for a particular die size is much lower than that of a P-channel device. The significantly lower power dissipation in MOSFET mode means that the N-channel device is much better suited for applications demanding larger currents.


The N-channel simulation uses as an example 24.5 A rather than 5.69 A of the P-channel simulation. This is based on an ambient temperature of 105  $^{\circ}$ C and a near stable T<sub>j</sub> of 140  $^{\circ}$ C. The power dissipated in the MOSFET is around 1.165 W at 140  $^{\circ}$ C. The circuit board material used is assumed to be suitable for such high temperatures ("normal" FR4 is capable to around 105  $^{\circ}$ C only, this is the ambient temperature here).

Referring to the simulation it can be seen that the source is at the battery positive voltage. Therefore to bias the gate above battery positive voltage a charge pump is normally required. To prevent the MOSFET being in linear mode where its R<sub>DSon</sub> would cause the device to dissipate more power than desirable, gate switching must be delayed until a satisfactory threshold voltage can be achieved.

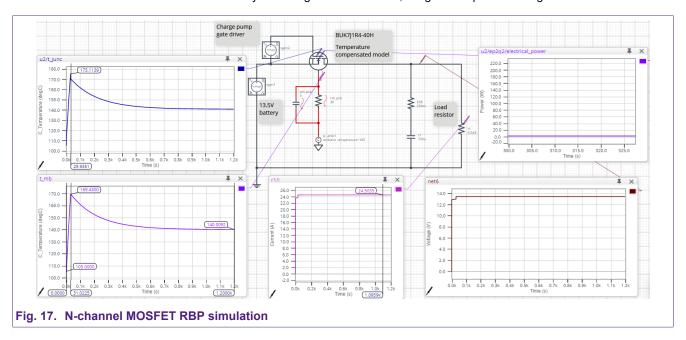In the simulation, there is a 30 second delay before the MOSFET switches on. During this time, the full load current is passing through the MOSFET body diode and the junction temperature reaches a peak of 175 °C, see Fig. 18. The power dissipated in the device is around 15 W. This demonstrates that by switching on the MOSFET, a significant power saving can be achieved.


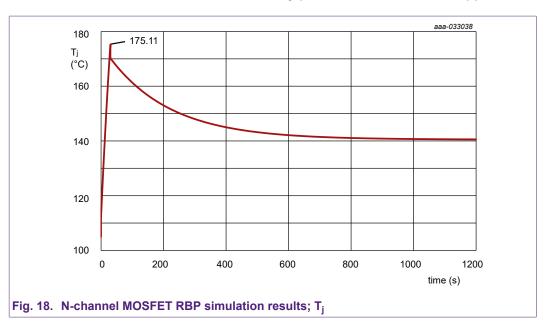
#### Reverse battery protection in automotive applications



### 6. Summary

The four key methods of reverse battery protection have been discussed.

Guidance has been provided to clarify the best approach to meet demands of the application while achieving optimal cost and performance.

Nexperia offers products which are very well suited for RBP applications.

Choose from very cost-effective Recovery rectifiers or Schottky rectifiers as solutions for lower power applications. Choose from P-channel and N-channel MOSFETs as the load current increases. Nexperia offers a range of thermally and electrically efficient device packages to support each area of application. To assist in that selection process electro-thermal simulation results are included in this application note and those simulations are available for the reader to explore via the Nexperia website interactive application note pages.

#### 7. References

- PNE20030EP data sheet
- PMEG045T150EPD data sheet
- BUK6Y14-40P data sheet
- BUK7J1R4-40H data sheet
- Nexperia interactive application notes

### 8. Revision history

Table 6. Revision history

Revision number	Date	Description
1.0	2021-01-12	Initial version

#### Reverse battery protection in automotive applications

### 9. Legal information

#### **Definitions**

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. Nexperia does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

#### **Disclaimers**

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, Nexperia does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. Nexperia takes no responsibility for the content in this document if provided by an information source outside of Nexperia.

In no event shall Nexperia be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, Nexperia's aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of Nexperia.

Right to make changes — Nexperia reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — Nexperia products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an Nexperia product can reasonably be expected to result in personal injury, death or severe property or environmental damage. Nexperia and its suppliers accept no liability for inclusion and/or use of Nexperia products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. Nexperia makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using Nexperia products, and Nexperia accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the Nexperia product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

Nexperia does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using Nexperia products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). Nexperia does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

**Translations** — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

#### **Trademarks**

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

### Reverse battery protection in automotive applications

## **List of Tables**

Table 1. Reverse battery positive rail protection options	2
Table 2. BUK6Y14-40P source-drain voltage characteristics	9
Table 3. BUK6Y14-40P thermal characteristics	10
Table 4. BUK6Y14-40P drain-source on-state resistance characteristics	. 11
Table 5. BUK6Y14-40P limiting values	11
Table 6. Revision history	.14

## Reverse battery protection in automotive applications

# **List of Figures**

Fig. 1. Recovery rectifier RBP	. 3
Fig. 2. Recovery rectifier RBP simulation schematic	. 4
Fig. 3. Recovery rectifier simulation results - junction and mounting base temperatures	. 5
Fig. 4. Recovery rectifier simulation results - D1 anode-to-cathode voltage	. 5
Fig. 5. Recovery rectifier simulation results - load current	5
Fig. 6. Schottky rectifier RBP	6
Fig. 7. Schottky rectifier RBP simulation	7
Fig. 8. Schottky rectifier simulation results - junction and mounting base temperatures	. 8
Fig. 9. Schottky rectifier simulation results - D1 anode-to-cathode voltage	8
Fig. 10. Schottky rectifier simulation results - load current	8.
Fig. 11. P-channel MOSFET RBP	8
Fig. 12. P-channel MOSFET RBP simulation	. 9
Fig. 13. P-channel MOSFET RBP simulation results; Tj and Tmb	10
Fig. 14. BUK6Y14-40P normalized drain-source on- state resistance as a function of junction temperature; typical values	11
Fig. 15. BUK6Y14-40P sub-threshold drain current as a function of gate-source voltage	12
Fig. 16. N-channel MOSFET RBP	13
Fig. 17. N-channel MOSFET RBP simulation	13
Fig. 18. N-channel MOSFET RBP simulation results; Tj	14

### Reverse battery protection in automotive applications

## **Contents**

1.	Introduction	2
2.	Recovery rectifier (PN diode) steady state induction loss	
3.	Schottky rectifier steady state conduction loss	6
	P-channel MOSFET solution steady state induction loss	8
	N-channel MOSFET solution steady state induction loss	13
6.	Summary	14
7.	References	14
8.	Revision history	14
	Legal information	

For more information, please visit: http://www.nexperia.com For sales office addresses, please send an email to: salesaddresses@nexperia.com Date of release: 12 January 2021

<sup>&</sup>lt;sup>©</sup> Nexperia B.V. 2021. All rights reserved