



# AN90030

## Paralleling of Nexperia GaN FETs in half-bridge topology

Rev. 2.0 — 19 October 2021


application note

### Document information

Information	Content
Keywords	NX-HB7000EV, GaN FET, TO-247, half-bridge, converter, paralleling, circuit design, PCB layout
Abstract	This application note explains the recommendations for circuit design and PCB layout when paralleling Nexperia TO-247 GaN FETs in a half-bridge configuration.

## 1. Introduction

GaN FETs are becoming increasingly important for modern power conversion systems, examples being inverters, power supplies and on-board chargers. The fundamental building block for many applications is the half-bridge as shown in [Fig. 1](#) below.

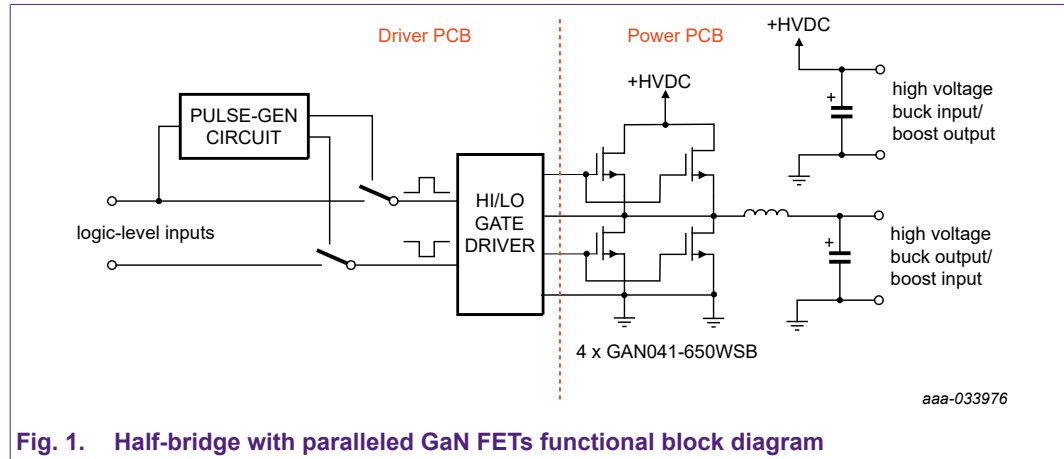

**Fig. 1. Half-bridge with paralleled GaN FETs functional block diagram**

To realise the power levels demanded by the growing number of high-power applications, designs using multiple GaN FETs in parallel are becoming more widespread.

With both the high currents in conjunction with the fast-switching speeds that are possible when utilising GaN FETs in these systems, these combinations of factors do present some challenges for the designer that will be discussed here.

One of the main challenges is current sharing between GaN FETs and associated switching stability. We will show how to parallel leaded TO-247 GaN FETs used for the high-side and low-side of a half-bridge driving an inductive load effectively.

It is obviously very important for paralleled GaN FETs to share current equally to prevent any individual device suffering from excessive power dissipation that could compromise reliability and lifetime. It is also very important that switching is stable without excessive oscillation which would in turn result in higher switching losses than are acceptable.

## 2. Half-bridge current sharing topology

For the purposes of this application note two paralleled GAN041-650WSB [\[1\]](#) GaN FETs in a side-by-side configuration for both the high-side and low-side have been selected for the half-bridge test circuit, which provides the following design benefits:

- Compact switching node
- Optimised current flow path

In addition to this, a separate PCB is utilised for the Gate drivers, which provides the following design benefits:

- Short and balanced gate drives


Symmetry is the key factor so that the effective impedance paths are matched as much as possible.

### 3. Gate drive design considerations

In this study we use a common gate driver for the paralleled GaN FETs. This means that the normal requirement for short gate-drive loops is complicated by the need for matched switching behaviour. Gate drive loops give the best performance when the Gate-Source loops are equalised in terms of path length (effective impedance) for each device being paralleled.

The drivers should be physically as close to the gates as possible to limit the track lengths, which provides the following benefits:

- Current shared equally by linear design
- Gate track lengths equal (as highlighted by the red rectangles in [Fig. 2](#)).

 

**Fig. 2. Gate driver PCB track lengths**

Best design practice is for the driver to be placed on the same PCB as the GaN FETs so that the inductance between the Source pin and driver are reduced as much as practically possible.

However, where this is not feasible due to design, placement or packaging constraints, and a separate driver board must be used, then the use of short wide tracks or ideally multiple signal planes on both boards, in association with large gauge terminals soldered between the boards, is advised. This will reduce the inductance between the GaN FET Source pin and driver as much as practically possible. Use of non-soldered connectors, such as plugs and sockets, are not recommended in the Gate-Source loop as these typically increase the inductance, leading to an increased risk of oscillation.

Also, for best Gate signal integrity, it is recommended that the connection between the Source pin and driver are to a “quiet” ground connection, where none of the main current is able to flow.

#### 3.1. Gate driver IC considerations

Isolated driver ICs offer packaging benefits as transformer isolation is a standard requirement for most designers to use between the controller and the power electronics and driver.

The gate driver IC utilized for the half-bridge test circuit is from the Silicon Labs Si827x series, specifically the Si8271<sup>[2]</sup>.

Features which make these gate drivers an appropriate choice include:

- high  $dv/dt$  immunity of 200 kV/ $\mu$ s CMTI
- fully isolated
- high output source/sink current capability

Similar features are available in gate driver ICs from other manufacturers also.

### 3.2. Gate Ferrite beads and resistors

Due to the extremely fast  $dv/dt$  that occurs during switching, this increases the possibility of oscillation in the half-bridge test circuit, which can very quickly lead to device damage or destruction. However, with very careful selection of the Gate ferrite bead and resistors for each connection to the GaN FETs, the possibility of oscillation can be minimised.

The GAN041-650WSB GaN FETs do not have an internal ferrite bead and as such allows the designer much more flexibility in selecting the optimal component required. As specified in the Nexperia GAN041-650WSB data sheet [\[1\]](#), the recommended ferrite bead is the BLM18AG221SN1D, supplied by Murata. This ferrite has a typical impedance of  $220\ \Omega$  at 100 MHz and has been found to be extremely effective in suppressing any gate circuit instability in the half-bridge test circuit.

Along with the ferrite bead, the value of the resistor(s) in the gate circuit also contributes significantly to the switching stability. Nexperia recommends that initial stability tests are conducted with a gate resistance of  $15\ \Omega$ . However, the final value(s) chosen will depend on the driver used and its respective current source/sink capabilities.

For the half-bridge test circuit, resistances of  $15\ \Omega$  and  $7.5\ \Omega$  are connected to the active high and low outputs of the drivers respectively.

While individual ferrite beads should be used in series with each gate, a single gate resistor can be used at the driver output. Refer to the schematics [Fig. 21](#) and [Fig. 26](#) for further details.

## 4. DC bus snubbers and decoupling

DC bus snubbers must be connected between the high voltage and ground planes (very large voltage overshoots are seen without appropriate suppression) and should be located as close as possible to each GaN FET. Typically, these DC Bus snubbers would consist of a  $10\ \Omega$  resistor in series with  $10\ \text{nF}$  capacitor.

Also, decoupling capacitances of  $10\ \text{nF}$  and  $100\ \text{nF}$  value should be located as close as possible to each GaN FET and be connected between the high voltage and ground planes. See [Fig. 3](#) and [Fig. 4](#).

 


Fig. 3. Bus snubber RC networks and decoupling capacitors schematic

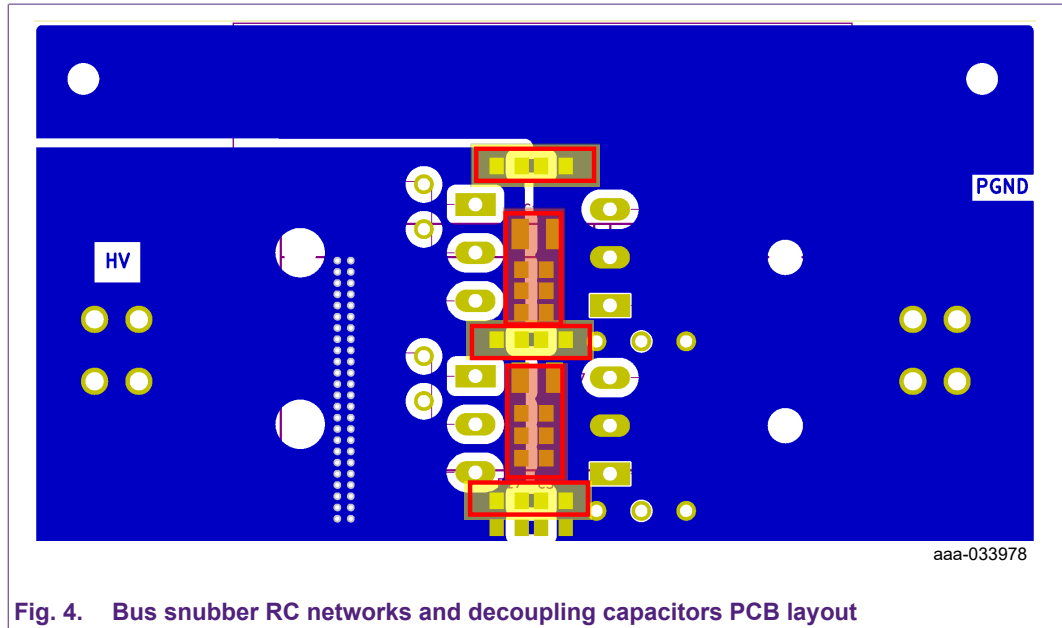


Fig. 4. Bus snubber RC networks and decoupling capacitors PCB layout

#### 4.1. Switching node snubber

Switching node snubbers are only recommended to achieve maximum stability at high switching currents. These will increase the switching loss and are only recommended at high power levels where the losses are a very small percentage of the total power.

Although provision has been made in the half-bridge test circuit for multiple snubbers between the DC bus and switch node and between the Switch Node and Ground, none were required to be populated to achieve switching stability and excellent switch node voltage overshoot control and damping.

#### 4.2. Thermal considerations

The  $R_{DS(on)}$  of the cascode GaN HEMT has a positive temperature coefficient. The  $V_{GS(th)}$  of the GaN FET has a negative temperature coefficient which means that the device with the higher junction temperature will turn on first and therefore be subjected to a higher share of the current. However, the GaN FETs have been mounted so that even heat distribution is achieved, which results in even current sharing between devices. So, when paralleling GaN FETs, it is very important for them to be effectively heatsinked and implicitly very well connected thermally together.

## 5. Layout optimisation for current Sharing

Testing has shown that current sharing can be improved by positioning the devices in line with the current and load path to keep the distances between the inputs and outputs symmetrical.

The current path is much better with balanced copper flood planes. For balanced operation, a layout should aim to have the parallel devices in line with the load and power as shown in [Fig. 5](#), keeping the current loop as small as possible.

Paralleling of Nexperia GaN FETs in half-bridge topology

 


Fig. 5. PCB current paths

## 6. Captured waveforms from single-shot staircase test

In this section are shown the test results from performing a seven pulse, single-shot staircase test at 100 kHz. The inductor is connected to the BUS voltage set at 400 V and the current flows through the low-side GaN FETs and recirculates through the high-side GaN FETs. Each pulse has a width of 1.9  $\mu\text{s}$ , leading to a peak inductor current of 114 A.

See Fig. 6, the oscilloscope channel identifications are as follows:

- C1 – low-side GaN FET Q2 gate signal
- C2 – low-side GaN FET Q4 gate signal
- C3 – inductor current
- C4 – switch node voltage



Fig. 6. Single-Shot staircase test waveforms

Note : An air-cored non-overlapped inductor is used, avoiding saturation and keeping winding parasitic capacitance low.



Fig. 7. Zoom of final pulse

Notice how closely matched the gate signals are, and that they are nicely damped at switch off - as such there is no risk of sustained oscillation.

The impedance of the ferrite bead permits the ringing on the internal Source inductance to be visible at the Gate pin. This is a natural consequence of the decoupling effect of the ferrite. If the Gate potential were held rigidly, then instead of observable voltage oscillations, there would be unobservable current oscillations which would be coupled and amplified.

Fig. 8 shows the individual GaN FET currents measured in the same seven pulse, 100 kHz, staircase test.

The oscilloscope channel identification are as follows:

- C1 – low-side GaN FET Q2 gate signal
- C2 – switch node voltage
- C3 – low-side GaN FET Q2 device current
- C4 – low-side GaN FET Q4 device current



Paralleling of Nexperia GaN FETs in half-bridge topology



Fig. 8. Individual GaN FET currents

Note - the magenta and green traces are measured GaN FET currents, showing excellent current sharing between devices.

## 7. System performance running in BUCK mode

In this section are shown the captured oscilloscope traces and test results when the system is running in BUCK mode. The operating conditions are as follows:

- Input voltage = 400 V
- Output voltage = 225 V
- Output power = 6.6 kW
- Switching frequency = 100 kHz
- Ambient temperature = 34 °C

In [Fig. 9](#) the oscilloscope channel identification are as follows:


- C1 – low-side GaN FET Q2 Gate signal
- C2 – low-side GaN FET Q4 Gate signal
- C3 – Inductor current
- C4 – Switch Node voltage



Fig. 9. System running in BUCK mode

Paralleling of Nexperia GaN FETs in half-bridge topology

Fig. 10 and Fig. 11 show zooms of the low-side GaN FETs during switch ON and switch OFF.

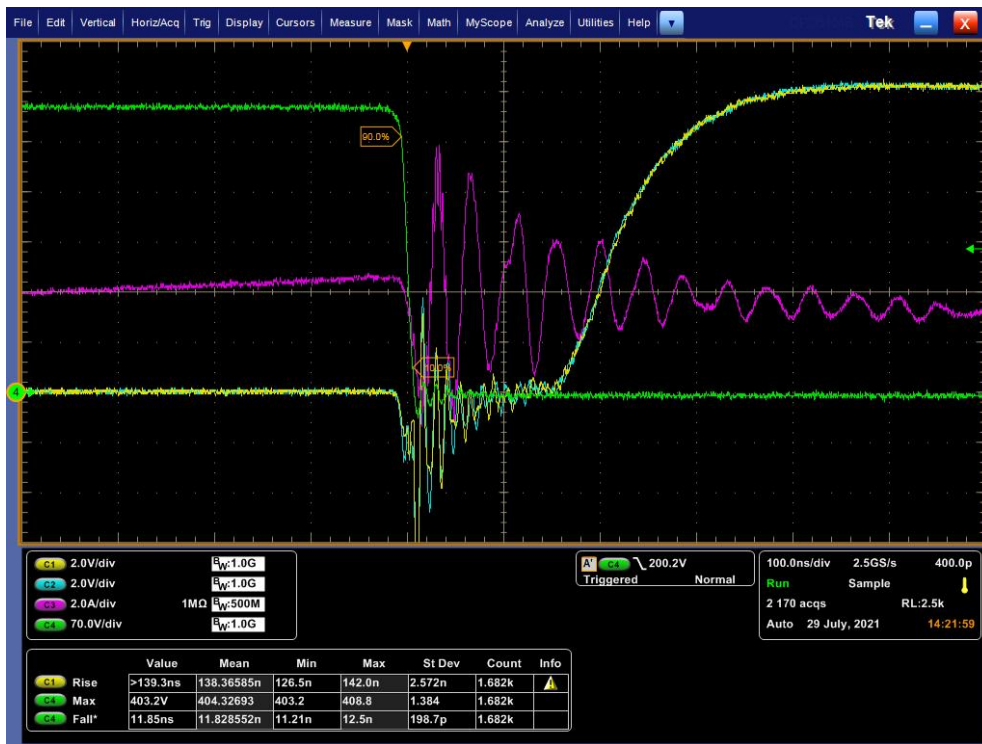

aaa-033984

Fig. 10. Zoom of Q2 and Q4 low-side GaN FETs - switch ON



aaa-033985

Fig. 11. Zoom of Q2 and Q4 low-side GaN FETs - switch OFF

Paralleling of Nexperia GaN FETs in half-bridge topology

Note that during switching events any voltage oscillations on both the Gate and Switch Node signals have been very effectively damped.

Fig. 12 shows the high-side currents, the oscilloscope channel identification are as follows:

- C1 – low-side GaN FET Q2 Gate signal
- C2 – Switch Node voltage
- C3 – high-side GaN FET Q1 device current
- C4 – high-side GaN FET Q3 device current



aaa-033986

Fig. 12. System running in BUCK mode - GaN FET high-side currents



Paralleling of Nexperia GaN FETs in half-bridge topology

Fig. 13 shows the low-side device currents, the oscilloscope channel identification are as follows:


- C1 – low-side GaN FET Q2 Gate signal
- C2 – Switch Node voltage
- C3 – low-side GaN FET Q2 device current
- C4 – low-side GaN FET Q4 device current



Fig. 13. System running in BUCK mode - GaN FET low-side currents

## 7.1. Efficiency sweep and device temperatures

Fig. 14 shows the measured efficiency of the circuit using 2 parallel GAN041-650WSB GaN FETs while operating in BUCK mode.

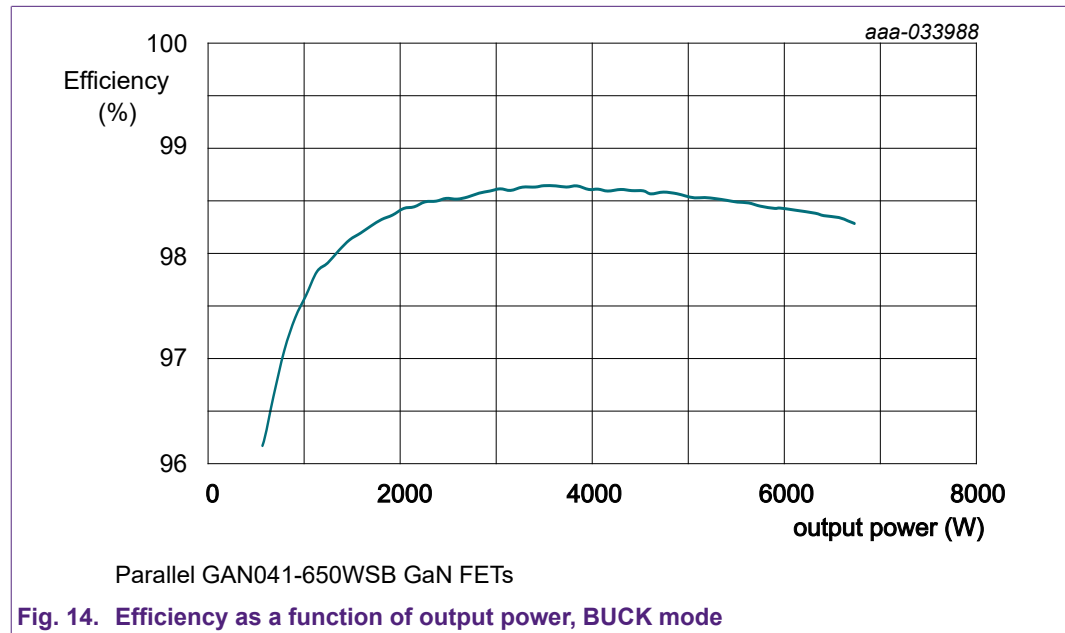

Device temperatures were measured using thermocouples bonded to the front face of the mounting bases and are all very close to each other:

- high-side GaN FET Q1 = 69.6 °C
- high-side GaN FET Q3 = 74.9 °C
- low-side GaN FET Q2 = 72.3 °C
- low-side GaN FET Q4 = 69.1 °C

These results confirm excellent current sharing and thermal connection of all devices.

## 8. System performance running in BOOST mode

In this section are shown the captured oscilloscope traces and test results when the system is running in BOOST mode. The operating conditions are as follows:

- Input voltage = 225 V
- Output voltage = 400 V
- Output power = 6.6 kW
- Switching frequency = 100 kHz
- Ambient temperature = 32 °C

In [Fig. 15](#) the oscilloscope channel identification are as follows:

- C1 – low-side GaN FET Q2 Gate signal
- C2 – low-side GaN FET Q4 Gate signal
- C3 – Inductor current
- C4 – Switch Node voltage



aaa-033989

Fig. 15. System running in BOOST mode

Paralleling of Nexperia GaN FETs in half-bridge topology

Fig. 16 and Fig. 17 show zooms of the low-side GaN FETs during switch ON and switch OFF.



aaa-033990

Fig. 16. Zoom of Q2 and Q4 low-side GaN FETs - switch ON



aaa-0339915

Fig. 17. Zoom of Q2 and Q4 low-side GaN FETs - switch OFF



Paralleling of Nexperia GaN FETs in half-bridge topology

Note that during switching events any voltage oscillations on both the Gate and Switch Node signals have been very effectively damped.

Fig. 18 shows the high-side currents, the oscilloscope channel identification are as follows:

- C1 – low-side GaN FET Q2 Gate signal
- C2 – Switch Node voltage
- C3 – high-side GaN FET Q1 device current
- C4 – high-side GaN FET Q3 device current



Fig. 18. System running in BOOST mode - GaN FET high-side currents

Fig. 19 show the low-side device currents, the oscilloscope channel identification are as follows:

- C1 – low-side GaN FET Q2 Gate signal
- C2 – Switch Node voltage
- C3 – low-side GaN FET Q2 device current
- C4 – low-side GaN FET Q4 device current

Paralleling of Nexperia GaN FETs in half-bridge topology


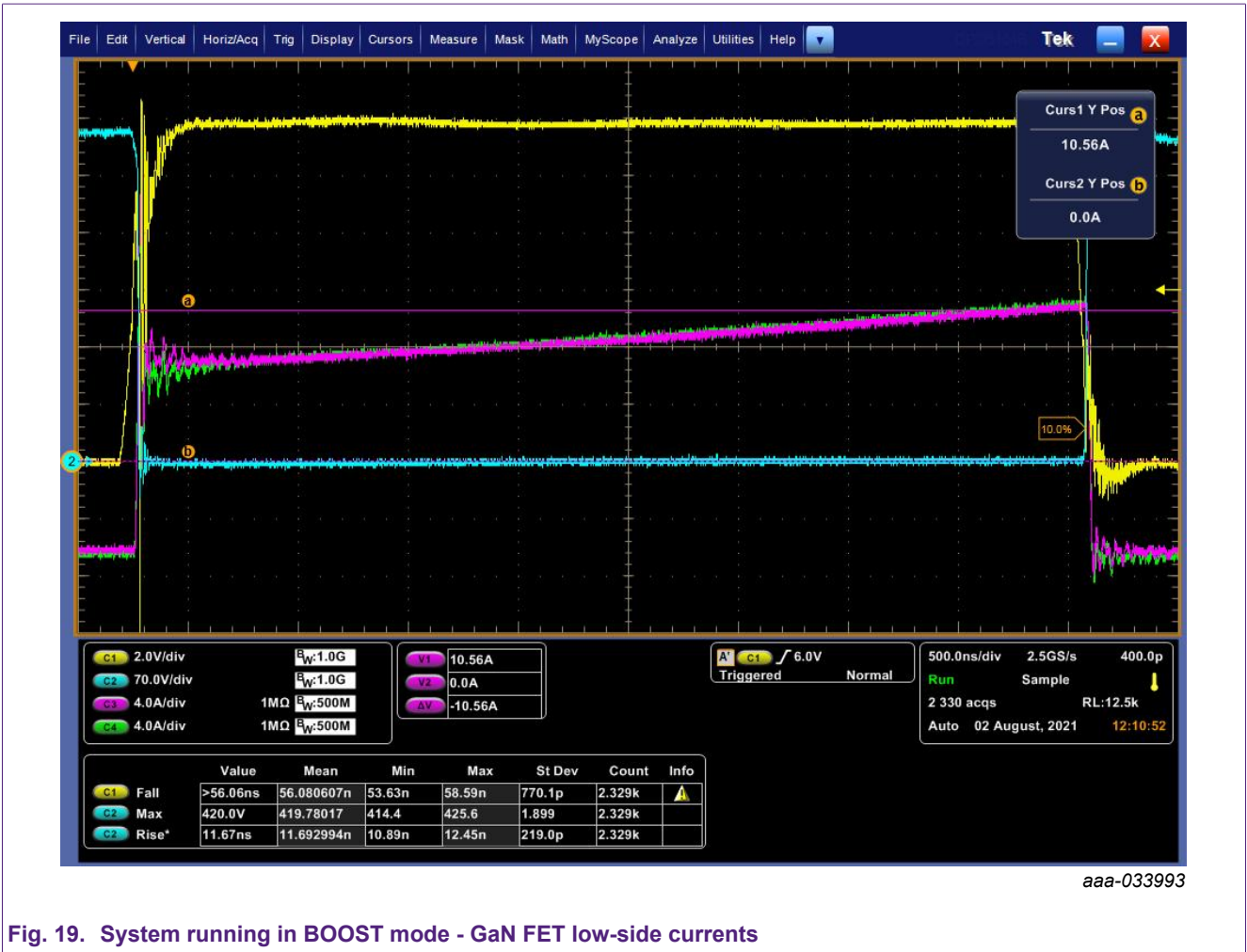


Fig. 19. System running in BOOST mode - GaN FET low-side currents

### 8.1. Efficiency sweep and device temperatures

Fig. 20 shows the measured efficiency of the circuit using 2 parallel GAN041-650WSB GaN FETs while operating in BOOST mode.

 

Device temperatures were measured using thermocouples bonded to the front face of the mounting bases and are all very close to each other:

- high-side GaN FET Q1 = 60.3 °C
- high-side GaN FET Q3 = 67.2 °C
- low-side GaN FET Q2 = 78.0 °C
- low-side GaN FET Q4 = 71.0 °C

These results confirm excellent current sharing and thermal connection of all devices.

## 9. Probing considerations

Nexperia application note AN90004<sup>[3]</sup>, “*Probing considerations for fast switching applications*” should be followed to ensure accurate measurement of any switching circuits.

Additionally, the low-side ground spring should either be soldered directly to the Source pin on the package or alternatively to a “quiet” ground connection, where none of the main current is able to flow.

## 10. Design Details

The half-bridge converter circuit detail in this application note has been implemented on two 4-layer PCBs with 2oz copper for the outer layers and 1.5 oz copper for the inner layers.

The circuit schematic, PCB layout and Bill of Material for the two PCBs are shown in the next sections.

10.1. Power board schematic

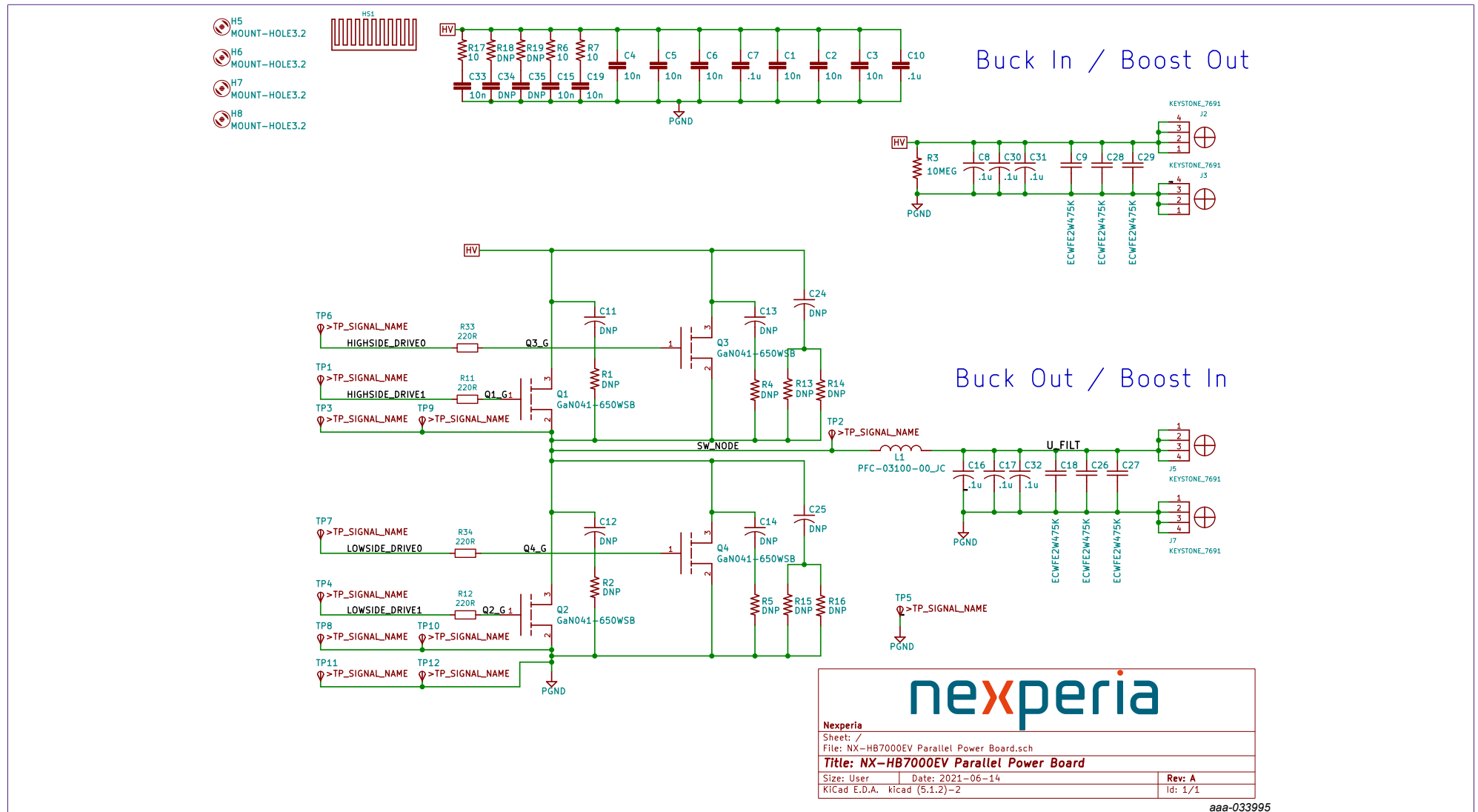


Fig. 21. Power board schematic

## 10.2. Power board PCB layout, planes and tracking

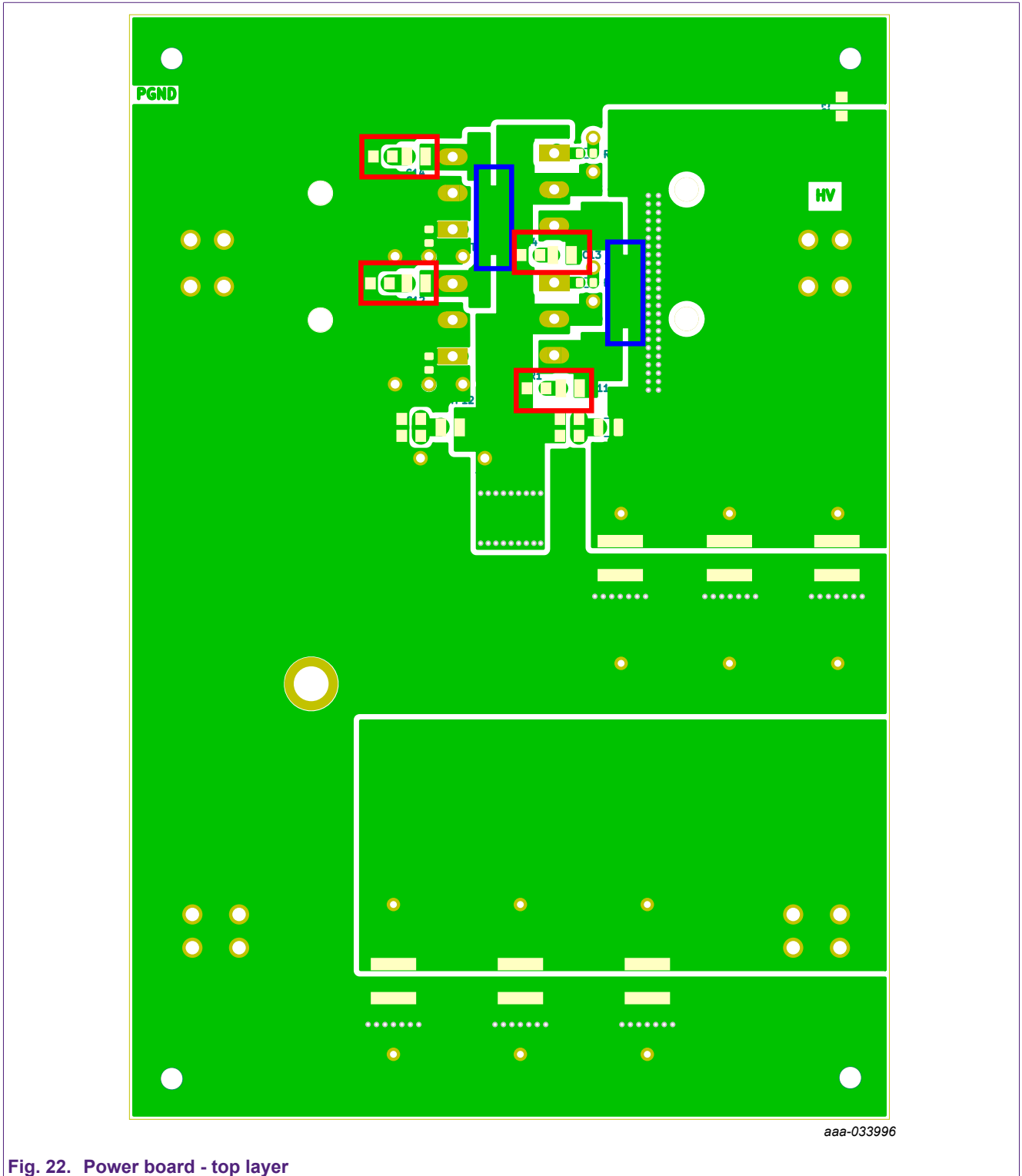


Fig. 22. Power board - top layer

Note how the Drain connections identified by the blue rectangles have been made symmetrically to Switch Node and HV, the snubbers identified by the red rectangles are placed directly on the Drain pins and the use of stitch vias between planes.


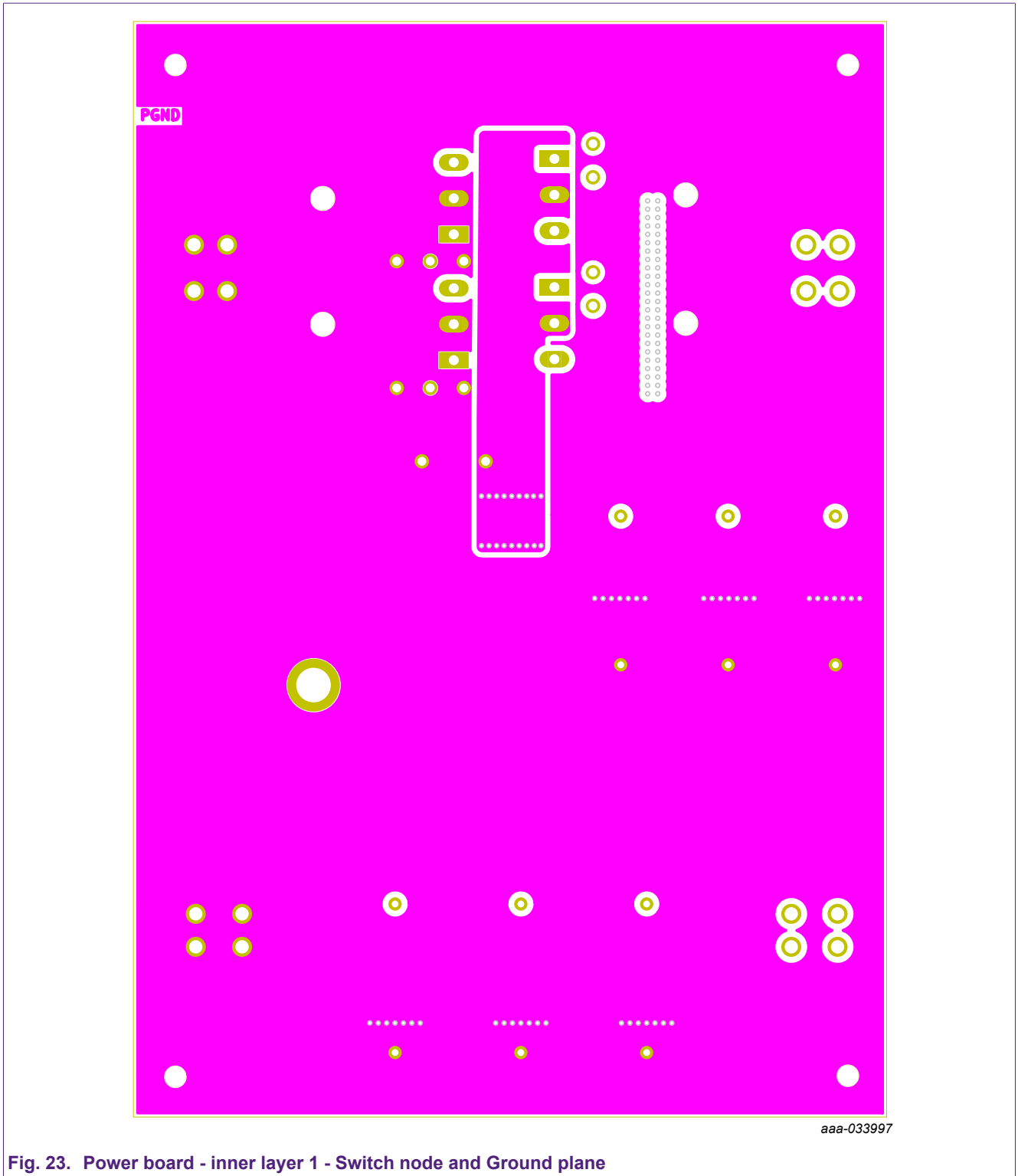


Fig. 23. Power board - inner layer 1 - Switch node and Ground plane

Note the extremely compact Switch Node.

 

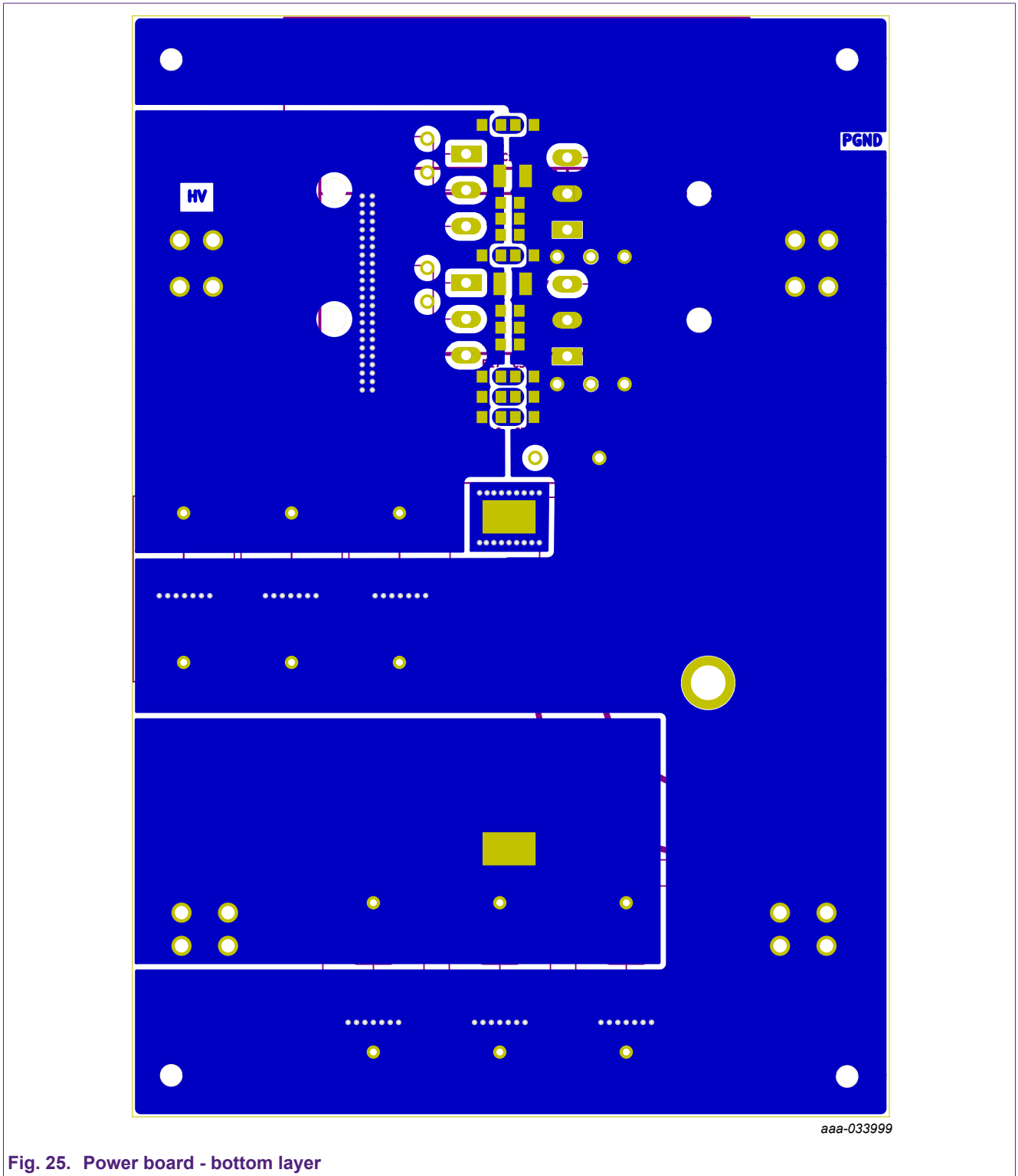


Fig. 25. Power board - bottom layer



### 10.3. Power board Bill of Materials

Table 1. Power board Bill of Material

Part	Value	Voltage	Package	Description	Supplier	Supplier P/N
C1	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C2	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C3	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C4	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C5	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C6	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C7	100n	1kV	C1812	Capacitor, Ceramic	Farnell	2085218
C8	100n	1kV	C2225	Capacitor, Ceramic	Farnell	1838767 or 2896821
C9	2.2uF	630V	PHE450_2U	Capacitor, PP Film	RS	105-1057
C10	100n	1kV	C1812	Capacitor, Ceramic	Farnell	2085218
C11	-	-	C1210	Capacitor, Ceramic	-	-
C12	-	-	C1210	Capacitor, Ceramic	-	-
C13	-	-	C1210	Capacitor, Ceramic	-	-
C14	-	-	C1210	Capacitor, Ceramic	-	-
C15	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C16	100n	1kV	C2225	Capacitor, Ceramic	Farnell	1838767 or 2896821
C17	100n	1kV	C2225	Capacitor, Ceramic	Farnell	1838767 or 2896821
C18	2.2uF	630V	PHE450_2U	Capacitor, PP Film	RS	105-1057
C19	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C24	-	-	C1210	Capacitor, Ceramic	-	-
C25	-	-	C1210	Capacitor, Ceramic	-	-
C26	2.2uF	630V	PHE450_2U	Capacitor, PP Film	RS	105-1057
C27	2.2uF	630V	PHE450_2U	Capacitor, PP Film	RS	105-1057
C28	2.2uF	630V	PHE450_2U	Capacitor, PP Film	RS	105-1057
C29	2.2uF	630V	PHE450_2U	Capacitor, PP Film	RS	105-1057
C30	100n	1kV	C2225	Capacitor, Ceramic	Farnell	1838767 or 2896821
C31	100n	1kV	C2225	Capacitor, Ceramic	Farnell	1838767 or 2896821
C32	100n	1kV	C2225	Capacitor, Ceramic	Farnell	1838767 or 2896821
C33	10n	630V	C1206	Capacitor, Ceramic	Farnell	1759518
C34	-	-	C1210	Capacitor, Ceramic	-	-
C35	-	-	C1210	Capacitor, Ceramic	-	-
HS1			COOL_INNO_1	Heatsink	Cool Innovations	
J2			KEYSTONE_7691	Screw Terminal	Mouser	534-7691-SEMS
J3			KEYSTONE_7691	Screw Terminal	Mouser	534-7691-SEMS

## Paralleling of Nexperia GaN FETs in half-bridge topology

J5			KEYSTONE _7691	Screw Terminal	Mouser	534-7691-SEMS
J7			KEYSTONE _7691	Screw Terminal	Mouser	534-7691-SEMS
L1	220uH					
Q1	GAN041-650WSB	650V	TO-247	GaN FET	Nexperia	GAN041-650WSB
Q2	GAN041-650WSB	650V	TO-247	GaN FET	Nexperia	GAN041-650WSB
Q3	GAN041-650WSB	650V	TO-247	GaN FET	Nexperia	GAN041-650WSB
Q4	GAN041-650WSB	650V	TO-247	GaN FET	Nexperia	GAN041-650WSB
R1	-	-	R1206	Resistor	-	-
R2	-	-	R1206	Resistor	-	-
R3	10MEG		R1206	Resistor	Farnell	1469973
R4	-	-	R1206	Resistor	-	-
R5	-	-	R1206	Resistor	-	-
R6	10	-	R1206	Resistor	Farnell	1738986
R7	10	-	R1206	Resistor	Farnell	1738986
R11	220		0603	Ferrite	Farnell	1515674
R12	220		0603	Ferrite	Farnell	1515674
R13	-	-	R1206	Resistor	-	-
R14	-	-	R1206	Resistor	-	-
R15	-	-	R1206	Resistor	-	-
R16	-	-	R1206	Resistor	-	-
R17	10	-	R1206	Resistor	Farnell	1738986
R18	-	-	R1206	Resistor	-	-
R19	-	-	R1206	Resistor	-	-
R33	220		0603	Ferrite	Farnell	1515674
R34	220		0603	Ferrite	Farnell	1515674
				Alumina insulator	Mouser	532-4169G
				Alumina insulator	Mouser	532-4169G
				Alumina insulator	Mouser	532-4169G
				Alumina insulator	Mouser	532-4169G
				Cooling Fan	RS	922-6248
				Standoff	Farnell	1733422
				Standoff	Farnell	1733422
				Standoff	Farnell	1733422
				Standoff	Farnell	1733422
				Screw M3 x 6mm	RS	560-754
				Screw M3 x 6mm	RS	560-754
				Screw M3 x 6mm	RS	560-754
				Screw M3 x 6mm	RS	560-754
				PCB	PCBWay	NX-HB7000EV Parallel TO-247 Current Board Rev1.1

10.4. Driver board schematics

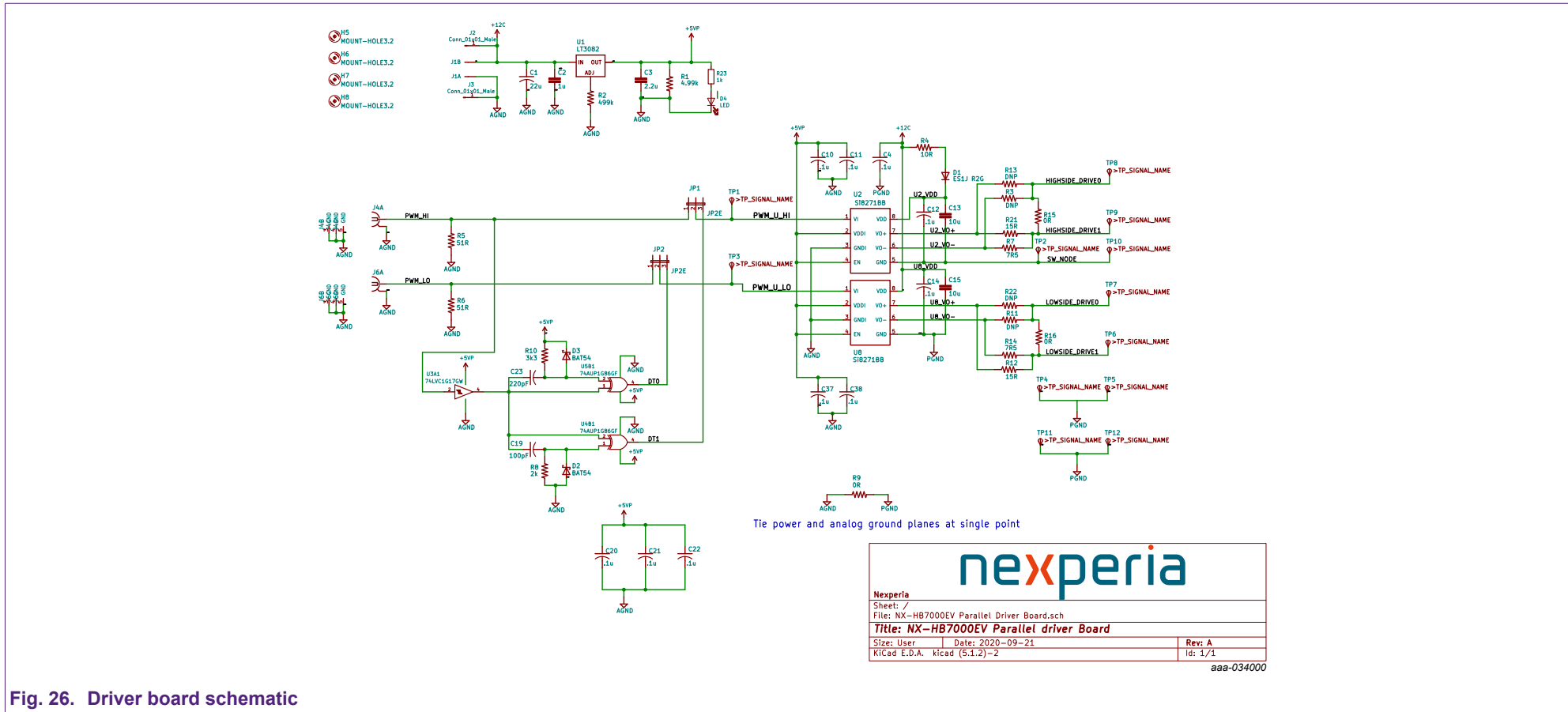


Fig. 26. Driver board schematic

### 10.5. Driver board PCB layout, planes and tracking

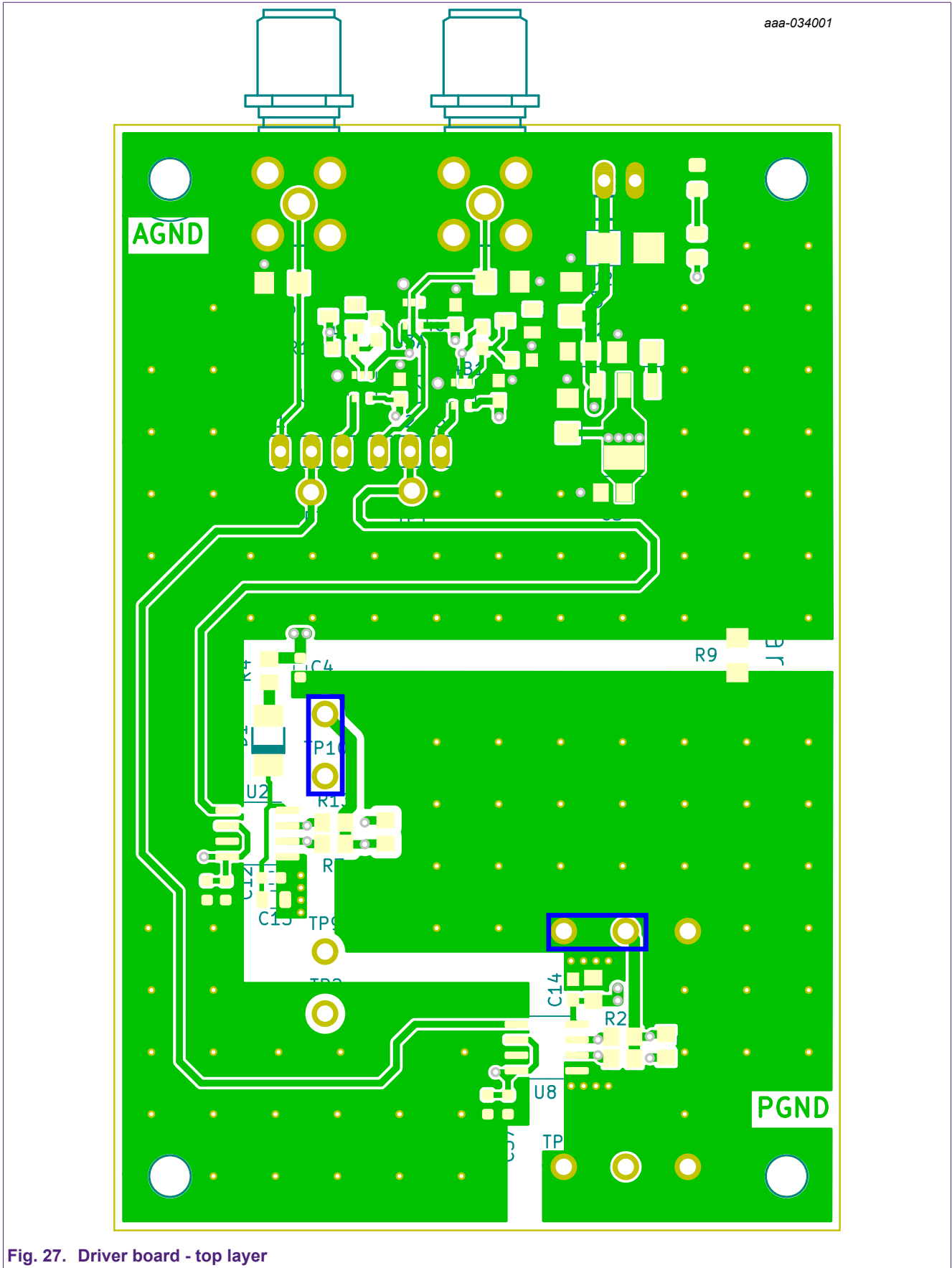


Fig. 27. Driver board - top layer

Paralleling of Nexperia GaN FETs in half-bridge topology

Note the top layer, (Fig. 27), uses symmetrical GaN FET Gate connections for one high-side and one low-side identified by the blue rectangles – the Gate connections for the associated paralleled GaN FET are routed on the Bottom Layer.

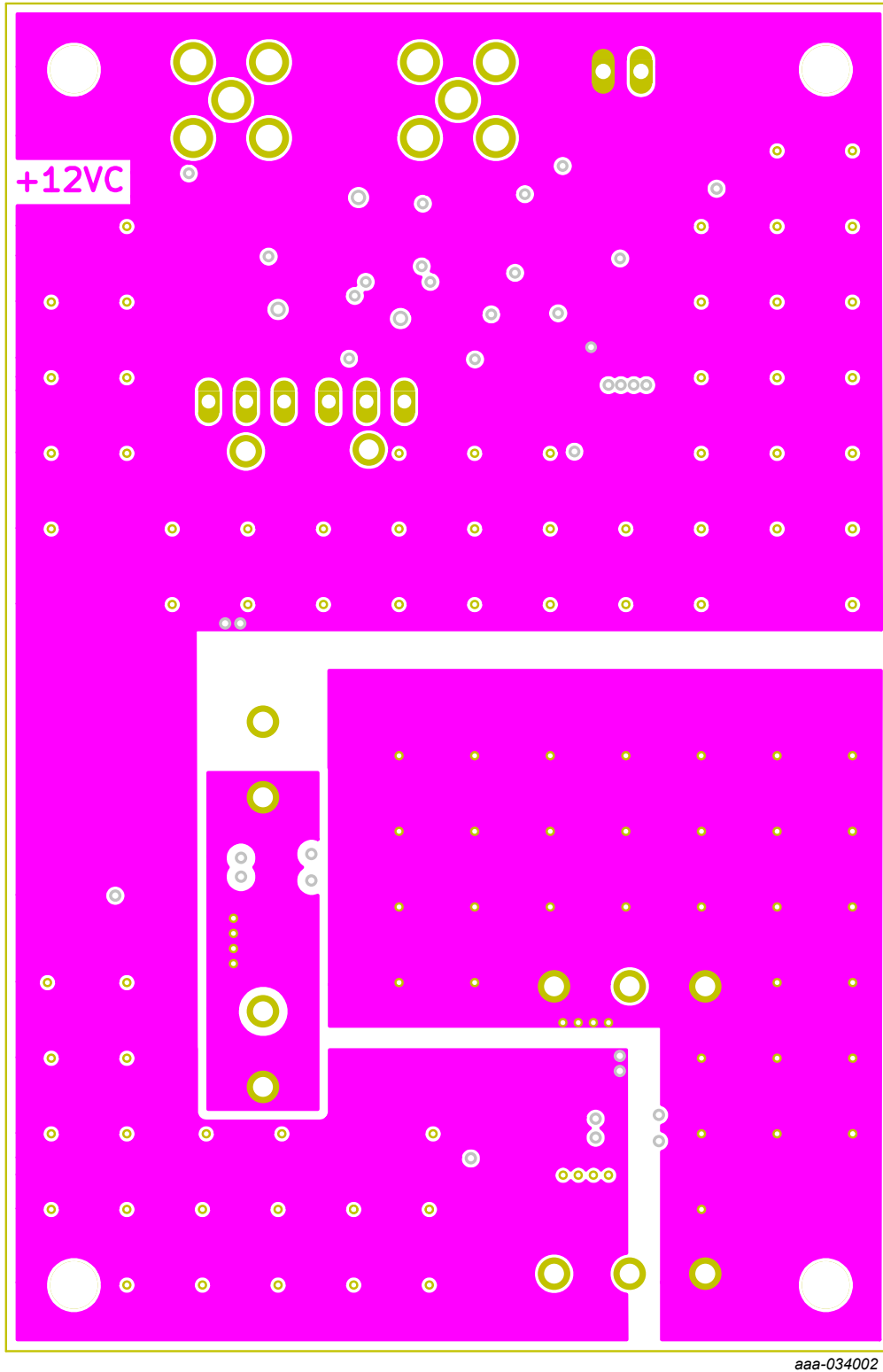


Fig. 28. Driver board - inner layer 1 – Switch Node, 12 V, Analogue Ground and Power Ground Planes

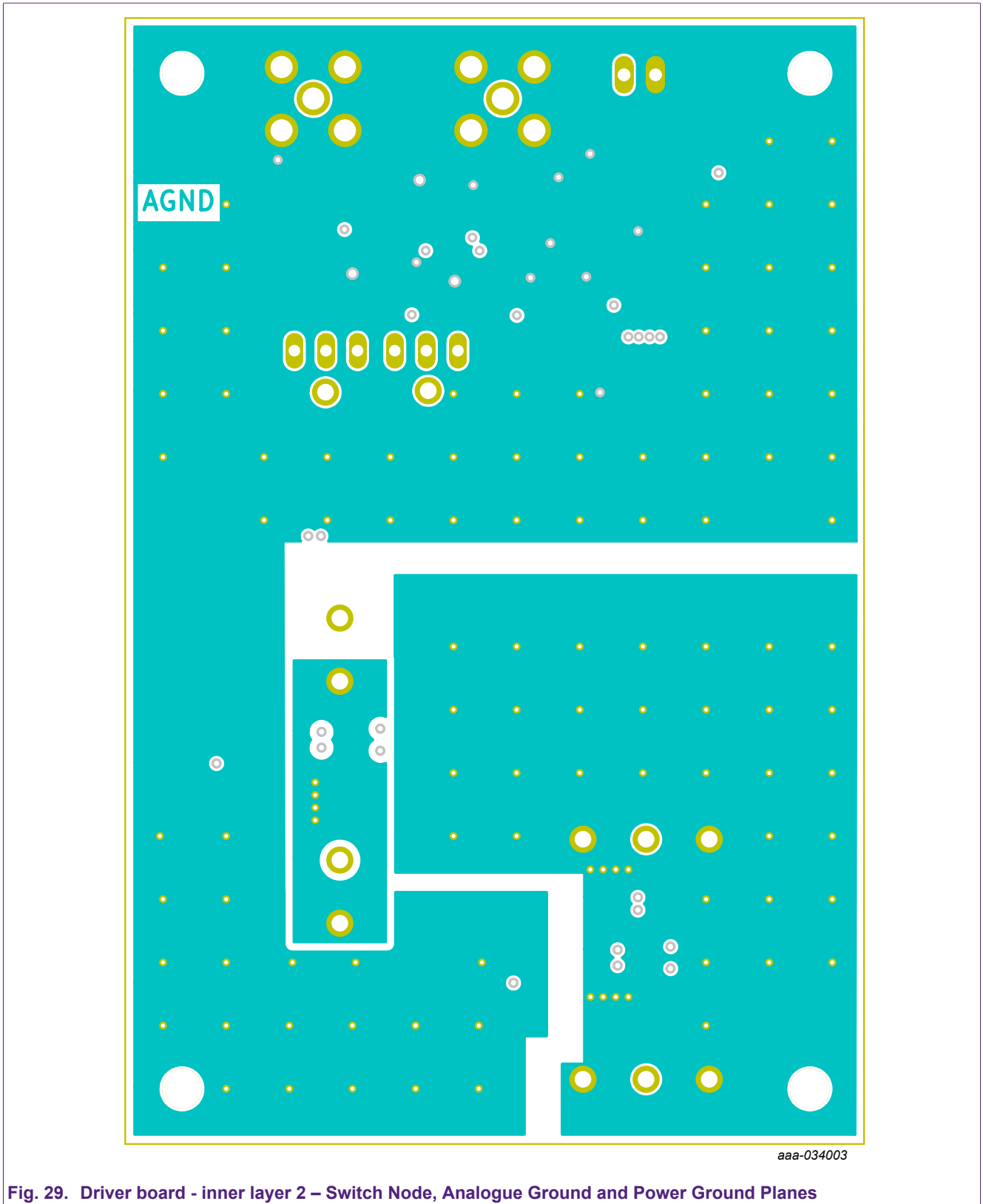


Fig. 29. Driver board - inner layer 2 – Switch Node, Analogue Ground and Power Ground Planes

 


Fig. 30. Driver board - bottom layer

## 10.6. Driver board Bill of Materials

Table 2. Driver board Bill of Material

Part	Value	Voltage	Package	Description	Supplier	Supplier P/N
C1	22uF	35V	C1206	Capacitor, Ceramic	Farnell	2525173
C2	1uF	50V	C0805	Capacitor, Ceramic	Farnell	2094043
C3	2.2uF	50V	C0805	Capacitor, Ceramic	Farnell	2346931
C4	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C10	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C11	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C12	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C13	10uF	35V	C0805	Capacitor, Ceramic	Farnell	2547034
C14	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C15	10uF	35V	C0805	Capacitor, Ceramic	Farnell	2547034
C19	100pF	100V	C0603	Capacitor, Ceramic C0G	Farnell	1740605
C20	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C21	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C22	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C23	220pF	50V	C0603	Capacitor, Ceramic C0G	Farnell	498579
C37	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
C38	100nF	100V	C0603	Capacitor, Ceramic	Farnell	2749806
D1	ES1J	600V	DO-214AC	Diode	Farnell	3519291
D2	BAT54	30V	SOT23	Diode, Schottky	Nexperia	BAT54,215
D3	BAT54	30V	SOT23	Diode, Schottky	Nexperia	BAT54,215
D4	LED	-	D0805	LED, Green	Farnell	2610419
J1	22-23-2021	-	2.54mm	2-pin header	Farnell	1462926
J4	BU-SMA-G	-	BU-SMA-G	Female SMA Connector	Farnell	2112448
J6	BU-SMA-G	-	BU-SMA-G	Female SMA Connector	Farnell	2112448
JP1	-	-	2.54mm	3-pin header	Farnell	1248150
JP2	-	-	2.54mm	3-pin header	Farnell	1248150
R1	4.99k	-	R1206	Resistor	Farnell	1470015
R2	499k	-	R1206	Resistor	Farnell	1470019
R3	-	-	R0805	Resistor	-	-
R4	10R	-	R0805	Resistor	Farnell	2303326
R5	51R	-	R1206	Resistor	Farnell	1470021
R6	51R	-	R1206	Resistor	Farnell	1470021
R7	7R5	-	R0805	Resistor	Farnell	3235185
R8	2k	-	R0603	Resistor	Farnell	2059343
R9	0R	-	R1206	Resistor	Farnell	1469963
R10	3k3	-	R0603	Resistor	Farnell	2303173
R11	-	-	R0805	Resistor	-	-
R12	15R	-	R0805	Resistor	Farnell	1750730



## Paralleling of Nexperia GaN FETs in half-bridge topology

R13	-	-	R0805	Resistor	-	-
R14	7R5	-	R0805	Resistor	Farnell	3235185
R15	0R	-	R0805	Resistor	Farnell	9233750
R16	0R	-	R0805	Resistor	Farnell	9233750
R21	15R	-	R0805	Resistor	Farnell	1750730
R22	-	-	R0805	Resistor	-	-
R23	1k	-	R0805	Resistor	Farnell	1469847
U1	LT3082	-	SOT223-3	Linear Regulator	Mouser	584-LT3082EST#PBF
U2	Si8271BB-IS	-	SOIC8	HI/LO ISO Gate Driver	Farnell	2524443
U3A1	74LVC1G17GW	-	TSSOP-5	Schmitt Trigger Buffer	Nexperia	74LVC1G17GW
U4B1	74HCT1G86GW	-	TSSOP-5	2-input X-OR gate	Nexperia	74HCT1G86GW
U5B1	74HCT1G86GW	-	TSSOP-5	2-input X-OR gate	Nexperia	74HCT1G86GW
U8	Si8271BB-IS	-	SOIC8	HI/LO ISO Gate Driver	Farnell	2524443
				Shorting Link	RS	251-8503
				Shorting Link	RS	251-8503
				PCB	PCBWay	NX-HB7000EV Parallel TO-247 Driver Board Rev1.1

## 11. Summary

By using careful layout, short and impedance balanced gate drives, correctly placed DC Bus snubbers and decoupling, it is possible to achieve excellent current sharing in paralleled GaN FETs driving an inductive load. This has been effectively shown using leaded parts on a 4-layer FR4 PCB.

## 12. References

1. [GAN041-650WSB data sheet](#).
2. [Si8271 data sheet](#).
3. Nexperia application note [AN90004](#).

## 13. Revision history

Table 3. Revision history

Revision number	Date	Description
2.0	2021-10-19	Minor changes to <a href="#">Section 2</a> and <a href="#">Section 4</a> .
1.0	2021-09-21	Initial version.

## 14. Legal information

### Definitions

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. Nexperia does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

### Disclaimers

**Limited warranty and liability** — Information in this document is believed to be accurate and reliable. However, Nexperia does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. Nexperia takes no responsibility for the content in this document if provided by an information source outside of Nexperia.

In no event shall Nexperia be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, Nexperia's aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the Terms and conditions of commercial sale of Nexperia.

**Right to make changes** — Nexperia reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — Nexperia products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an Nexperia product can reasonably be expected to result in personal injury, death or severe property or environmental damage. Nexperia and its suppliers accept no liability for inclusion and/or use of Nexperia products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. Nexperia makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using Nexperia products, and Nexperia accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the Nexperia product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

Nexperia does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using Nexperia products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). Nexperia does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

**Translations** — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

### Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

**List of Tables**

Table 1. Power board Bill of Material..... 25  
Table 2. Driver board Bill of Material..... 32  
Table 3. Revision history..... 33

## List of Figures

Fig. 1. Half-bridge with paralleled GaN FETs functional block diagram.....	2
Fig. 2. Gate driver PCB track lengths.....	3
Fig. 3. Bus snubber RC networks and decoupling capacitors schematic.....	4
Fig. 4. Bus snubber RC networks and decoupling capacitors PCB layout.....	5
Fig. 5. PCB current paths.....	6
Fig. 6. Single-Shot staircase test waveforms.....	7
Fig. 7. Zoom of final pulse.....	8
Fig. 8. Individual GaN FET currents.....	9
Fig. 9. System running in BUCK mode.....	10
Fig. 10. Zoom of Q2 and Q4 low-side GaN FETs - switch ON.....	11
Fig. 11. Zoom of Q2 and Q4 low-side GaN FETs - switch OFF.....	11
Fig. 12. System running in BUCK mode - GaN FET high-side currents.....	12
Fig. 13. System running in BUCK mode - GaN FET low-side currents.....	13
Fig. 14. Efficiency as a function of output power, BUCK mode.....	14
Fig. 15. System running in BOOST mode.....	15
Fig. 16. Zoom of Q2 and Q4 low-side GaN FETs - switch ON.....	16
Fig. 17. Zoom of Q2 and Q4 low-side GaN FETs - switch OFF.....	16
Fig. 18. System running in BOOST mode - GaN FET high-side currents.....	17
Fig. 19. System running in BOOST mode - GaN FET low-side currents.....	18
Fig. 20. Efficiency as a function of output power, BOOST mode.....	19
Fig. 21. Power board schematic.....	20
Fig. 22. Power board - top layer.....	21
Fig. 23. Power board - inner layer 1 - Switch node and Ground plane.....	22
Fig. 24. Power board - inner layer 2 - Switch node, HV and Ground planes.....	23
Fig. 25. Power board - bottom layer.....	24
Fig. 26. Driver board schematic.....	27
Fig. 27. Driver board - top layer.....	28
Fig. 28. Driver board - inner layer 1 – Switch Node, 12 V, Analogue Ground and Power Ground Planes.....	29
Fig. 29. Driver board - inner layer 2 – Switch Node, Analogue Ground and Power Ground Planes.....	30
Fig. 30. Driver board - bottom layer.....	31

## Contents

---

<b>1. Introduction.....</b>	<b>2</b>
<b>2. Half-bridge current sharing topology.....</b>	<b>2</b>
<b>3. Gate drive design considerations.....</b>	<b>3</b>
3.1. Gate driver IC considerations.....	3
3.2. Gate Ferrite beads and resistors.....	4
<b>4. DC bus snubbers and decoupling.....</b>	<b>4</b>
4.1. Switching node snubber.....	5
4.2. Thermal considerations.....	5
<b>5. Layout optimisation for current Sharing.....</b>	<b>5</b>
<b>6. Captured waveforms from single-shot staircase test</b>	<b>7</b>
<b>7. System performance running in BUCK mode.....</b>	<b>10</b>
7.1. Efficiency sweep and device temperatures.....	14
<b>8. System performance running in BOOST mode.....</b>	<b>15</b>
8.1. Efficiency sweep and device temperatures.....	19
<b>9. Probing considerations.....</b>	<b>19</b>
<b>10. Design Details.....</b>	<b>19</b>
10.1. Power board schematic.....	20
10.2. Power board PCB layout, planes and tracking.....	21
10.3. Power board Bill of Materials.....	25
10.4. Driver board schematics.....	27
10.5. Driver board PCB layout, planes and tracking.....	28
10.6. Driver board Bill of Materials.....	32
<b>11. Summary.....</b>	<b>33</b>
<b>12. References.....</b>	<b>33</b>
<b>13. Revision history.....</b>	<b>33</b>
<b>14. Legal information.....</b>	<b>34</b>

---

© Nexperia B.V. 2021. All rights reserved

For more information, please visit: <http://www.nexperia.com>

For sales office addresses, please send an email to: [salesaddresses@nexperia.com](mailto:salesaddresses@nexperia.com)

Date of release: 19 October 2021

---