

Driver Circuit Design Considerations for ADS855x

Dale Li
High Performance Analog/Field Application

ABSTRACT

ADS8556, ADS8555 is a 6 channel, 16bit, simultaneous sampling, successive approximation register (SAR) analog-to-digital converter with true bipolar input, supports up to 630 Ksps sampling rate per channel. ADS855x's structure is suitable for power line measurement and protection systems of industrial application. This application report presents the solution with system performance improvement test to resolve the challenges of designing the driver circuit for ADS855x.

Contents

1	Introduction	2
2	Design Challenge for driver circuit without amplifier	2
2.1	Driver circuit without amplifier	3
2.2	Design Challenges	3
2.2.1	Sampling rate and Acquisition time	3
2.2.2	Challenges	4
3	Choose the right RC filter Components	5
4	Performance Test	5
4.1	Test System	5
4.2	Performance Comparison Test	6
5	Conclusion	8
6	References	8
	Appendix A. FFT for test data	9

Figures

Figure 1.	Typical Driver Circuit for SAR ADC	2
Figure 2.	ADS8556's Driver Circuit Without Front-end Amplifier	3
Figure 3.	ADS8556's Acquisition time and Conversion time	4
Figure 4.	Performance test system for ADS8556 circuit	6
Figure A-1.	FFT for $R_{FLT} = 10k\Omega$, $C_{FLT} = 680pF$ ($V_S = -1dBFS$)	9
Figure A-2.	FFT for $R_{FLT} = 10k\Omega$, $C_{FLT} = 1nF$ ($V_S = -1dBFS$)	9
Figure A-3.	FFT for $R_{FLT} = 10k\Omega$, $C_{FLT} = 22nF$ ($V_S = -1dBFS$)	10

Tables

Table 1.	Test Result for $R_{FLT} = 10k\Omega$, $C_{FLT} = 22nF$ (unit: dBc)	6
Table 2.	Test Result for $R_{FLT} = 10k\Omega$, $C_{FLT} = 1nF$ (unit: dBc)	7
Table 3.	Test Result for $R_{FLT} = 10k\Omega$, $C_{FLT} = 680pF$ (unit: dBc)	7

1 Introduction

In power line measurement and protection systems, it is common to sample large numbers of voltage and current channels of multiphase power line networks, but it is critical to have the simultaneous sampling capability to maintain the phase information between the voltage and current channels in high voltage and high accurate systems. ADS8556/8555 is 6-channel, 16bit simultaneous sampling SAR ADC with true bipolar input up to $\pm 12V$, these features make it ideal for this kind of system application.

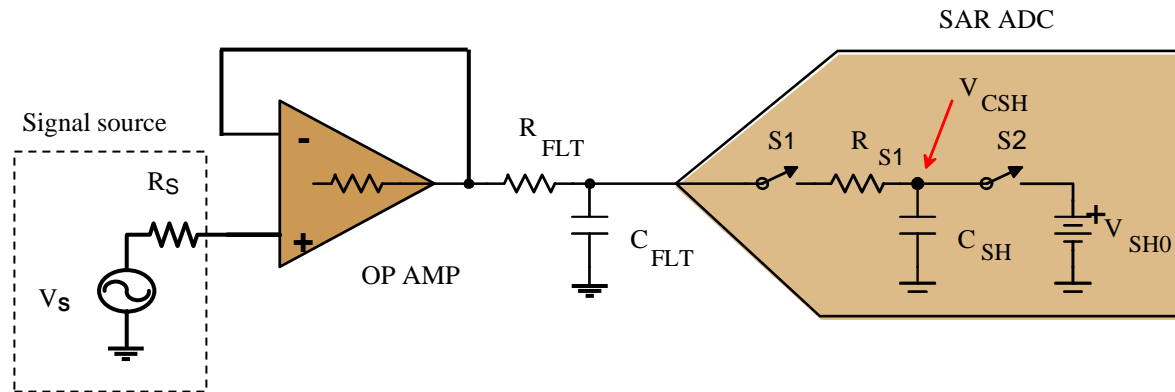


Figure 1. Typical Driver Circuit for SAR ADC

SAR ADC's driving circuit generally includes a front-end amplifier in combination with a low-pass RC filter (Figure 1), this driver circuit's major functions include: (a) signal conditioning for input signal from the source; (b) as a filter, including an RC lowpass filter and active filter with amplifier; (c) isolation between signal source and ADC, typical SAR ADC with switched-capacitor network is a dynamic load; (d) provide enough charges to ADC's internal sampling capacitor during ADC's acquisition time. Right selections of components of the drive circuit can make it possible to get optimal system performance, including the value selections of R_{FLT} and C_{FLT} .

2 Design Challenge for driver circuit without amplifier

To simplify circuit design and save cost, it is popular to design the driver circuit of SAR ADC without any amplifier by engineers in power line measurement and protection systems, only use a passive RC filter. But, if the correct values of R_{FLT} and C_{FLT} are not selected, the system performance suffers in the area of DC and AC performance, THD (total harmonic distortion), and so on.

2.1 Driver circuit without amplifier

The circuit in Figure 2 is a typical circuit without amplifier used widely in power line protection systems. The second order RC filters or much bigger value R_{FLT} and C_{FLT} are often used in this kind of application, thus providing bad system performance. The input signal resource (V_s) is usually $\pm 10V$ or $\pm 5V$ bipolar, 50Hz sine wave signal. To filter the noise and get optimal filter result, a larger value resistor (R_{FLT}) and capacitor (C_{FLT}) are used. This also provides a lower cutoff frequency of filter. The reason for using this big resistor is the demand of isolation between the SAR ADC and signal resource because there is no front-end amplifier. In general, 48 sample point per cycle is often used, so the sampling rate of the ADC is 2.4ksps for 50Hz sine wave.

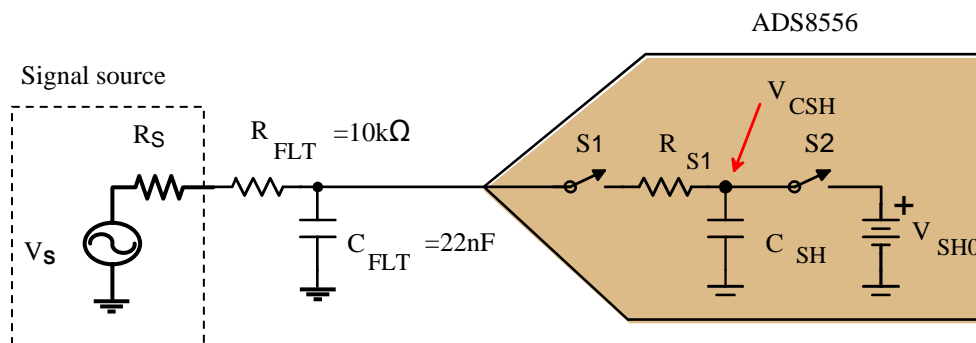


Figure 2. ADS8556's Driver Circuit Without Front-end Amplifier

After tests, the system performances are bad for this circuit configuration, especially THD, SINAD (Signal-to-noise and distortion ratio) and SFDR (Spurious Free Dynamic Range) performances (Table 1). If the sampling rate is increased, the performances for the same circuit decrease.

2.2 Design Challenges

SAR ADC's sampling rate and acquisition time are important parameters in the design challenges.

2.2.1 Sampling rate and Acquisition time

SAR ADC's sampling rate is usually correlative to ADC's Acquisition time (t_{ACQ}) and Conversion time (t_{CONV}).

$$T = \frac{1}{f_s} = t_{ACQ} + t_{CONV}$$

f_s is the sampling rate.

For ADS8556,

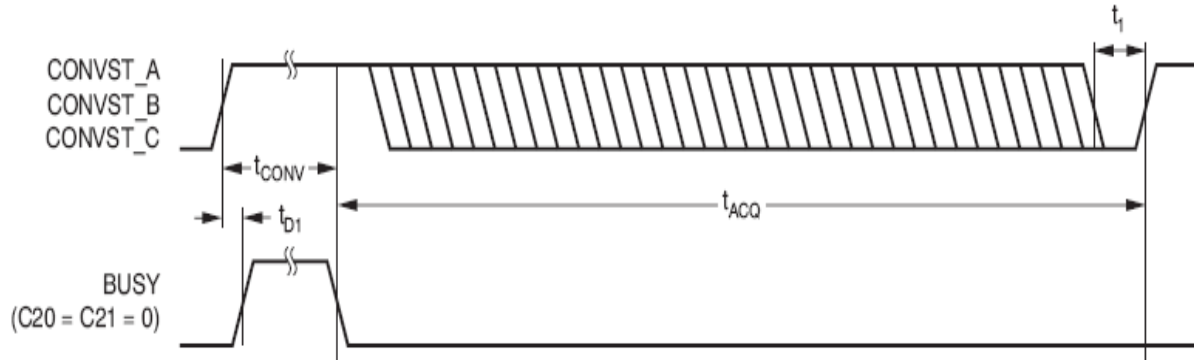


Figure 3. ADS8556's Acquisition time and Conversion time

The conversion time (1.26 μ s) in ADS8556's data sheet is the maximum time ADS8556 needs for one conversion. The acquisition time (280ns) in ADS8556's data sheet is minimum time to specify the excellent performance at the highest sampling rate. The real acquisition time to ADC depends on the real sampling rate because the conversion time is approximately fixed and ADC will enter into the acquisition status automatically after the conversion is finished.

2.2.2 Challenges

For the application in Figure 2, the sampling rate (f_s) is 2.4ksp/s, the conversion time (t_{CONV}) of ADS8556 is 1.26 μ s:

$$t_{ACQ} = \frac{1}{f_s} - t_{CONV} = 415.4\mu s$$

Because $t_{ACQ} \geq k \times \tau$

Where t_{ACQ} is ADC's acquisition time (Reference 3)

k is time-constant multiplier, 11.78 for 16 bit ADC

τ is time-constant

Calculate the required time constant of ADC:

$$\tau \leq \frac{t_{ACQ}}{k} = \frac{415.4\mu s}{11.78} = 35.26\mu s$$

If $R_s = 0\Omega$, the front-end RC filter's time constant:

$$\tau_{FLT} = (R_s + R_{FLT}) \times C_{FLT} = 10k\Omega \times 22nF = 220\mu s$$

This cannot meet the requirement charging the ADC's internal sampling capacitor to the proper value and maintaining stability during ADC's acquisition time.

Considering the ADC acquisition time first, the cutoff frequency of the RC filter is ($R_S = 0\Omega$):

$$f_{-3dB} = \frac{1}{2\pi R_{FLT} C_{FLT}} = \frac{1}{2\pi \tau_{FLT}} = \frac{1}{2\pi \frac{t_{ACQ}}{k}} = \frac{1}{2\pi \times 35.26\mu s} = 4.514\text{kHz}$$

Because no amplifier is used as an active filter in Figure 2, the RC filter acts as all filter functions. The input signal from power lines is only 50Hz frequency signal, so to get a better filter effect, the low cutoff frequency RC filter is often selected by engineers. That is why the larger resistor and capacitor values are used. The cutoff frequency of designed RC filter in Figure 2 is:

$$f_{-3dB} = \frac{1}{2\pi(R_S + R_{FLT})C_{FLT}} = \frac{1}{2\pi \times 10k \times 22nF} = 723.4\text{Hz}$$

So for the circuit design of the SAR ADC's driver without an amplifier, it is critical to consider the tradeoff between the RC filter time constant and the cutoff frequency.

3 Choose the right RC filter Components

The proper value for C_{FLT} of front-end RC filter can be determined by following equation:

$$20 \times C_{SH} \leq C_{FLT} \leq 60 \times C_{SH}$$

Where C_{SH} is SAR ADC's internal sampling capacitor (Reference 3)

It is ideal for C_{FLT} to use a Silver mica or a C0G type capacitor.

The proper value for R_{FLT} of front-end RC filter can be determined by following equation:

$$R_{FLT} \approx \frac{t_{ACQ}}{k \times C_{FLT}}$$

Where t_{ACQ} is the ADC acquisition time and k is time-constant multiplier (Reference 3)

4 Performance Test

4.1 Test System

Figure 3 is the typical test system for AC performance in this report. The software for this report was developed with *Code Composer Studio*™ V3.3 based on TI's TMS320F28335 Digital Signal Processor (DSP™) in ADS855x test board. The FFT wave forms are created in ADCPro software, which is available for download from the Texas Instruments website www.ti.com.

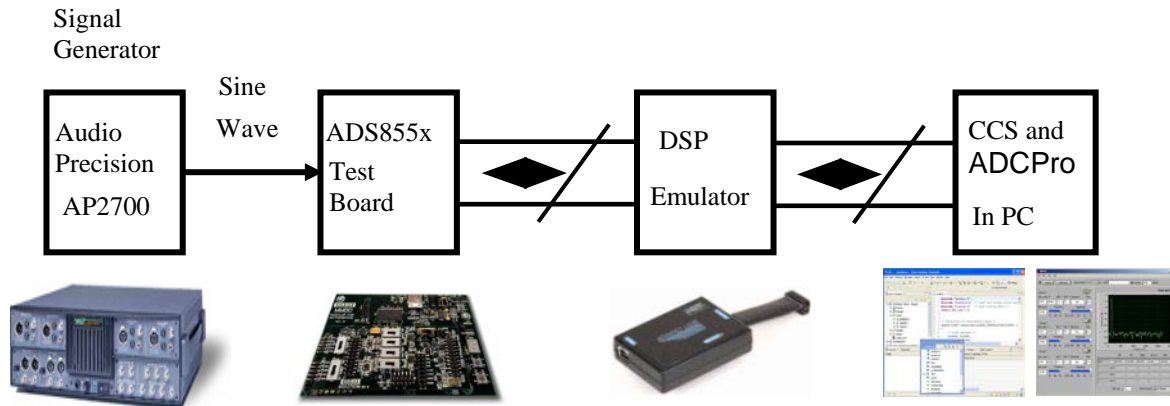


Figure 4. Performance test system for ADS8556 circuit

4.2 Performance Comparison Test

Table 1 is the system AC performance results based on original design in Figure 2 ($R_{FLT} = 10k\Omega$, $C_{FLT} = 22nF$) and different input signal amplitudes of V_S , which is bipolar and 50Hz signal from AP2700 generator. The ADS8556 sampling rate is 2.4ksps for these tests. From the test data, the system THD, SINAD, SFDR performances are poor.

Table 1. Test Result for $R_{FLT} = 10k\Omega$, $C_{FLT} = 22nF$ (unit: dBc)

V_S ($V_{P-P}/dBFS$)	SNR	THD	SINAD	Tone	Signal power	SFDR
50mV/-46	45.94	-46.06	42.99	50.00Hz	-45.85	48.4
100mV/-40	51.71	-52.35	49.01	50.00Hz	-39.94	55.4
316mV/-30	61.83	-61.11	58.44	50.00Hz	-30.01	64.9
500mV/-26	65.96	-65.66	62.80	50.00Hz	-26.03	69.7
1V/-20	72.00	-68.03	66.57	50.00Hz	-20.02	70.0
3.16V/-10	82.22	-63.10	63.04	50.00Hz	-10.03	63.5
5V/-6	85.65	-62.10	62.08	50.00Hz	-6.05	62.5
8.91V/-1	89.71	-58.57	58.57	50.00Hz	-1.04	58.8
9.44V/-0.5	90.25	-58.18	58.18	50.00Hz	-0.54	58.4

If according to the guidelines in item No. 3, reduce the value for C_{FLT} to 1nF (the ADS8556 input capacitor is 20pF for ± 5 input range), Table 2 provides new test results:

Table 2. Test Result for $R_{FLT} = 10k\Omega$, $C_{FLT} = 1nF$ (unit: dBc)

V_S (V_{P-P} /dBFS)	SNR	THD	SINAD	Tone	Signal power	SFDR
50mV/-46	45.69	-59.64	45.52	50.00Hz	-45.91	68.7
100mV/-40	51.69	-64.46	51.46	50.00Hz	-39.93	73.4
316mV/-30	61.73	-72.60	61.39	50.00Hz	-29.99	78.0
500mV/-26	65.42	-76.71	65.11	50.00Hz	-26.01	83.9
1V/-20	71.59	-83.71	71.33	50.00Hz	-20.00	90.5
3.16V/-10	82.21	-92.62	80.91	50.00Hz	-10.00	96.1
5V/-6	84.92	-95.03	84.52	50.00Hz	-6.02	97.3
8.91V/-1	89.30	-94.25	88.09	50.00Hz	-1.00	98.9
9.44V/-0.5	90.01	-93.42	88.38	50.00Hz	-0.50	94.4

Table 2 shows that the system performance is significantly improved. The THD improvement with -1dBFS input is about 35dB, SFDR improvement is about 40dB.

Continue reducing the value for C_{FLT} to 680pF according to the guidelines (the ADS8556 input capacitor is 20pF for ± 5 input range):

Table 3. Test Result for $R_{FLT} = 10k\Omega$, $C_{FLT} = 680pF$ (unit: dBc)

V_S (V_{P-P} /dBFS)	SNR	THD	SINAD	Tone	Signal power	SFDR
50mV/-46	45.20	-62.45	45.12	50.00Hz	-45.91	72.0
100mV/-40	51.35	-68.71	51.27	50.00Hz	-39.94	76.5
316mV/-30	61.33	-74.35	61.12	50.00Hz	-29.99	80.1
500mV/-26	65.18	-76.82	64.89	50.00Hz	-26.01	84.1
1V/-20	71.17	-83.88	70.94	50.00Hz	-20.00	92.7
3.16V/-10	81.08	-93.43	80.83	50.00Hz	-9.99	100.8
5V/-6	84.87	-96.85	84.60	50.00Hz	-6.02	103.5
8.91V/-1	89.24	-101.16	88.97	50.00Hz	-1.00	107.8
9.44V/-0.5	89.27	-100.81	88.97	50.00Hz	-0.50	107.7

The THD and SFDR performances are much better than before. THD improvement with -1dBFS input is about 42dB, SFDR is about 49dB, so 680pF C_{FLT} is a perfect choice for better system performance.

5 Conclusion

This application report presents a popular driver circuit without amplifier to SAR ADC in industrial application, discusses the challenges which may meet between the performance demand and RC filter design. Based on the input signal, the ADC sampling rate and the input capacitor, the system performance demand and the filter demand, it is important to balance the values of R_{FLT} and C_{FLT} . This application report is also suitable for ADS8557 and ADS8558 TI's SAR ADCs.

6 References

1. ADS8556 data sheet (SBAS404B)
2. ADS8555 data sheet (SBAS531B)
3. Oljaca, M. and B. Baker. (2008). Start with the right op amp when driving SAR ADCs. EDN. October 16, 2008. Pp. 43-58.
Download at: www.edn.com/article/CA6602451

Appendix A. FFT for test data

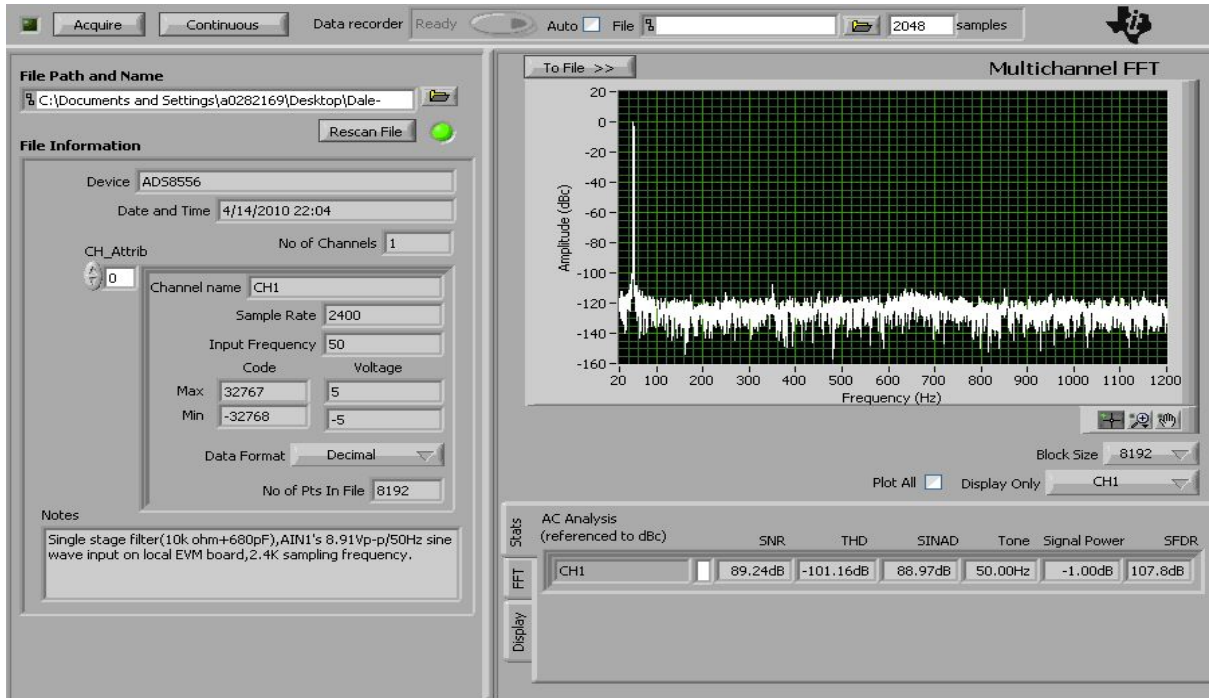


Figure A-1. FFT for $R_{FLT} = 10k\Omega$, $C_{FLT} = 680pF$ ($V_s = -1dBFS$)

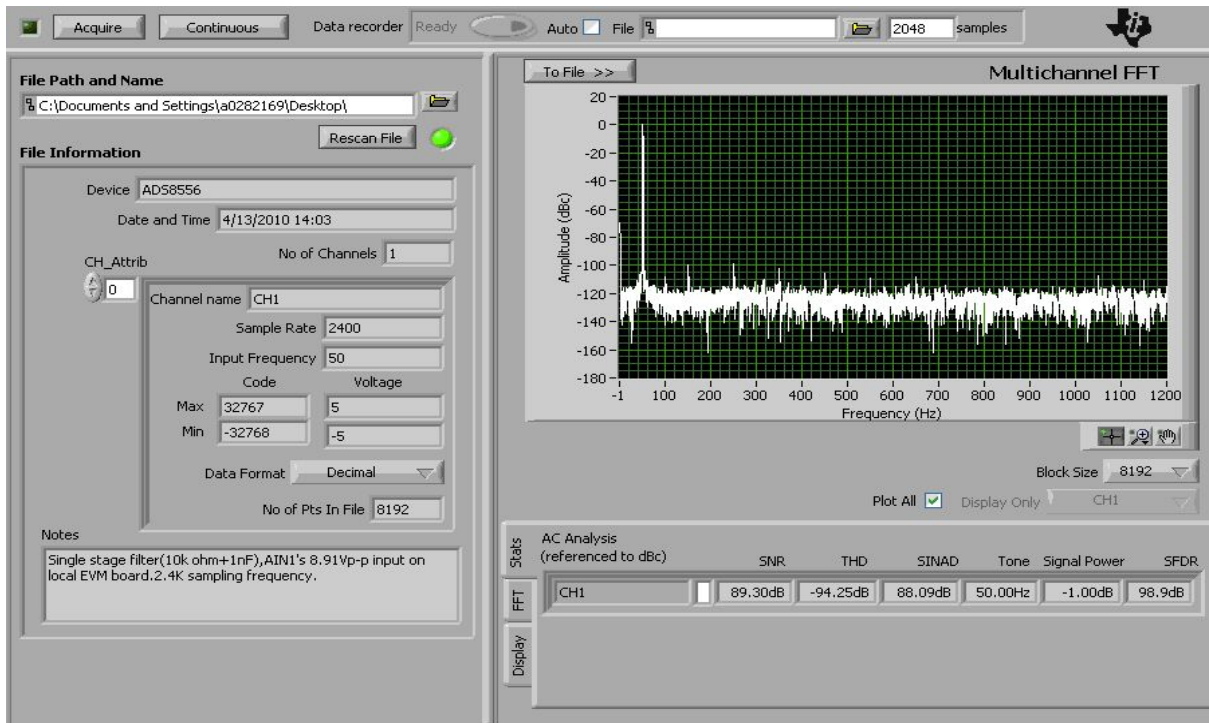


Figure A-2. FFT for $R_{FLT} = 10k\Omega$, $C_{FLT} = 1nF$ ($V_s = -1dBFS$)

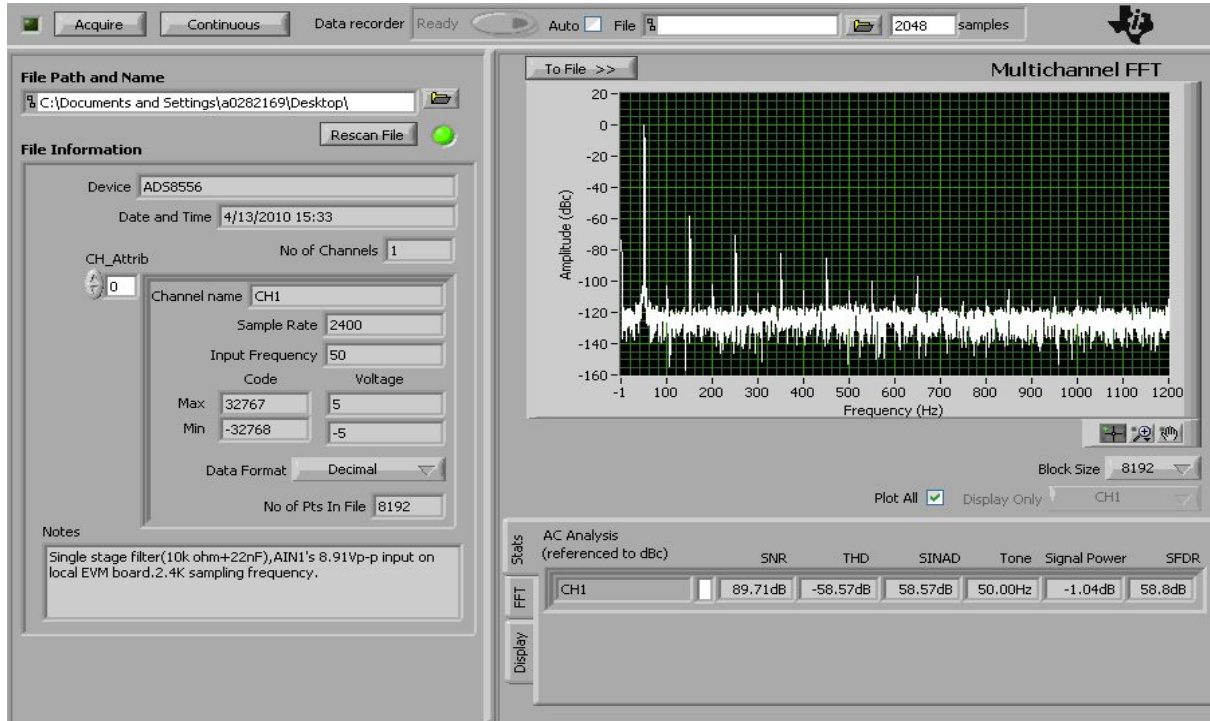


Figure A-3. FFT for $R_{FLT} = 10k\Omega$, $C_{FLT} = 22nF$ ($V_S = -1dBFS$)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46C and to discontinue any product or service per JESD48B. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community e2e.ti.com