
Comparing the bq29312A to the bq29312

Garry Elder

PMP Portable Power

ABSTRACT

The bq29312A analog front end (AFE) IC contains a minor change to the existing bq29312 AFE that improves overall system-level ESD performance. The specifications of the bq29312 and bq29312A are identical.

System-Level ESD Improvement

Internal Regulator Change

The bq29312 contains an internal regulator that provides a controlled power supply to the rest of the device. This power supply is used to hold the RAM data valid, to power the state machine, and to provide voltage reference. A power-on-reset (POR) circuit controls the power supply. If this supply is disturbed, it could cause the bq29312 to reset.

Internal Reset Circuit Power Supply

The bq29312 has an internal reset circuit that drives the I²C circuit (see Figure 1). One of the bq29312A integrated circuit (IC) design goals was to reduce the overall current consumption of the IC. The bq29312A reset circuit power supply current was reduced compared to the bq29312 although the circuit remained the same.

Analysis of the bq29312 indicated that the extra low current change caused an increase in board-level ESD susceptibility. As a result, the reset circuit's power supply current of the bq29312A was increased, although this change did not change the data sheet specification of supply current.

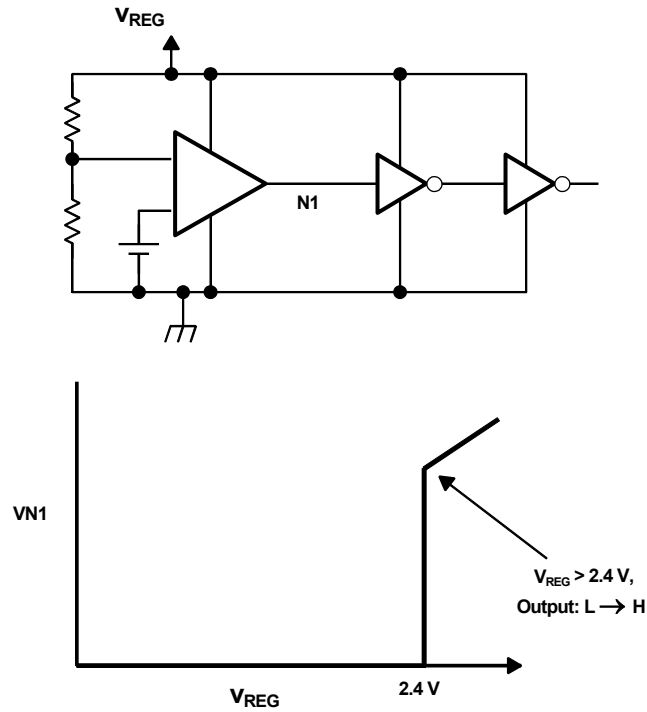


Figure 1. I²C Reset Circuitry and Voltage Thresholds

Reset to I²C Line Change

During an ESD event, it was observed that the connection of the reset output and I²C block was being affected. As a result, the signal line was separated from the reset circuit to the internal I²C circuit and a filter was added in front of I²C block to absorb any noise (see Figure 2).

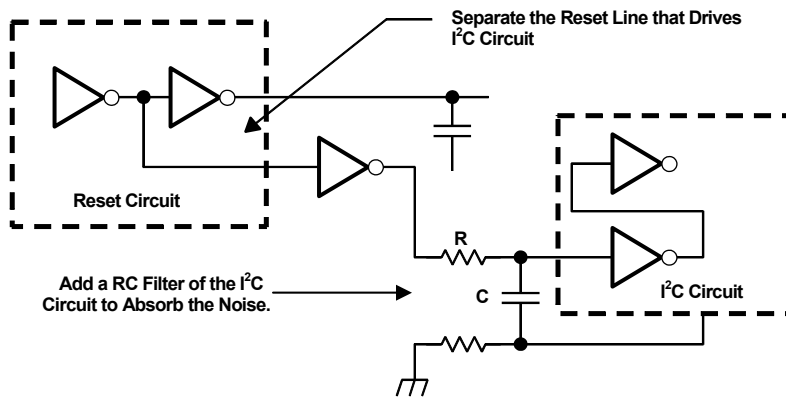


Figure 2. Internal Reset Circuit

Layout Recommendations

Texas Instruments recommends connecting the capacitor on REG (pin 22) to the bq29312A as closely as possible as this affects the stability of the regulator output, which is in turn connected to the internal regulator circuit. TI also recommends that the BAT input does not have traces where pulsed current or high-frequency signals could be present (including transients) placed close to it, although this is a more general PCB layout principle in analog designs.

The change made in the bq29312A routes the ground connection of this internal regulator to a node less sensitive to transients, thus providing a more stable power supply under extreme transient conditions. In addition to this improvement, Figure 3 illustrates another layout recommendation.

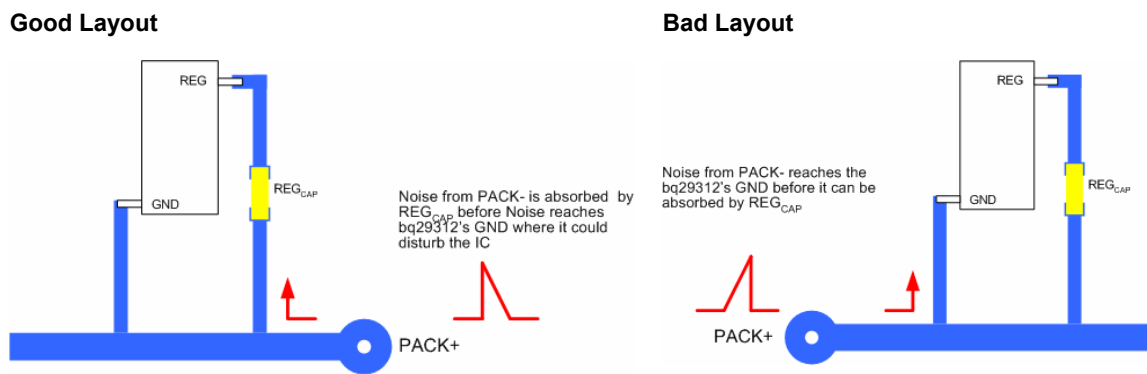


Figure 3. Layout Example

Summary

Both the bq29312 and bq29312A AFE ICs provide an excellent solution for good ESD levels, but the bq29312A is less sensitive to the PCB layout items previously noted.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265