

AN-1071 Information About the LM2650 Evaluation Board Rev. 1

1 Introduction

This application report contains information about the printed circuit board (PCB).

2 General Description


The LM2650 evaluation board is provided as a tool for developing DC/DC converters based on the LM2650 IC. It is configured for single-output, step-down DC/DC converters. [Figure 1](#) is a complete schematic of the board that can accommodate up to 28 components including the LM2650. [Table 1](#) is a complete list of pads for placing components.

Note: Not all applications will require the placement of all 28 components. The number of components placed depends on the requirements of the application and the use of features like programmable soft-start. The LM2650 evaluation board is intended to be a reusable tool on which many different converters meeting the requirements of many different applications can be built. It is not intended to demonstrate only one application of the LM2650.

For convenience, a sample of the LM2650 and eight other components have been assembled: a 0.1 μF capacitor at each of C1, C2, C6, and CB, a 0.2 μF capacitor at CV_{DD} , a 0.01 μF capacitor at CSS, a 24.9 k Ω resistor at R2, and a 0 Ω resistor at R4. Of the eight, the first seven are common to many applications, and the last is simply a jumper grounding the SYNC input. When the synchronization feature is not being used, the SYNC input should be grounded.

3 Example Circuits

The components contained in [Table 2](#), [Table 3](#), and [Table 4](#) can be used to build typical application circuits. As with the design of any DC/DC converter, the design of these involved tradeoffs between efficiency, size, and cost. The converters detailed in [Table 2](#) were designed with efficiency as the number one criteria. Those detailed in [Table 4](#) trade slightly higher switching losses for a much smaller inductor.

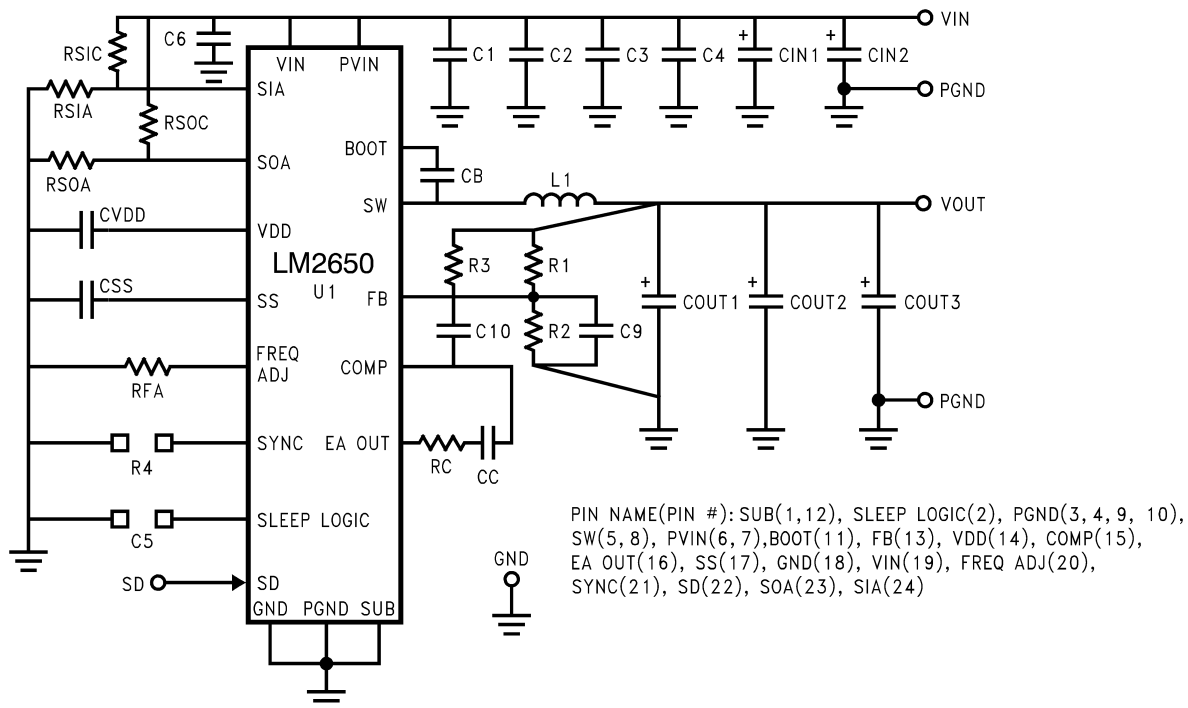
Figure 1. The LM2650 Evaluation Board Rev. 1 Schematic

4 Thermal Performance

The 24-lead SO package is a molded plastic package with a solid copper lead frame. Most of the heat generated at the die flows through the lead frame into the 3-ounce copper planes on the board. The board then acts as a heat sink. The junction-to-ambient thermal resistance of the packaged IC mounted on the board has been measured to be 38°C/W, 37 °C/W, and 35 °C/W for the dissipation of 1.0W, 1.5W, and 2.0W respectively. These measurements were made in still air. The junction-to-ambient thermal resistance of the packaged IC alone in still air is 78°C/W. The board is 0.063" thick FR-4 material.

5 Art

Figure 2 through Figure 4 show the PCB art work.

Table 1. A Complete List of Pads for Placing Components

Label	No	Notes
U1	1	For placing the LM2650.
C1, C2, C3, and C4	4	Capacitors placed here filter high-frequency switching noise from the input power rail.
C5	0	These pads should not be labeled with a C. No component is placed here. They can be used to ground the SLEEP LOGIC input. The pad connected to the SLEEP LOGIC pin can be used to pull the input up.
C6	1	A capacitor placed here also filters high-frequency switching noise from the input power rail but at the VIN rail, the rail used by the signal-level circuits inside the IC.
C9	1	Usually no component is placed here. A capacitor might be placed here for loop compensation purposes, but most applications don't use it.
C10	1	A capacitor is placed here for loop compensation purposes.
CB	1	The bootstrap capacitor is placed here.
CC	1	A capacitor is placed here for loop compensation purposes. This capacitor and an internal 6.5 kΩ resistor create an integrator pole.
CIN1 and CIN2	2	The bulk input capacitors are placed here.

Table 1. A Complete List of Pads for Placing Components (continued)

Label	No	Notes
COUT1, COUT2, and COUT3	3	The output filter capacitors are placed here.
C _{SS}	1	A capacitor placed here programs the soft-start interval.
CV _{DD}	1	A capacitor placed here bypasses the output of the V _{DD} regulator.
L1	1	The inductor is placed here.
R1	1	One of the feedback resistors is placed here.
R2	1	The other feedback resistor is placed here.
R3	1	A resistor is placed here for loop compensation purposes.
R4	1	These pads can be used to ground the SYNC input when the synchronization feature is not being used. The pad connected to the SYNC input can be used to connect the synchronization signal. The evaluation board has a 0 Ω jumper placed here to ground the SYNC input.
RC	1	A resistor is also placed here for loop compensation purposes. This resistor and the capacitor placed at CC create an integrator zero.
RFA	1	A resistor placed here adjusts the switching frequency up from the nominal 90 kHz. No component is placed here for applications switching at 90 kHz.
RSIA and RSIC	2	Resistors placed here program the sleep-in threshold.
RSOA and RSOC	2	Resistors placed here program the sleep-out threshold.

Table 2. Components for Two Typical 90 kHz Application Circuits

Input Voltage	7 to 18 V IN	
Applicable Cell Stacks	8- to 12-Cell NiCd or NiMH, 3- to 4-Cell Li Ion, 8- to 11-Cell Alkaline, 6-Cell Lead Acid	
Output	5 V, 3A Out	3.3 V, 3A Out
Input Filter Capacitors C1, C2, and C6	0.1 μF ceramic chip capacitor	0.1 μF ceramic chip capacitor
Bootstrap Capacitor CB	0.1 μF ceramic chip capacitor	0.1 μF ceramic chip capacitor
Soft-start Capacitor CSS	0.01 μF ceramic chip capacitor	0.01 μF ceramic chip capacitor
V _{DD} Bypass Capacitor CV _{DD}	0.2 μF ceramic chip capacitor	0.2 μF ceramic chip capacitor
Input Bulk Capacitors CIN1 and CIN2	22 μF, 35 V AVX TPS Series or Sprague 593D Series tantalum chip capacitor	22 μF, 35 V AVX TPS Series or Sprague 593D Series tantalum chip capacitor
Inductor L1	40 μH (see Table 3)	33 μH (see Table 3)
Output Capacitors COUT1, COUT2, and COUT3	220 μF, 10 V AVX TPS Series or Sprague 593D Series tantalum chip capacitor	220 μF, 10 V AVX TPS Series or Sprague 593D Series tantalum chip capacitor
Feedback Resistors R1 and R2	R1 = 75 kΩ, 1%, R2 = 24.9 kΩ, 1%	R1 = 41.2 kΩ, 1%, R2 = 24.9 kΩ, 1%
Compensation Components RC, CC, R3, and C10	RC = 37.4 kΩ, CC = 4.7 nF, R3 = 3.57 kΩ, C10 = 5.6 nF	RC = 23.2 kΩ, CC = 8.2 nF, R3 = 2.0 kΩ, C10 = 10 nF
Sleep Resistors RSIA and RSOA	RSIA = 33 kΩ, RSOA = 200 kΩ	RSIA = 39 kΩ, RSOA = 130 kΩ

Table 3. Toroidal Inductors Using Cores From MICROMETALS, INC.

	Core No	Core Material	Wire Gauge	No of Strands	No of Turns
15 μH	T38	-52	AWG #23	1	21
20 μH	T38	-52	AWG #23	1	25
33 μH	T50	-52	AWG #21	1	41
40 μH	T50(B)	-18	AWG #21	1	41

Table 4. Components for Two Typical 200 kHz Application Circuits

Input Voltage	7 to 18 V IN	
Applicable Cell Stacks	8- to 12-Cell NiCd or NiMH, 3- to 4-Cell Li Ion, 8- to 11-Cell Alkaline, 6-Cell Lead Acid	
Output	5 V, 3A Out	3.3 V, 3A Out
Input Filter Capacitors C1, C2, and C6	0.1 μ F ceramic chip capacitor	0.1 μ F ceramic chip capacitor
Bootstrap Capacitor CB	0.1 μ F ceramic chip capacitor	0.1 μ F ceramic chip capacitor
Soft-start Capacitor CSS	0.01 μ F ceramic chip capacitor	0.01 μ F ceramic chip capacitor
V _{DD} Bypass Capacitor CV _{DD}	0.2 μ F ceramic chip capacitor	0.2 μ F ceramic chip capacitor
Input Bulk Capacitors CIN1 and CIN2	22 μ F, 35 V AVX TPS Series or Sprague 593D Series tantalum chip capacitor	22 μ F, 35 V AVX TPS Series or Sprague 593D Series tantalum chip capacitor
Inductor L1	20 μ H (see Table 3)	15 μ H (see Table 3)
Output Capacitors COUT1, COUT2, and COUT3	220 μ F, 10 V AVX TPS Series or Sprague 593D Series tantalum chip capacitor	220 μ F, 10 V AVX TPS Series or Sprague 593D Series tantalum chip capacitor
Feedback Resistors R1 and R2	R1 = 75 k Ω , 1%, R2 = 24.9 k Ω , 1%	R1 = 41.2 k Ω , 1%, R2 = 24.9 k Ω , 1%
Compensation Components RC, CC, R3, and C10	RC = 53.6 k Ω , CC = 2.7 nF, R3= 4.02 k Ω , C10 = 4.7 nF	RC = 33.2 k Ω , CC= 3.9 nF, R3 = 3.01 k Ω , C10 = 6.8 nF
Sleep Resistors RSIA and RSOA	RSIA = 47 k Ω , RSOA = 200 k Ω	RSIA = 47 k Ω , RSOA = 91 k Ω
Frequency Adjusting Resistor RFA	RFA = 24.9 k Ω	RFA = 24.9 k Ω

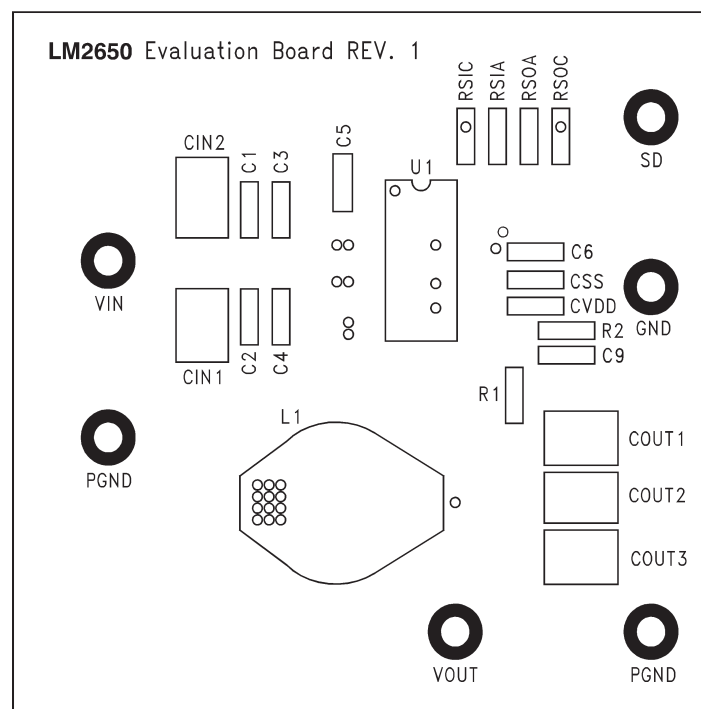


Figure 2. LM2650 Evaluation Board Top Silk Screen (Scale 1:1)

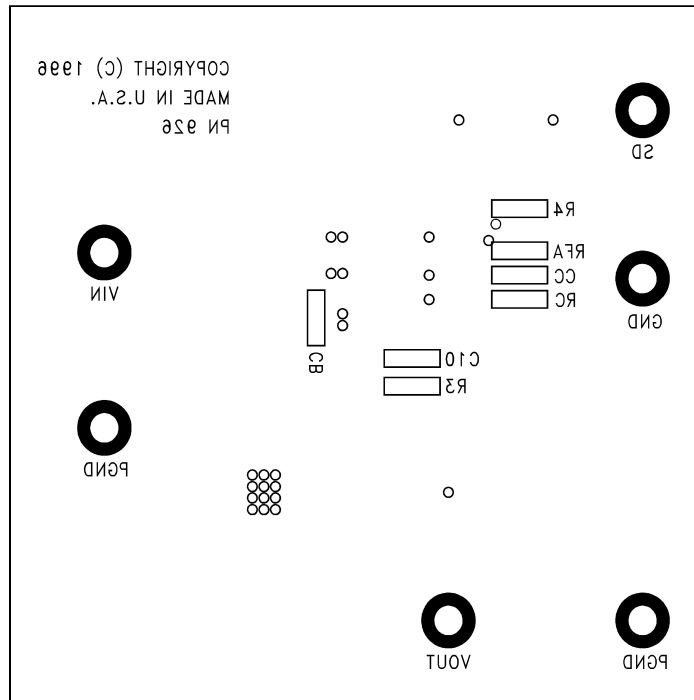


Figure 3. LM2650 Evaluation Board Bottom Silk Screen (Scale 1:1)

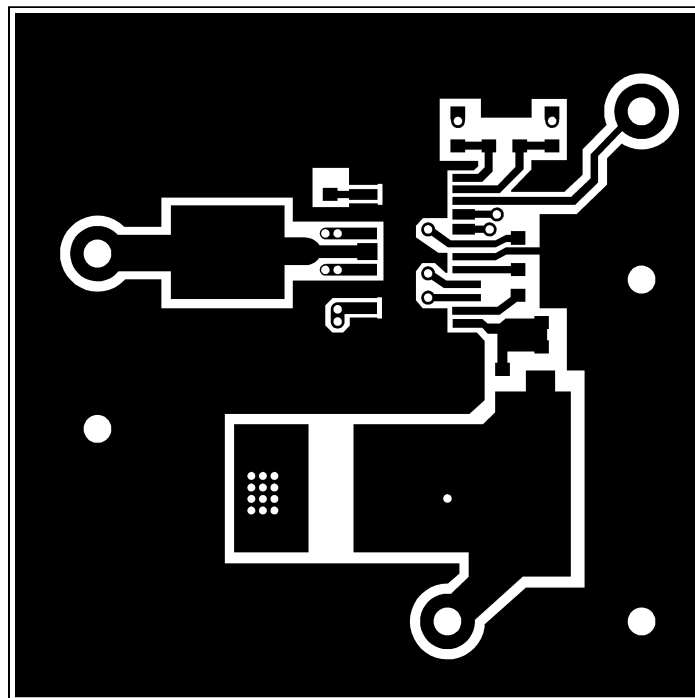


Figure 4. LM2650 Evaluation Board Component Side (Scale 1:1)

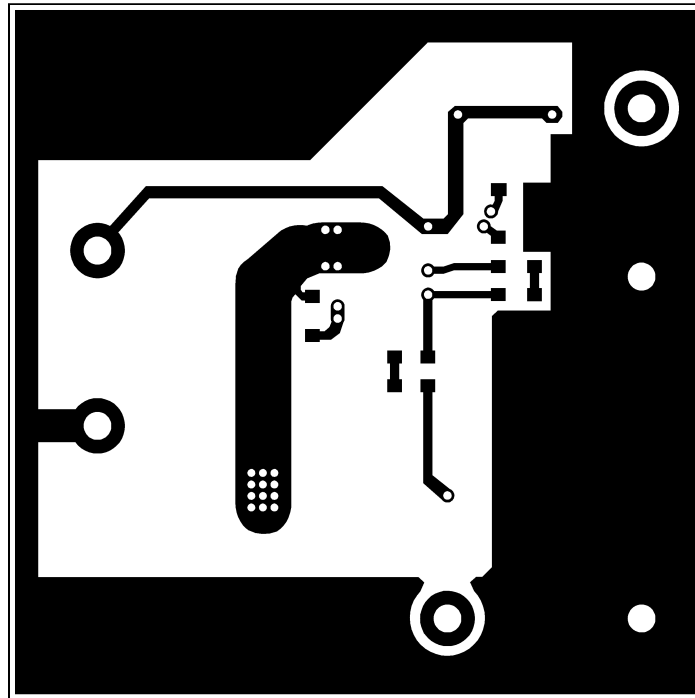


Figure 5. LM2650 Evaluation Board Solder Side (Scale 1:1)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com