

AN-1525 Single Supply Operation of the DAC0800 and DAC0802

ABSTRACT

This application report develops the positive-only bias voltages needed to successfully operate the ADC0800 and the DAC0802 with a single supply voltage. The principles here also apply to the DAC0808, which is a two quadrant multiplying DAC with a single output.

Contents

1	Executive Summary	2
2	Overview	2
3	General Biasing Requirements	2
4	Unipolar Supply Modification	3
	4.1 Reference Considerations	4
	4.2 Output Biasing	4
	4.3 Input Level Threshold	4
	4.4 Output Considerations	4
	4.5 Complete Circuit Example	5
5	Summary	6

List of Figures

1	General Circuit for the DAC0800	3
2	Positive Only Supply Circuit for the DAC0800	4
3	Simple Digital Input Level Shifting Circuit.....	4
4	Current-to-Voltage Converter With Offset Correction	5
5	Complete Single Supply DAC0800 Design With 0 V to 5 V Output.....	5

List of Tables

1	DAC0800 Voltages and Currents	2
---	-------------------------------------	---

1 Executive Summary

The ADC0800 and the ADC0802 are versatile four quadrant multiplying digital-to-analog converters (DACs) with a current reference and complementary current outputs. The data sheet indicates a need for bipolar (positive and negative) power supply voltages, but a consideration of relative potentials allows these DACs to be used with positive only supplies, to include a single positive supply.

The DAC0800 is functionally equivalent to the industry standard DAC-08 and the DAC0802 is equivalent to the industry standard DAC-08A. The DAC0808 is functionally equivalent to the industry standard MC1408.

Product Applicability:

DAC0800

DAC0802

DAC0808

2 Overview

The DAC0800, the DAC0802 and the DAC0808 seem to suffer from the apparent need for bipolar supplies. But, by setting the negative supply to ground and shifting all other voltages up by 5 V, these DACs will behave normally without a negative supply. The requirement is that all of the voltages associated with the DAC are correct relative to each other, and that the proper current levels are maintained.

This application report does not discuss the operation or specifications of the DACs to which this document applies. For information relating to the operation of the product in question, see the device-specific data sheet.

Reference to the DAC0800 herein also includes the DAC0802, which is just a more accurate version of the DAC0800. The principles apply equally well to the DAC0808, except that pin 2 of the DAC0808 is normally ground rather than an output.

3 General Biasing Requirements

As long as the relative voltages are correct, the DAC0800 will behave normally. With this in mind, the potentials around the DAC0800 can be modified as indicated in [Table 1](#).

The positive supply voltage, V+ at pin 13, must be at least 10 V and no more than 30 V more positive than V- at pin 3 for proper operation.

There will be no change to the capacitor connection to pin 16, but it should be noted that this capacitor should be connected directly to pin 3, then this connection should be connected to the negative supply voltage or grounded.

Pin 1, the Logic Control pin, controls the logic threshold of the digital inputs. The logic threshold of the digital input is about 1.35V above this pin 1 potential at room temperature and varies linearly between about 1.7 V at -55°C and about 0.95V at 125°C. The assumption throughout this application report is 5 V TTL logic levels.

Table 1. DAC0800 Voltages and Currents

Pin	Function	Normal V or I (or Range)	New V or I (or Range)
1	Logic Control	0V	+5V
2	\overline{I}_O	-10V to +18V	(V-) + 5V to +28V
3	V-	-15V to -5V	0V
4	I_O	-10V to +18V	(V-) +5 to +28

Table 1. DAC0800 Voltages and Currents (continued)

Pin	Function	Normal V or I (or Range)	New V or I (or Range)
5	B1 (MSB)	0V to 0.8V (logic low)	5.0V to 5.8V (logic low)
6	B2		
7	B3		
8	B4		
9	B5	2.4V to V+ (logic high)	7.4V to V+ (logic high)
10	B6		
11	B7		
12	B8 (LSB)		
13	V+	+5V to +15V	0V to +20V
14	REF+	200 μ A to 4 mA	200 μ A to 4 mA
15	REF-	0V thru R	+5V thru R
16	COMP	cap	cap

The general circuit for the DAC0800 is as shown in Figure 1.

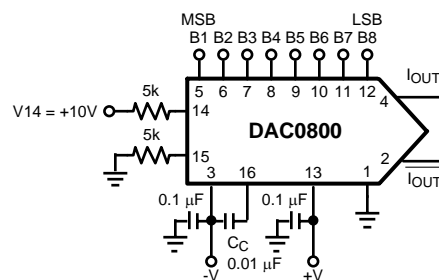


Figure 1. General Circuit for the DAC0800

The requirements for reference pins 14 and 15 are that they be at least 5 V above the negative supply pin 3, that the resistance in series with these two pins be of equal value and that the value of these two resistors be $(V14 - V15) / I_{REF}$, where V14 and V15 are the potentials to which the resistors at pins 14 and 15 are returned and I_{REF} is the reference current required and is equal to the value of the maximum output currents at pins 4 and 2. The total of these two output currents is always equal to

$$I_{OUT} + \overline{I_{OUT}} = (2^n - 1) I_{REF} / 2^n \tag{1}$$

For 8 bits this becomes:

$$I_{OUT} + \overline{I_{OUT}} = 255 I_{REF} / 256 \tag{2}$$

I_{OUT} increases with an increase in the digital code or the reference current and $\overline{I_{OUT}}$ decreases with an increase in the digital code or the reference current.

You see from Figure 1 that:

$$I_{REF} = (V14 - V15) / 5k \tag{3}$$

$$I_{REF} = (10V - 0V) / 5k = 2 \text{ mA} \tag{4}$$

4 Unipolar Supply Modification

Again, if you consider the relative circuit potentials and maintain proper current levels, you can make whatever circuit changes you need.

4.1 Reference Considerations

The modified circuit is as shown in Figure 2. Here you find that:

$$I_{REF} = (V_{14} - V_{15}) / 2.49k \quad (5)$$

$$I_{REF} = (10V - 5V) / 2.49k = 2.008 \text{ mA} \quad (6)$$

and you have about the same reference current as for the general case.

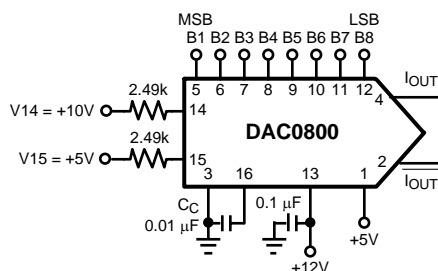


Figure 2. Positive Only Supply Circuit for the DAC0800

4.2 Output Biasing

Another requirement of the DAC0800 is that output pins 2 and 4 must always be at least 5 V more positive than the potential at pin 3. Since pin 3 is grounded, these output pins must never go below +5 V. The +28 V maximum output voltage indicated in Table 1 comes from the maximum voltage with respect to pin 3 that the output transistors can withstand without excessive leakage or breakdown.

4.3 Input Level Threshold

The logic inputs need to be level shifted up by 5 V. This can be done with two resistors at each logic input pin, as shown in Figure 3.

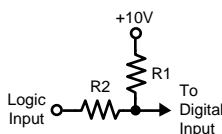


Figure 3. Simple Digital Input Level Shifting Circuit

For driving with 5 V TTL devices, R1 and R2 of Figure 3 are 2.65k and 3.3k, respectively. For driving with 3.3 V TTL devices, R1 and R2 are 3.48k and 4.75k, respectively. These resistance values would change for bias voltages other than the +10 V shown in Figure 3. If the bias voltage is +12 V, R1 and R2 of are 5.83k and 4.75k, respectively, for 5 V TTL devices and 5.62k and 4.75k, respectively, for driving with 3.3 V TTL devices.

Tolerance requirements of both the resistors and of the bias voltage is 1%, so it is best to use a reference source for the bias voltage.

4.4 Output Considerations

The DAC0800 has a current output. The data sheet indicates how to connect an amplifier to the outputs to derive a voltage output. Keep in mind that the DAC0800 outputs must never transition to a potential that is lower than 5 V above its pin 3 voltage.

This means that an op-amp at the output must have its non-inverting input returned to a voltage that is at least +5 V, leading to a minimum op-amp output of +5 V. In some cases this may be acceptable, but in most cases it is much more desirable to have a minimum output voltage of zero volts.

This minimum zero volts output can be obtained by adding a Zener diode in series with the output to subtract the bias potential from the output, but a Zener diode generally has a large tolerance and a large temperature coefficient. Using an LM4040-5.0 in place of a Zener will provide the same subtraction function, but with a lot better tolerance and lower temperature drift. An example circuit, where the DAC0800 output bias is 5 V, is shown in Figure 4.

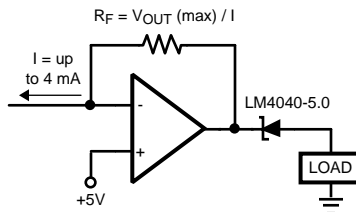


Figure 4. Current-to-Voltage Converter With Offset Correction

There are three things to note about the circuit of Figure 4. The supply voltage should be more positive than the maximum amplifier output, even if a rail-to-rail output amplifier is used. Otherwise there could be linearity problems at and near full scale.

Second, the maximum current through the LM4040-5.0 is 15 mA, which limits the load current to that value.

The third thing is that the LM4040-5.0 should have a minimum current of 100 μ A at all times if it is to reliably subtract 5 V from the amplifier output. When the amplifier output is 5 V, there is insufficient current through the LM4040-5.0, resulting in an inaccurate load voltage at low load currents. That is, the load voltage can not be reduced to zero at low load currents. The minimum voltage will be a function of the load impedance and the individual LM4040-5.0. For this reason, this circuit may not be practical for applications where the load current can be reduced to a value below 100 microamps.

4.5 Complete Circuit Example

Figure 5 gives a complete positive supply circuit solution to provide an output range of 0 V to 5 V. The op-amp is a rail-to-rail output type to minimize its output error at very low output voltages. The positive supply voltage for the op-amp should be greater than its maximum output voltage.

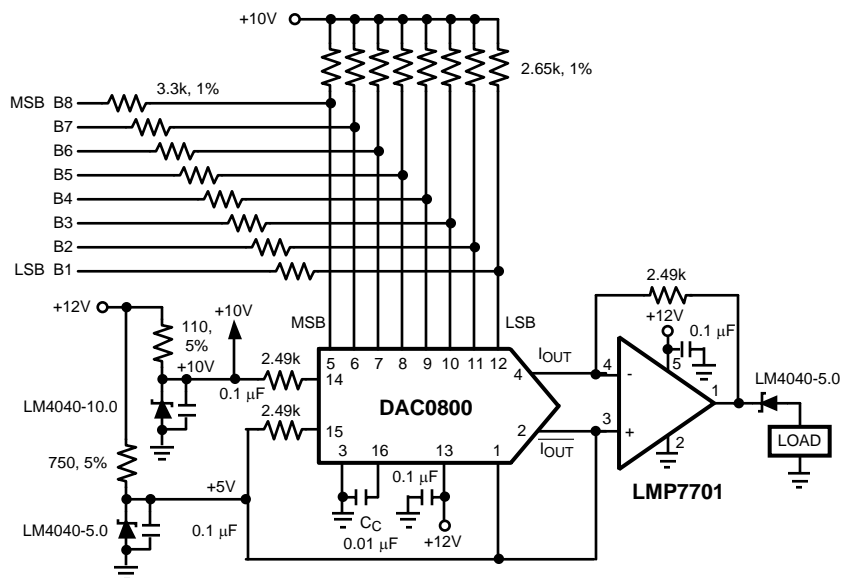


Figure 5. Complete Single Supply DAC0800 Design With 0 V to 5 V Output

5 Summary

The DAC0800 is a versatile DAC that has found many uses. The perceived drawback has been its need for a negative supply. However, because the important thing for any electrical component is the relative potentials and correct currents, it is possible to come up with a method to eliminate the need for a negative supply.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com