

# **AN-2213 LM5045 Based 240W Power Converter Using Full-Wave Rectification on the Secondary**

---

---

---

## **1 Introduction**

The LM5045 based 240W reference board is designed to evaluate the performance of the full-wave rectification scheme on the secondary side. The reference board is designed in an industry standard quarter brick footprint.


The performance of the evaluation board is as follows:

- Input operating range: 36V to 75V
- Output voltage: 12V
- Measured efficiency at 48V: 94.8% @ 20A with a peak of 95.2%
- Frequency of operation: 400 kHz
- Board size: 2.28 x 1.45 x 0.5 inches
- Load Regulation: 0.2%
- Line Regulation: 0.1%
- Line UVLO (34V/32V on/off)
- Hiccup Mode Current Limit

The printed circuit board consists of 6 layers; 2 ounce copper outer layers and 3 ounce copper inner layers on FR4 material with a total thickness of 0.062 inches. The unit is designed for continuous operation at rated load at <40°C and a minimum airflow of 200 CFM.

## **2 Theory of Operation**

Power converters based on the full-bridge topology offer high-efficiency and good power handling capability up to 1kW. [Figure 1](#) illustrates the circuit arrangement for the full-bridge topology with full-wave rectification. The switches, in the diagonal, Q1,Q3 and Q2,Q4 are turned alternatively with a pulse width determined by the input and output voltages and the transformer turns ratio. Each diagonal (Q1 and Q3 or Q2 and Q4), when turned ON, applies input voltage to the primary of the transformer. The resulting secondary voltage is then full-wave rectified and filtered with an LC filter to provide a smoothed output voltage. The full-wave rectification on the secondary is a good alternative to the center-tapped rectification for high output voltages. The ratings of the synchronous MOSFETs are at least half that of the center-tapped arrangement. Lower the maximum VDS rating, better the  $Q \cdot R_{\text{DS(on)}}$  figure of merit and therefore leading to better efficiency. Further in a full-bridge topology, the primary switches are turned on alternatively energizing the windings in such a way that the flux swings back and forth in the first and the third quadrants of the B-H curve. The use of two quadrants allows better utilization of the core resulting in a smaller core volume compared to the single-ended topologies such as a forward converter.

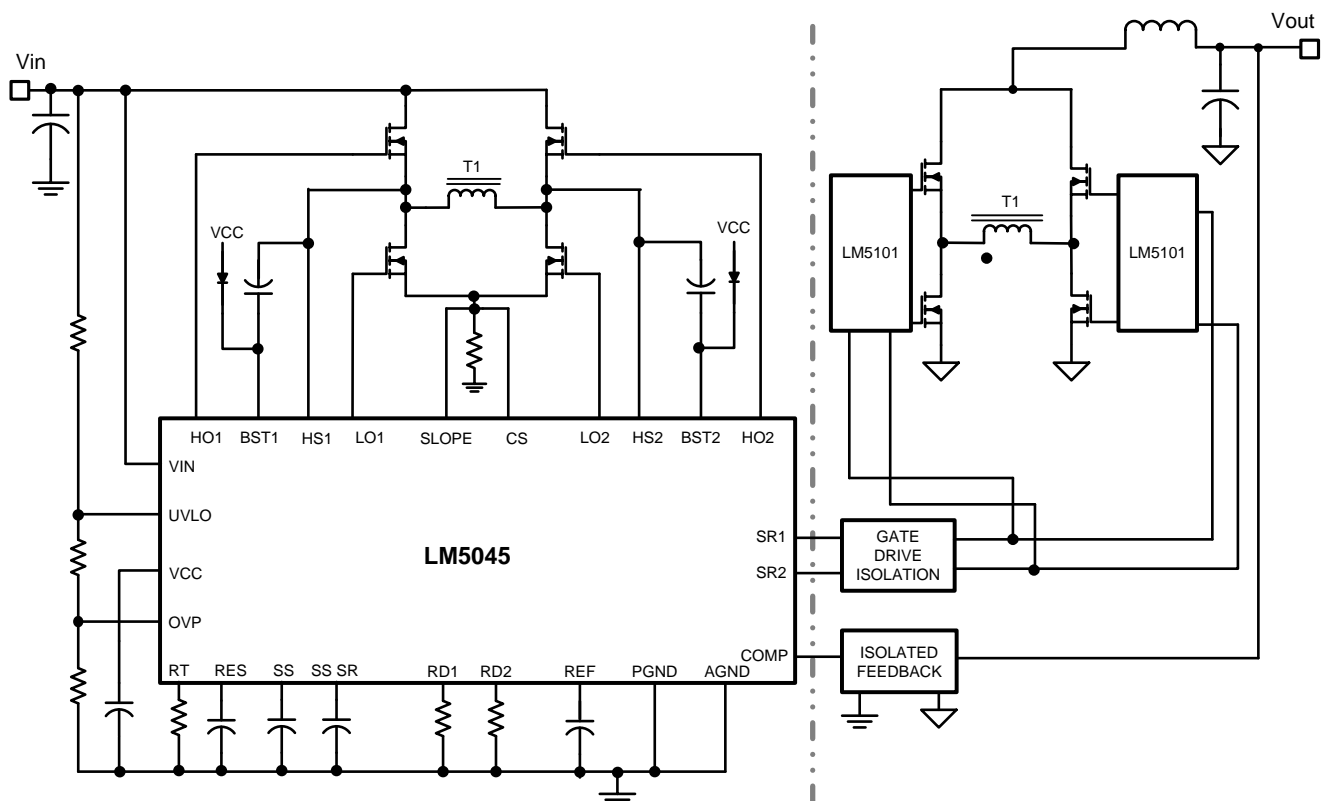

**Figure 1. Simplified Full-Bridge Converter with Full-Wave Rectification**

The secondary side employs full-wave synchronous rectification scheme, which is controlled by the LM5045. In addition to the basic soft-start already described, the LM5045 contains a second soft-start function that gradually turns on the synchronous rectifiers to their steady-state duty cycle. This function keeps the synchronous rectifiers off during the basic soft-start allowing a linear start-up of the output voltage even into pre-biased loads. Then the SR output duty cycle is gradually increased to prevent output voltage disturbances due to the difference in the voltage drop between the body diode and the channel resistance of the synchronous MOSFETs. Once, the soft-start is finished, the synchronous rectifiers are engaged with a non-overlap time programmed by the RD1 and RD2 resistors. Feedback from the output is processed by an amplifier and reference, generating an error voltage, which is coupled back to the primary side control through an opto-coupler. The LM5045 evaluation board employs peak current mode control and a standard “type II” network is used for the compensator.

### 3 Powering and Loading Considerations

When applying power to the LM5045 240W evaluation board certain precautions need to be followed. A misconnection can damage the assembly.


### 4 Proper Connections

When operated at low input voltages the evaluation board can draw up to 7.5A of current at full load. The maximum rated output current is 20A. Be sure to choose the correct connector and wire size when attaching the source supply and the load. Monitor the current into and out of the evaluation board. Monitor the voltage directly at the output terminals of the evaluation board. The voltage drop across the load connecting wires will give inaccurate measurements. This is especially true for accurate efficiency measurements.
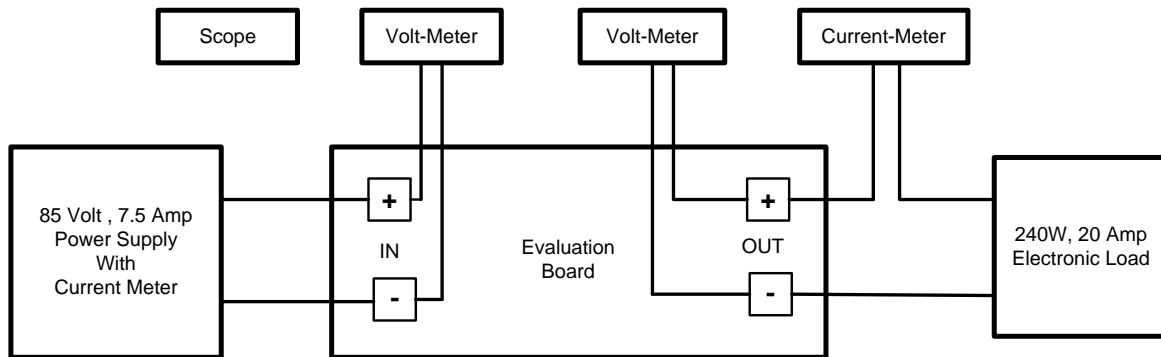
## 5 Source Power

The evaluation board can be viewed as a constant power load. At low input line voltage (36V) the input current can reach 7.5A, while at high input line voltage (72V) the input current will be approximately 3.5A. Therefore, to fully test this LM5045 reference board a DC power supply capable of at least 85V and 8A is required. The power supply must have adjustments for both voltage and current.

The power supply and cabling must present low impedance to the evaluation board. Insufficient cabling or a high impedance power supply will droop during power supply application with the evaluation board inrush current. If large enough, this droop will cause a chattering condition upon power up. This chattering condition is an interaction with the evaluation board under voltage lockout, the cabling impedance and the inrush current.



## 6 Loading

An appropriate electronic load, with specified operation down to 3.0V minimum, is desirable. The resistance of a maximum load is 0.6Ω. The high output current requires thick cables! If resistor banks are used there are certain precautions to be taken. The wattage and current ratings must be adequate for a 20A, 240W supply. Monitor both current and voltage at all times. Ensure that there is sufficient cooling provided for the load.

## 7 Air Flow

Full power loading should never be attempted without providing the specified 300 LFM of air flow over the evaluation board. A stand-alone fan should be provided.

## 8 Powering Up

It is suggested that the load be kept low during the first power up. Set the current limit of the source supply to provide about 1.5 times the wattage of the load. As soon as the appropriate input voltage is supplied to the board, check for 3.3 volts at the output.

A most common occurrence, that will prove unnerving, is when the current limit set on the source supply is insufficient for the load. The result is similar to having the high source impedance referred to earlier. The interaction of the source supply folding back and the evaluation board going into undervoltage shutdown will start an oscillation, or chatter, that may have undesirable consequences.


A quick efficiency check is the best way to confirm that everything is operating properly. If something is amiss you can be reasonably sure that it will affect the efficiency adversely. Few parameters can be incorrect in a switching power supply without creating losses and potentially damaging heat.

## 9 Over Current Protection

The evaluation board is configured with hiccup over-current protection. In the event of an output overload (approximately 25A) the unit will discharge the SS capacitor, which disables the power stage. After a delay, programmed by the RES capacitor, the SS capacitor is released. If the overload condition persists, this process is repeated. Thus, the converter will be in a loop of shot bursts followed by a sleep time in continuous overload conditions. The sleep time reduces the average input current drawn by the power converter in such a condition and allows the power converter to cool down.


## 10 Performance Characteristics

Once the circuit is powered up and running normally, the output voltage is regulated to 12V with the accuracy determined by the feedback resistors and the voltage reference. The frequency of operation is selected to be 420 kHz, which is a good compromise between board size and efficiency. Please refer to [Figure 2](#) for efficiency curves.

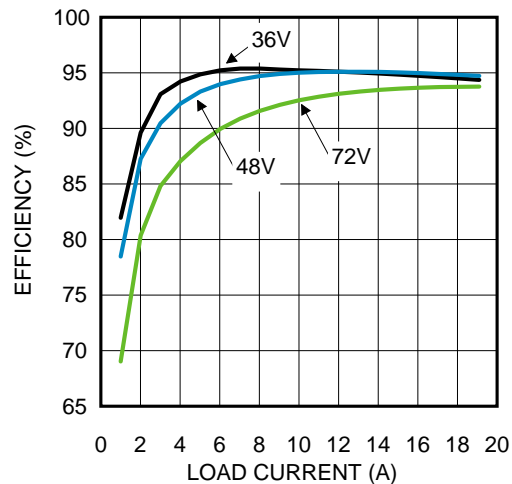

**Figure 2. Typical Efficiency Curves**

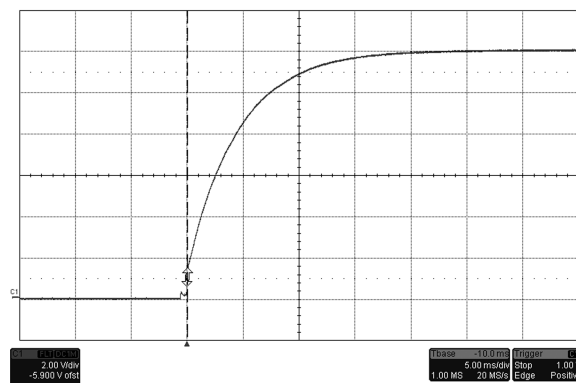
When applying power to the LM5045 evaluation board a certain sequence of events occurs. Soft-start capacitor values and other components allow for a minimal output voltage for a short time until the feedback loop can stabilize without overshoot. [Figure 3](#) shows the output voltage during a typical start-up with a 48V input and a load of 25A. There is no overshoot during start-up.



Output Current = 6A  
 Trace 1: Output Voltage Volts/div = 2V  
 Horizontal Resolution = 5.0 ms/div

**Figure 3. Soft-Start**

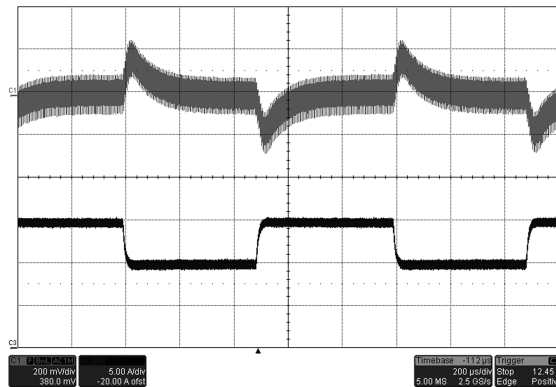
[Figure 4](#) shows minimal output voltage droop and overshoot during the sudden change in output current shown by the lower trace.



Conditions: Input Voltage = 48V  
 Output Current = 5A  
 Upper Trace: Output Voltage Volts/div = 200mV  
 Lower Trace: Output Current = 10A to 15A to 10A  
 Horizontal Resolution = 200 µs/div


**Figure 4. Transient Response**

Figure 5 and Figure 6 show the typical SW node voltage waveforms with a 20A load. Figure 5 shows an input voltage represents an input voltage of 48V and Figure 6 represents an input voltage of 72V.

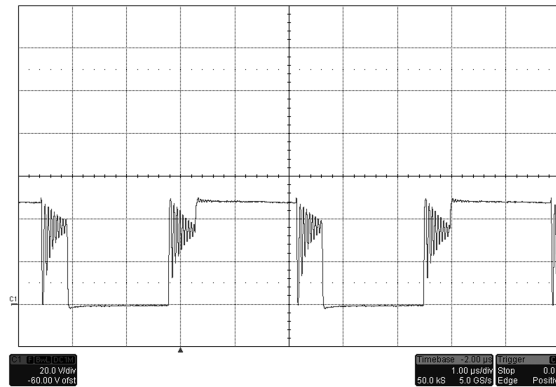

Conditions: Input Voltage = 48V, Output Current = 20A  
 Trace 1: Q1 Drain Voltage Volts/div = 20V  
 Horizontal Resolution = 1µs/div


**Figure 5. Switch Node Waveforms**

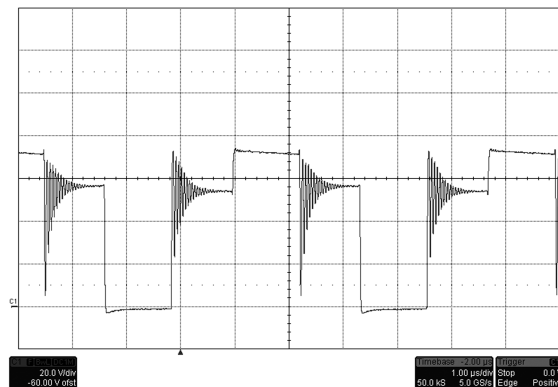

Conditions: Input Voltage = 72V  
 Output Current = 20A  
 Trace 1: Q1 Drain Voltage Volts/div = 20V  
 Horizontal Resolution = 1 µs/div

**Figure 6. Switch Node Waveforms**

Figure 7 shows a typical startup of the reference into a 5V pre-biased load.

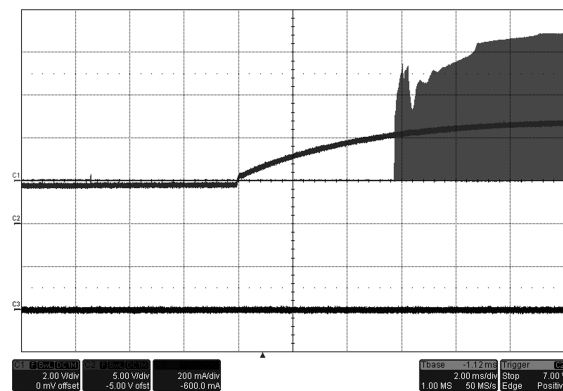


Conditions: Input Voltage = 48V, Output Pre-Bias = 5V  
 Trace 1: SR Gate Voltage Volts/div = 2V  
 Trace 2: Output Voltage Volts/div = 5V  
 Trace 3: Output Current Amps/div = 200mA


**Figure 7. Soft-Start Into 5V Pre-Biased Load**

### Conversion to Phase-Shifted Full-Bridge Topology

The LM5045 reference board can be turned into a phase shifted full-bridge by swapping the LM5045 full-bridge controller with the LM5046 phase shifted full-bridge controller. However, it is advised to rearrange the windings in the power transformer such that the leakage inductance is increased. Higher leakage inductance will aid in achieving ZVS. Leakage inductance can be increased by not interleaving the primaries and secondary's of the power transformer.

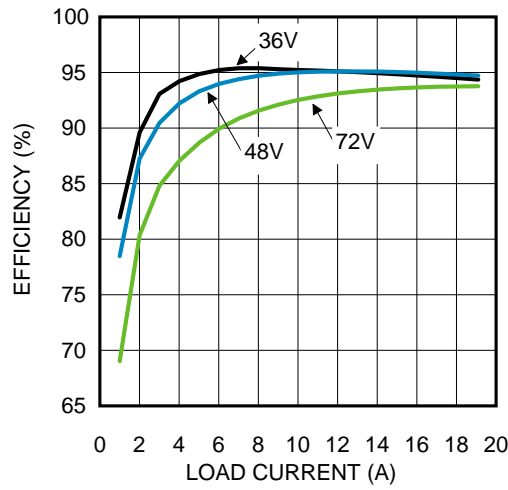

**Figure 8. Efficiency Using the PSFB Approach**

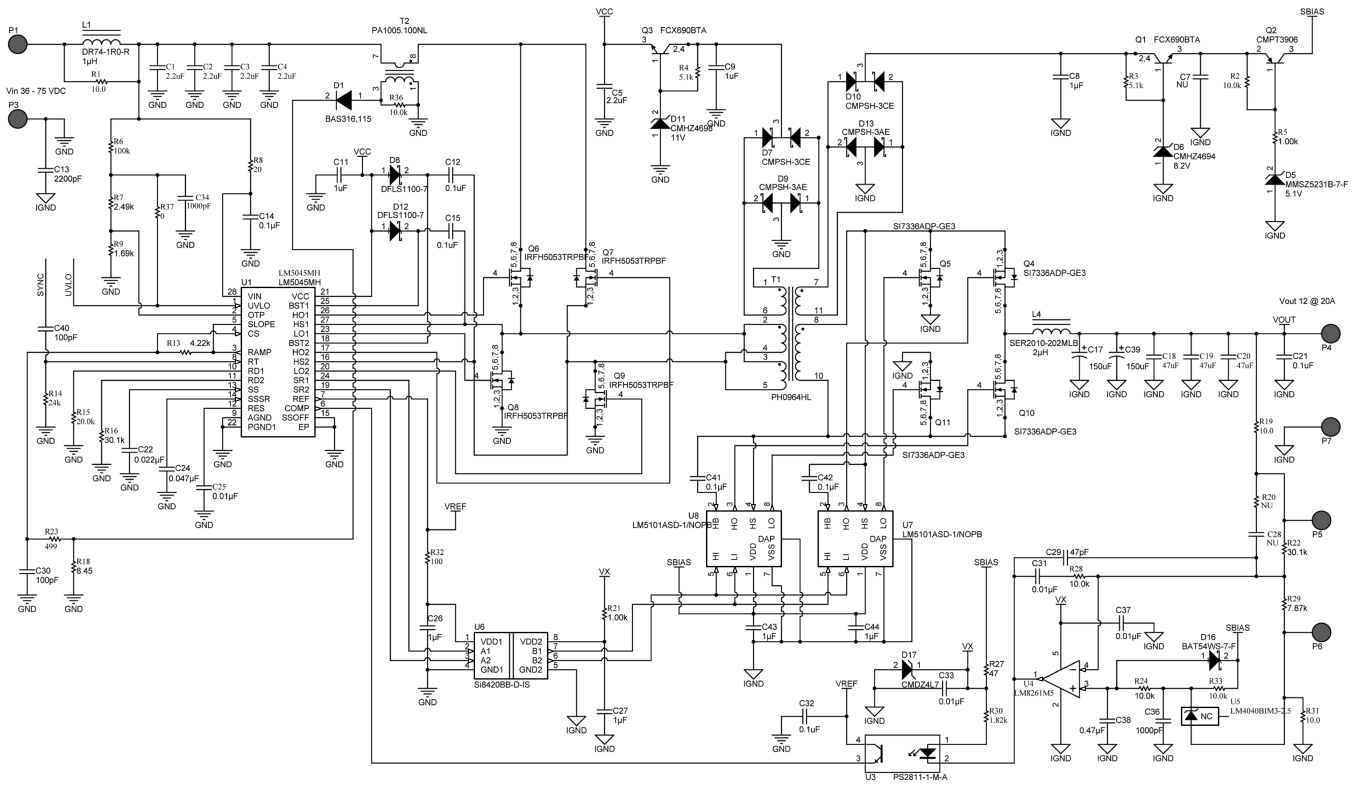

**Figure 9. Application Circuit: Input 36V to 75V, Output 12V at 20A**

**11 Bill of Materials**

Item	Designator	Description	Manufacturer	Part Number
1	C1, C2, C3, C4	CAP, CERM, 2.2uF, 100V, +/-10%, X7R, 1210	MuRata	GRM32ER72A225KA35L
2	C5	CAP, CERM, 2.2uF, 16V, +/-10%, X7R, 0805	MuRata	GRM21BR71C225KA12L
3	C8, C9	CAP, CERM, 1uF, 50V, +/-10%, X7R, 0805	MuRata	GRM21BR71H105KA12L
4	C11	CAP, CERM, 1uF, 16V, +/-10%, X7R, 0603	TDK	C1608X7R1C105K
5	C12, C15, C21, C32	CAP, CERM, 0.1uF, 25V, +/-10%, X7R, 0603	AVX	06033C104KAT2A
6	C13	CAP, CERM, 2200pF, 2000V, +/-10%, X7R, 1808	Johanson Dielectrics	202R29W222KV4E
7	C14, C41, C42	CAP, CERM, 0.1uF, 100V, +/-10%, X7R, 0603	MuRata	GRM188R72A104KA35D
8	C17, C39	CAP TANT 150uF 16V 20% SMD	KEMET	T530X157M016ATE015
9	C18, C19, C20	CAP, CERM, 47uF, 16V, +/-20%, X5R, 1210	MuRata	GRM32ER61C476ME15L
10	C22	CAP, CERM, 0.022uF, 16V, +/-10%, X7R, 0402	TDK	C1005X7R1C223K
11	C24	CAP, CERM, 0.1uF, 6.3V, +/-10%, X5R, 0402	TDK	C1005X5R0J104K
12	C25, C31, C33, C37	CAP, CERM, 0.01uF, 16V, +/-10%, X7R, 0402	TDK	C1005X7R1C103K
13	C26, C27, C43, C44	CAP, CERM, 1uF, 16V, +/-20%, X7R, 0805	MuRata	GRM21BR71C105MA01L
14	C29	CAP, CERM, 47pF, 50V, +/-5%, C0G/NP0, 0402	MuRata	GRM1555C1H470JZ01
15	C30, C40	CAP, CERM, 100pF, 50V, +/-5%, C0G/NP0, 0603	TDK	C1608C0G1H101J
16	C34, C36	CAP, CERM, 1000pF, 25V, +/-5%, C0G/NP0, 0402	TDK	C1005C0G1E102J
17	C38	CAP CER .47uF 6.3V X5R 0402	TDK	C1005X5R0J474K
18	D1	Diode, Ultrafast, 100V, 0.25A, SOD-323	NXP Semiconductor	BAS316,115
19	D5	Diode, Zener, 5.1V, 500mW, SOD-123	Diodes Inc.	MMSZ5231B-7-F
20	D6	Diode, Zener, 8.2V, 500mW, SOD-123	Central Semiconductor	CMHZ4694
21	D7, D10	Diode, Schottky, 40V, 0.2A, Common Cathode, SOT-23	Central Semiconductor	CMP5H-3CE
22	D8, D12	Vr = 100V, Io = 1A, Vf = 0.77V	Diodes Inc.	DFLS1100-7
23	D9, D13	Diode, Schottky, 40V, 0.2A, Common Anode, SOT-23	Central Semiconductor	CMP5H-3AE
24	D11	Diode, Zener, 11V, 500mW, SOD-123	Central Semiconductor	CMHZ4698
25	D16	Vr = 30V, Io = 0.2A, Vf = 0.7V	Diodes Inc.	BAT54WS-7-F
26	D17	Low Level Zener Diode, 4.7V, 250mW, SOD-323	Central Semiconductor	CMDZ4L7
27	L1	Inductor, Shielded Drum Core, Ferrite, 1uH, 5.39A, 0.0099 ohm, SMD	Coiltronics	DR74-1R0-R
28	L4	PCB Pin	Coilcraft	SER2010-202MLB



Item	Designator	Description	Manufacturer	Part Number
29	P1, P3, P5, P6	PCB Pin	Mill-Max	3104-2-00-34-00-00-08-0
30	P4, P7	PCB Pin	Mill-Max	3231-2-00-34-00-00-08-0
31	Q1, Q3	Transistor, NPN, 45V, 1A, SOT-89	Diodes Inc.	FCX690BTA
32	Q2	Transistor, PNP, 40V, 0.2A, SOT-23	Central Semiconductor	CMPT3906
33	Q4, Q5, Q10, Q11	MOSFET, N-CH, 30V, PowerPAK SO-8	Texas Instruments	CSD17303Q5
34	Q6, Q7, Q8, Q9	MOSFET, N-CH, 100V, 9.3A, PQFN 8L 5x6 A	International Rectifier	IRFH5053TRPBF
35	R1	RES, 10.0 ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW080510R0FKEA
36	R2, R24, R28, R33, R36	RES, 10.0k ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW040210k0FKED
37	R3, R4	RES, 5.1k ohm, 5%, 0.125W, 0805	Panasonic	ERJ-6GEYJ512V
38	R5	RES, 1.00k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW08051K00FKEA
39	R6	RES, 100k ohm, 1%, 0.125W, 0805	Vishay-Dale	CRCW0805100KFKEA
40	R7	RES, 2.49k ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW04022K49FKED
41	R8	RES, 20 ohm, 5%, 0.125W, 0805	Panasonic	ERJ-6GEYJ200V
42	R9	RES, 1.69k ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW04021K69FKED
43	R13	RES, 4.22k ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW04024K22FKED
44	R14	RES, 24k ohm, 5%, 0.063W, 0402	Vishay-Dale	CRCW040224k0JNED
45	R15	RES, 20.0k ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW040220k0FKED
46	R16, R22	RES, 30.1k ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW040230K1FKED
47	R18	RES, 8.45 ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW04028R45FKED
48	R19, R31	RES, 10.0 ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW040210R0FKED
49	R21, R23	RES, 499 ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW0402499RFKED
50	R27	RES 47 OHM .25W 5% 0603 SMD	Vishay	CRCW060347R0JNEAHP
51	R29	RES, 7.87k ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW04027K87FKED
52	R30	RES, 1.82k ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW04021k82FKED
53	R32	RES, 100 ohm, 1%, 0.063W, 0402	Vishay-Dale	CRCW0402100RFKED
54	R37	RES, 0 ohm, 5%, 0.063W, 0402	Vishay-Dale	CRCW04020000Z0ED
55	T1	High Frequency Planar Transformer	Pulse	PA3542NL
56	T2	SMT Current Sense Tranformer	Pulse Engineering	PA1005.100NL
57	U1	Full-Bridge Controller	Texas Instruments	LM5045MH
58	U3	Low Input Current, Hight CTR Photocoupler	NEC	PS2811-1-M-A

<b>Item</b>	<b>Designator</b>	<b>Description</b>	<b>Manufacturer</b>	<b>Part Number</b>
59	U4	RRIO, High Output Current & Unlimited Cap Load Op Amp in SOT23-5	Texas Instruments	LM8261M5
60	U5	Precision Micropower Shunt Voltage Reference, 3-pin SOT-23	Texas Instruments	LM4040BIM3-2.5
61	U6	Digital Isolator	Texas Instruments	ISO7420FED
62	U7, U8	3A High Voltage High-Side and Low-Side Gate Driver, 8 pin LLP	Texas Instruments	LM5101ASD-1/NOPB
63	C7	CAP, CERM, 3.3uF, 16V, +/- 10%, X5R, 0805	MuRata	GRM21BR61C335KA88L(optional)

11.1 PCB Layouts

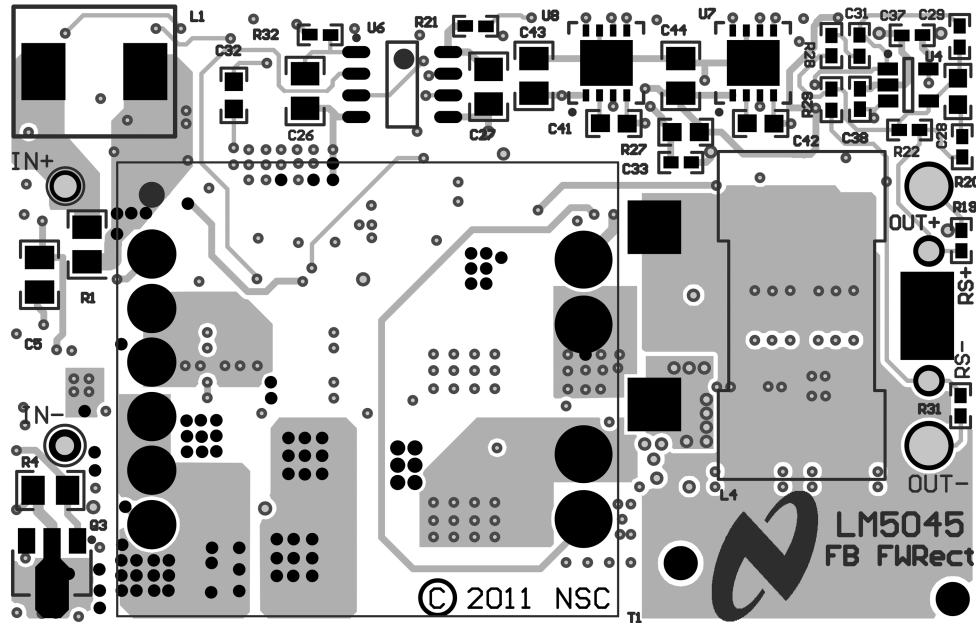


Figure 10. Top Side Assembly

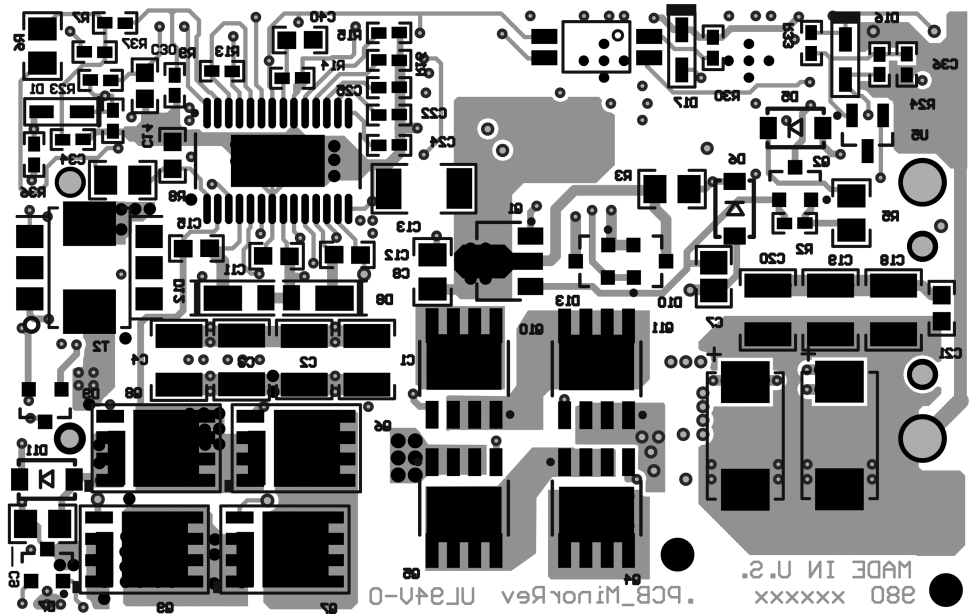


Figure 11. Bottom Side Assembly

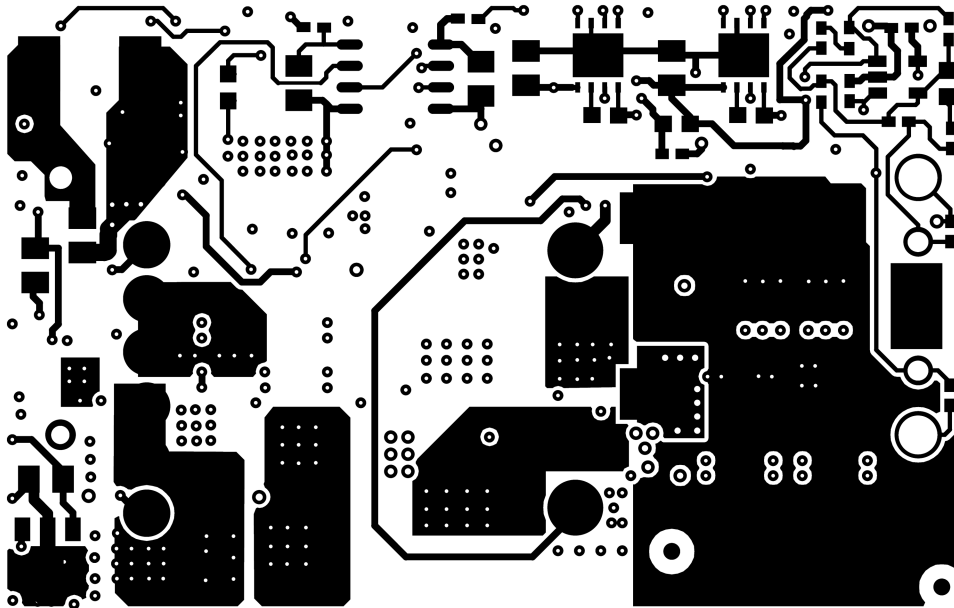


Figure 12. Layer 1 (Top Side)

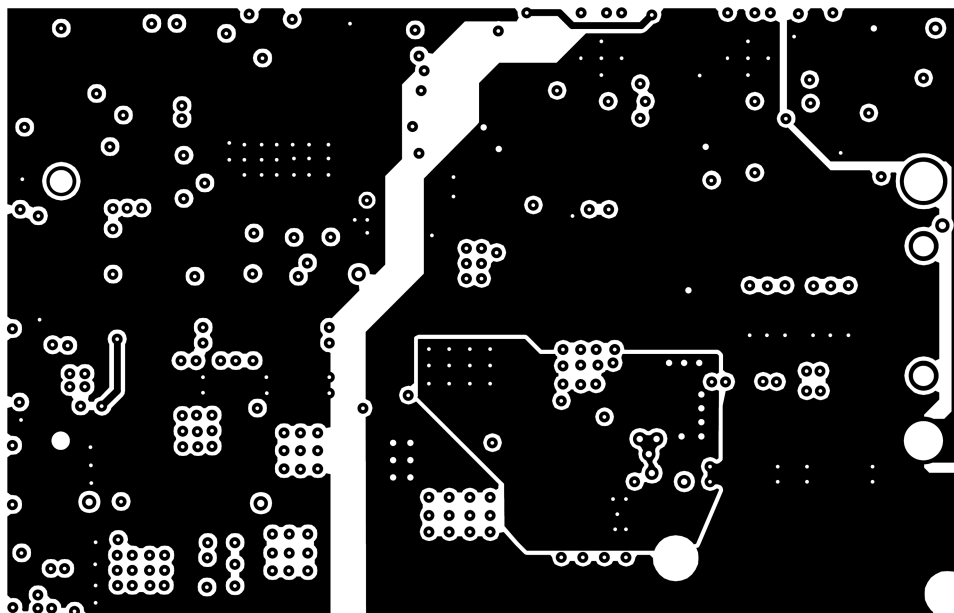


Figure 13. Layer 2

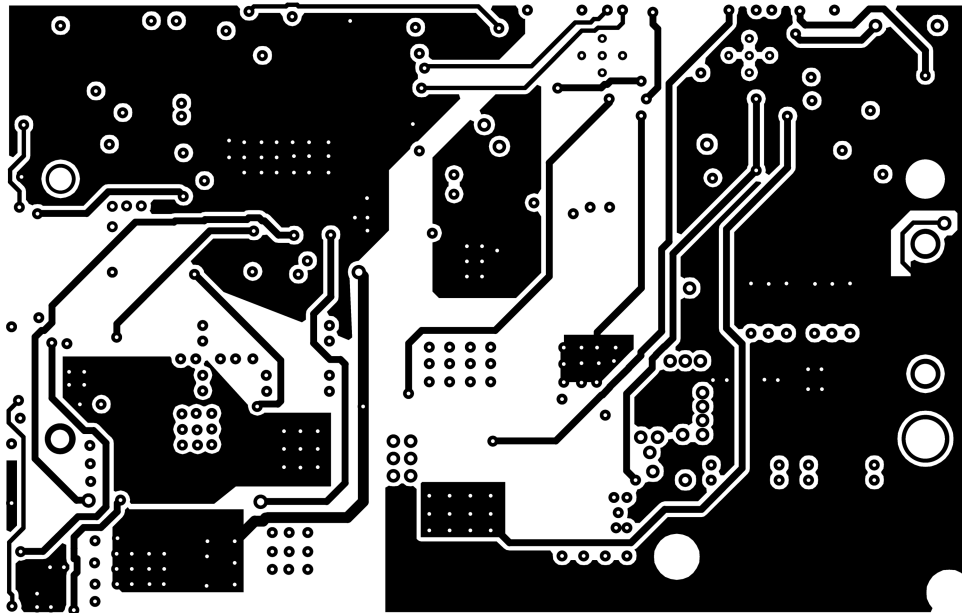


Figure 14. Layer 3

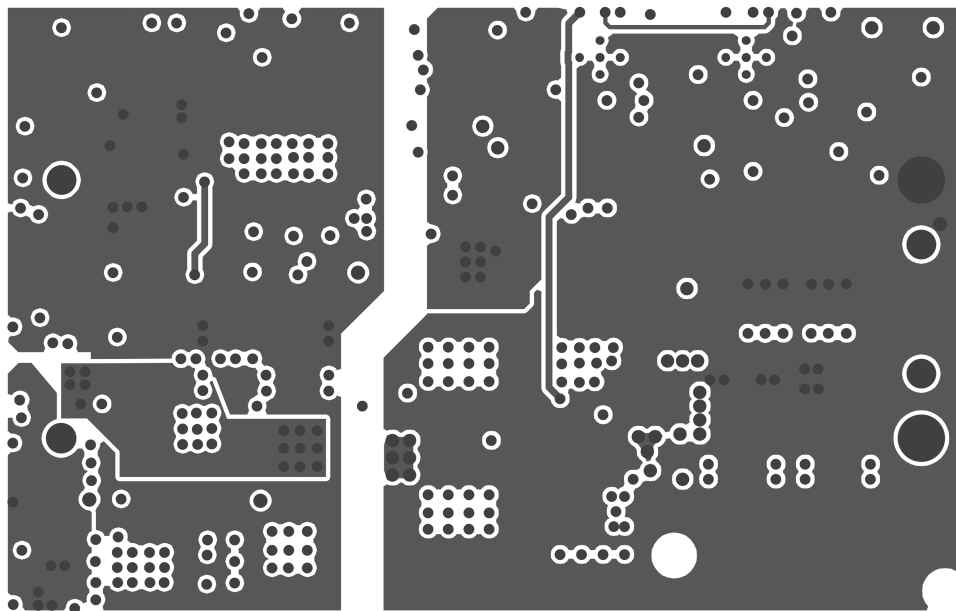


Figure 15. Layer 4

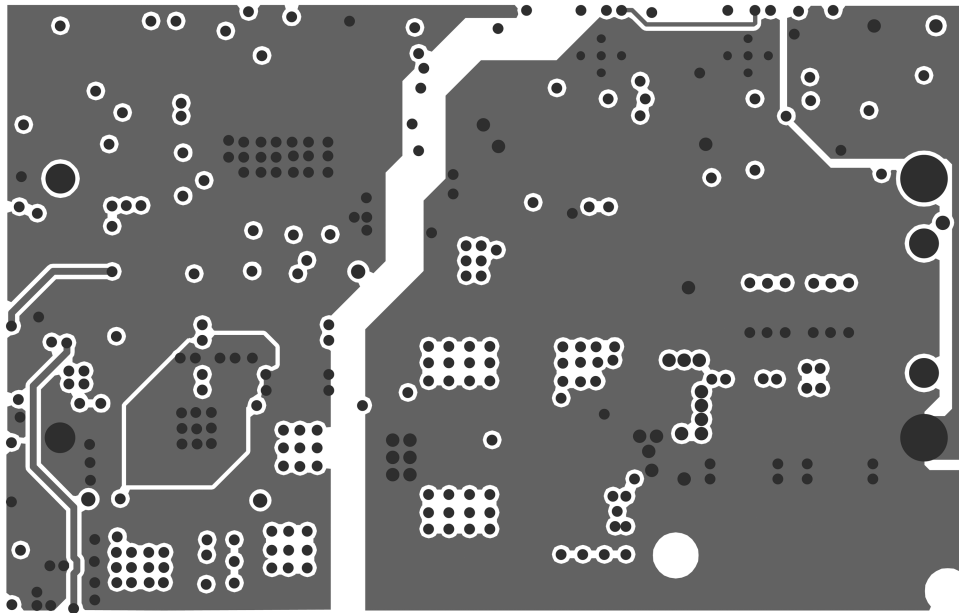


Figure 16. Layer 5

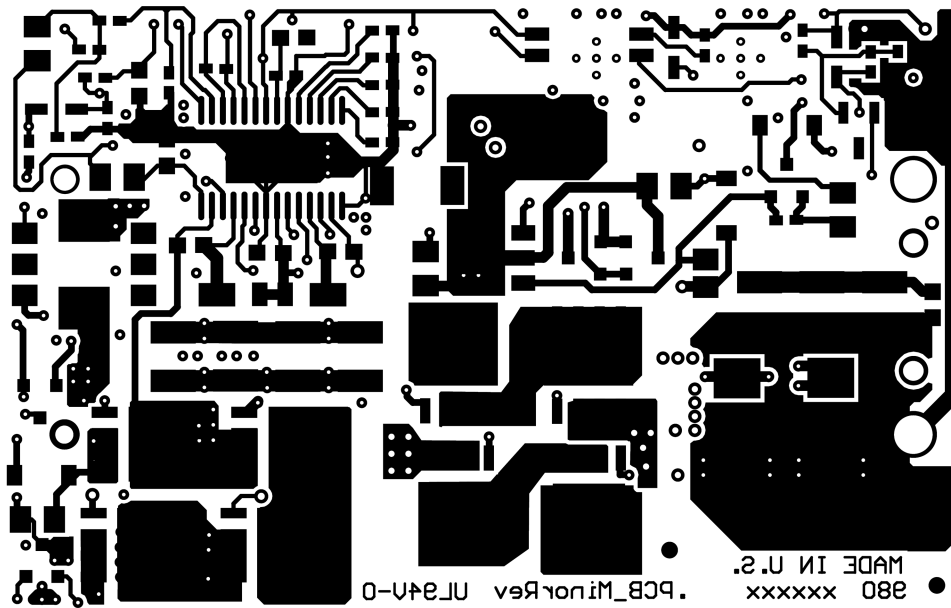


Figure 17. Layer 6 (Bottom Side)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)