
AN-1244 Photo-Diode Current-to-Voltage Converters

ABSTRACT

Converting the small output current of a photo-diode transducer to a fast responding voltage is often challenging. This application report provides some ways to use high-speed current feedback and voltage feedback op amps to do the job.

Contents

1	Current Feedback Amplifier Solution	2
2	Voltage Feedback Amplifier Solution	3

List of Figures

1	Single-Supply Photo-Diode Amplifier Using CLC450 Current-Feedback Amplifier	2
2	R_A - R_B Resistor Divider Allows Use of Practical Value for C_f	2
3	Single-Supply Photo-Diode Amplifier Using LMH6642 Voltage-Feedback Op Amp	3
4	Output Step Response 20 ns/div, 0.2 V/div	3

1 Current Feedback Amplifier Solution

Current feedback amplifiers (CFA) are especially suited to implement this function, as shown in Figure 1. With an effective internal buffer on the inverting node of the op amp, the output impedance R_O (internal to U1, not shown) and the photo-diode's output capacitance C_{IN} (typically 10-200pF) introduce a zero in the noise gain at approximately $1/2\pi \times (R_O \times C_{IN})$. In comparison, the zero produced by a voltage feedback op amp in a similar configuration $[1/2\pi \times (R_{IN} || R_F || R_{BIAS}) \times C_{IN}]$ tends to be much lower in frequency and more troublesome. This being the case, C_{IN} has less of an effect on reduction of the converter bandwidth, and achieving stability is easier when using a CFA.

If C_{IN} is sufficiently large, the closed loop phase shift will approach -180° at the cross-over frequency (where open loop transimpedance gain crosses the noise gain function). As with voltage feedback amplifiers, the closed loop amplifier can be compensated by adding a small capacitor (C_F) across R_F . In the case of Figure 1, using the CLC450 CFA, C_F was experimentally determined to be around 2 pF for about 10% overshoot in the step response. C_F improves stability by counteracting the effect of the zero discussed in the paragraph above by introducing a low frequency pole ($1/2\pi \times R_F \times C_F$) and an inconsequential zero ($1/2\pi \times R_O \times C_F$).

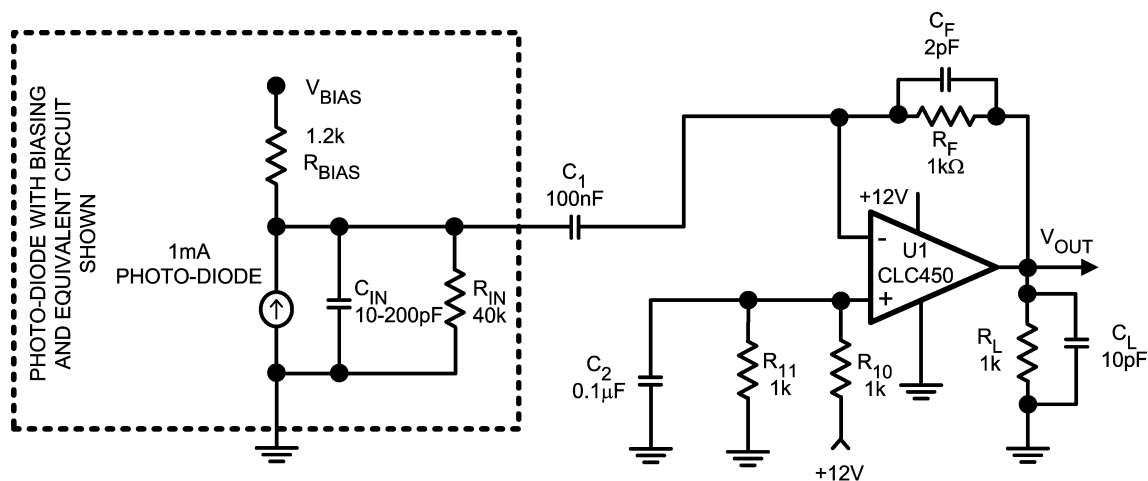


Figure 1. Single-Supply Photo-Diode Amplifier Using CLC450 Current-Feedback Amplifier

It is possible to change the required 2 pF compensation capacitor to a more practical value, by adding R_A and R_B in a voltage divider, as shown in Figure 2. The new value of C'_F is $(1+R_B/R_A) \times C_F$. This relationship holds true as long as $R_B \ll R_F$.

For this example, select $R_A = 50 \Omega$, and $R_B = 500 \Omega$. Therefore, $C'_F = (1+500/50) \times 2 \text{ pF} = \sim 22 \text{ pF}$, which is a much more practical component value. This value needs to be "fine tuned" in the real application for proper step response.

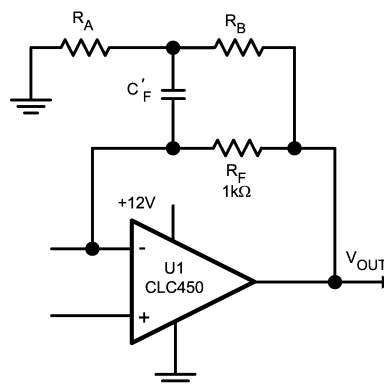


Figure 2. R_A - R_B Resistor Divider Allows Use of Practical Value for C'_F

2 Voltage Feedback Amplifier Solution

It's more difficult to design a good current-to-voltage converter using a voltage feedback amplifier (VFA). As discussed in [Section 1](#), phase shift caused by photo-diode capacitance is often a source of instability. Furthermore, wide bandwidth usually comes at the expense of supply currents and higher supply voltage. However, the new LMH6642 high-speed low-voltage VFA op amp has excellent performance in a transimpedance gain block, as shown in [Figure 3](#). This device can operate down to 2.7 V single supply and its -3dB BW ($A_v = +1$) is more than 100 MHz (with a supply current of only 2.7 mA). Because of the "Dielectric Isolation" process this device is based on, the traditional supply voltage versus speed trade-off has been alleviated to a great extent allowing low power consumption and operation at lower supply voltages. In addition, the device has rail-to-rail output swing capability to maximize the output swing, and is capable of driving ± 50 mA into the load.

With 5 V single supply, the device common mode voltage is shifted to near half-supply using R_{10} - R_{11} as a voltage divider from V_{CC} . The common-base transistor stage (Q1) isolates the photo-diode's capacitance from the inverting terminal, allowing wider bandwidth and easing the compensation required. Note that the collector of Q1 does not have any voltage swing, so the Miller effect is minimized. The diode on the base of Q1 is for temperature compensation of its bias point. Q1 bias current was set to be large enough to handle the peak-to-peak photo-diode excitation, yet not too large as to shift the U1 output too far from mid-supply. The overall circuit draws about 4.5 mA from the +5 V power supply and achieves about 35 MHz of closed loop bandwidth @1 V_{pp} . [Figure 4](#) shows the output large signal step response. C_F can be increased to reduce the overshoot, at the expense of bandwidth.

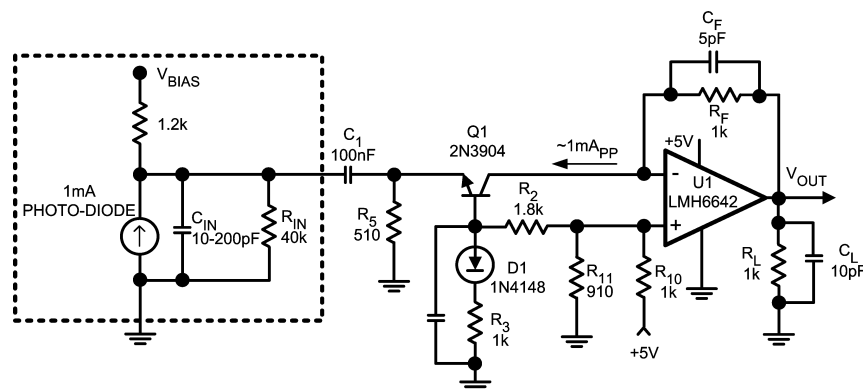


Figure 3. Single-Supply Photo-Diode Amplifier Using LMH6642 Voltage-Feedback Op Amp

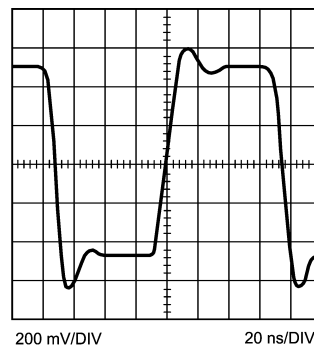


Figure 4. Output Step Response 20 ns/div, 0.2 V/div

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com