

No. 102

Feature Article1-7

Precision Amplifiers.....2


1 MSPS ADCs4

Current-Sensing
Amplifier6

Design Tools8

Maximizing Signal-Path Performance

— By Chuck Sims, Applications Engineer

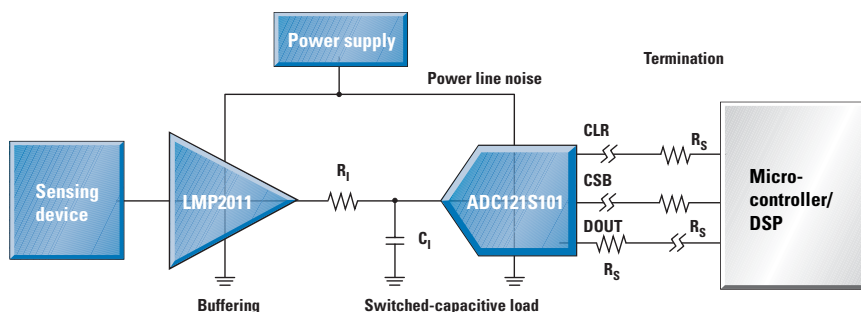

Precision Signal Path

The signal path offers many opportunities for the system designer. In the analog-to-digital converter (ADC) signal path, making good design choices in buffering a sensing device, charging the switch-capacitive input of an ADC, and minimizing noise sources will maximize performance. All of these examples will be addressed in this issue of the *Signal Path Designer*.

Buffering a Sensing Device

When a sensing device is unable to drive the capacitive load of an ADC, it can be buffered with an operational amplifier (op amp). Since many applications require operation from a single supply, it is important to select an op amp that operates at the same voltage as the ADC. While sharing supply voltages helps reduce system complexity and cost, supply voltages place constraints on the input and output capability of the op amp. For ADCs such as the ADC121S101 where the reference voltage (V_{REF}) is both the supply voltage and the reference, op amps such as the LMP2011 with rail-to-rail output (RRO) capability are preferred. The LMP2011 with RRO capability allows the system designer to utilize the full dynamic range of the ADC, providing access to all of the output codes.

Once an op amp with suitable input/output capabilities has been selected, its gain bandwidth needs to be considered. For cases where the stimulus source's maximum output is less than V_{REF} , gain may be required from the buffering stage. The gain bandwidth product (GBWP) of an op amp specifies its band-

NEXT ISSUE:
High-Speed Signals,
Clocks, and Data Capture


 **National
Semiconductor**
The Sight & Sound of Information



High Precision-Rail-to-Rail Output Amplifiers



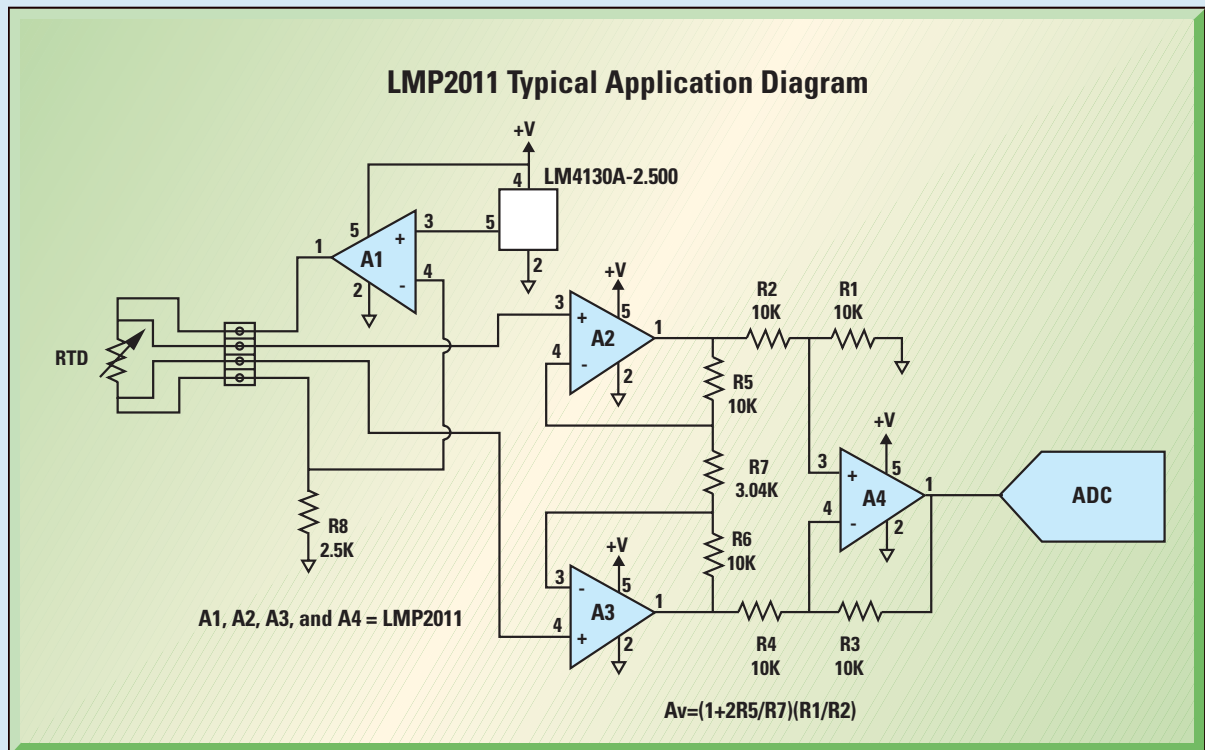Delivering High Precision Over Time and Temperature



LMP2011/12/14 Key Features

- 60 μV V_{OS} max over temp (- 40°C to +125°C)
- Low voltage noise (35 $\text{nV}/\sqrt{\text{Hz}}$) and no 1/f
- High CMRR (130 dB), PSRR (120 dB)
- Gain (130 dB) and 3 MHz GBW product

System Benefits

- Offers high accuracy measurements with continued accuracy over temperature
- Increase signal accuracy during low frequency measurements
- High accuracy across voltages
- Wide frequency range at higher gains

Maximizing Signal-Path Performance

width (-3 dB frequency) when configured as a unity gain amplifier. Since GBWP remains constant for a given op amp, a closed loop configuration with a gain of A_{CL} lowers the bandwidth by a factor of A_{CL} : $BW = \frac{GBWP}{A_{CL}}$

For example, the LMP2011 with a GBWP of 3 MHz will have a bandwidth of 300 kHz when configured with an A_{CL} of 10 V/V.

Because the closed-loop bandwidth is the -3 dB frequency of the amplifier, it is the frequency where the amplifier output is 70.7% of its input value. So at the -3 dB frequency there is a 29.3% error in output amplitude. Errors in ADCs are measured in units of least significant bits (LSBs). One LSB is defined as $V_{REF}/2^n$ where V_{REF} is the reference voltage and n is the ADC resolution. For example, 1 LSB of an 8-bit ADC is $V_{REF}/256$. For a system requiring $1/2$ LSB of accuracy from its ADC, the input stimulus must have gain accuracy of $(1-1/2^{n+1})$ or 99.8% for an 8-bit ADC. To guarantee that the op amp has sufficient gain accuracy for a given system requirement, it is necessary to calculate the maximum operating frequency (f_{max}) for the op amp. This is accomplished by approximating the frequency response of an op amp to be that of a single pole filter. The curve shown in *Figure 1* has the gain (A_v) and -3 dB frequency (f_0) normalized to 1.

The expression for this curve is

$$A_v = \frac{1}{\sqrt{1+(f)^2}}$$

or solving for f ,

$$f = \sqrt{\frac{1}{A_v^2} - 1}$$

To achieve $1/2$ LSB of error from an 8-bit system, the normalized f_{max} of an op amp is

$$f = \sqrt{\frac{1}{(0.998)^2} - 1} = 0.062$$

Therefore, for an 8-bit ADC with a $1/2$ LSB accuracy requirement, the op amp's effective bandwidth is $0.062 \times GBWP$. The LMP2011 with a GBWP of 3 MHz would have an effective bandwidth of 186 kHz when configured for unity gain. The effective bandwidth is further reduced if a gain greater than unity is required. The normalized f_{max} for

 


Figure 1. Op-Amp Frequency Response

$1/2$ LSB of error for ADCs of various resolutions can be calculated as:

$$\text{Normalized } f_{max} = \sqrt{\frac{1}{(1-\frac{1}{2^{n+1}})^2} - 1}$$

Transferring Charge to a Switched-Capacitive Load

The op amp was added to the ADC signal path to drive the capacitive load. However, the ADC's input is a switched-capacitive load (*see Figure 2*).


 



Figure 2. ADC121S101 Input

The ADC121S101 in “hold” mode has an input capacitance, C_{PIN} , of less than 4 pF, and in “track” mode has an input capacitance, C_{SAMPLE} plus C_{PIN} , of less than 30 pF. To minimize the error caused by the changing input capacitance, a capacitor (C_1) is connected from the input pin to ground. The C_1 , which is much larger than the input capacitance of the ADC when in “track” mode, provides the current to quickly charge the ADC's sampling capacitor. An isolation resistor is generally added to isolate the additional load capacitance from the op-amp output (*see Figure 3*).

 Low power, high precision 8/10/12-bit, 1 MSPS ADCs



ADC121S101 Typical Application Diagram

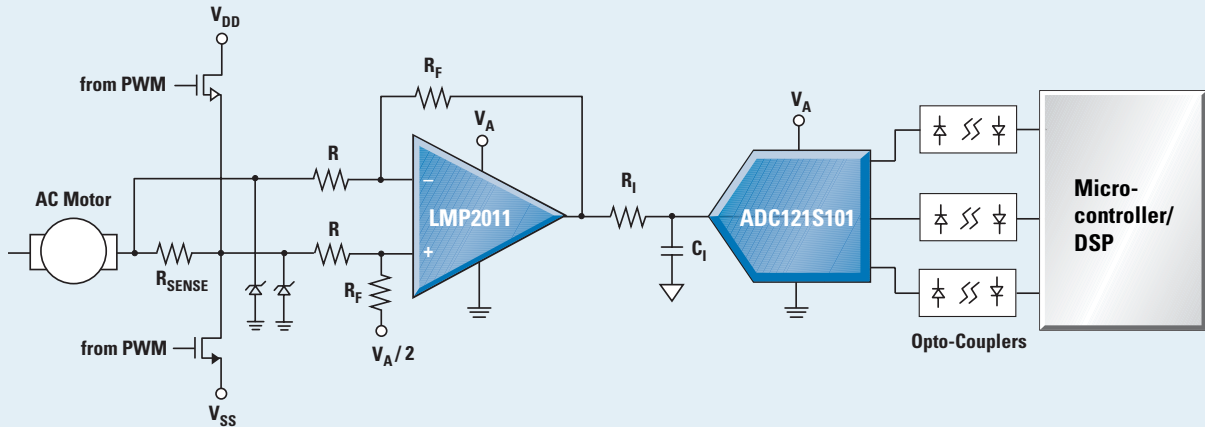


ADC121S101, ADC101S101, and ADC081S10 Features (typical)

- Speed range: 500 KSPS to 1 MSPS
- Integral non-linearity (INL): ± 0.4 LSB
- Differential non-linearity (DNL): ± 0.5 LSB
- Signal-to-noise ratio (SNR): 72.5 dB
- Signal-to-noise and distortion ratio (SINAD): 72 dB
- Spurious free dynamic range (SFDR): 82 dB
- Power consumption: 2 mW at 3V
- Supply voltage: 2.7 to 5.25V

Family Benefits

 - Guaranteed performance over speed
- Pin and function compatible family
- Excellent static and dynamic performance
- Extremely low power
- Miniature packages reduce board space



Maximizing Signal-Path Performance

 


Figure 3. Quick-Charge Circuit

There are three important factors to consider in choosing appropriate values for the RC network. First, the designer needs to be aware that the RC network forms a low pass filter in the signal path. Therefore, the network can attenuate the sampled signal as the input frequency approaches the pole defined by $\frac{1}{2\pi RC}$. This is extremely critical for applications where ADC gain is important and no gain-calibration scheme is employed. Second, refrain from making the series resistor too large. While an increased resistance value decreases the phase delay at the output of the op amp (maintaining op-amp stability), it prevents the parallel combination of internal and external capacitance at the ADC input from fully charging during the ADC “track” time. Typical resistor values are less than 100 ohms. Third, make the external capacitor many times larger than the input capacitance while in “track” mode. Achieving this will minimize the drop in voltage on the capacitor when the ADC switches from “hold” to “track” mode.

The settling-time requirement of the op amp is determined by the amount of time the ADC spends in “track” mode. This is the amount of time that the op amp has to replenish the charge and reestablish the voltage on the capacitor prior to the ADC switching to “hold” mode. The time constant for recharging the capacitance at the input pin is defined by the series resistance value and the parallel combination of the internal and external capacitances. If the op amp fails to stabilize the voltage at the input by the time the ADC enters “hold” mode, inconsistent and erroneous conversions will result.

As a starting point for selecting values for R_I and C_I , the pole of the RC network may be set to the sampling frequency of the ADC. If this causes too

much attenuation for the highest input frequency, the designer can decrease the capacitance or resistance values accordingly. The minimum resistor value should be set by the output drive capability of the op amp. Smaller resistor values are preferred since they limit distortion. However, the amplifier stability must be guaranteed over the full input frequency range, amplitude, and temperature of the application.

Managing Component Tolerance

If an inverting amplifier is used for the amplifier configuration (see Figure 4), it is easy to calculate the error coefficient due to component tolerance. Since the gain is defined as $-R_F/R_G$, the maximum deviation from the ideal will occur when R_F is maximum and R_G is minimum or when R_F is minimum and R_G is maximum. If resistors with a tolerance of 1% are used, the maximum error will be 2%.

 


Figure 4. Inverting Amplifier Configuration

Applications where gain calibration schemes are not utilized must limit the dynamic range of the ADC. For an 8-bit ADC, 1 LSB represents 0.39% of V_{REF} ($V_{REF}/2^8$). Therefore, a 2% gain error due to resistor tolerance equates to a 12 LSB loss in dynamic range, 6 LSB (rounded up from 5.13) from the maximum output code and 6 LSB from the minimum.


Minimizing Power Line Noise

While component tolerance is one source of error in the ADC signal path, noise on power lines due to digital circuitry is another. Noise can couple into an ADC and an op amp through their supply pins. Typically, devices such as the LMP2011 have excellent power supply rejection ratios (PSRR) and will not be affected. However, ADCs such as the

High Common Mode, Voltage-Difference Amplifier



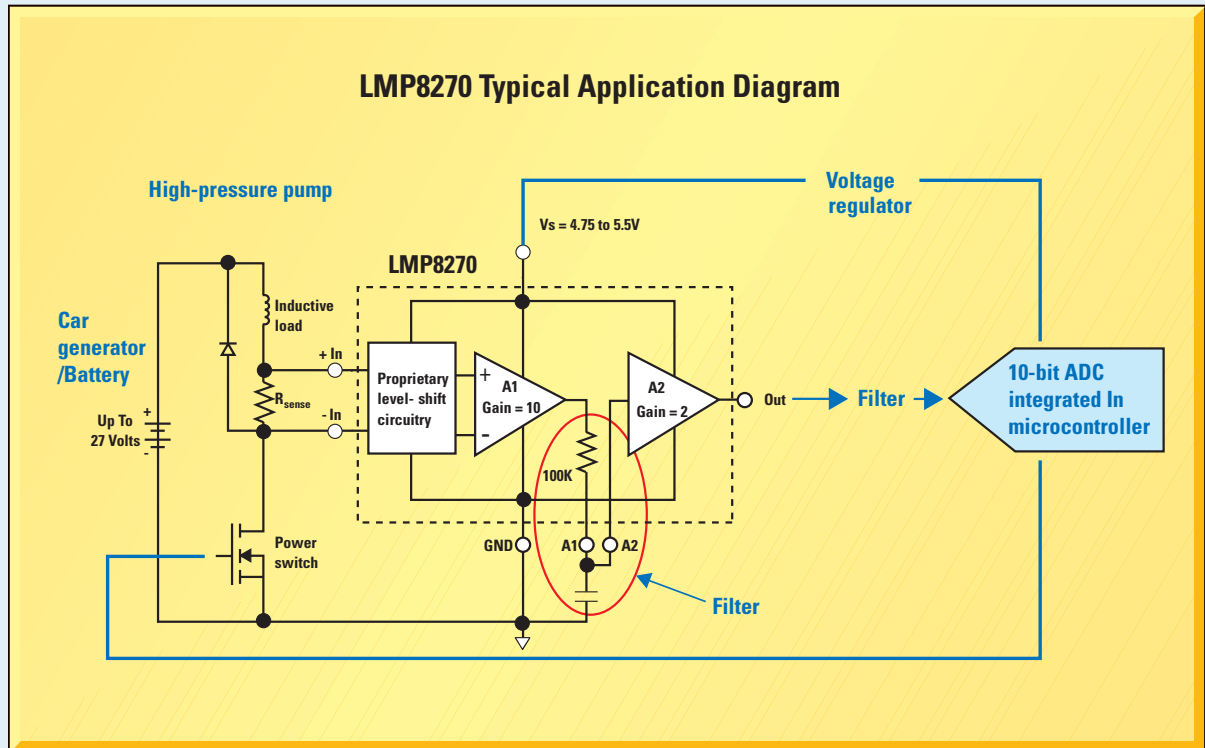Precision Current Measurement in Automotive and Industrial Environments



LMP8270 Key Features

- Input offset voltage 1 mV max
- TCVOs 15 $\mu\text{V}/^\circ\text{C}$ max
- CMRR 80 dB min
- Extended CMVR -2V to 36V
- Output voltage swing rail-to-rail
- Supply voltage 4.75V to 5.5V
- Temp range -40°C to 125°C
- Supply current 1 mA

System Benefits

- > • Initial system accuracy
- > • Continued accuracy over temperature
- > • Accurate under wide dynamic input currents
- > • Supports a wide range of input voltages
- > • Supports ADC input voltage levels
- > • Compatible with ADC voltage supplies
- > • Supports most automotive/industrial applications
- > • Minimum power consumption

Maximizing Signal-Path Performance

ADC121S101 whose supply voltage is also the V_{REF} have a PSRR value of 0 dB (no PSRR). The output drivers of the ADC itself have fast edge rates that cause the ADC to draw varying amounts of current. The noise introduced on the supply line can upset the ADC and other analog circuitry connected to it. A dual capacitor decoupling scheme with the smallest capacitor, typically 0.1 μF , placed within 1 cm of the supply pin and a 1.0 μF to 10 μF capacitor placed nearby is an excellent starting place for limiting supply noise. If analog and digital supply pins are connected to the same voltage source, a choke may be used between the pins. The choke will appear as a short at DC and a resistor at the higher frequencies where isolation is desired.

While good supply decoupling is always recommended, it is best to try and minimize the load capacitance seen by the output of the ADC so less current is required. Charging load capacitance causes noise spikes on the supply line while discharging load capacitance adds noise to the ADC substrate. There are several techniques to minimize load capacitance. The easiest way is to drive only a single device and place it as close as possible to the ADC output. It is also helpful to limit the effect of driving load capacitance by using series resistors, which limit the current required to charge or discharge the load capacitance and reduce the slew rate of the output. Limit the value of the series resistance to less than 100Ω to avoid violating the timing requirements of the digital circuitry. High-frequency systems may not tolerate the use of series resistors. Thus, it is essential that the driven circuitry be very close to the ADC output.

Maximizing Clock Integrity

Similar to ADC outputs, the ADC clock line can add noise to the system. The clock line should be treated as a transmission line when its length exceeds its rise time divided by 6 times the trace delay:

$$\text{line length} > \frac{t_{\text{rise}}}{6 \times t_{\text{delay}}}$$

Trace delay is typically 150 ps per inch on an FR4 board. Treating a trace as a transmission line involves making the trace a controlled impedance with proper termination. This will help avoid signal reflection

that can cause distortion. Distortion of the clock waveform leads to changes in the cycle-to-cycle clock period, better known as jitter. As the clock timing changes, there is variation in the exact point an ADC samples the waveform. With jitter, the ADC samples a point higher or lower on the signal than it ideally would. The net result of the time variation in the signal sampling point is noise. The maximum amount of jitter allowed for 1 LSB of error is $\frac{1}{2\pi f_{in}}$. For half an LSB of error, replace n with $n+1$.

Another technique for avoiding line reflection is line termination. There are two methods for terminating traces, near-end and far-end termination. Near-end termination requires a resistor in series with the line located close to the output of the signal source. The signal source resistance plus this series resistor should equal the characteristic impedance of the line. When near-end termination is insufficient, far-end termination is required. Far-end termination requires a resistor to ground at the clock input to the ADC. The terminating resistor is placed very close to the ADC input pin and the value should equal the characteristic impedance of the line.

When the clock source is required to drive multiple inputs, far-end termination alone may not be satisfactory. Far-end termination attenuates the signal level. Driving several inputs, each with a terminating resistor, may attenuate the clock voltage to the point that the logic thresholds are no longer met. For this instance, AC-termination is more appropriate. AC-termination requires a resistor in series with a capacitor to ground at the input to the ADC. This attenuates the AC component but not the DC component. For example, a signal that swings from 0 to 5V would remain centered around 2.5V in a system that is AC-terminated. The clock would still be attenuated but would be optimally centered between the CMOS trip points, allowing minimum signal swing to meet logic level-specifications.


Summary

By making smart design choices in buffering a sensing device, charging the switch-capacitive input of an ADC, and minimizing noise sources, the performance of the analog signal path is maximized. ■

Design Tools

INTRODUCING...

Signal-Path Design Tool

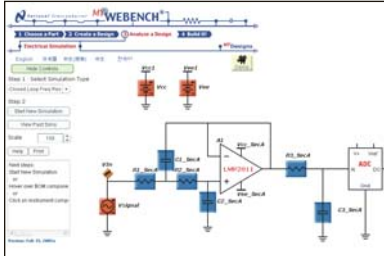

National's newest online innovation is the Signal-Path Designer toolset on the WEBENCH platform. This unique analog design tool allows you to synthesize an anti-aliasing filter, amplifier selection, and analog-to-digital converter combination that is precisely tailored to your needs.

Once you select a filter, it allows you to choose a matching ADC. Or, you can select an ADC first, then have the tool guide you to selecting the optimal filter to fit the ADC. This fast and easy tool allows you to select the best combination of components that are designed to work together and achieve your system goals for cost and performance.

Visit webench.national.com to start designing today.

WaveVision 4.0 Evaluation Board

Test and evaluate A/D converters with National's easy-to use WaveVision 4.0 evaluation board. Each evaluation board comes complete with USB and software.

Features and benefits:

- Plug-n-play ADC evaluation board
- USB interface to PC
- PC-based data capture
- Easy data capture and evaluation
- Highlighted harmonic and SFDR frequencies
- Easy waveform examination
- Produces and displays FFT plots
- Dynamic performance parameter readout with FFT
- Produces and displays histograms



National Semiconductor

2900 Semiconductor Drive
PO Box 58090
Santa Clara, CA 95052
1 800 272 9959

Visit our website at:
signalpath.national.com

For more information,
send email to:
new.feedback@nsc.com



Don't miss a single issue!



Subscribe now to receive email alerts when new issues are available:

signalpath.national.com/designer

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated