

## ***Design of UVLO for LM27313***

---

---

---

*Dheemanth Prabhu Hejamady; Dilip Mohol*

### **ABSTRACT**

This application note describes a novel and economic design of an undervoltage lockout (UVLO) for LM27313. The UVLO is designed to prevent switching current from increasing beyond the maximum rated limit, hence, preventing the device from overheating.

---

### **Contents**

1	Introduction .....	2
2	Need for Undervoltage Shutdown .....	2
3	Characteristics of the Shutdown Pin .....	3
4	UVLO Circuit .....	3
5	Conclusion .....	4
6	References .....	4

### **List of Figures**


1	Initial Boost Converter Design .....	2
2	UVLO Circuit .....	3
3	Final Circuit with UVLO .....	4

### **List of Tables**

1	Design Efficiency.....	2
2	Operating State at the Shutdown Pin .....	3

## 1 Introduction

The LM 27313 is a boost converter with a fixed switching frequency of 1.6 MHz. The design illustrated in [Figure 1](#) is for a mobile charging application. The charging is being performed with an output current of 500 mA.

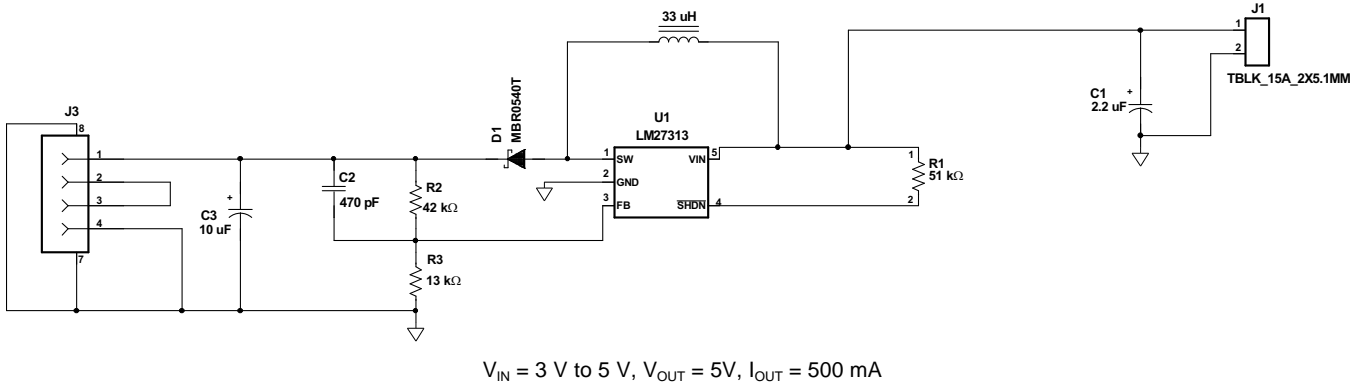

**Figure 1. Initial Boost Converter Design**

## 2 Need for Undervoltage Shutdown

Now observations on efficiency for variations in input voltages were made on this design and are listed in [Table 1](#).

**Table 1. Design Efficiency**

$V_{IN}$	$I_{IN}$	$V_{OUT}$	$I_{OUT}$	$P_{IN}$	$P_{OUT}$	Efficiency
2.989	0.99	4.799	0.398	2.95911	1.910002	64.546502
3.464	0.71	4.915	0.41	2.45944	2.01515	81.935319
3.766	0.62	4.922	0.411	2.33492	2.022942	86.6386
4.025	0.57	4.927	0.411	2.29425	2.024997	88.264008
4.234	0.54	4.931	0.411	2.28636	2.026641	88.640503

From the observations in [Table 1](#), it is evident that the input current increases above 700 mA for an input voltage below 3.5 V. Also, the efficiency of the same reduces rapidly to as low as 64.5% at  $V_{IN} = 3\text{ V}$ .

This increase in input current exceeds the current limit of the device (1.25 A – peak current) and causes the device to heat up, therefore, the IC must be shut down when the input voltage falls below 3.5 V. This can be achieved by utilizing the characteristics of the shutdown pin of LM27313.

### 3 Characteristics of the Shutdown Pin

The device's state of operation (ON/OFF) can be decided by the voltage at the shutdown pin ( $V_{SHDN}$ ).

Table 2 shows its characteristics:


**Table 2. Operating State at the Shutdown Pin**

$V_{SHDN}$	Operating State	Units
$\leq 0.5$	OFF	Volts
$\geq 1.5$	ON	Volts

Hence, a circuit is to be designed such that the  $V_{SHDN} \leq 0.5$  V for  $V_{IN} \leq 3.5$  V and  $V_{SHDN} > 1.5$  V for  $V_{IN} > 3.5$  V.

### 4 UVLO Circuit

Figure 2 shows a UVLO circuit.

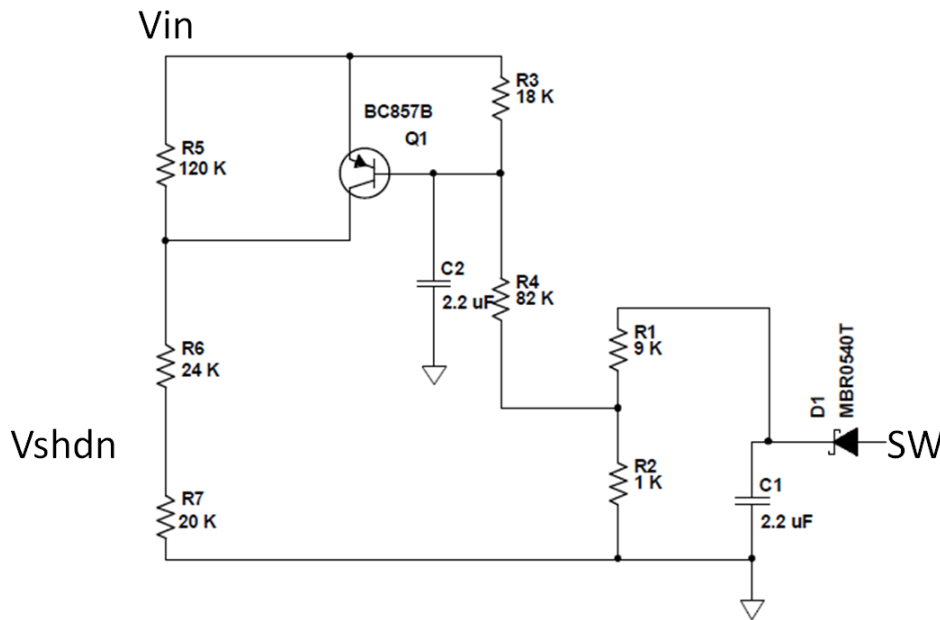

**Figure 2. UVLO Circuit**

#### 4.1 Circuit Behavior

When the voltage across  $V_{IN} \geq 3.6$  V, the transistor T1 turns on, hence bypassing resistor R5. This causes the voltage at the SHDN pin to go above 1.5 V, turning the IC on. But when  $V_{IN} \leq 3.5$  V, the device turns OFF.



## Revision History

<b>Changes from Original (April 2014) to A Revision</b>	<b>Page</b>
• Changed quality of image, improved position of values and units. ....	2
• Changed quality of image, improved position of values and units. ....	4
• Deleted TPS61241 and TPS61240 from the conclusion section .....	4
• Added LMR62421 and LM4510 to the conclusion section.....	4

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

## Revision History

<b>Changes from A Revision (April 2014) to B Revision</b>	<b>Page</b>
• Changed <i>UVLO Circuit</i> image, was missing $V_{in}$ and $V_{shdn}$ .....	3
• Changed equation in third step of the <i>Design Procedure</i> section.....	4
• Changed equation in fourth step of the <i>Design Procedure</i> section. ....	4

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)