

AN-1684 Saving Power in an AC-Coupled Amplifier Circuit

ABSTRACT

AC-coupled circuits are often used for single supply operation to bring the input voltage into the input range of the amplifier. This circuit topology can be used in AC smoke detectors or in AC proximity sensors.

Contents

1	Introduction	2
2	LPV531 Programmable Amplifier	2
3	Faster Settling Time With The LPV531 Amplifier	4
4	Conclusion	4

List of Figures

1	AC-Coupled Inverting Amplifier With Shutdown Pin.....	2
2	AC-Coupled Inverting Amplifier With the LPV531 Amplifier	3
3	Power-Mode Control ($R_{EXT} = 20\Omega$).	3
4	Output Signal With the LPV531 Op Amp	4
5	Output Signal With an Amplifier With Shutdown.....	4

1 Introduction

Figure 1 shows an AC-coupled inverting-amplifier circuit.

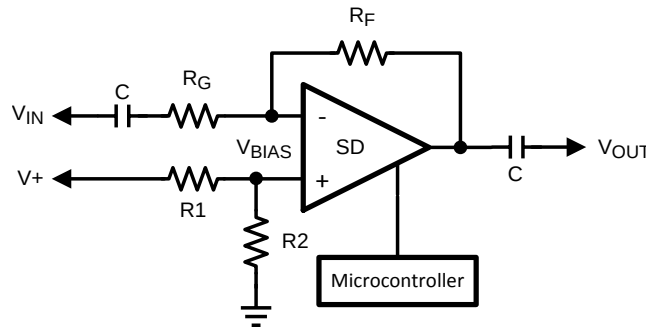


Figure 1. AC-Coupled Inverting Amplifier With Shutdown Pin

In the previous circuit, the non-DC input voltage is multiplied by the desired negative gain as shown in Equation 1:

$$V_{OUT} = -\frac{R_F}{R_G} \times V_{IN} + V_{BIAS} \quad (1)$$

The biasing voltage (V_{BIAS}) is half of the supply voltage ($V+$) and is added to the non-inverting input to bring the input voltage within the normal operating range of the amplifier. It also provides an off set for the output so that it is within its operating range.

In battery-operated circuits such as a smoke detector, an effective way to save power is to power down the circuit for a few seconds, and only sense smoke for a few microseconds. Usually when power saving is necessary, the conventional implementation is to power off the circuit by using an amplifier with a shutdown pin. This method has the disadvantage of allowing the coupling capacitors to discharge during the shutdown state. When the amplifier is turned on again, the circuit needs to reestablish the quiescent DC voltages. During this time, the amplifier's output is not usable because the output signal is a mixture of the amplified input signal and the charging voltage on the coupling capacitors. And the settling time can range from several microseconds to several milliseconds, depending on the resistor and capacitor values.

2 LPV531 Programmable Amplifier

The LPV531 programmable operational amplifier is ideal for AC-coupled circuits; its programmable-power mode allows the circuit to be kept active to maintain, in low-power mode, a quiescent charge on the coupling capacitor. The advantage of this method is the reduction of time needed to re-establish a quiescent operating point when the amplifier is switched to full-power mode.

The LPV531 op amp offers the capability to adjust the supply current, which is made possible by the ISEL control pin. The supply current is 40 times higher than the ISEL current. The maximum current that can flow from the ISEL pin is determined by an internal 110 mV reference voltage, and an 11 kΩ internal resistor. The supply current can be reduced by connecting an external resistance to the ISEL pin.

$$I_S = I_{\mu A} + 40 \times \frac{110 \text{ mV} - V_{CONTROL}}{R_{EXT} + 11 \text{ k}\Omega} \quad (2)$$

Figure 2 shows an example of how to control the supply current.

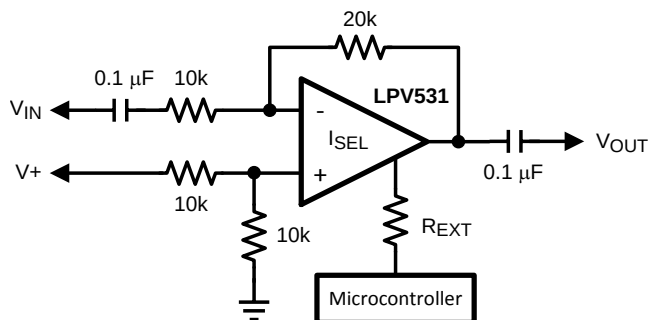


Figure 2. AC-Coupled Inverting Amplifier With the LPV531 Amplifier

The power mode of the amplifier can be controlled by the microcontroller. By increasing the control voltage up to 110 mV, the supply current of the amplifier will decrease. Therefore, it is possible to choose between a full-power mode and a low-power mode, while maintaining an active circuit. Figure 3 illustrates the relationship between the control voltage and the supply current of the amplifier.

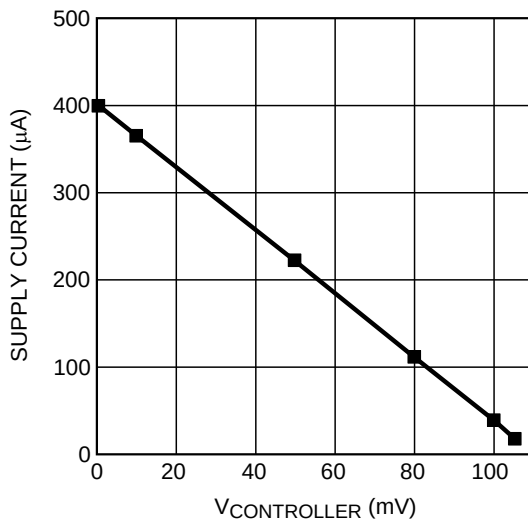


Figure 3. Power-Mode Control ($R_{EXT} = 20\Omega$).

3 Faster Settling Time With The LPV531 Amplifier

Comparing the results obtained with the LPV531 op amp and an amplifier with shutdown mode such as the LMV981 will further illustrate the much shorter settling time. Figure 4 shows the measurement obtained with the LPV531 amplifier.

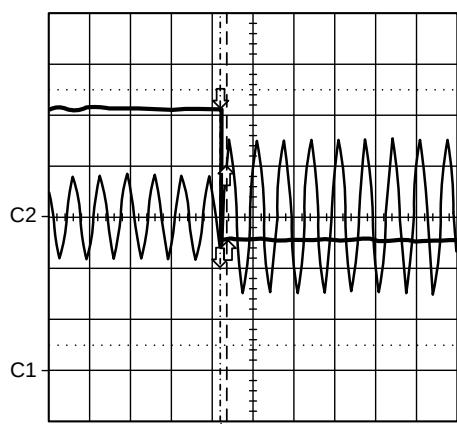


Figure 4. Output Signal With the LPV531 Op Amp

The yellow line is the control voltage. When the control voltage passes from high level to low, the amplifier switches to full-power mode. As Figure 3 and Figure 4 indicate, you can estimate that for a control voltage of 105 mV (low-power mode), the supply current is 20 μ A. For a control voltage of 55 mV (high-power mode), it is 200 μ A. The yellow signal is the output signal, where you can estimate that the settling time to obtain a stable signal is around 634 ns.

Figure 5 shows the results obtained with the LMV981 amplifier featuring a shutdown pin. The voltage applied on the shutdown pin is the yellow signal. To shut down the LMV981 amplifier, the turn-off voltage is 0.55 V. The turn-on voltage to enable the device is 1 V.

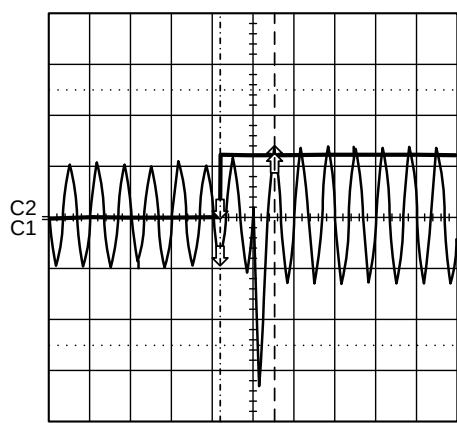


Figure 5. Output Signal With an Amplifier With Shutdown

The measurement illustrates the fact that the set-up time is really longer with this kind of circuit. The circuit needs approximately 6.7 μ s to be stable, which is ten times more than the circuit using the LPV531 op amp. During this settling time, the output signal is not usable.

4 Conclusion

This application report has shown that the LPV531 amplifier is ideal for use in AC-coupled applications to reduce the settling time of the output signal by maintaining a quiescent charge on the capacitors. For battery-operated applications that are non-AC coupled, the LMV981 amplifier is a very good choice. This amplifier can be supplied from 1.8 V to 5 V, has a supply current of only 100 μ A, and has rail-to-rail input and output.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com