
AN-2078 PCB Layout for Texas Instrument's SIMPLE SWITCHER® Power Modules

Donald Rhodes

ABSTRACT

This application report discusses the best PCB layout methods, practices and techniques to maximize the module's performance.

Contents

1	Thermal Design Recommendations	3
2	References	4

List of Figures

1	High Current Loops	2
2	High Current Loops on Demo Board	2
3	Circuit Designed Using SMS4.2.1	3

SIMPLE SWITCHER is a registered trademark of Texas Instruments.
All other trademarks are the property of their respective owners.

Texas Instrument's Simple Switcher® power modules offer an alternative to complex power designs and the PCB layout issues typically related to DC – DC converters. Nonetheless, there is still some engineering to be done when designing with and laying out these power modules.

When planning a power converter layout, the first thing to consider is the physical loop area of the two switched current loops. Even though these are primarily hidden from view in a power module it's important that we understand the current paths in each of the two loops since they do extend beyond the module. In Loop 1, shown in [Figure 1](#), the current flow originates at the energized input bypass capacitor, C_{in1} , and then continues through the internal high side MOSFET during its on-time, followed by the internal inductor and the output bypass capacitor, $CO1$, finally returning to the input bypass capacitor.

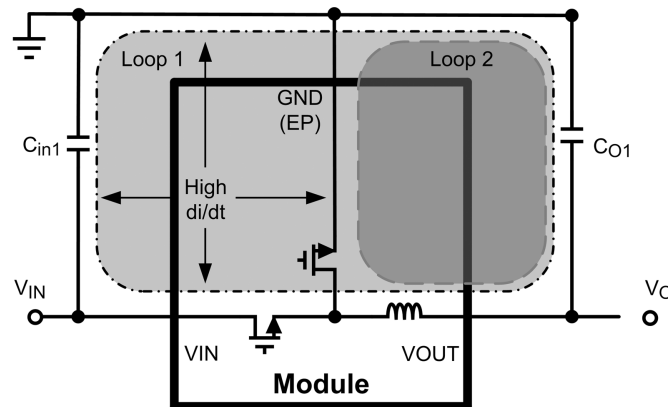


Figure 1. High Current Loops

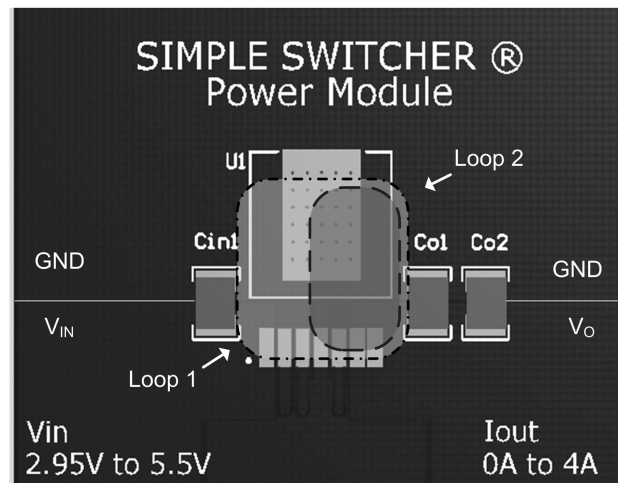


Figure 2. High Current Loops on Demo Board

Loop 2 is formed during the off-time of the internal high side MOSFET and the on-time of the low side MOSFET. The energy stored in the internal inductor flows through the output bypass capacitor and the low side MOSFET returning to GND as shown. The area where these two loops don't overlap, and including the boundary between the loops, is a high di/dt current area. The input bypass capacitor, C_{in1} plays a critical role in supplying high frequency currents to the converter and returning them to their source. The output bypass capacitor $Co1$ does not supply large ac current but does act as a high frequency filter for switching noise. For these reasons, the input and output capacitors should be placed as close as possible to their respective V_{IN} and V_{OUT} pins on the module. As shown in [Figure 1](#), make the traces between the bypass capacitors and their respective V_{IN} and V_{OUT} pins as short and wide as possible; thereby, minimizing the inductance of these connections.

There are two primary benefits in minimizing the inductance of the layout. The first benefit is improving part performance, by enhancing the transfer of energy to and from Cin1 and CO1, respectively. This will make sure the module has good high frequency bypassing to minimize inductive voltage spikes from the high di/dt currents. This minimizes noise and voltage stress to the device, ensuring proper operation. The second benefit is minimized EMI. A capacitor connected with less parasitic inductance will exhibit low impedance to much higher frequencies, and consequently reduce conducted emissions. Ceramic (X7R or X5R) or other low ESR type capacitors are recommended. Adding more input capacitance is only effective if additional caps are placed close to GND and VIN. The Simple Switcher power modules have inherently lower radiated and conducted EMI as a result of their design. However, maximum performance will be achieved by following the layout guidelines discussed in this application report

The routing of return currents are often overlooked and yet play an essential role in the optimization of any power design. Again, ground traces from Cin1 and CO1 should be kept as short and wide as possible, with a direct connection of the exposed pad (EP). This is especially important for the ground connection of the input cap Cin1 that carries large ac currents.

The ground connected pins of the module (including the EP), input and output capacitors, soft start cap and feedback resistor should all be connected to a return plane on your PCB. This return plane serves as a very low inductance current return path and a heat spreader as discussed in the following section.

The feedback resistors should also be placed as close as possible to the FB (feedback) pin of the module. Keeping the trace between the FB pin and the center tap of the feedback resistors as short as possible is important in minimizing potential noise pick-up on this high impedance node. The compensation components or feed forward capacitor, as applicable, should be placed as close as possible to the upper feedback resistor. For examples, see the PCB layout diagrams in the device-specific module data sheets.

For a layout example of the LMZ14203, see AN-2024 LMZ1420x / LMZ1200x Evaluation Board (SNVA422).

1 Thermal Design Recommendations

The electrical benefit derived from the compact layout of a module finds its tradeoff in thermal design. The same amount of power needs to be dissipated from a smaller space. With this in mind the Simple Switcher power modules were designed with a single large exposed pad on the back of the package that is electrically connected to ground. This pad provides very low thermal impedance from the internal mosfets, (where most of the heat is generated) to the printed circuit board. θ_{JC} , the thermal impedance from the junction of the semiconductor to the case for these devices is $1.9^{\circ}\text{C} / \text{W}$. An industry leading θ_{JC} is great, but if the thermal impedance from the case to the ambient air, θ_{CA} , is too large, then a low θ_{JC} means nothing! The heat becomes trapped at the exposed pad when no low resistance thermal path is offered to the ambient air. And what determines θ_{CA} ? The thermal resistance from the exposed pad to the ambient air is completely controlled by the design of the printed circuit board and any associated heat sinks.

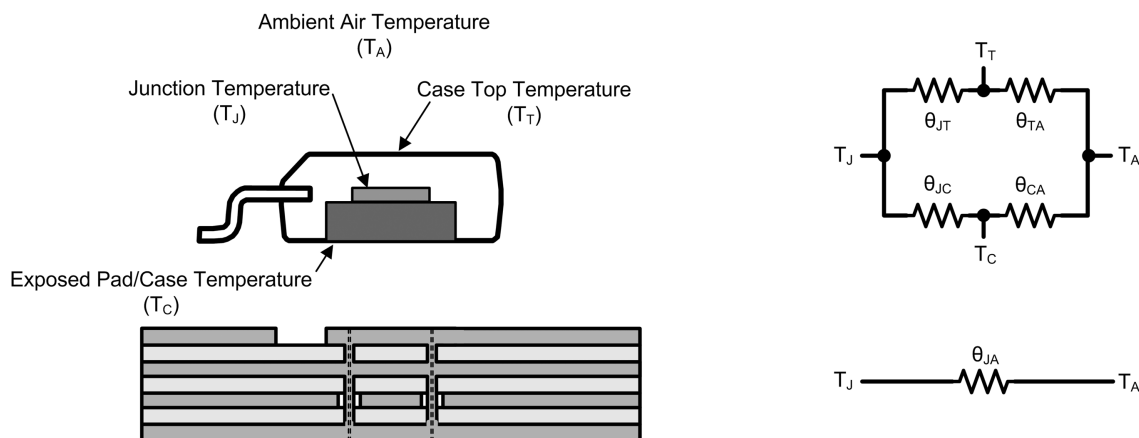


Figure 3. Circuit Designed Using SMS4.2.1

Let's quickly look at how to do a simple thermal design with a printed circuit board and no heat-sink. [Figure 3](#) illustrates the module and the printed circuit board as thermal resistances. Due to the relatively high thermal impedance between the junction and the case top, compared to the thermal impedance from the junction to the exposed die attach pad, the θ_{JT} thermal path can be ignored for our first pass estimate of the thermal resistance from the junction to the ambient air, θ_{JA} .

The first step in a thermal design is to determine how much power you need to dissipate. The power dissipated by a module, P_D , can be easily calculated from the efficiency graphs, η , published in the device-specific data sheet.

$$P_D = V_{OUT} \times I_{OUT} \times \left(\frac{1}{\eta} - 1\right) \quad (1)$$

We then use the design's temperature constraints, the maximum $T_{Ambient}$ and the rated junction temperature $T_{Junction}$, (125°C) to determine the required thermal resistance of the module mounted on a printed circuit board.

$$\theta_{JA} = \frac{T_{JUNCTION} - T_{AMBIENT}}{\text{Power Dissipation}} \quad (2)$$

Finally, you can use a greatly simplified approximation for the convective heat transfer from the surface of a printed circuit board (which has unbroken one-ounce copper heat-sinking on both the top and bottom layers and infinite thermal vias) to determine the board area required for heat sinking.

$$\begin{aligned} \text{Board Area (cm}^2\text{)} &\geq \frac{500 \frac{^\circ\text{C} \times \text{cm}^2}{\text{W}}}{\theta_{JA} - \theta_{JC}} \\ \text{Board Area (in}^2\text{)} &\geq \frac{77.5 \frac{^\circ\text{C} \times \text{in}^2}{\text{W}}}{\theta_{JA} - \theta_{JC}} \end{aligned} \quad (3)$$

This approximation of required PCB board area does not include the effect of thermal vias, which are used to transfer heat from the top layer metal, where the package connects to the PCB, to the bottom layer metal. The bottom layer is used as a second surface where convection can transfer heat away from the board. For the board area approximation to be effective, use at least 8-10 thermal vias. The thermal resistance for vias is approximated in [Equation 4](#).

$$\theta_{VIAS} \approx \frac{261 \frac{^\circ\text{C}}{\text{W}}}{\# \text{ of Thermal Vias}} \quad (4)$$

This approximation is for a typical 12 mil diameter through hole via with a 0.5 ounce copper sidewall. Use as many vias as will fit underneath the exposed pad using 1 to 1.5 mm spacing to form an array.

For further information, see *AN-2020 Thermal Design By Insight, Not Hindsight* ([SNVA419](#)) and *AN-2026 The Effect of PCB Design on the Thermal Performance of SIMPLE SWITCHER® Power Modules* ([SNVA424](#)).

Texas Instrument's Simple Switcher® power modules offer an alternative to complex power designs and the PCB layout issues typically related to DC – DC converters. While the layout headaches have been eliminated, there is still some engineering to be done to maximize the performance of the modules through good bypassing and thermal design.

2 References

- *LMZ14203*, see *AN-2024 LMZ1420x / LMZ1200x Evaluation Board* ([SNVA422](#))
- *AN-2020 Thermal Design By Insight, Not Hindsight* ([SNVA419](#))
- *AN-2026 The Effect of PCB Design on the Thermal Performance of SIMPLE SWITCHER® Power Modules* ([SNVA424](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com