



Tomi Koskela

ABSTRACT

This document details the design considerations of a power solution for the Semidrive X9P/X9U SoC (system-on-chip) power rails using the LP8756x-Q1, LP8752x-Q1, and LP8732-Q1 family power management ICs. Additional TPS74501-Q1 LDOs are used for the peripheral rails. This power solution assumes an input voltage of 5 V ($\pm 5\%$). If the system input voltage is higher, for example a car battery, a buck converter as a pre-regulator with high enough current capability should be used to generate a supply voltage of 5 V. Automotive qualified components are used for the power solution.

The LP875610B-Q1 has four buck converters configured to work as single 4-phase converter with maximum 16A load current for the core rail. LP87562R-Q1 is configured to work as 3-phase converter for the CPU rail and then additional single phase rail for the peripherals. LP87521S-Q1 has four buck converters configured to work as single 4-phase converter with maximum 10A load current for the GPU rail. LP875241J-Q1 is configured to work as four single phase converter for the peripheral rails. LP873248-Q1 is used for the safety power rails. These devices are OTP programmable, meaning default register values are set in TI production line to desired values for this platform without further need for customer to change settings through I²C bus. Full orderable part numbers for these OTP spins are LP875610BRNFRQ1, LP87562RRNFRQ1, LP87521SRNFRQ1, LP875241JRNFRQ1, and LP873248RHDRQ1. See the Technical Reference Manuals for the specific part numbers for more details on the OTP settings.

This power solution is an example how Semidrive X9P/U required rails can be powered with TI PMICs. Sequencing is handled through programmable startup and or shutdown delays of the PMICs and GPIOs and it only requires a single Enable signal from the system to initiate the sequencing. This power solution is possible to customize and optimize based on the actual use case regarding current requirements and used peripherals.

Table of Contents

1 Design Parameters	2
2 Power Solution	3
3 Sequencing	5
3.1 Startup, Application Processor.....	5
3.2 Shutdown, Application Processor.....	6
3.3 Startup, Safety.....	6
3.4 Shutdown, Safety.....	7
3.5 Startup, RTC.....	7
3.6 Shutdown, RTC.....	8
4 Schematic	9
5 Software Drivers	13
6 Recommended External Components	14
7 Measurements	15
8 Summary	16
9 References	17

List of Figures

Figure 2-1. Semidrive X9P/U AP Power Block Diagram.....	3
Figure 2-2. Semidrive X9P/U Safety Power Block Diagram.....	4
Figure 2-3. Semidrive X9P/U RTC Power Block Diagram.....	4
Figure 3-1. Application Processor Power Startup Timing Diagram.....	5
Figure 3-2. Application Processor Shutdown Timing Diagram.....	6

Figure 3-3. Safety Power Startup Timing Diagram.....	6
Figure 3-4. Safety Shutdown Timing Diagram.....	7
Figure 3-5. RTC Power Startup Timing Diagram.....	7
Figure 3-6. RTC Shutdown Timing Diagram.....	8
Figure 4-1. X9P/X9U Top Level Schematic.....	9
Figure 4-2. LP875610B-Q1 Schematic.....	10
Figure 4-3. LP87562R-Q1 Schematic.....	10
Figure 4-4. LP87521S-Q1 Schematic.....	11
Figure 4-5. LP875241J-Q1 Schematic.....	11
Figure 4-6. LP873248-Q1 Schematic.....	11
Figure 4-7. TPS74501-Q1 Schematic.....	12
Figure 7-1. LP873248-Q1 Efficiency with Vin = 5 V, 25°C.....	15

List of Tables

Table 1-1. Design Parameters.....	2
Table 6-1. Bill of Materials.....	14

Trademarks

All trademarks are the property of their respective owners.

1 Design Parameters

[Table 1-1](#) shows the power rails, load requirements and [Measurements](#) shows typical performance data.

Table 1-1. Design Parameters

VOLTAGE (V)	RAIL NAME	MAX LOAD (mA)	LOAD CAPABILITY (mA)	SOURCE	Domain
1.8	VDD_RTC_1V8	< 500	500	TPS74501-Q1 (LDO)	RTC
0.8	VDDIO_RTC_0V8	< 500	500	TPS74501-Q1 (LDO)	RTC
0.8	VSFT_0V8	1500	2000	LP873248-Q1 Buck0	Safety
1.8	VDDA_SAF	720	2000	LP873248-Q1 Buck1	Safety
3.3	VDDIO_GPIO(1)	< 300	300	LP873248-Q1 LDO0	Safety
3.3	VDDIO_GPIO(2)	< 300	300	LP873248-Q1 LDO1	Safety
0.8	VDD_AP_0V8, VDD_DRAM_0V8	16000	16000	LP875610B-Q1 B0+B1+B2+B3	Application Processor
0.85	VDD_CPU_0V8	12000	12000	LP87562R-Q1 B0+B1+B2	Application Processor
0.8	VDD_MIPI_0V8, VDD_PCIE_0V8, VDD_USB	900	4000	LP87562R-Q1 B3	Application Processor
0.85	VDD_GPU_0V8	10000	10000	LP87521S-Q1 B0+B1+B2+B3	Application Processor
1.8	VDDA_1V8	2280	2500	LP875241J-Q1 B0	Application Processor
3.3	VDDH_3V3	1200	2500	LP875241J-Q1 B1	Application Processor
1.1	VDDQ_DRAM	3000	4000	LP875241J-Q1 B2	Application Processor
0.6	VDDL_P_DRAM	600	1000	LP875241J-Q1 B3	Application Processor
1.8	VDD_LP4_1V8	200	500	TPS74501-Q1 (LDO)	Application Processor

2 Power Solution

Figure 2-1 shows power tree with LP875610B-Q1, LP87562R-Q1, LP87521S-Q1, LP875241J-Q1, and TPS74501-Q1 devices powering the X9P/U application processor rails.

Figure 2-2 shows power tree with LP873248-Q1 PMIC powering the X9P/U safety rails.

Figure 2-3 shows power tree with two TPS74501-Q1 LDOs powering the X9P/U RTC rails.

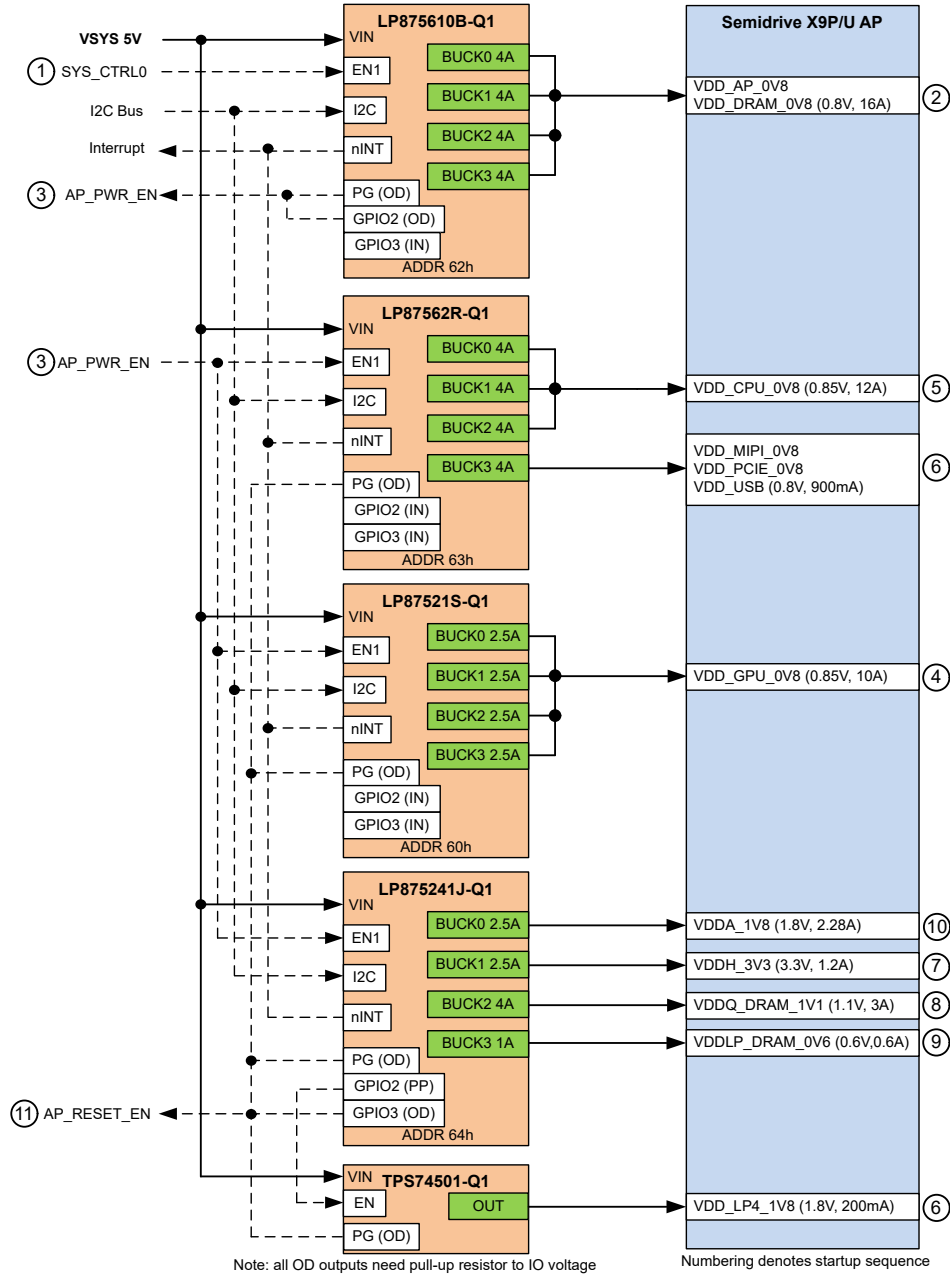


Figure 2-1. Semidrive X9P/U AP Power Block Diagram

Main features:

- 5 V supplied from pre-regulator
- After the devices are powered, the microcontroller or preregulator PGOOD can set the SYS_CTRL0 high to initiate the startup sequence for application processor rails.
- Startup and or shutdown delays are controlled internally in the LP875x-Q1 sequencers and discrete LDO is controlled with PMIC GPIO with pre-set delays.

- I²C can be used to read status registers and reset interrupts.
- PMIC devices have dedicated I²C address so they can share the same I²C bus.
- Combined PG signal from LP875x-Q1 and TPS74501-Q1 act as AP_RESET_EN signal for the SoC. Any failure on the rail voltages will keep the SoC in reset state until fault is cleared.

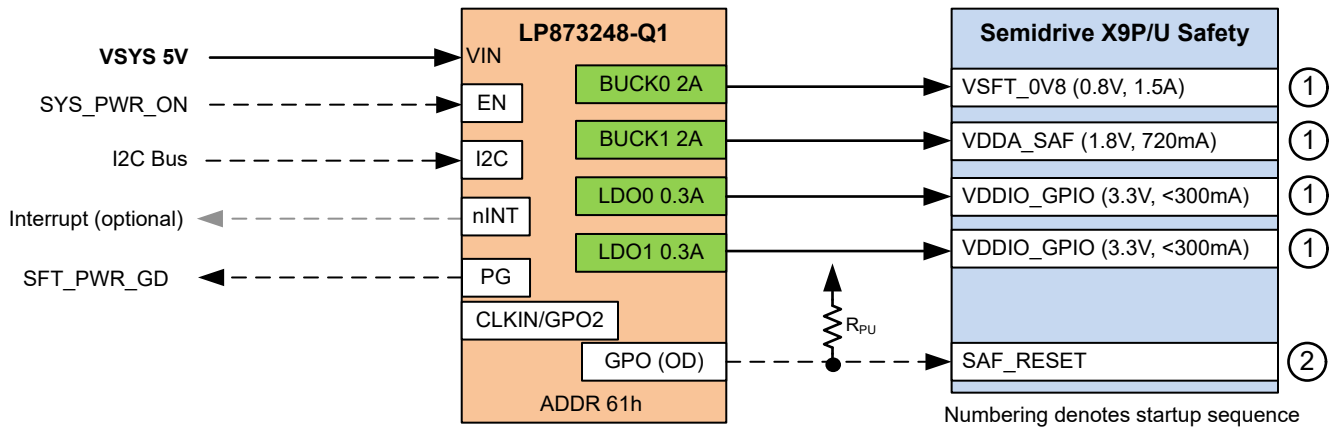


Figure 2-2. Semidrive X9P/U Safety Power Block Diagram

Main features:

- 5 V supplied from pre-regulator
- After the devices are powered, the microcontroller or preregulator PGOOD can set the SYS_PWR_ON high to initiate the startup sequence for safety rails.
- Startup delays are controlled internally in the LP873248-Q1 sequencer.
- I²C can be used to read status registers and reset interrupts.
- All PMIC devices in this system have dedicated I²C address so they can share the same I²C bus.
- GPO signal from LP873248-Q1 act as SAF_RESET signal for the SoC. SFT_PWR_GD signal can be used for fault indication, or combined with the SAF_RESET signal (both outputs are open-drain).

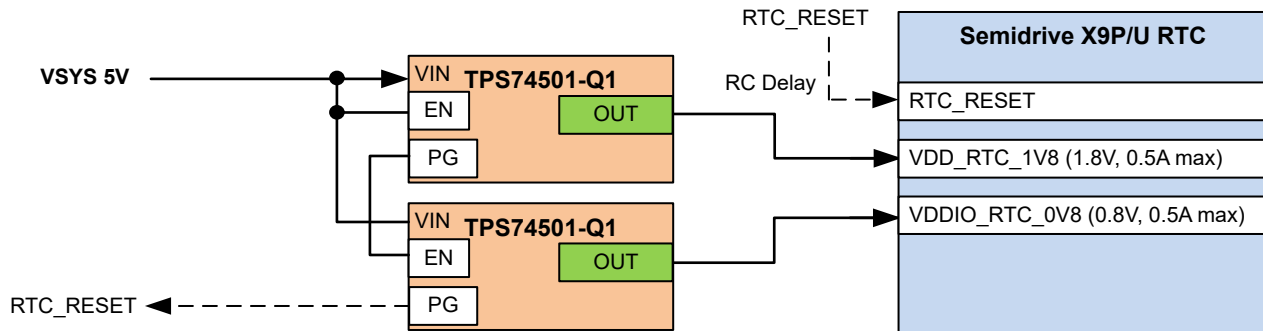


Figure 2-3. Semidrive X9P/U RTC Power Block Diagram

Main features:

- 5 V supplied from pre-regulator
- VDD_RTC_1V8 supply starts as soon as supply voltage reaches TPS74501-Q1 UVLO rising threshold (1.33-V typ).
- VDDIO_RTC_0V8 starts when VDD_RTC_1V8 has reached the target voltage and PG is set high.
- When VDDIO_RTC_0V8 has reached the target voltage level the PG is set high. Additional RC delay is used for the RTC_RESET signal.

3 Sequencing

3.1 Startup, Application Processor

Figure 3-1 shows startup timing of the power rails and corresponding signals.

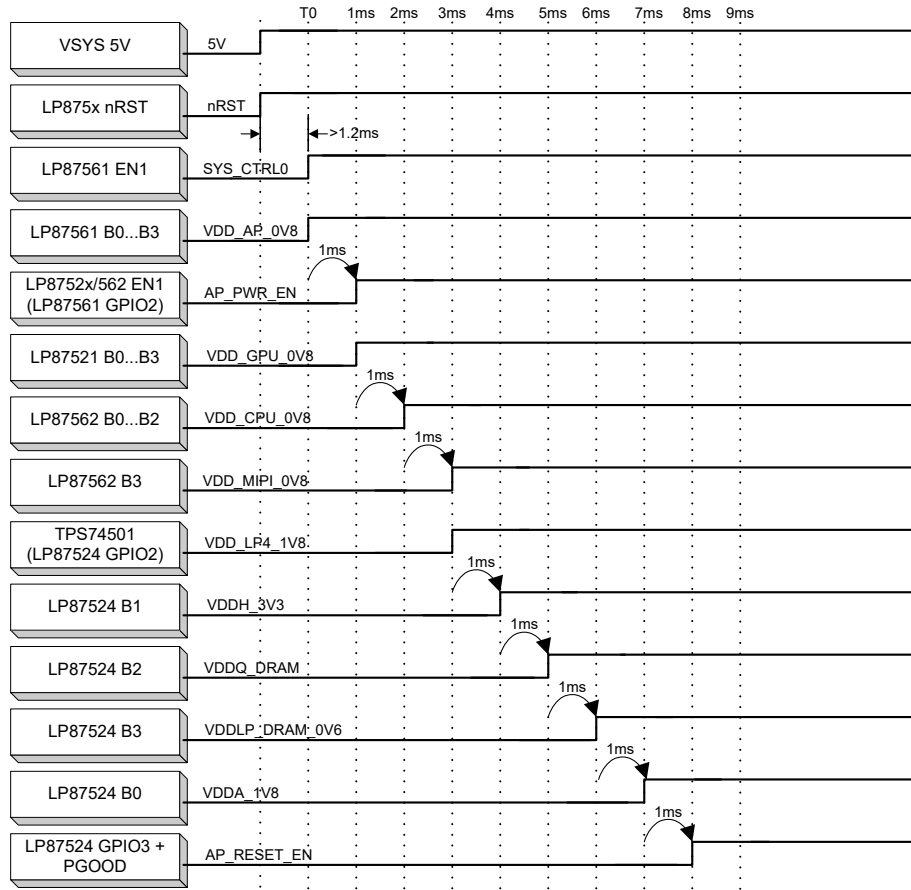


Figure 3-1. Application Processor Power Startup Timing Diagram

3.2 Shutdown, Application Processor

Figure 3-2 shows an example of shutdown timing of the application processor power rails and corresponding signals.

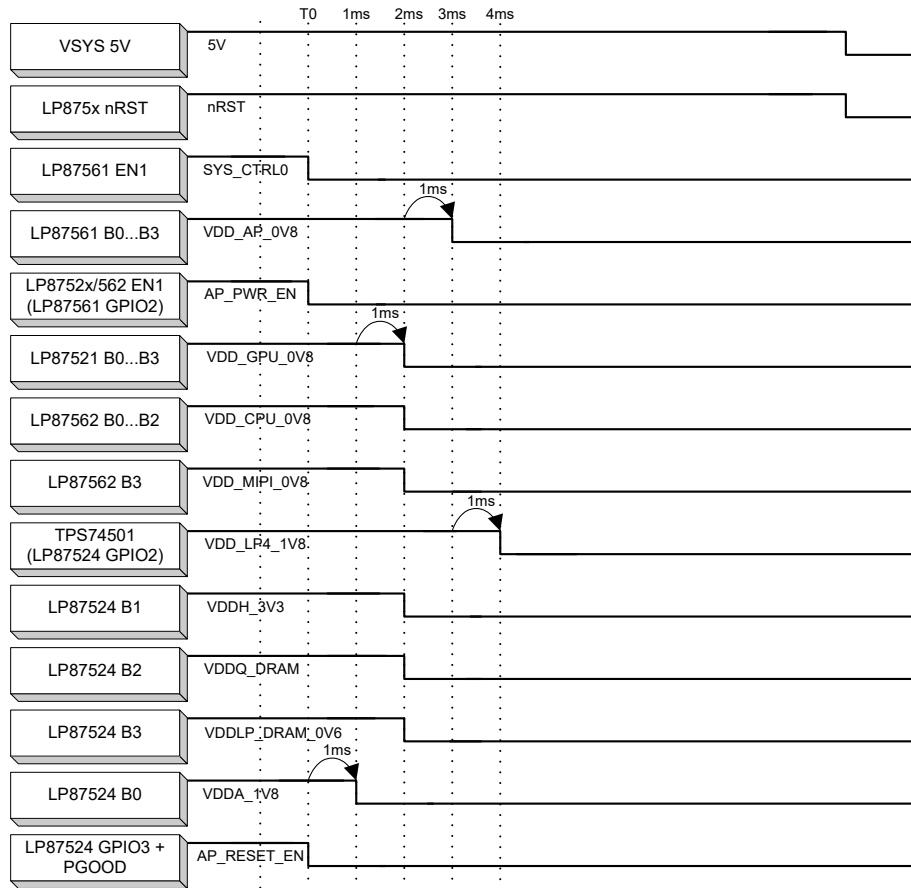


Figure 3-2. Application Processor Shutdown Timing Diagram

3.3 Startup, Safety

Figure 3-3 shows startup timing of the safety power rails and corresponding signals.

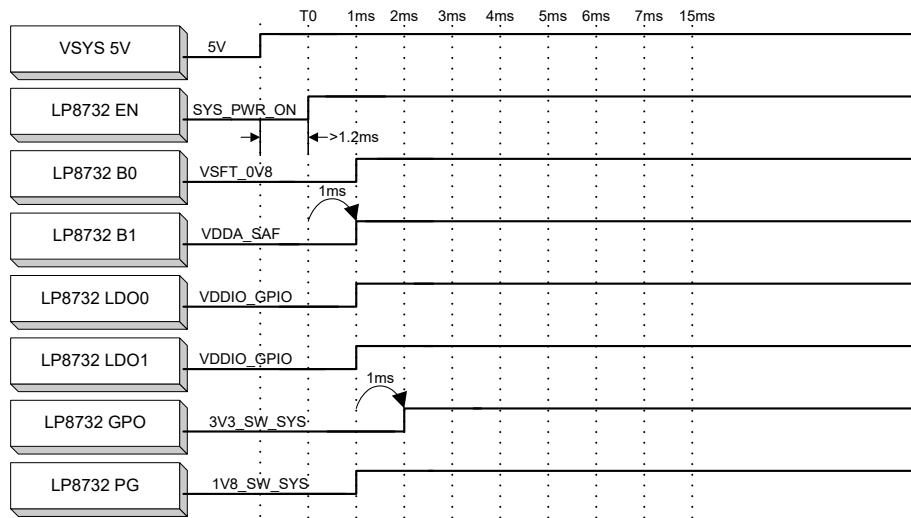


Figure 3-3. Safety Power Startup Timing Diagram

3.4 Shutdown, Safety

Figure 3-4 shows an example of shutdown timing of the safety power rails and corresponding signals.

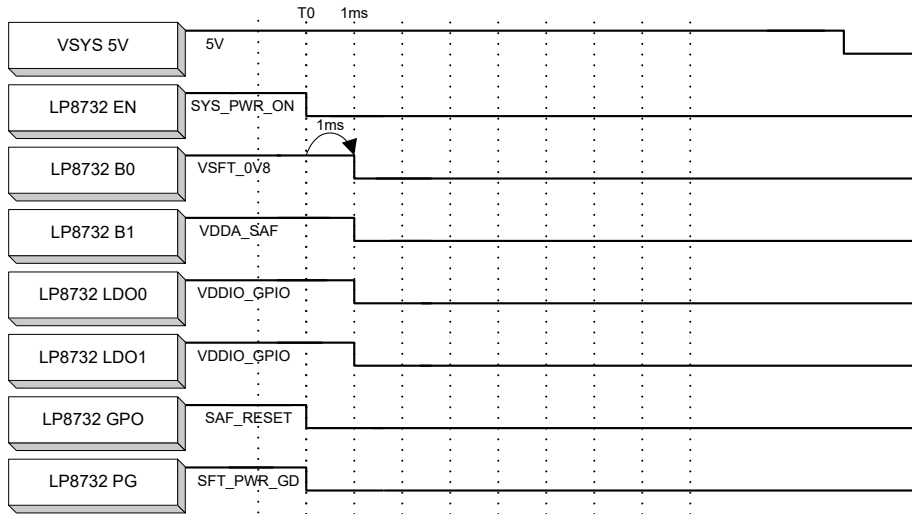


Figure 3-4. Safety Shutdown Timing Diagram

3.5 Startup, RTC

Figure 3-1 shows startup timing of the RTC power rails and corresponding signals.

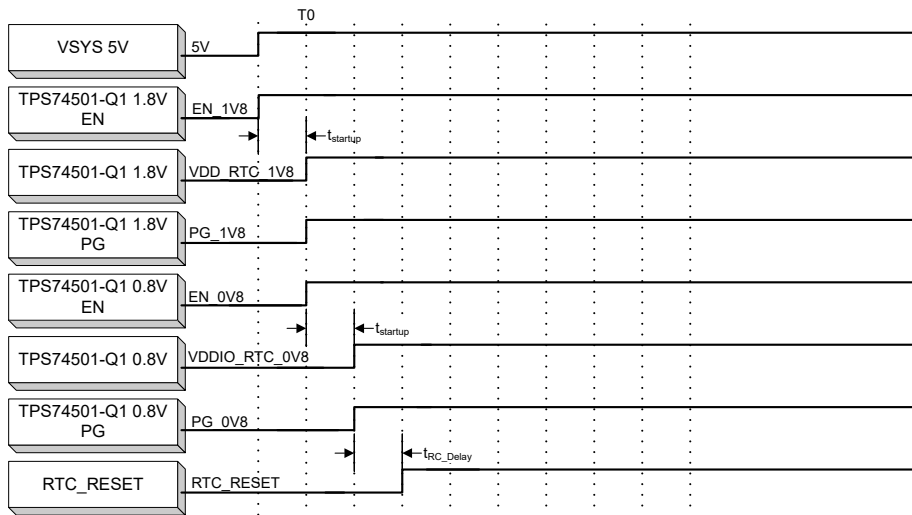


Figure 3-5. RTC Power Startup Timing Diagram

3.6 Shutdown, RTC

Figure 3-2 shows an example of shutdown timing of the RTC power rails and corresponding signals.

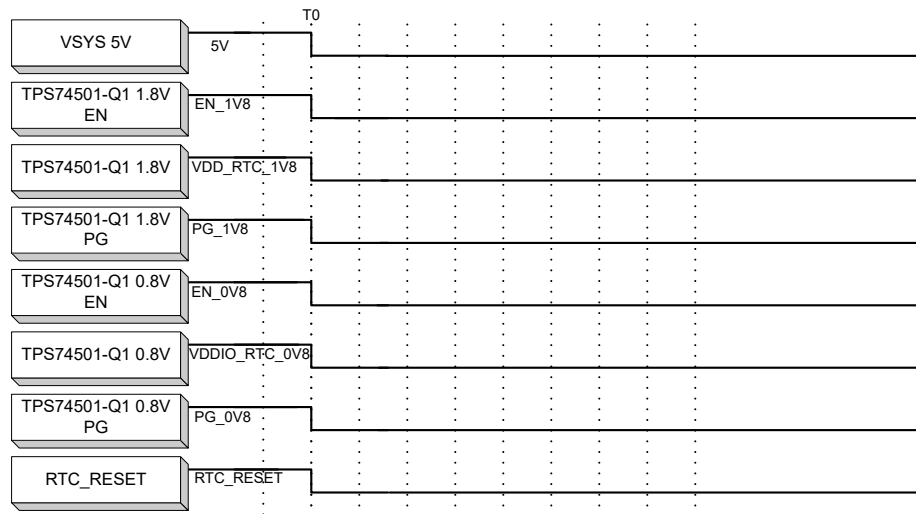


Figure 3-6. RTC Shutdown Timing Diagram

4 Schematic

Figure 4-1 through Figure 4-7 show the Semidrive X9P/X9U power tree schematic with critical components.

For guidance on layout, please refer to the data sheet application section and EVM user guide for the particular device.

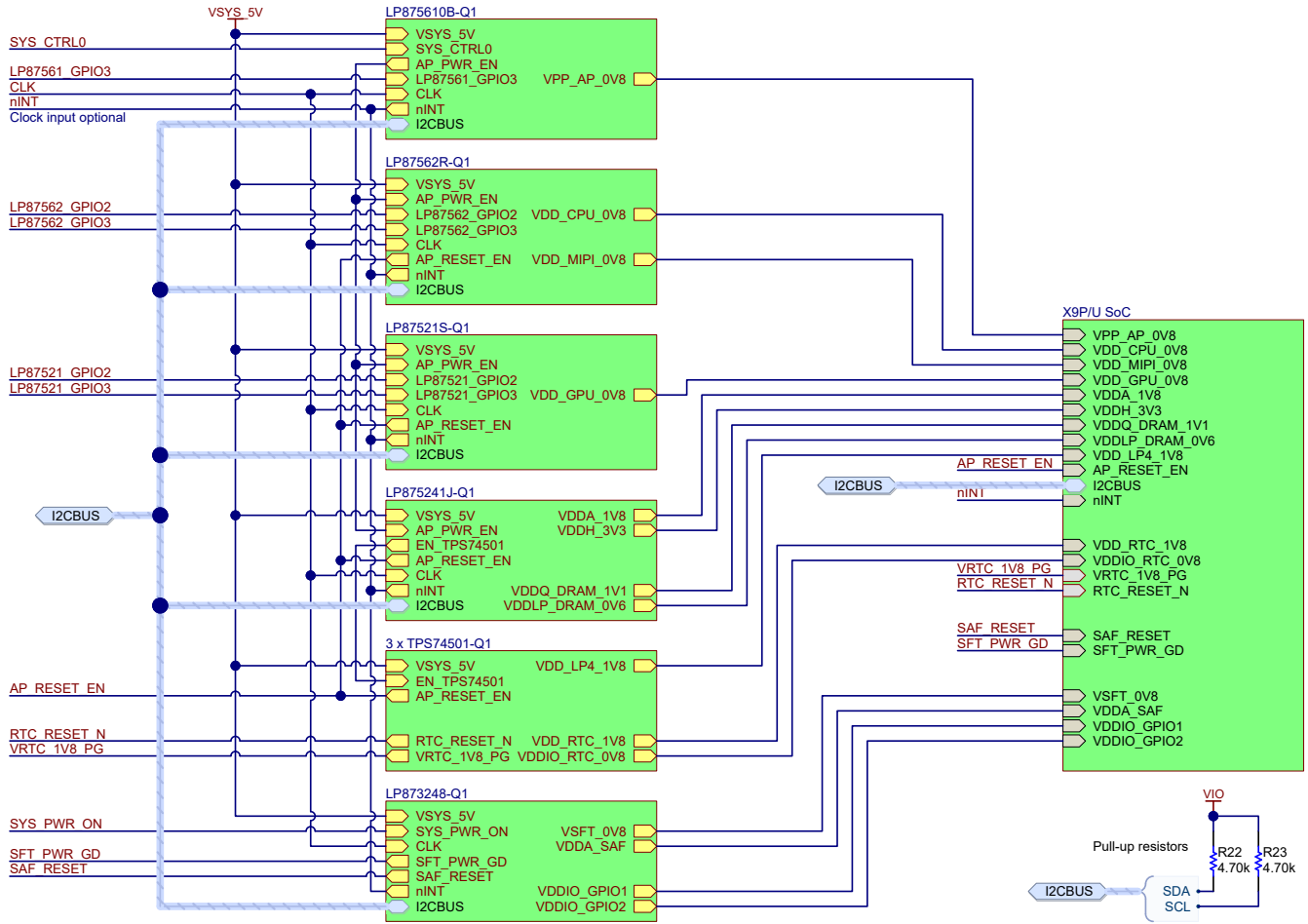


Figure 4-1. X9P/X9U Top Level Schematic

 


Figure 4-2. LP875610B-Q1 Schematic

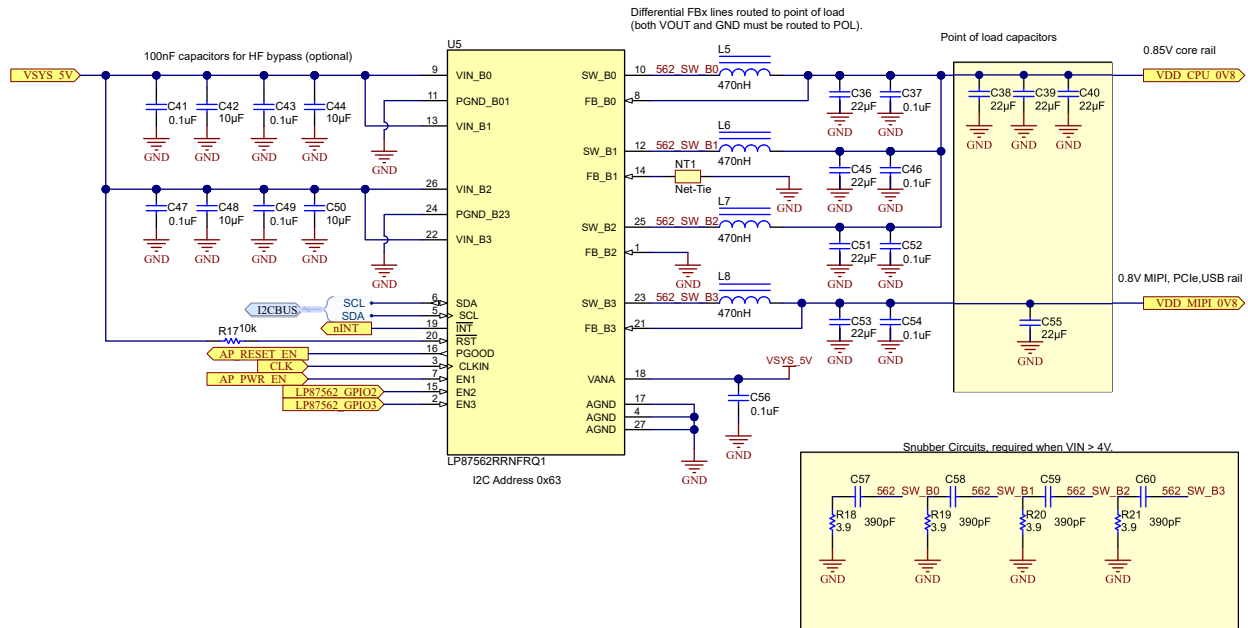


Figure 4-3. LP87562R-Q1 Schematic

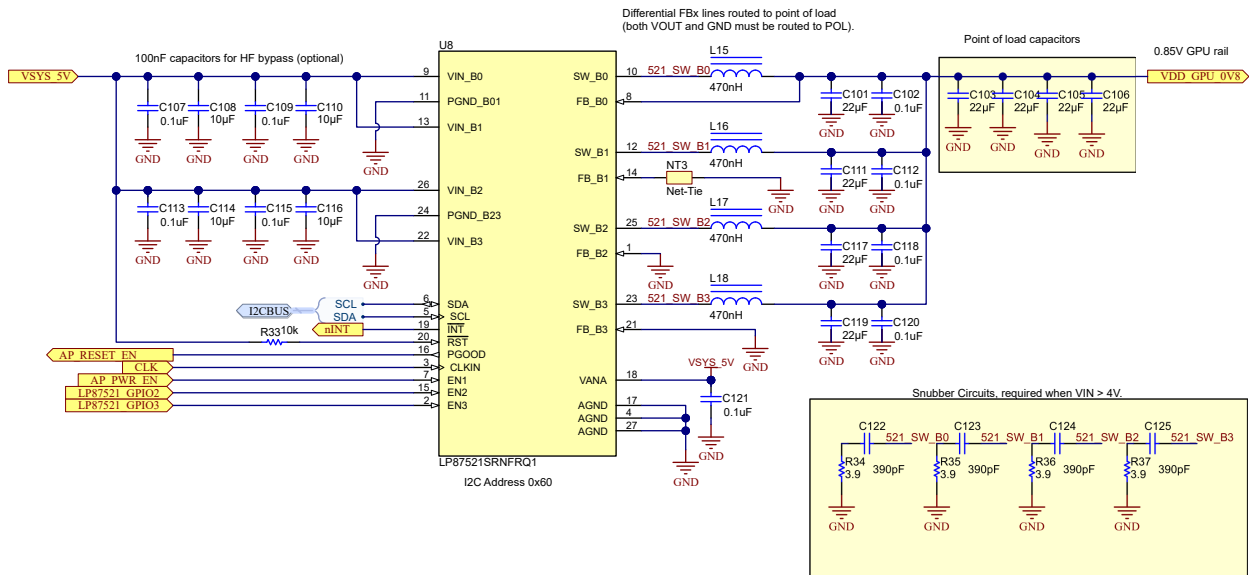


Figure 4-4. LP87521S-Q1 Schematic

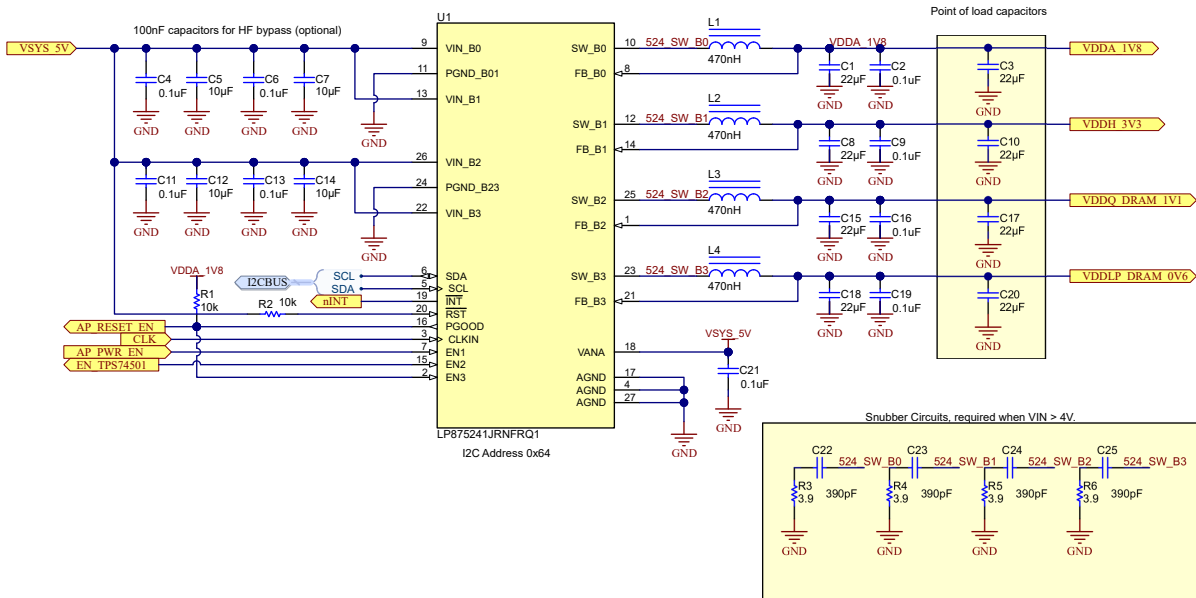


Figure 4-5. LP875241J-Q1 Schematic

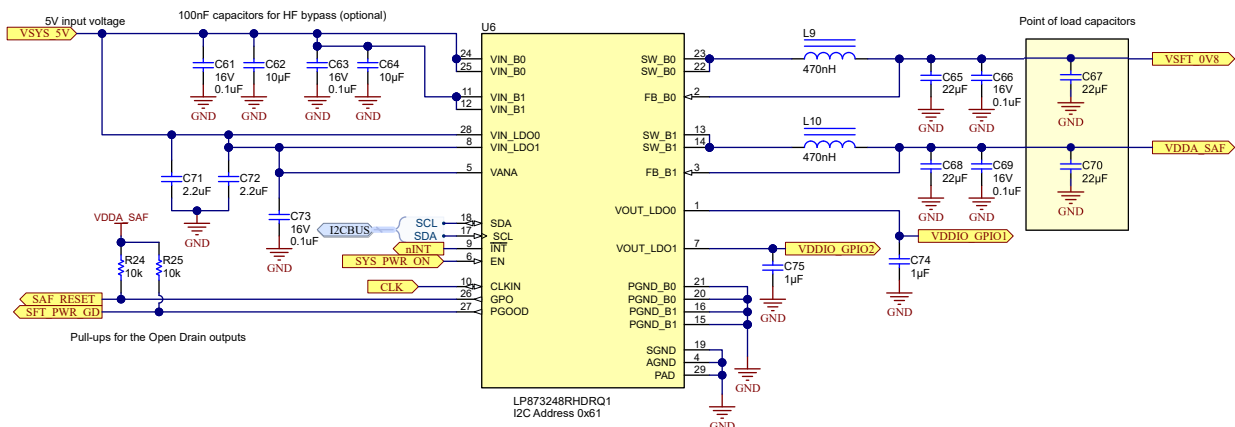


Figure 4-6. LP873248R-Q1 Schematic

 


Figure 4-7. TPS74501-Q1 Schematic

5 Software Drivers

This solution supports control through I²C bus.

Linux drivers for the LP875x-Q1 and LP8732-Q1 are available in public git repository. These can be used to help integrate the LP875x-Q1 / LP8732-Q1 control to system software:

LP8756x-Q1

- <https://github.com/torvalds/linux/blob/master/drivers/mfd/lp87565.c>
- <https://github.com/torvalds/linux/blob/master/drivers/regulator/lp87565-regulator.c>
- <https://github.com/torvalds/linux/blob/master/drivers/gpio/gpio-lp87565.c>

LP8732-Q1

- <https://github.com/torvalds/linux/blob/master/drivers/mfd/lp873x.c>
- <https://github.com/torvalds/linux/blob/master/drivers/regulator/lp873x-regulator.c>
- <https://github.com/torvalds/linux/blob/master/drivers/gpio/gpio-lp873x.c>

Note: Every header file is in the *include* folder starting from the root directory. So once in *include folder*, the user can navigate to the relevant header file. For example, the LP87565.h file: <https://github.com/torvalds/linux/blob/master/include/linux/mfd/lp87565.h>.

6 Recommended External Components

Table 6-1 shows the recommended external components to use in this solution with the LP8756x-Q1, LP8752x-Q1, LP873248-Q1, and TPS74501-Q1. It also shows the total solution size, including the PMIC device and the external components.

Table 6-1. Bill of Materials

COUNT	VENDOR	PART NUMBER	SYSTEM COMPONENT	W (mm)	L (mm)	H (mm)	UNIT AREA ⁽¹⁾	TOTAL BOARD AREA ⁽¹⁾
4	TI	LP875x-Q1	Configurable 4-phase Buck	4.00	4.50	0.90	27.50	110.00
16	Murata	DFE252012PD-R47M	LP875x Inductor 0.47 μ H, I _{max} 4.0A, R _{dc} typ 21mOhm	2.50	2.00	1.20	10.50	168.00
16	Murata	GCM21BR71A106KE22	LP875x SMPS Input Capacitor 10 μ F, 10 V, 10%	2.00	1.25	1.25	6.75	108.00
32	Murata	GCM21BD70J226ME35	LP875x SMPS Output Capacitor 22 μ F, 10 V, 10%	2.00	1.25	1.25	6.75	216.00
4	Murata	GCM155R71C104KA55D	LP875x Input Capacitor 0.1 μ F, 16 V, 10%	1.00	0.50	0.50	3.00	12.00
16	TDK	CGA2B2C0G1H391J050BA	LP875x Snubber capacitor, 390 pF	1.00	0.50	0.50	3.00	48.00
16	Vishay-Dale	CRCW04023R90JNED	LP875x Snubber resistor, 3R9	1.00	0.50	0.50	3.00	48.00
1	TI	LP8732-Q1	Configurable 2 Bucks and 2 LDOs	5.00	5.00	0.90	36.00	36.00
2	Murata	DFE252012PD-R47M	LP8732-Q1 Inductor 0.47 μ H, I _{max} 4.0 A, R _{dc} typ 21mOhm	2.50	2.00	1.20	10.50	21.00
2	Murata	GCM21BR71A106KE22	LP8732-Q1 SMPS Input Capacitor 10 μ F, 10 V, 10%	2.00	1.25	1.25	6.75	13.50
4	Murata	GCM21BD70J226ME35	LP8732-Q1 SMPS Output Capacitor 22 μ F, 10 V, 10%	2.00	1.25	1.25	6.75	27.00
2	Murata	GRT155C71A225KE13	LP8732-Q1 LDO Input Capacitor 2.2 μ F, 6.3 V, 10%	1.00	0.50	0.50	3.00	6.00
2	Murata	GCM155C71A105KE38	LP8732-Q1 LDO Output Capacitor 1.0 μ F, 16 V, 10%	1.00	0.50	0.50	3.00	6.00
1	Murata	GCM155R71C104KA55D	LP8732-Q1 Input Capacitor 0.1 μ F, 16 V, 10%	1.00	0.50	0.50	3.00	3.00
3	TI	TPS74501-Q1	Low Dropout Regulator	2.00	2.00	1.00	9.00	27.00
3	Murata	GCM188R71C105KA64D	LDO Input Capacitor 1 μ F	1.00	0.50	0.50	3.00	9.00
3	Murata	GRT155C71A225KE13	LDO Output Capacitor 2.2 μ F, 6.3 V, 10%	1.00	0.50	0.50	3.00	9.00
6			LDO Set resistors	1.00	0.50	0.50	3.00	18.00
3	TDK	CGA2B3X7R1H103K050BB	LDO CFF Capacitor 10 nF, 50 V, 10%	1.00	0.50	0.50	3.00	9.00
TOTAL								894.50 mm ²
Routing area calculated with 0.3 routing factor								383.36 mm ²
Total area								1277.86 mm ²

(1) Assuming 1 mm keep-out around each component, and multiplying by component count

7 Measurements

Test data can be found in the Application Curves section of the following data sheets:

- [LP8756x-Q1 16A Buck Converter With Integrated Switches](#)
- [LP8752x-Q1 10-A Buck Converter With Integrated Switches](#)
- [LP8732xx-Q1 Dual High-Current Buck Converter and Dual Linear Regulator](#)
- [TPS745-Q1 500-mA LDO With Power-Good in Small Wettable Flank WSON Packages](#)

Additional bench test data for efficiency in specific conditions for this power tree can be seen in this section. TI PMIC Efficiency Estimation Tool (PEET) can be used also for calculating efficiency and thermal performance: [PEET-GUI](#).

Measurements were taken on the [LP87320Q1EVM](#) with default components.

 


Figure 7-1. LP873248-Q1 Efficiency with Vin = 5 V, 25°C

8 Summary

With this presented solution with the LP875610B-Q1, LP87562R-Q1, LP87521S-Q1, LP875241J-Q1, and LP873248-Q1 PMICs + discrete LDOs, it is possible to meet power requirements for Semidrive X9P/X9U application processor while maintaining good efficiency. Sequencing is handled in PMICs and only one EN signal is needed from the controller. Solution is compact due to minimum number of external components. I²C control allows diagnostic and PMIC control if needed.

9 References

See these references for additional information:

1. Texas Instruments, [LP8756x-Q1 16A Buck Converter With Integrated Switches](#) data sheet.
2. Texas Instruments, [LP875610B-Q1 Technical Reference Manual](#),
3. Texas Instruments, [LP87562R-Q1 Technical Reference Manual](#),
4. Texas Instruments, [LP8752x-Q1 10-A Buck Converter With Integrated Switches](#) data sheet.
5. Texas Instruments, [LP87521S-Q1 Technical Reference Manual](#).
6. Texas Instruments, [LP875241J-Q1 Technical Reference Manual](#).
7. Texas Instruments, [LP8732xx-Q1 Dual High-Current Buck Converter and Dual Linear Regulator](#) data sheet.
8. Texas Instruments, [LP873248-Q1 Technical Reference Manual](#) .
9. Texas Instruments, [TPS745-Q1 500-mA LDO With Power-Good in Small Wettable Flank WSON Packages](#) data sheet.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated