

TLC555-Q1 Used as a Positive and Negative Charge Pump

Mahmoud Harmouch
Mixed Signal Automotive

ABSTRACT

This application report describes an alternative use of the TLC555-Q1 device as a charge pump. The square-wave output switching between the supply voltage and GND with few additional capacitors and diodes makes the device suitable for generating a positive or negative voltage multiplier. Using the TLC555-Q1 device as a charge pump is a cheap and easy solution for doubling, tripling, or inverting the supply voltage.

A charge pump can be used in automotive applications requiring reverse battery protection. A diode can also be used for battery protection; however, it causes a voltage drop and lowers efficiency. The charge pump is also capable of driving a MOSFET transistor with low drain-to-source on resistance.

Charge pumps can be used in a nonsynchronous rectifier when in low dropout mode to cause a high output ripple with light load. The charge-pump output can be connected to the BOOT pin for providing the necessary voltage to drive the upper-pass transistor.

Contents

1	Block Diagram Description	2
2	Setup for Positive Charge Pump	2
	2.1 Power Up and Power Down	3
	2.2 Characterization.....	3
3	Setup for Negative Charge Pump	4
	3.1 Power Up and Power Down	4
	3.2 Characterization.....	5
4	Summary.....	5

List of Figures

1	Functional Block Diagram	2
2	Positive Charge-Pump Circuit.....	2
3	Power-Up Timing—RESET Switching from Low to High	3
4	Power-Down Timing—RESET Switching from High to Low	3
5	Charge-Pump Output Voltage versus Load Current	3
6	Negative Charge Pump Circuit.....	4
7	Power-Up Timing—RESET Switching from Low to High	5
8	Power-Down Timing—RESET Switching from High to Low	5
9	Charge Pump Output Voltage versus Load Current	5

List of Tables

1	Operation of Positive Charge Pump.....	3
2	Operation of Negative Charge Pump	4

1 Block Diagram Description

This device uses two window comparators, an RS flip-flop, an open-drain MOSFET, and a totem-pole output stage. The device also has a RESET pin for enabling and disabling the output. The supply voltage range of 2 V to 15 V enables the devices to work in an automotive environment with a fully-charged 12-V battery and during cold cranking.


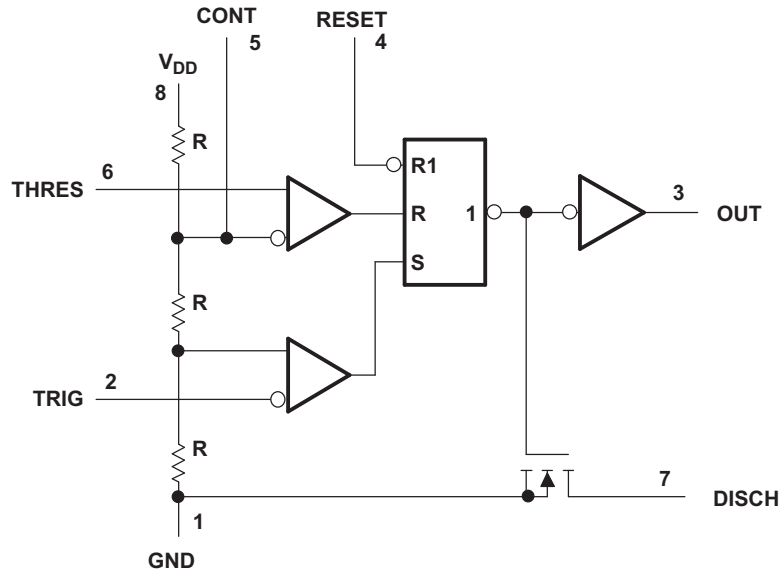


Figure 1. Functional Block Diagram

2 Setup for Positive Charge Pump

The TLC555-Q1 device is configured as typical timer. The switching frequency and duty cycle is determined by the timing components R1, R2, and C5. The two diodes (D1, D2) and two ceramic capacitors (C3, C4) generate the positive charge pump $2V_{CC} - 2V_f$. The D2 anode connected to V_{CC} makes the charge pump voltage at $V_{CC} - 2V_f$ when the TLC555-Q1 device is disabled. The charge pump can be at 0 V if the TLC555-Q1 device is disabled by connecting the D2 anode to the OUT pin (pin 3).

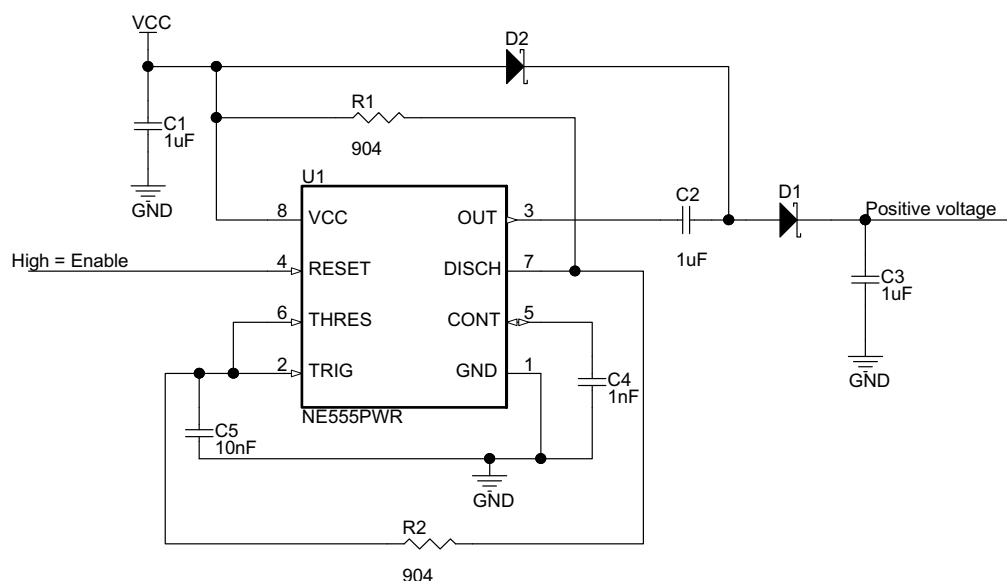

Copyright © 2016, Texas Instruments Incorporated

Figure 2. Positive Charge-Pump Circuit


2.1 Power Up and Power Down

The device RESET pin can be used to enable and disable the charge pump according to [Table 1](#).

Table 1. Operation of Positive Charge Pump

RESET	OUT pin 3	Charge Pump	Doubler Level
High	Switching	ON	$2V_{CC} - 2V_f$
Low	Low	OFF	$V_{CC} - 2V_f$

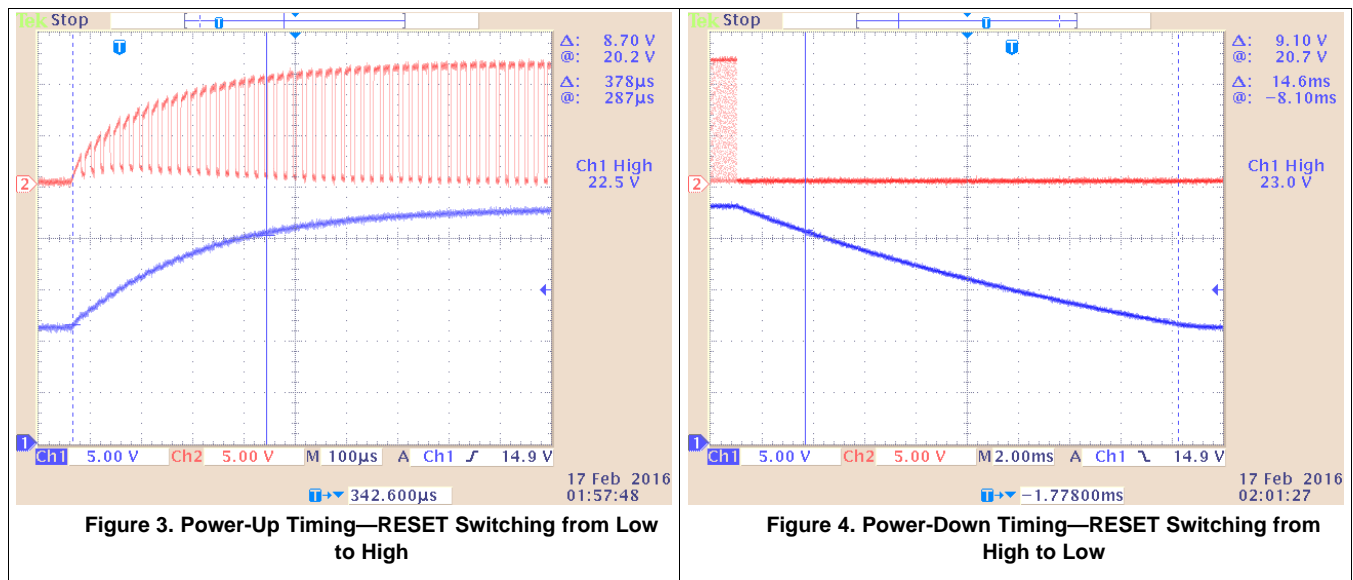[Figure 3](#) shows the power up timing by switching the RESET pin from low to high. [Figure 4](#) shows the power down timing by switching the RESET pin from high to low.



2.2 Characterization

The characterization of the doubler charge-pump circuit is at $V_{CC} = 12\text{ V}$. The output is $2V_{CC} - 2V_f$, where V_f is the drop across a diode. [Figure 5](#) shows the doubler charge pump versus the load current


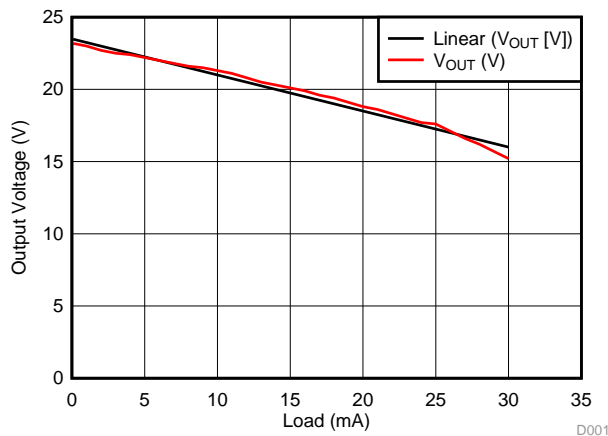


Figure 5. Charge-Pump Output Voltage versus Load Current

3 Setup for Negative Charge Pump

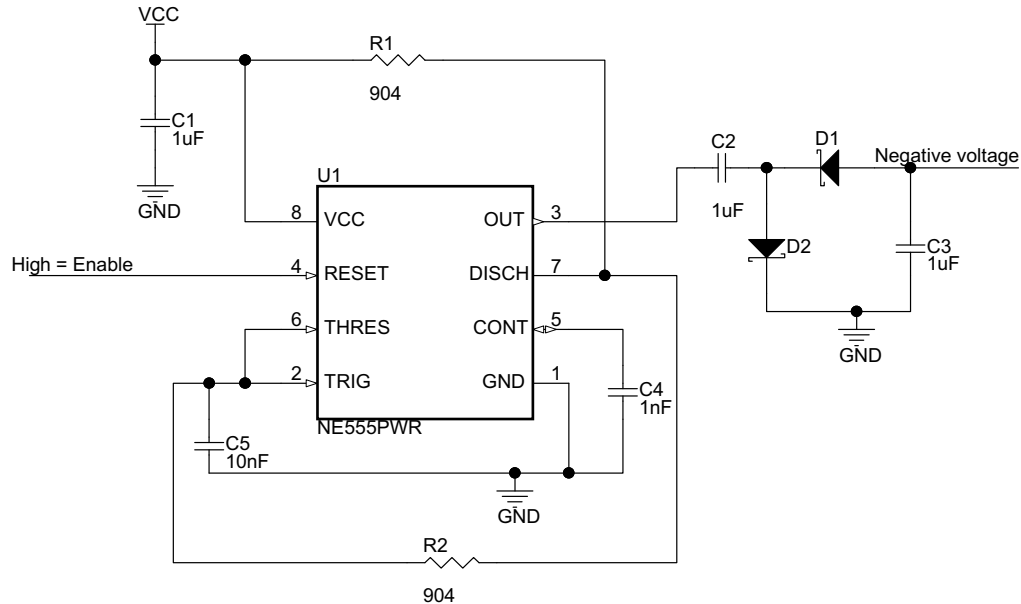The TLC555-Q1 device is configured as typical timer. The switching frequency and duty cycle is determined by the timing components R1, R2 and C5. The 2 diodes (D1, D2) and 2 ceramic capacitors (C3, C4) generate the negative charge-pump inverter. The charge pump is at 0 V when the TLC555-Q1 device is disabled.



Copyright © 2016, Texas Instruments Incorporated

Figure 6. Negative Charge Pump Circuit

3.1 Power Up and Power Down

The device RESET pin can be used to enable and disable the charge pump according to [Table 2](#).

Table 2. Operation of Negative Charge Pump

RESET	OUT pin 3	Charge pump	Inverting level
High	Switching	ON	$-V_{CC} + 2V_f$
Low	Low	OFF	0

Figure 7 shows the power up timing by switching the RESET pin from low to high. Figure 8 shows the power down timing by switching the RESET pin from high to low.

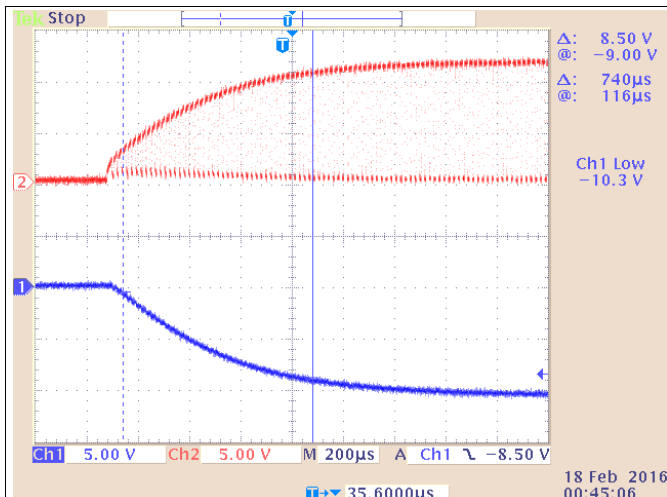


Figure 7. Power-Up Timing—RESET Switching from Low to High

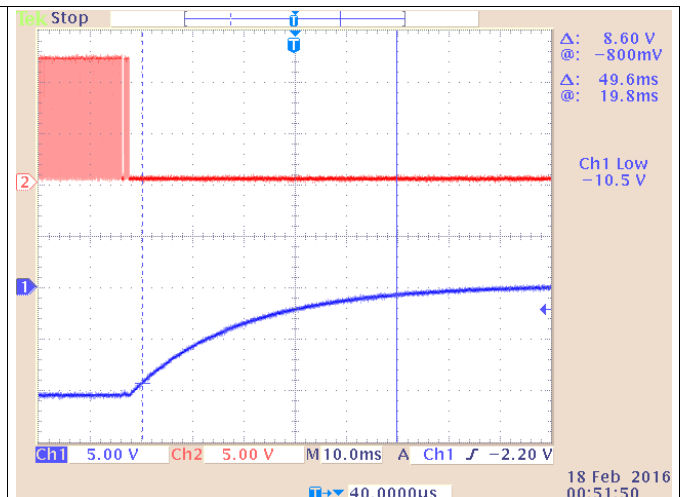


Figure 8. Power-Down Timing—RESET Switching from High to Low

3.2 Characterization

The characterization of the doubler charge-pump circuit is at $V_{CC} = 12\text{ V}$. The output is $-2V_{CC} + 2V_f$, where V_f is the drop across a diode. Figure 9 shows the negative doubler charge pump versus the load current.

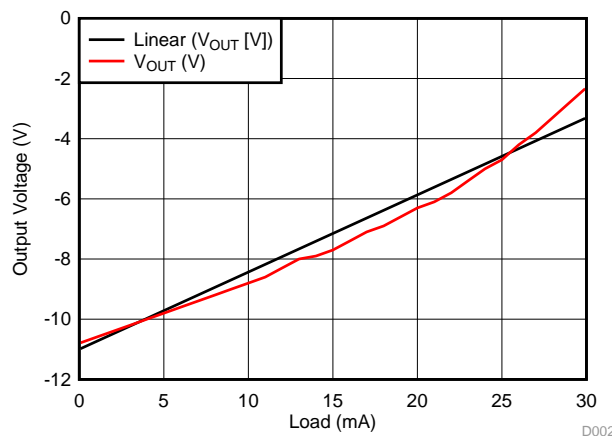


Figure 9. Charge Pump Output Voltage versus Load Current

4 Summary

The TLC555-Q1 device can be configured in multiple charge-pump configurations with few external components. The device can be used as a cost-saving measure in many applications.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com