

Guidelines for Measuring Audio Power Amplifier Performance

Richard Palmer

ABSTRACT

This application note provides guidelines for measuring the data sheet parameters of Texas Instruments audio power amplifiers (APAs) using prefabricated evaluation modules (EVMs). The primary equipment used for the measurements consists of the System Two™ audio measurement system by Audio Precision™, a digital multimeter (DMM), and a DC power supply.

Contents

1	Introduction	2
2	Basic Measurement System.....	2
3	Interfacing to the APA	4
4	Total Harmonic Distortion Plus Noise (THD+N)	8
5	Noise	11
6	Gain and Phase	12
7	Crosstalk.....	14
8	Supply Rejection	15
9	Power Measurements and Related Calculations.....	18
10	Measurement Pitfalls.....	22
11	References	24

List of Figures

1	Audio Measurement Systems: (a) Class-AB APAs and (b) Filter-Free Class-D APAs.....	4
2	Differential Input—BTL Output Measurement Circuit	5
3	SE Input—SE Output Measurement Circuit	6
4	Measurement Low-Pass Filter Derivation Circuit—Class-D APAs	7
5	THD+N Measurement Circuit Using the AP-II Measurement System: Differential-BTL	8
6	THD+N Versus POUT for the TAS2770. 4-Ω Load. 1 KHz.	9
7	THD+N Versus POUT for the TAS2770. 8-Ω Load. 1 KHz.	9
8	THD+N Versus POUT for the TAS2562. 4-Ω load. 1 KHz.	9
9	THD+N Versus POUT for the TAS2562. 4-Ω Load. 1 KHz.	10
10	THD+N Versus Frequency for the TPA2001D1 and the TPA731	10
11	Noise Measurement Circuit	11
12	Measured Results of Noise Circuit.....	12
13	Gain and Phase Measurement Circuit	13
14	TPA731 Gain and Phase Measurements	13
15	TPA2001D1 Gain and Phase Measurements	14
16	Crosstalk Measurement Circuit	14
17	Crosstalk Measurements.....	15
18	PSRR and kSVR Measurement Circuit	16
19	kSVR Filter Circuit.....	17
20	kSVR of the TPA2001D1 and TPA731	18

21	Impact of CBYPASS on kSVR for the TPA711 Class-AB APA	18
22	Efficiency Measurement Circuit for Class-AB and Class-D BTL APAs	19
23	Efficiency Graphs of the TPA731 and TPA2001D1	21
24	Graph of Power Dissipated Versus Output Power.....	21
25	Supply and Output Power Versus CF for the TPA731 and TPA2001D1	22
26	Effect of Generator Interface on APA Measurements, THD+N Versus Power Shown.....	23

List of Tables

1	Recommended Minimum Wire Size for Power Cables	5
2	Typical RC Measurement Filter Values	8
3	Efficiency Data for the TPA731 and TPA2001D1	20
4	Power Versus Crest Factor	22

Trademarks

Audio Precision is a trademark of Audio Precision.
All other trademarks are the property of their respective owners.

1 Introduction

The primary goal of audio measurements is to determine the performance of a device in the audible spectrum, 20 Hz to 20 kHz. Although most people do not hear frequencies below 50 Hz or above 17 kHz, the broad spectrum is an industry standard that allows a more accurate comparison of devices. The performance can be quickly analyzed, and only a few basic pieces of equipment are required. A method for measuring standard data sheet information for audio power amplifiers (APAs) is presented for several key parameters. These are:

- THD+N versus output power
- THD+N versus frequency
- Gain and phase versus frequency
- Integrated noise
- Signal-to-noise ratio
- Crosstalk versus frequency
- Power supply rejection ratio
- Supply ripple voltage rejection ratio
- Efficiency
- Power dissipated in the device

The measurements in this application note were made using TI Plug-N-Play APA evaluation modules (EVMs). The TPA2001D1 and TPA731 mono devices were used for most measurements. The TAS2770 and TAS2562 were used for THD+N versus output power measurements. The TPA2001D2 and TPA0212 devices were used for the crosstalk measurements, which require a stereo device.

Note that the measurements are dependent upon the layout of the printed-circuit board (PCB), particularly with class-D APAs. The graphs in the data sheet reflect typical specifications and were measured on test boards specifically designed to allow accuracy and ease of measurement. The measurements in this application note, however, were taken using circuits on EVMs that reflect real-world layout constraints. The measurements of a particular audio circuit may vary from the typical specifications. A large variance is usually indicative of a PCB layout or measurement system issue.

2 Basic Measurement System

This application note focuses on methods that use the basic equipment listed below:

- Audio analyzer or spectrum analyzer
- Oscilloscope
- Signal generator


- Linear regulated power supply
- EVM or other complete audio circuit
- Digital multimeter (DMM)
- Twisted pair wires
- Power resistor(s)
- Filter components

[Figure 1](#) shows the block diagrams of basic measurement systems for class-AB and class-D amplifiers. A sine wave is normally used as the input signal since it consists of the fundamental frequency only (no other harmonics are present). An analyzer is then connected to the APA output to measure the voltage output. The analyzer must be capable of measuring the entire audio bandwidth. A regulated DC power supply is used to reduce the noise and distortion injected into the APA through the power pins. A System Two audio measurement system (AP-II) (Reference 1) by Audio Precision includes the signal generator and analyzer in one package.


The generator output and amplifier input must be AC-coupled. However, the EVMs already have the ac-coupling capacitors, (CIN), so no additional coupling is required. The generator output impedance should be low to avoid attenuating the test signal, and is important since the input resistance of APAs is not very high (about 10 k Ω). Conversely the analyzer-input impedance should be high. The output impedance, ROUT, of the APA is normally in the hundreds of milli-ohms and can be ignored for all but the power-related calculations.

[Figure 1\(a\)](#) shows a class-AB amplifier system, which is relatively simple because these amplifiers are linear—their output signal is a linear representation of the input signal. They take analog signal input and produce analog signal output. These amplifier circuits can be directly connected to the AP-II or other analyzer input.

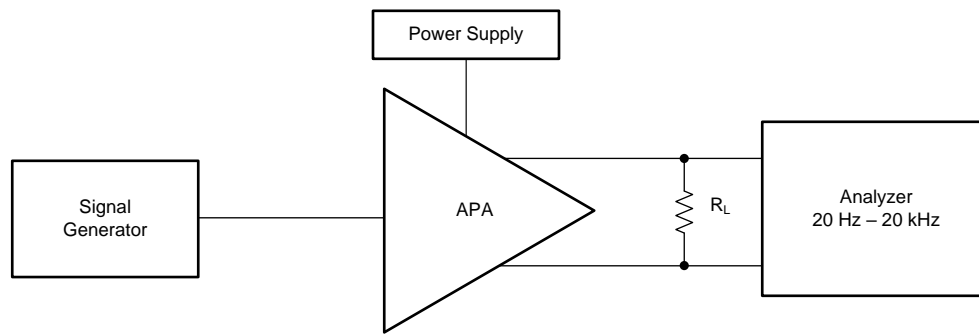This is not true of the class-D amplifier system shown in [Figure 1\(b\)](#), which requires low pass filters in most cases in order to measure the audio output waveforms. This is because it takes an analog input signal and converts it into a pulse-width modulated (PWM) output signal that is not accurately processed by some analyzers.



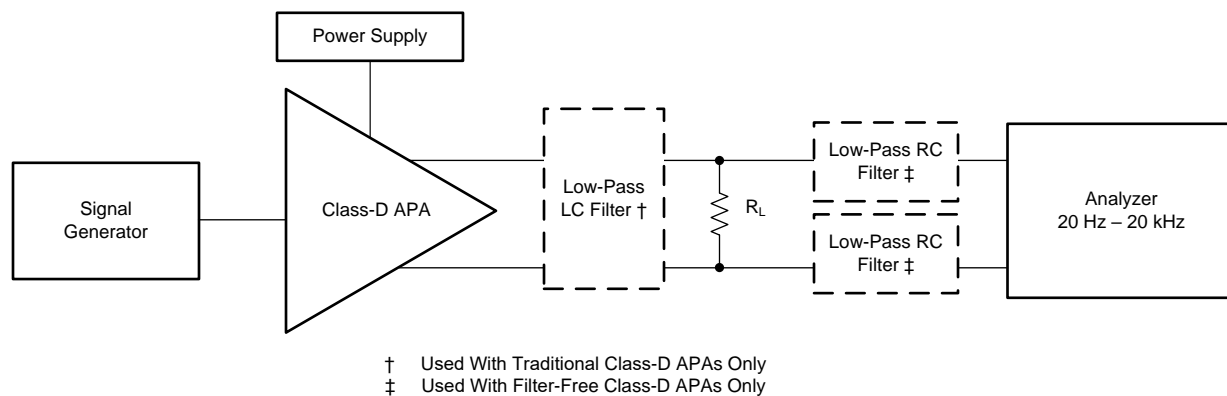(a) Basic Class-AB Audio Measurement System



(b) Filter-Free and Traditional Class-D Audio Measurement System

Figure 1. Audio Measurement Systems: (a) Class-AB APAs and (b) Filter-Free Class-D APAs

Two types of class-D amplifiers exist: traditional class-D that requires a low-pass LC filter to produce an analog output, and TI's new filter-free class-D which does not require a low-pass output filter for normal operation because the speaker provides the inductance necessary to achieve high efficiency.

Two families of class-D APAs (TPA032D0x, TPA005Dxx) use the traditional modulation scheme that requires the LC filter for proper operation. The data sheets, EVM manuals, and application notes (References 2 and 3) provide more information about this filter.

The filter-free class-D APA families (TPA2000Dx and TPA2001Dx) use a modulation scheme that does not require an output filter for operation, but they do sometimes require an RC low-pass filter when making measurements. This is because some analyzer inputs cannot accurately process the rapidly changing square-wave output and therefore record an extremely high level of distortion. The RC low-pass measurement filter is used to remove the modulated waveforms so the analyzer can measure the output sine wave.

Additionally, the class-D APA outputs can be also connected to optional electromagnetic interference filters (EMI filters). These filters are normally suggested for applications with output power around 5 W, and sensitivity to external electromagnetic signals. These filters are normally used in TI's digital input Class-D audio amplifiers with output sense (TAS2770 and TAS2562 are examples of these families).


3 Interfacing to the APA

This section describes the important points to be considered when connecting the test equipment to the APA. The first two subsections describe the connections to differential and single-ended (SE) APA inputs and outputs. The last subsection discusses the RC low-pass filter design that is sometimes required for filter-free class-D measurements.

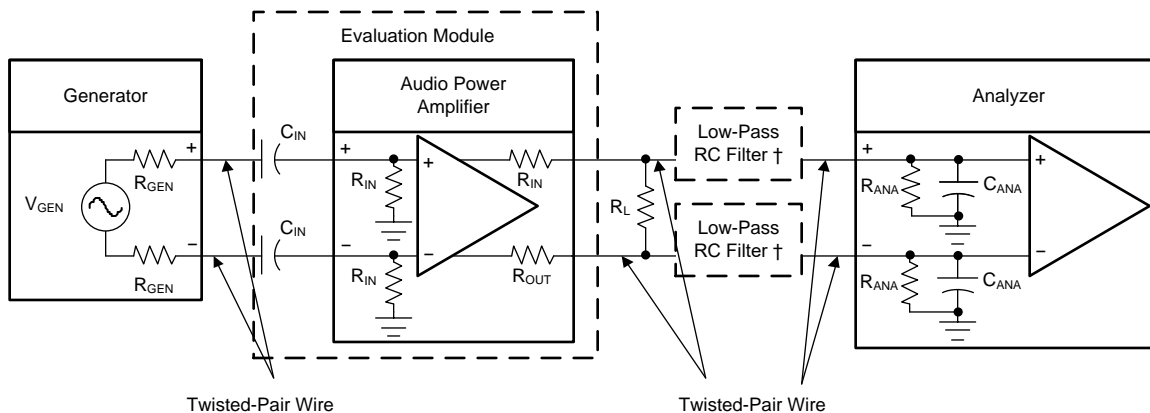3.1 Differential Input and BTL Output (TPA731 and TPA2000D1)

All of the class-D APAs and many class-AB APAs have differential inputs and bridge-tied load (BTL) outputs. Differential inputs have two input pins per channel and amplify the difference in voltage between the pins. Differential inputs reduce the common-mode noise and distortion of the input circuit. BTL is a term commonly used in audio to describe differential outputs. BTL outputs have two output pins providing voltages that are 180 degrees out of phase. The load is connected between these pins. This has the added benefits of quadrupling the output power to the load and eliminating a DC blocking capacitor.

A block diagram of the measurement circuit is shown in Figure 2. The differential input is a balanced input, meaning the positive (+) and negative (-) pins will have the same impedance to ground. Similarly, the BTL output equates to a balanced output.



† The RC low-pass filter is required only for measuring the filter-free class-D audio power amplifiers.

Figure 2. Differential Input—BTL Output Measurement Circuit

The generator should have balanced outputs and the signal should be balanced for best results. An unbalanced output can be used, but it may create a ground loop that will affect the measurement accuracy. The analyzer must also have balanced inputs for the system to be fully balanced, thereby cancelling out any common mode noise in the circuit and providing the most accurate measurement.

The following general rules should be followed when connecting to APAs with differential inputs and BTL outputs:

- Use a balanced source to supply the input signal.
- Use an analyzer with balanced inputs.
- Use twisted-pair wire for all connections.
- Use shielding when the system environment is noisy.
- Ensure the cables from the power supply to the APA, and from the APA to the load, can handle the large currents (see Table 1 below).

Table 1 shows the recommended wire size for the power supply and load cables of the APA system. The real concern is the DC or AC power loss that occurs as the current flows through the cable. These recommendations are based on 12-inch long wire with a 20-kHz sine-wave signal at 25°C.

Table 1. Recommended Minimum Wire Size for Power Cables

P_{OUT}	$R_L (\Omega)$	AWG SIZE	DC POWER LOSS (mW)	AC POWER LOSS (mW)
10	4	18	16	18
		22	40	42
2	4	18	3.2	3.7
		22	8.0	8.5
1	8	22	2.0	2.1
		28	8.0	8.1


Table 1. Recommended Minimum Wire Size for Power Cables (continued)

P_{OUT}	R_L (Ω)	AWG SIZE	DC POWER LOSS (mW)	AC POWER LOSS (mW)
< 0.75	8	22	1.5	1.6
		28	6.1	6.2

3.2 SE Input and SE Output (TPA0211 and TPA711)

The SE input and output configuration is used with class-AB amplifiers only. A block diagram of a fully SE measurement circuit is shown in Figure 3. Fully SE APAs are, in general, headphone or headset amplifiers, though the TPA0211 and TPA711 are APAs with SE capability. SE inputs normally have one input pin per channel. In some cases two pins are present; one is the signal and the other is ground. SE outputs have one pin driving a load through an output AC coupling capacitor and the other end of the load is tied to ground. SE inputs and outputs are considered to be unbalanced, meaning one end is tied to ground and the other to an amplifier input/output.

The generator should have unbalanced outputs, and the signal should be referenced to the generator ground for best results. Unbalanced or balanced outputs can be used when floating, but they may create a ground loop that will effect the measurement accuracy. The analyzer should have balanced inputs to cancel out any common-mode noise in the measurement.

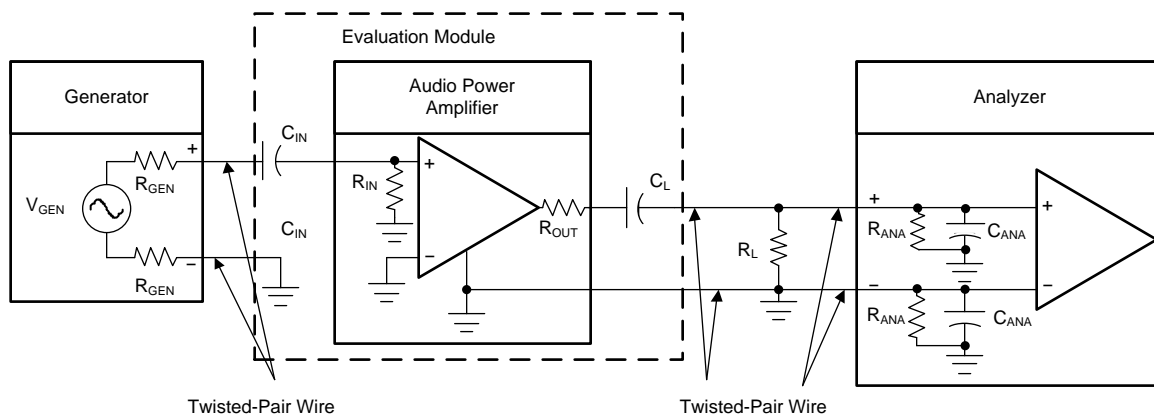
Figure 3. SE Input—SE Output Measurement Circuit

The following general rules should be followed when connecting to APAs with SE inputs and outputs:

- Use an unbalanced source to supply the input signal
- Use an analyzer with balanced inputs
- Use twisted pair wire for all connections
- Use shielding when the system environment is noisy
- Ensure the cables from the power supply to the APA, and from the APA to the load, can handle the large currents (see Table 1, Section 3.1)

3.3 Other Configurations

Some APAs are designed to operate in some combination of the two previously discussed configurations. For example, the TPA0312 is configured with differential inputs and SE outputs while the TPA711 is configured with SE inputs and BTL outputs. The TPA0212 can be operated with any combination of inputs and outputs. The relevant portions of Sections 3.1 and 3.2 are then used to configure the measurement system properly.

3.4 Class-D RC Low-Pass Filter

An RC filter is used to reduce the square-wave output when the analyzer inputs cannot process the pulse-width modulated class-D output waveform. This filter has little effect on the measurement accuracy because the cutoff frequency is set above the audio band. The high frequency of the square wave has negligible impact on measurement accuracy because it is well above the audible frequency range and the speaker cone cannot respond at such a fast rate. The RC filter is not required when an LC low-pass filter is used, such as with the class-D APAs that employ the traditional modulation scheme (TPA032D0x, TPA005Dxx).

The component values of the RC filter are selected using the equivalent output circuit as shown in Figure 4. RL is the load impedance that the APA is driving for the test. The analyzer input impedance specifications should be available and substituted for RANA and CANA. The filter components, RFILT and CFILT, can then be derived for the system. The filter should be grounded to the APA near the output ground pins or at the power supply ground pin to minimize ground loops.

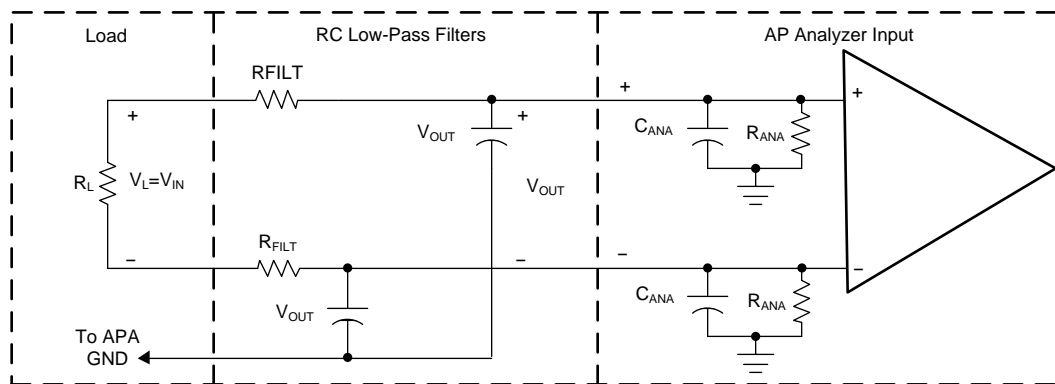


Figure 4. Measurement Low-Pass Filter Derivation Circuit—Class-D APAs

The transfer function for this circuit is shown in Equation 1 where $\omega_0 = \text{REQCEQ}$, $\text{REQ} = \text{RFILT} \parallel \text{RANA}$ and $\text{CEQ} = (\text{CFILT} + \text{CANA})$. The filter frequency should be set above fMAX, the highest frequency of the measurement bandwidth, to avoid attenuating the audio signal. Equation 2 provides this cutoff frequency, fc. The value of RFILT must be chosen large enough to minimize current that is shunted from the load, yet small enough to minimize the attenuation of the analyzer-input voltage through the voltage divider formed by RFILT and RANA. A rule of thumb is that RFILT should be small (~100 Ω) for most measurements. This reduces the measurement error to less than 1% for RANA ≥ 10 kΩ.

$$\left(\frac{V_{\text{OUT}}}{V_{\text{IN}}} \right) = \frac{\left(\frac{R_{\text{ANA}}}{R_{\text{ANA}} + R_{\text{FILT}}} \right)}{1 + j \left(\frac{\omega}{\omega_0} \right)} \quad (1)$$

$$f_c = \sqrt{2} \quad (2)$$

An exception occurs with the efficiency measurements, where RFILT must be increased by a factor of ten to reduce the current shunted through the filter. CFILT must be decreased by a factor of ten to maintain the same cutoff frequency. See Table 2 for the recommended filter component values.

Once fc is determined and RFILT is selected, the filter capacitance is calculated using Equation 3. When the calculated value is not available, it is better to choose a smaller capacitance value to keep fc above the minimum desired value calculated in Equation 2.

$$C_{\text{FILT}} = \frac{1}{2\pi \cdot f_c \cdot R_{\text{FILT}}} \quad (3)$$

Table 2 shows recommended values of RFILT and CFILT based on common component values. The value of fc was originally calculated to be 28 kHz for an fMAX of 20 kHz. CFILT, however, was calculated to be 57 000 pF, but the nearest values of 56 000 pF and 51 000 pF were not available. A 47 000 pF capacitor was used instead, and fc is 34 kHz, which is above the desired value of 28 kHz.

Table 2. Typical RC Measurement Filter Values

MEASUREMENT	R _{FILT}	C _{FILT}
Efficiency	1 000 Ω	5 600 pF
All Other Measurements	100 Ω	5 6000 pF


4 Total Harmonic Distortion Plus Noise (THD+N)

The THD+N measurement combines the effects of noise, distortion, and other undesired signals into one measurement and relates it (usually as a percentage) to the fundamental frequency. Ideally, only the fundamental frequency of the sine-wave input is present at the output of the APA, which in practice is never the case. Nonlinearities in the APA, internal and external noise sources, and layout or grounding issues are some of the contributors that distort the original input signal.

THD+N requires measuring the value of everything that remains, which includes harmonics and noise, after the fundamental frequency has been filtered. This value is then divided by the fundamental frequency and expressed as a percentage. The bandwidth is often limited to record only the portion of the noise in the audible spectrum. The signal generator, audio analyzer, and filters should have a noise floor and distortion that is at least 10 dB lower than the APA distortion in order to achieve an accurate measurement (Reference 4).

Figure 5 shows an Audio Precision II (AP-II) system setup for measuring the THD+N of differential-BTL APAs. The bandwidth is usually limited with filters in the analyzer to reduce the out-of-band noise; however, this also reduces relevant harmonics of the higher frequency signals. A filter cutoff frequency of 30 kHz is used for class-AB and class-D APAs to allow measurement of the third harmonic for a 10 kHz signal. The narrow bandwidth attenuates the distortion at higher frequencies, but these harmonics are beyond the audible threshold of the human ear and are not a factor.

Three measurements that express THD+N in some manner in the data sheets are THD+N versus output power, THD+N versus frequency, and the maximum output power bandwidth, covered respectively in the following Sections 4.1 through 4.3. Section 4.4 provides a means to calculate and measure the maximum input voltage for an APA. These measurements vary with CBYPASS for devices that have a BYPASS pin, with THD+N increasing as CBYPASS decreases.

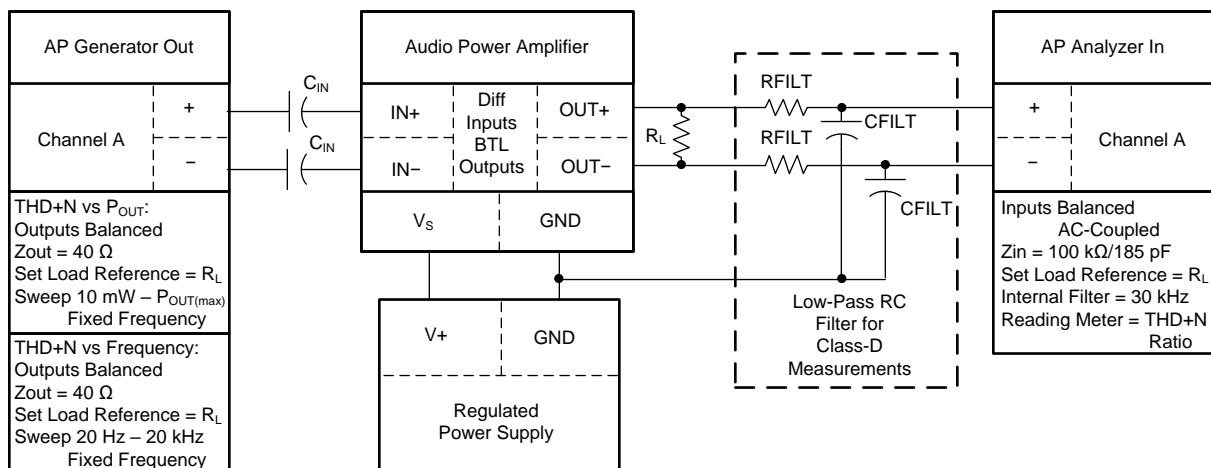
Figure 5. THD+N Measurement Circuit Using the AP-II Measurement System: Differential-BTL

4.1 THD+N Versus Output Power

Figure 6–Figure 9 show examples of THD+N versus output power. The digital signal generator sweeps the input voltage from low to high amplitude at a fixed frequency. The output power is calculated for a given load impedance that is entered into the audio analyzer software. At each voltage step the fundamental frequency is measured first, then filtered out and the amplitude of all the remaining harmonics is measured. This value is then divided by the amplitude of the fundamental frequency and graphed as a percentage of the fundamental.

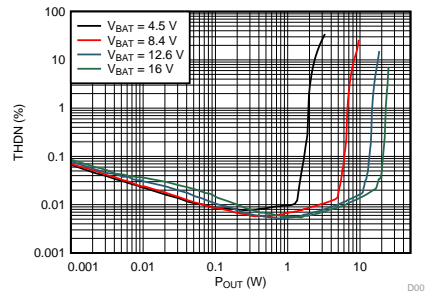


Figure 6. THD+N Versus POUT for the TAS2770. 4-Ω Load. 1 KHz.

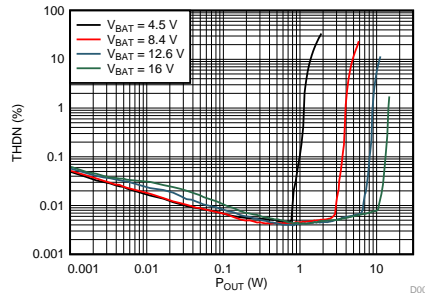


Figure 7. THD+N Versus POUT for the TAS2770. 8-Ω Load. 1 KHz.

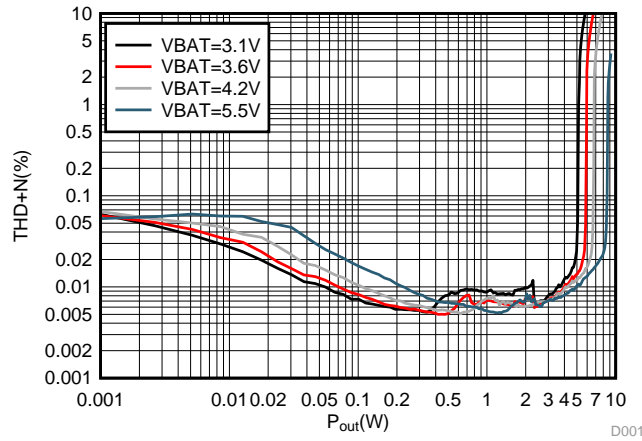


Figure 8. THD+N Versus POUT for the TAS2562. 4-Ω load. 1 KHz.

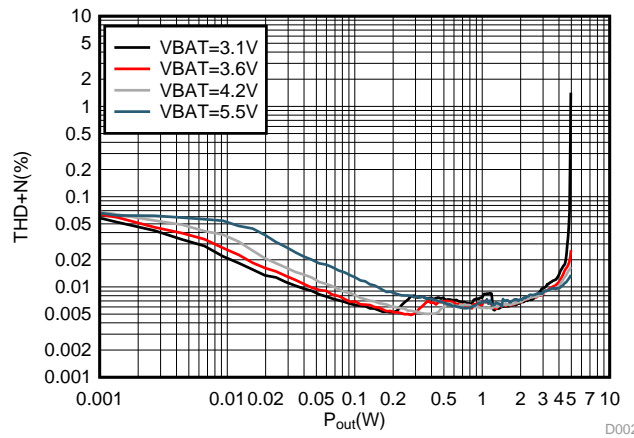


Figure 9. THD+N Versus POUT for the TAS2562. 4-Ω Load. 1 KHz.

4.2 THD+N Versus Frequency

Figure 10 shows a graph of THD+N versus frequency. The signal generator sweeps the frequency from 20 kHz to 20 Hz at a fixed voltage. The harmonics and noise of the APA output are measured at specified frequency steps. Each step is divided by the amplitude of the fundamental frequency and graphed as a percentage of the fundamental. This graph provides a check when compared to the THD+N versus power since they should match at one specific frequency and power.

The increased THD+N at low frequencies is primarily due to the 1/f noise. The high frequency THD+N increase is due to device nonlinearities, primarily crossover distortion, and is expected because the APA open loop gain decreases with frequency. The audio quality is unaffected because the harmonics are above the audible threshold of the human ear (Reference 5). The rolloff at high frequencies is due to the band-limiting filter in the analyzer, which attenuates the upper harmonics above 30 kHz. Setting the filter frequency higher reduces the accuracy of the measurement with class-D APAs, and will have little or no impact on class-AB APAs. The class-AB graph continues in a relatively straight line if there is no filter present. The class-D rolls off more than class-AB because of the RC measurement filter, which adds another pole at 30 kHz.

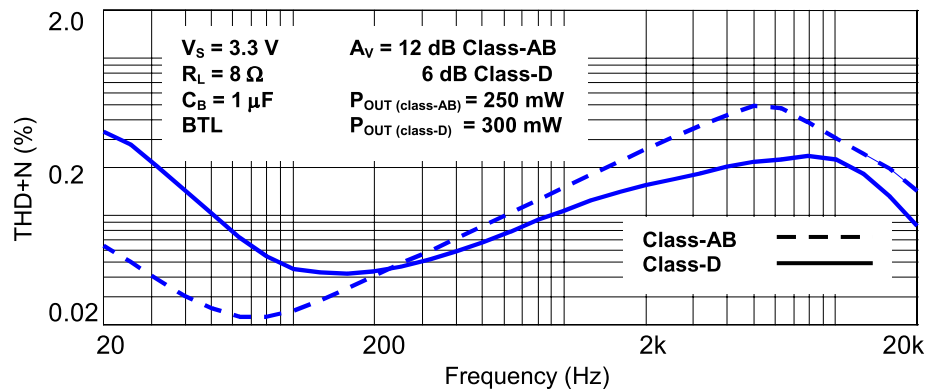


Figure 10. THD+N Versus Frequency for the TPA2001D1 and the TPA731

4.3 Maximum Output Power Bandwidth

The maximum output power bandwidth is a THD+N versus frequency measurement. The APA is driven at the maximum output power into the load and the frequency is swept from 20 Hz to 20 kHz. The maximum power bandwidth is then specified as the frequency range over which the THD+N remains below a specified percentage, which is normally one percent.

4.4 Maximum Input Voltage

The maximum input voltage required for producing maximum output power can be found by increasing the input until the output clips, then reducing it until it is just below clipping. Another method is to calculate the maximum peak-to-peak input voltage using the maximum-rated RMS output power from the data sheet or back-calculate it from the THD+N versus power measurement at the maximum desired value of distortion. Equation 4 provides the maximum peak-to-peak input voltage, where P_{OUT(max)} is the maximum rated RMS output power, R_L is the load resistance, and A_V is the voltage gain of the APA, measured in V/V.

$$V_{IN(P-P)} = \frac{2 \cdot \sqrt{2} \cdot P_{OUT(max)} \cdot R_L}{A_V} \tag{4}$$

5 Noise

Two types of measurements fall under the noise category, integrated noise over the audio band and signal-to-noise ratio (SNR) of the output signal.

5.1 Integrated Noise Versus Frequency

Figure 11 shows the noise measurement circuit for an APA with differential inputs and BTL outputs. Figure 12 shows a graph depicting the output noise voltage of the TPA2001D1 and the TPA731. All of the inputs of the APA should be AC-coupled to ground through the input resistor, whether internal or external, to reduce noise pickup and accurately simulate the system. Figure 6 shows a graph of THD+N versus P_{OUT}. The AP generator outputs are not used in this measurement and must be turned off.

The analyzer should be set to measure amplitude and should be limited to measure the noise in the audio spectrum only. The bandwidth is limited to the range of 22 Hz – 22 kHz with filters in the analyzer. The data field of the sweep panel is set to measure the analyzer amplitude (Anlr Ampl) and the source field is set to sweep the generator frequency (Gen Freq) which is swept from 20 kHz to 20 Hz. The output should be set to V RMS and may be divided by the gain to get the input referred noise voltage, though the data sheets normally specify the output noise voltage in μV RMS.

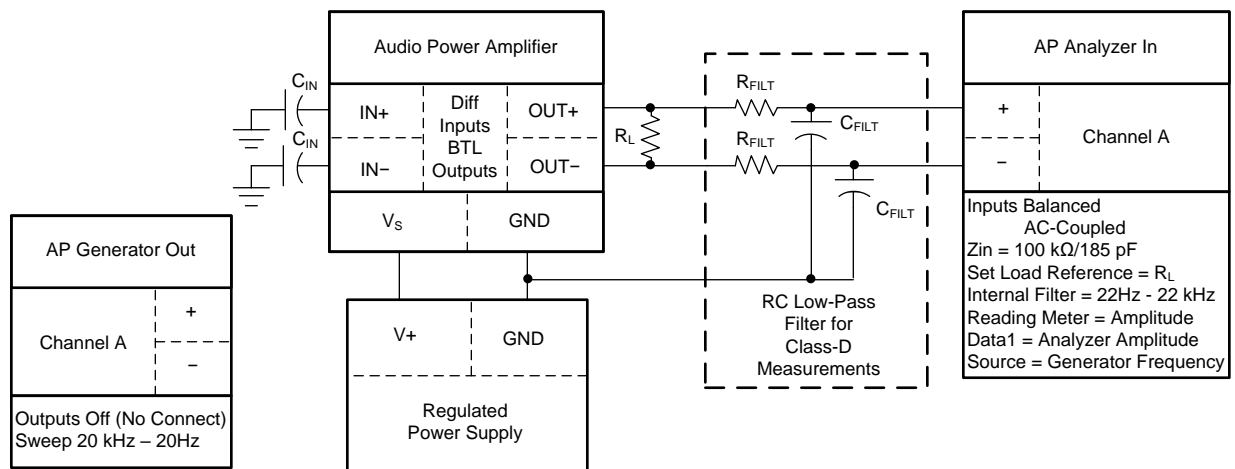


Figure 11. Noise Measurement Circuit

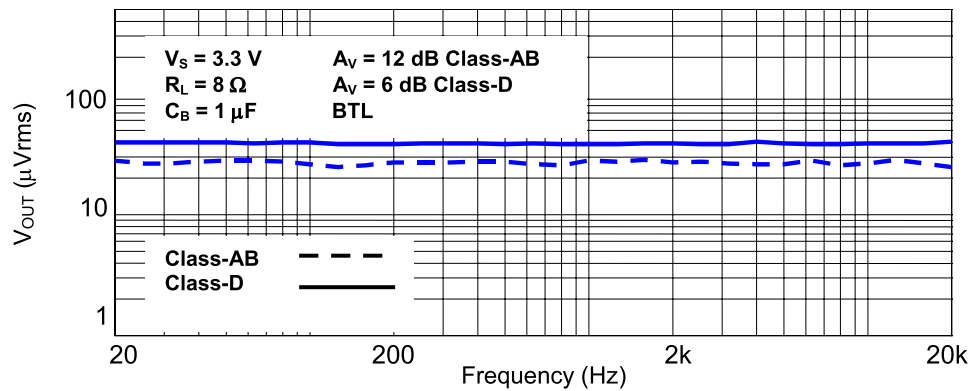


Figure 12. Measured Results of Noise Circuit

5.2 Signal-to-Noise Ratio

The signal-to-noise ratio (SNR) is the measure of the maximum output voltage compared to the integrated noise floor over the audio bandwidth, expressed in dB. It is normally specified at a precise power in the data sheet tables. The integrated noise floor is measured using the technique described in Section 5.1. The distortion of the output waveform is then measured at 1 kHz by sweeping the input voltage. The AP setup is the same as per the THD+N versus power measurements, with V_{OUT} , in V RMS, graphed on the x-axis rather than P_{OUT} . The point at which the output voltage begins to clip (the THD+N increases sharply) is considered to be the maximum output voltage. The SNR is calculated using Equation 5. The noise and signal data can also be expressed in decibel-volts (dBV), which is the dB ratio of the measured voltage to 1 V, and Equation 5 then simplifies to Equation 6.

$$\text{SNR} = 20 \cdot \log \left(\frac{V_{\text{OUT}}^{\text{RMS}}}{V_{\text{NOISE}}^{\text{RMS}}} \right) \quad (5)$$

$$\text{SNR} = \text{dBV}_{\text{OUT}} - \text{dBV}_{\text{NOISE}} \quad (6)$$

Any unused input should be ac-grounded. The measurement bandwidth should be limited to provide an accurate measurement of the integrated noise floor.

6 Gain and Phase

Figure 13 shows the AP measurement circuit for a mono-channel, BTL-output APA. Figure 14 and Figure 15 show measurements for the TPA731 and TPA2001D1. The gain and phase can also be measured at multiple points with an oscilloscope using Equation 7 for the gain and Equation 8 for the phase, where Δt is the time delay between the input and output voltages and f is the frequency of the input signal. The data is then plotted versus frequency.

$$A_V (\text{dB}) = 20 \cdot \log \left(\frac{V_{\text{OUT}}}{V_{\text{IN}}} \right) \quad (7)$$

$$\theta = \Delta t \cdot f \cdot 360^\circ \quad (8)$$

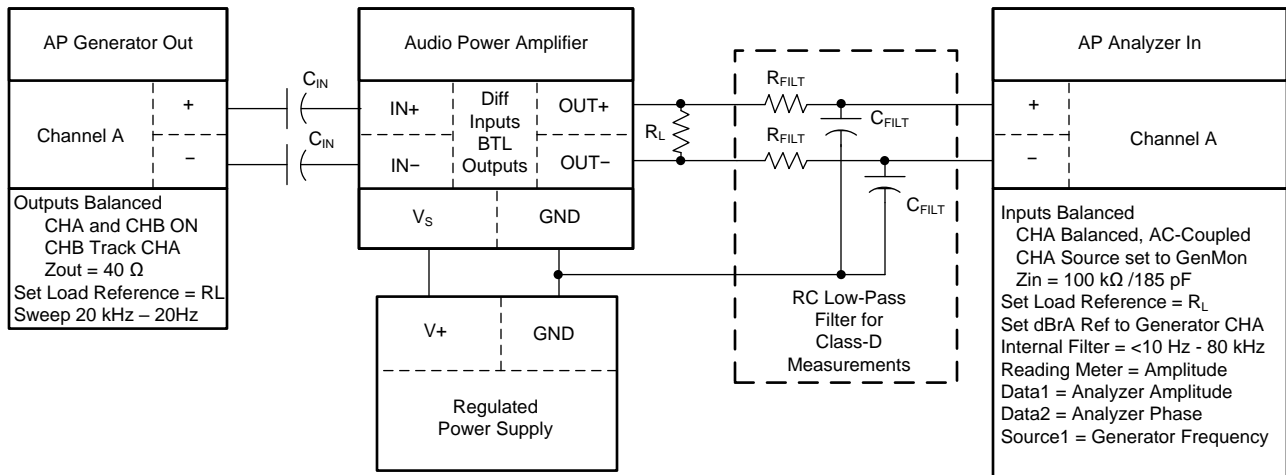


Figure 13. Gain and Phase Measurement Circuit

Figure 13 is the AP-II setup for measuring a single channel of the APA. Both channels must be turned on at the generator panel in the software and CHB set to track CHA. The analyzer CHB is set to GenMon (generator monitor), which means it takes its input directly from the generator output of the selected channel internal to the AP-II and uses it as the input phase reference for the analyzer measurement. The reference dBrA value should be set equal to the channel being swept, which in this case is CHA. This sets the input voltage of channel A as the reference for the gain measurement. It may be necessary to subtract 180° from the phase measurement to get the actual phase value.

The APA input ac-coupling capacitors produce the phase shift and attenuation at low frequencies. As seen in Figure 15, the class-D RC filter introduces some attenuation and phase shift at the measurement endpoints. The AP analyzer band-pass filters should be set < 10Hz and ≥ 30 kHz to minimize their impact on the measurement.

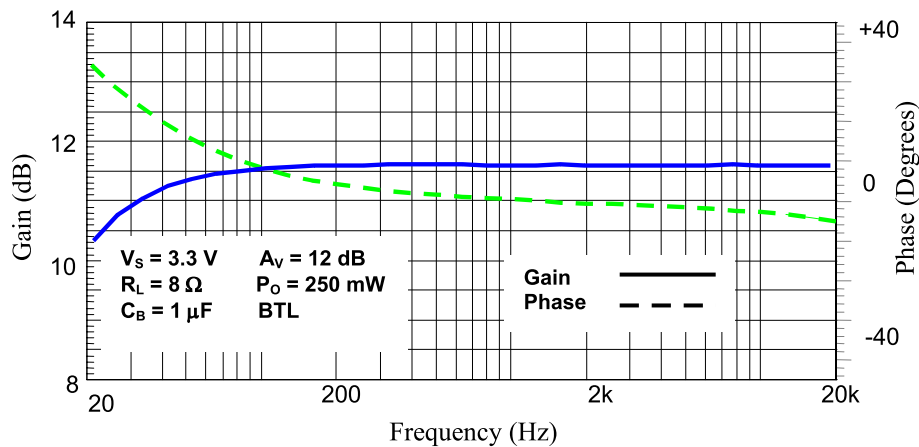


Figure 14. TPA731 Gain and Phase Measurements

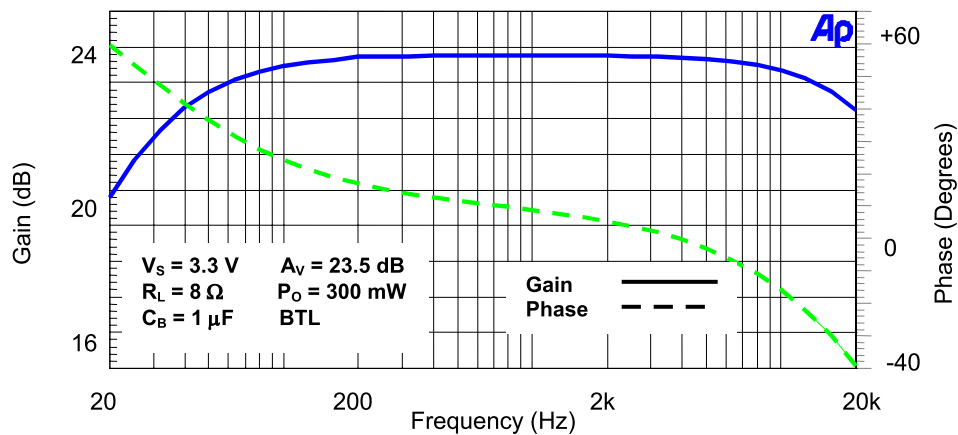


Figure 15. TPA2001D1 Gain and Phase Measurements

7 Crosstalk

Crosstalk is the measure of the signal coupling between channels of a stereo device. Figure 16 shows the crosstalk measurement circuit for an APA with differential inputs and BTL outputs. This particular circuit is set up to measure right-to-left (R-L) channel crosstalk, or the amount of signal that couples from the right channel (CHA) into the left channel (CHB). An input signal is fed into the right channel and the outputs of both channels are measured and compared as shown in Equation 9. The input voltage is fixed and is swept from 20 kHz to 20 Hz. The setup is inverted to graph the L-R channel crosstalk and the terms in parentheses in Equation 9 are inverted.

$$\text{Crosstalk} = 20 \cdot \log \left(\frac{V_{\text{CHB}}^{\text{OUT}}}{V_{\text{CHA}}^{\text{OUT}}} \right) \tag{9}$$

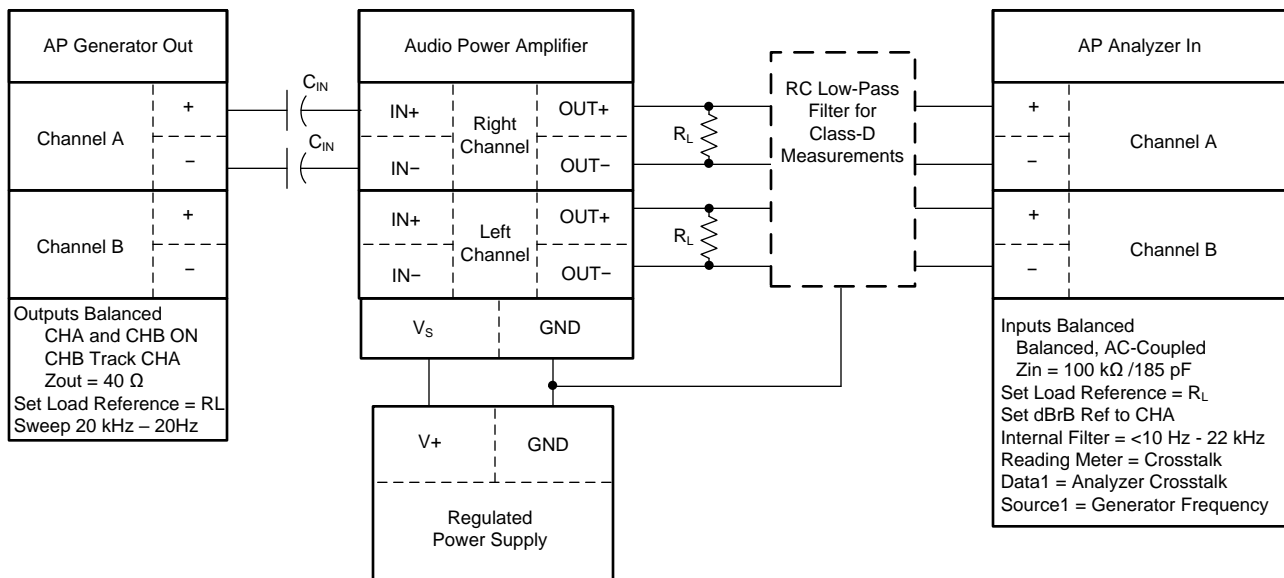


Figure 16. Crosstalk Measurement Circuit

Both channels must be turned on at the generator panel in the software and CHB set to track CHA. The input is swept over the audio frequency range at constant amplitude. The input voltage should be set to the highest amplitude that does not cause the output voltage to clip. Equation 10 is used for deriving the maximum peak-to-peak input voltage, where P_{OUT(max)} is the maximum rated RMS output power, R_L is the load resistance, and A_V is the voltage gain of the APA. The internal filter can be set to 30 kHz or greater to limit noise, but is otherwise not required. The output cables of each channel should be separated to minimize capacitive coupling between them.

$$V_{IN(P-P)} = \frac{2 \cdot \sqrt{2} \cdot P_{OUT(max)} \cdot R_L}{A_V} \quad (10)$$

Connections for the measurements of SE devices are made in the same way as for BTL devices, but with one end of R_L tied to ground and a capacitor inserted between R_L and OUT+ of the APA. The measurement is taken across R_L only, and not across R_L and the capacitor.

A graph of the R-L crosstalk is shown in Figure 17. When both R-L and L-R crosstalk measurements are shown, the graphs of both channels of the device are different. This is due to impedance mismatch between the channels, which is caused by nonsymmetrical layout of the IC.

The crosstalk was measured for the TPA0212 class-AB APA and TPA2001D2 class-D APA. The values are in close agreement with the data sheet graphs. The class-D crosstalk improves as the supply voltage is decreased because the radiation from the traces is decreased. Class-AB amplifiers are relatively unaffected by changes in supply voltage. The crosstalk increases in all amplifiers as the signal gain increases.

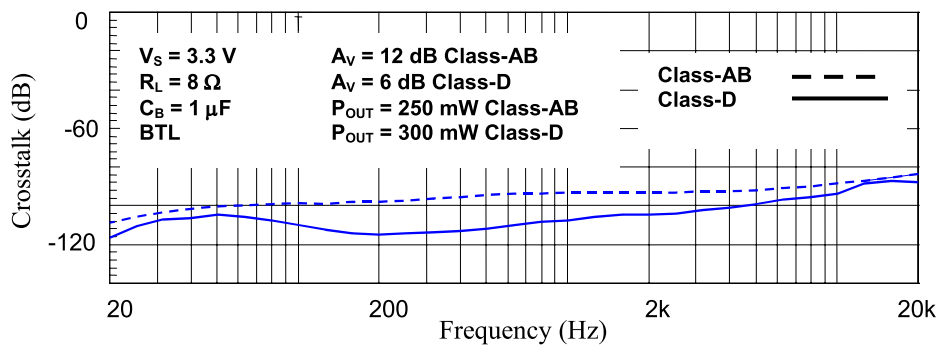


Figure 17. Crosstalk Measurements

8 Supply Rejection

Two types of supply rejection specifications exist: power supply rejection ratio (PSRR) and supply ripple rejection ratio (kSVR). PSRR is a DC specification measuring the change in output offset voltage for a change in supply voltage. kSVR is an AC specification measuring the ability of the APA to reject ac-ripple voltage on the power supply bus. All power supply decoupling capacitors are removed from class-AB circuits, and class-D measurements have a small 0.1μF decoupling capacitor placed close to the APA power pins to provide reverse path for recovery switching currents. It is recommended that the designer use equal decoupling capacitance values when comparing devices from different manufacturers to get a valid comparison of the performance, because a higher capacitance equates to a better kSVR.

PSRR is the ratio of the change in the output voltage, V_{OUT(DC)} for a change in the power supply voltage, V_S, expressed in dB as shown in Equation 11. For example, the output voltage of an audio power amplifier that has a PSRR of -70 dB would change by 31.6 μV if the supply voltage changed by 0.1 V.


$$PSRR = 20 \log \left(\frac{\Delta V_{OUT(dc)}}{\Delta V_S} \right) \quad (11)$$

kSVR is the ratio of the output ripple voltage, $V_{OUT(AC)}$, to the supply ripple voltage, expressed in dB as shown in Equation 12. This parameter is normally listed as a typical value in the data sheet tables at a specified frequency and temperature of 1 kHz and 25°C, respectively. A graph is provided in the data sheet of the typical values of kSVR over the audio bandwidth, because it is a frequency-dependent parameter.

$$k_{SVR} = 20 \log \left(\frac{\Delta V_{OUT(ac)}}{\Delta V_S} \right) \quad (12)$$

Figure 18 shows the PSRR and kSVR measurement circuit. The PSRR measurement requires only the two DMMs; therefore RSVR, CSVr, the generator and analyzer, and the RC measurement filter are not needed. The power supply voltage, V_S , is initially set, then read from the meter on the power supply. When the power supply meter does not have the desired resolution, DMM1 is used to measure V_S . DMM2 then measures V_{OUT} across the load. V_S is then stepped up or down by a specific amount and the corresponding value of V_{OUT} is measured.

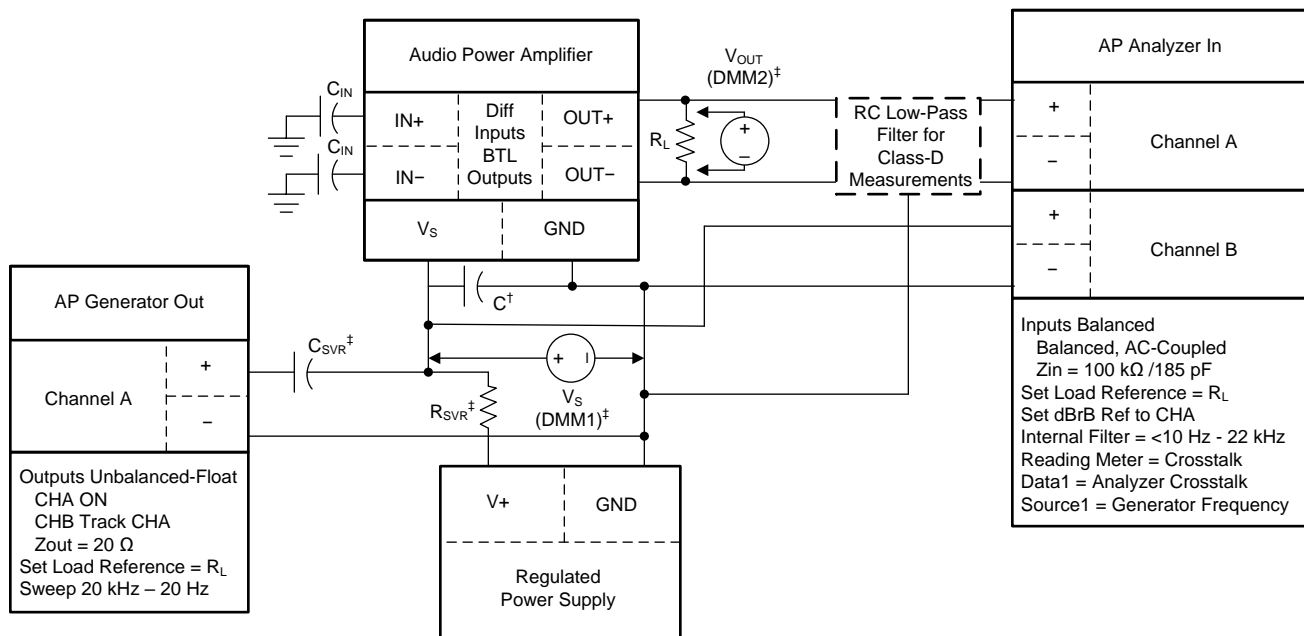The differences of the two measurements are then substituted into Equation 11 and the PSRR is calculated for that specific change in supply voltage. PSRR is specified as a typical value that is valid for a given supply voltage range at 25°C. All APA inputs are AC-coupled to ground.



† The 0.1 μ F capacitor, C, is required for class-D operation.

‡ The PSRR measurement uses the DMMs only because it is a dc value. k_{SVR} measurements use either the analyzer, oscilloscope or DMMs because it is an ac value. R_{SVR} and C_{SVR} are used for k_{SVR} measurements only.

Figure 18. PSRR and kSVR Measurement Circuit

The kSVR measurement requires the generator, analyzer, a DMM, and the kSVR filter components RSVR and CSVr. The RC measurement filter is used when the analyzer cannot accurately process the square wave output of the filter-free class-D APAs. DMM1 is used to measure V_S at the APA power pins. The generator injects a small sine-wave signal onto the power bus, and the audio analyzer measures this AC voltage at the APA power pin and at the output. Here the AP-II is configured for a crosstalk measurement, and sweeps the AC voltage at constant amplitude over the audio band, measuring and presenting a graph of the data points in dB.

Alternatives to the generator are to use a power source that has the capability to add an AC component to the output, or use a transformer to couple the AC signal onto the power bus. In any case, check the voltage that is applied to the APA power pins to be sure that the absolute maximum ratings of the APA are not exceeded at any point during the process.

Figure 19 shows the kSVR filter circuit. The DC power supply output impedance, R_S , is normally in the milli-ohms. The input impedance of the APA power pin, R_{APA} , is very high compared to this (in the hundreds or the thousands). The generator output signal sees R_{APA} and R_S in parallel and, because of the low value of R_S , this appears to be an AC ground. The resistor R_{SVR} is added to the circuit to increase the equivalent impedance of the power supply and is chosen to be approximately equal to the output impedance of the AC signal generator, R_{GEN} . A voltage divider, formed between R_{SVR} and R_{GEN} , provides a reasonable amplitude AC signal at the APA power pin. The large value of R_{SVR} is tolerable because the DC and AC supply currents are low. This is because the APA is idling and does not have any audio signal at the inputs, so the power dissipated in R_{SVR} is small.

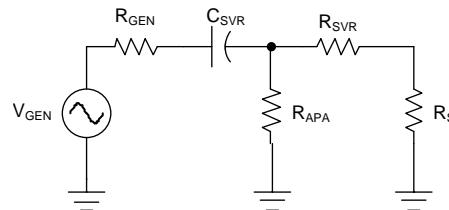


Figure 19. kSVR Filter Circuit

The addition of C_{SVR} ac-couples the generator to the power bus and provides a high-pass filter for injecting the AC signal into the APA. The filter cutoff frequency, f_c , should be set below the lowest frequency of the audio band, f_{MIN} , which in this case is 20 Hz. Equation 13 provides the value for f_c , which is ~14 Hz.

$$f_c = \frac{f_{MIN}}{\sqrt{2}} \quad (13)$$

The equivalent resistance of Figure 22 is then calculated with Equation 14, where R_{APA} is the supply voltage divided by the quiescent current of the device (V_S/I_Q). The value for C_{SVR} is then calculated using Equation 15.

$$R_{EQ} = R_{GEN} + R_{APA} \parallel (R_{SVR} + R_S) \approx R_{GEN} + R_{SVR} \quad (14)$$

$$C_{SVR} = \frac{1}{2\pi \cdot f_c \cdot R_{EQ}} \quad (15)$$



The capacitor is most likely electrolytic due to the value required. It will have some reactance that will vary with frequency range as shown by Equation 16. At 20 Hz the impedance is quite high—approximately the value of R_{GEN} and R_{SVR} —and at 20 kHz the value is in the milli-ohms.

$$X_{C_{SVR}} = \frac{1}{2\pi \cdot f_c \cdot C_{SVR}} \quad (16)$$

The actual values for the measurement circuit were $R_{GEN} = 20\Omega$, $R_S = 0$, $R_{APA} = 5V/6mA = 833\Omega$, $C_{SVR} = 330\mu F$, $R_{SVR} = 20\Omega$, $f_c = 12$ Hz. This yields a capacitive reactance of 24 Ω at 20 Hz, and 24 m Ω at 20 kHz. The value of the AC signal may need to be adjusted at low frequencies so that the desired voltage is applied to the APA power pin. The same is true for the DC voltage from the power supply, since I_Q will create a small voltage drop across R_{SVR} .

Those devices with BYPASS pins will have improved kSVR as the capacitance on the pin is increased. Devices operated SE have lower kSVR, particularly at the extreme low and high ranges of the audio frequency band. This is primarily due to the large output AC coupling capacitor, which dominates the frequency response both below and above the resonant frequency set by the equivalent series resistance (ESR) and equivalent series inductance (ESL) of the capacitor.

The kSVR graphs are shown in Figure 19 for a 100-mV RMS input sine wave. Both of these devices are differential input and BTL output. The TPA731 is measured with the inputs floating, though newer devices are measured with the inputs ac-grounded. Figure 20 is a data sheet graph from the TPA711 that provides an example of how CB impacts the kSVR measurement of an SE output.

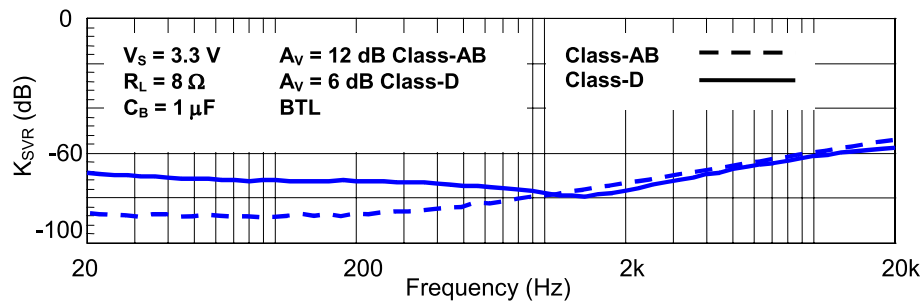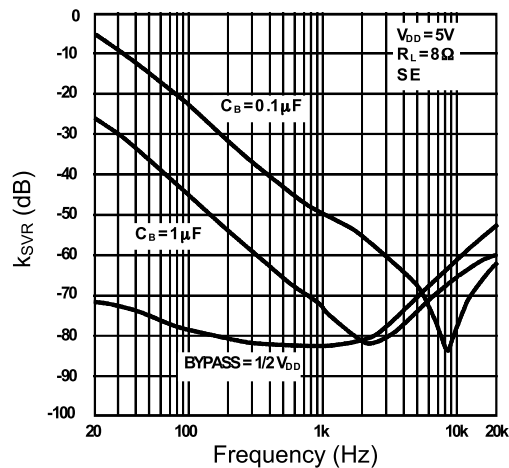
Figure 20. kSVR of the TPA2001D1 and TPA731

Figure 21. Impact of CBYPASS on kSVR for the TPA711 Class-AB APA

9 Power Measurements and Related Calculations

Several sets of data can be extracted from power measurements of a device. The power measurement process begins with the primary measurement of amplifier efficiency. The power that is dissipated by the amplifier is then calculated. This is useful for comparing the power supply requirements of different devices. The crest factor (CF) of the audio signal directly impacts the output power, and the effects are demonstrated from the dissipated power calculations.

9.1 Efficiency Measurements


Efficiency is the measure of the amount of power that is delivered to a load for a given input power provided by the supply. A class-AB APA acts like a variable resistor network between the power supply and the load, with the output transistors operating in the linear region. They dissipate quite a bit of power because of this mode of operation, and are therefore inefficient. The output stage in class-D APA acts as a switch that has a small resistance when operated in the saturation region, which provides a much higher efficiency.

A circuit for measuring the efficiency of a class-AB or class-D system is shown in [Figure 21](#). The simplest setup results when the power supply voltage and current meters have the resolution required. When the supply current meter is not sufficient, R1 is placed in the circuit. It should be a small value (0.1 Ω) and able to handle the power dissipated. A voltage drop occurs across R1, so the supply voltage must be adjusted to set the desired V_S at the device power pin. The average voltage, V_1 , across R1 provides the average supply current ($I_S = V_1/R_1$) that is used to calculate the average power provided by the supply.

The true-RMS DMMs and the audio analyzer provide an RMS value of both the voltage and the current, which, when multiplied together, provide the average power. When used, the power supply meters provide the average value of the supply voltage and current. The oscilloscope can measure the average or RMS values of the power supply and output voltage. Some oscilloscopes even have current probes that can be used to measure the current through a wire, in which case resistor R1 is not needed.

The load measurement is different for class-AB and class-D APAs. Two elements are shown; one is the actual load, Z_L, and the other is resistor R2. The Class-AB load is a noninductive power resistor, Z_L = R_L, that must be capable of handling the maximum power output without a significant temperature increase, which will change the resistance and impact the measurement accuracy. This purely resistive load makes the output measurement easy since only the voltage across the load, V_{OUT}, is required in order to calculate the output power. The output is sinusoidal so all measurement devices should be AC-coupled to the load. There is some quiescent power dissipation in R_L, but this is negligible. Resistor R2 is not required for class-AB efficiency measurements because the load is purely resistive.

The switching nature of the class-D makes the output measurement more challenging. First, a speaker is used as the load for the filter-free class-D because it has the inductance that helps provide the high class-D efficiency. A purely resistive load is not a true indicator of the operating environment of the filter-free class-D, and does not provide accurate efficiency numbers. Second, the output power must be calculated on the basis of current and voltage, not on the basis of impedance, because impedance varies with frequency. A small power resistor (R2) is placed in series with the load and a DMM or analyzer is used to measure the RMS value of the load current (I_{OUT} = V₂/R₂). The RMS voltage across the entire load (speaker and resistor R2) must be measured to provide the total power into the load.

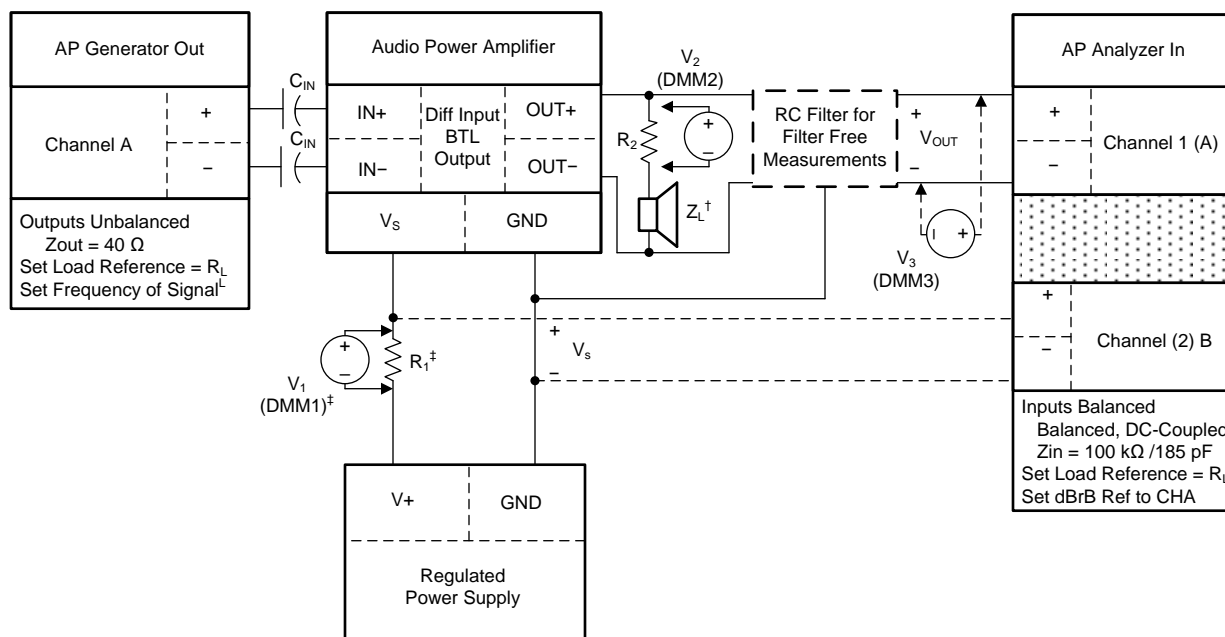

† Load Z_L is a speaker for class-D APAs and is a purely resistive load for class-AB APAs

‡ DMM1 and Channel 2 of the AP/oscilloscope (or a third DMM) are used to measure the average power supply current and voltage when power supply meters are not accurate. If not used, remove resistor R₁.

Figure 22. Efficiency Measurement Circuit for Class-AB and Class-D BTL APAs

Equation 17 provides the efficiency of the class-AB APA, and Equation 18 provides the efficiency of the class-D APA. The input power of both equations, as stated previously, is just the average voltage applied to the power pins of the APA multiplied by the average value of the power supply current. Average value is used for the power supply measurements since the voltage and current have DC and AC components and are typically nonsinusoidal. The output power is also an average value that comes from the multiplication of two RMS terms.

$$\eta_{\text{Class-AB}} = \left(\frac{P_{\text{OUT}}}{P_{\text{S}}} \right) = \frac{\left(\frac{V_{\text{L(RMS)}}^2}{Z_{\text{L}}} \right)}{V_{\text{S(ave)}} \cdot I_{\text{S(ave)}}} \quad (17)$$

$$\eta_{\text{Class-D}} = \frac{P_{\text{OUT}}}{P_{\text{S}}} = \frac{V_{\text{O(RMS)}} \cdot I_{\text{O(RMS)}}}{V_{\text{S(ave)}} \cdot I_{\text{S(ave)}}} = \frac{V_{\text{O(RMS)}} \cdot \left(\frac{V_{\text{R2(RMS)}}}{R_2} \right)}{V_{\text{S(ave)}} \cdot I_{\text{S(ave)}}} \quad (18)$$

The RC measurement filter is used for making filter-free class-D output measurements when the analyzer or DMM cannot accurately process the switching output waveform. The filter resistance must be large enough to minimize current flow through the filter, while the capacitance must be sized to achieve the desired cutoff frequency, which should be just above the audio band. If the filter resistor is not large enough, the filter current must be accounted for in the efficiency equation. The recommended values of RFILT and CFILT are 1 kΩ and 5.6 nF, respectively. This provides a filter cutoff frequency of ~28 kHz. The filter is only required with class-D APAs and is discussed in more detail in Section 3.

The efficiency was measured with a 3.3-V supply and the results are shown in [Table 3](#) and [Figure 22](#) using the power supply meter and a Fluke 87III DMM measuring the voltage across the load. The DMM, AP analyzer, and TDS 754 oscilloscope measurements for the class-AB data were in close agreement. The class-D DMM and AP data were similar, but the oscilloscope measured 5-10% higher and is due to the averaging of the oscilloscope, which introduced a somewhat large margin of error, particularly at high power output. The DMM reading is more reliable since it filters out the high frequency harmonics of the switching waveform to provide a more stable low-frequency value.

Table 3. Efficiency Data for the TPA731 and TPA2001D1

Vs (Vave)	Is (mAave)	Ps (mWave)	Vout (mVrms)	Pout (mWave)	Eff (%)	Is (mAave)	Ps (mWave)	Vr (mVrms)	Vout (mVrms)	Pout (mWave)	Eff (%)
3.3	23	75.9	200	5	6.6	3	9.9	0.7	58	0.4	4.1
3.3	28	92.4	250	7.8	8.5	4	13.2	1.3	104	1.4	10.2
3.3	40	132	354	15.7	11.9	5	16.5	2.3	200	4.6	27.9
3.3	45	148.5	400	20	13.5	8	26.4	3.7	335	12.4	47
3.3	56	184.8	500	31.3	16.9	10	33	4.5	393	17.7	53.6
3.3	67	221.1	600	45	20.4	13	42.9	5.1	486	24.8	57.8
3.3	79	260.7	708	62.7	24	17	56.1	6.3	594	37.4	66.7
3.3	89	293.7	798	79.6	27.1	22	72.6	7.4	688	50.9	70.1
3.3	111	366.3	998	124.5	34	29	95.7	8.8	824	72.5	75.8
3.3	134	442.2	1197	179.1	40.5	39	128.7	10.3	973	100.2	77.9
3.3	156	514.8	1397	244	47.4	55	181.5	12.7	1179	149.7	82.5
3.3	158	521.4	1417	251	48.1	74	244.2	15	1370	205.5	84.2
3.3	-	-	-	-	-	107	353.1	18.3	1664	304.5	86.2
3.3	-	-	-	-	-	144	475.2	21.2	1932	409.6	86.2

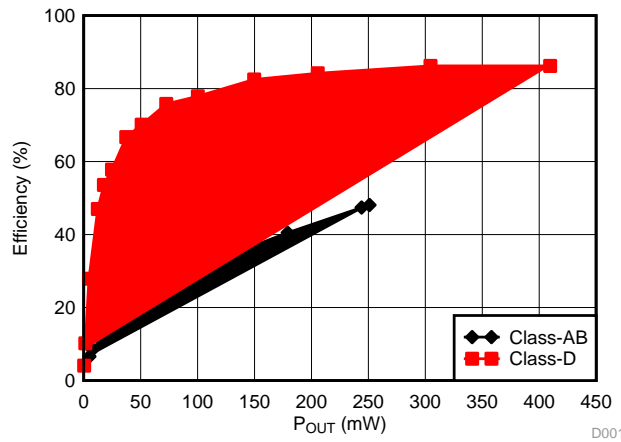


Figure 23. Efficiency Graphs of the TPA731 and TPA2001D1

9.2 Power Dissipated Versus Power to the Load

The efficiency measurements provide the information required to calculate the amount of power dissipated, P_D , in the amplifier. P_D provides some insight into the supply currents that are required. P_D is calculated using Equation 19 and the measured values of supply and output power from Table 3. It is assumed that the power dissipated in the RC filter, used for the filter-free class-D APA measurements, is negligible.

$$P_D = P_S - P_{OUT} \tag{19}$$

Figure 24 shows graphs of P_D versus the P_{OUT} for the TPA731 class-AB and the TPA2001D1 filter-free class-D APAs, calculated from the efficiency data using Equation 19. The data was measured up to the maximum output power, which occurs just prior to clipping, and can easily be discerned from the THD versus Power graph. The designer can choose the percent distortion (level of clipping) that is acceptable for a system and test the device through that power level.

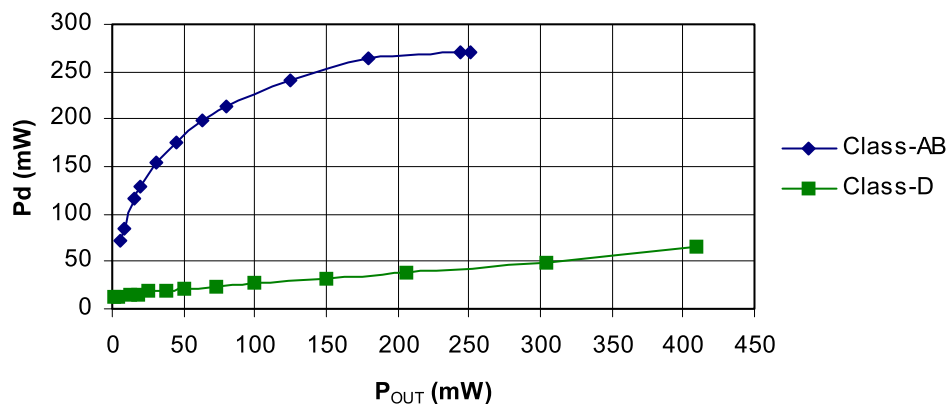


Figure 24. Graph of Power Dissipated Versus Output Power

9.3 Crest Factor and Output Power

The crest factor (CF) is the ratio of the peak output to the average output. It is typically graphed in terms of output power and is expressed in dB. For example, the CF of a sine wave is 3 dB. Sine waves are used in the characterization of APA performance, but do not give a clear idea of what the performance will be with music. The CF of music may vary between 6 dB and 24 dB. The CF directly impacts the amount of heat dissipated in the device. The higher the CF, the lower the heat dissipated and the higher the ambient operating temperature can be. The P_D data of Section 9.2 can be used to determine the CF of the device.

Equation 20 may be used to calculate CF. Since a sine wave was used for the measurements, the CF is 3 dB, and the average output power (POUT(ave)) is known. The peak output power (POUT(pk)) is calculated by manipulating Equation 20 into Equation 21, where POUT(pk) and POUT(ave) are expressed in watts and CF is expressed in dB.

$$CF(dB) = 10 \log \left(\frac{P_{OUT(pk)}}{P_{OUT(ave)}} \right) \tag{20}$$

$$P_{OUT(ave)} = \frac{P_{OUT(pk)}}{10^{(CF/10)}} \tag{21}$$

For example, the maximum peak output power is 500 mW at for the TPA731. This is calculated using 250 mW as POUT(ave) and a CF of 3 dB for the output sinusoid. The peak will not change throughout the calculations, as it is the maximum output power possible and is independent of the output waveform. The CF is then increased in 3 dB steps up to 18 dB and the corresponding POUT(ave) is calculated for each step. The PD in the device is measured for each value of POUT(ave) using the efficiency measurement circuit.

The efficiency data and CF calculations can help the designer approximate the power that must be provided by the power supply. Table 4 shows the values of power for the supply, load, and what is dissipated in the amplifier for various CFs of the TPA731 class-AB APA and the TPA2001D1 class-D APA. The table was generated from measured data and calculations using Equations (19) through (21).

Figure 25 shows the graph of PS and POUT versus CF from the data of Table 4. The graph allows easy comparison of the devices, and it is clear that the class-D APA provides more POUT with less power from the supply than the class-AB APA. The difference between PS and POUT is the dissipated power, PD.

Table 4. Power Versus Crest Factor

P _{OUT} (mWave)	Crest Factor (dB)	Ps (mWave)	Pd (mWave)	P _{OUT} (mWave)	Crest Factor (dB)	Ps (mWave)	Pd (mWave)
251	3	521	270	410	3	475	66
125	6	366	242	206	6	244	39
63	9	261	198	100	9	129	28
31	12	185	154	51	12	73	22
16	15	132	116	25	15	43	18
8	18	92	85	12	18	14	148

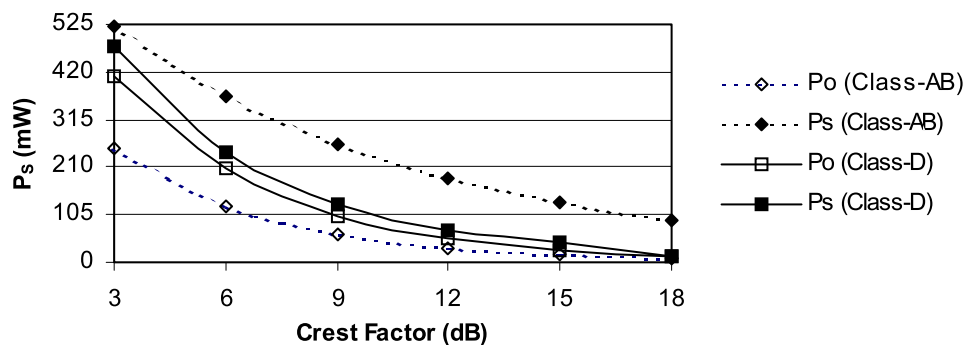


Figure 25. Supply and Output Power Versus CF for the TPA731 and TPA2001D1

10 Measurement Pitfalls

This section contains a compilation of reminders to help avoid the various common mistakes, or pitfalls, that are made when measuring the APA devices. While they are not all-inclusive, it is the hope of the author that these may offer some insight that will save time and effort spent troubleshooting the circuit.

10.1 Effects of Improper Interfacing and Grounding

The primary concern is establishing a good connection to the APA. A good connection allows ground current to flow through a low-resistance return path and reduces noise injection into the system through ground loops. Grounding is a critical part of this connection, particularly at the APA inputs. THD+N levels were measured for various generator connections to a TPA2001D2 Class-D APA and are shown in Figure 26. The class-D has differential inputs and BTL outputs.

A balanced generator, used with differential inputs, has a maximum deviation of 0.02% THD+N between a grounded and floating source at low power, a difference that is negligible. The balanced generator provided the lowest value of distortion. It is comparable to an unbalanced generator that has a floating source as long as the positive (+) and negative (-) pins of the source are connected to the corresponding pins of the APA. The performance is degraded by 0.2% at lower power, and 0.01% at high power when the negative (-) pin is grounded at the APA. If the generator source is grounded, the performance decreases by over 0.2% across the power spectrum. A balanced source must therefore be used to remove the common-mode noise and minimize offsets from ground currents to provide the most accurate measurement.

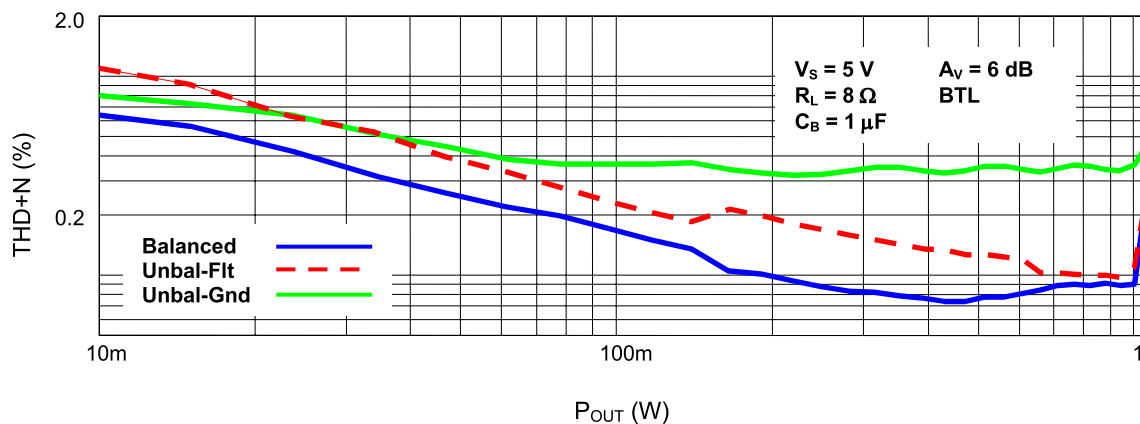


Figure 26. Effect of Generator Interface on APA Measurements, THD+N Versus Power Shown

It may be necessary to tie the ground pin of the power supply or other system device to chassis ground to remove any 60-Hz component, called AC line or 60-Hz hum, from the signal path. This must be done carefully or ground loops will be formed that will increase distortion. References 4 and 6 have more information on grounding and ground loops. To sum up the APA connections:

- Use a balanced source with differential inputs, unbalanced source with SE inputs
- Ground the power supply chassis to remove any 60-Hz hum
- The RC filter, used when measuring filter-free class-D APAs, should always be connected to ground at the APA to allow a path for return currents and to minimize the ground loop area
- The lead and/or wire lengths of the filter components should be kept as short as possible
- Power supply-to-APA and APA-to-load cables must be sized to avoid restricting the current flow
- AC-ground all unused inputs during measurements
- Check to be sure the source is warmed up and all measurement devices are calibrated

10.2 THD+N Measurements

- The load resistance must be properly set in the analyzer software for correct output power
- In the case of high distortion at lower power, check the ground connections, generator output configuration, and that the input and bypass capacitors are correct

10.3 Noise Measurements

- Limit the measurement to the audio band, because the noise value is integrated over the specified frequency range.

10.4 Gain and Phase Measurements

- Reference the output voltage to the input voltage
- Subtract 180 degrees from the phase when the phase shift is graphed greater than 180 degrees, which is often a characteristic of the analyzer
- Adjust the analyzer bandpass filters to less than 10 Hz and greater than 30 kHz to remove their contribution to the phase shift in the audio band

10.5 Crosstalk Measurements

- The output cables of both channels should be twisted pair wires to minimize ground loops
- Reversed output connections result in a crosstalk that is measured in positive dB
- Unused APA inputs should be AC-coupled to ground; floating inputs decrease crosstalk

10.6 Supply Rejection Measurements

- A 0.1 μF decoupling capacitor is required for class-D operation during these measurements. All other capacitors should be removed. All decoupling capacitors should be removed for class-AB measurements
- Be sure the output is being compared with the voltage at the power pins of the chip
- A small resistor (20 Ω) must be in series with the power supply to develop the input voltage
- As the value of bypass capacitance increases, kSVR improves (decreases)

10.7 Efficiency Measurements

- Measure the supply voltage at the power pins of the chip
- The filter-free class-D RC measurement filter should have a high resistance for RFILT, with a value of 1 k Ω recommended. The current through the filter must be considered when the value is smaller than this

11 References

1. www.audioprecision.com, Audio Precision Website
2. Texas Instruments, *Design Considerations for Class-D Audio Power Amplifiers Application Report*
3. Texas Instruments, *Reducing and Eliminating the Class-D Output Filter Application Report*
4. *Audio Measurement Handbook*, Metzler, Bob, Audio Precision, 1993
5. *Introduction to Electroacoustics and Audio Amplifier Design*, Leach, W. Marshall Jr., Kendall/Hunt Publishing, 1999
6. *Noise Reduction Techniques in Electronic Systems*; Ott, Henry W., Wiley Interscience, 1976

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Original (October 2001) to A Revision	Page
• Updated to current standards; changed part data throughout.....	2

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated