

Effective System ESD Protection Guidelines TPS254x USB Charging Port Controllers

Eric Wright


Linear Power/Power Interface

ABSTRACT

IEC 61000-4-2 electro-static discharge (ESD) protection of USB charging ports is a necessary system requirement for most products. The USB D+ and D- signals from the charging port controller make direct contact with a potentially charged USB cable and the discharge of energy from the cable to the product can damage the controller. The controller D+, D-, and even VBUS signals must have some form of ESD protection added to the application circuit. This document discusses the design and printed circuit board (PCB) layout of the ESD protection circuitry.

1 Description

The TPS254x family (TPS2540/40A, TPS2541/41A, TPS2543/43Q1, TPS2546/46Q1) of USB charging port controllers do not incorporate internal IEC 61000-4-2 ESD protection. In order to meet IEC 61000-4-2, level 4, external circuitry must be used. In some cases, protection of the D+ and D- signals starts with a transient voltage suppressor (TVS) and may include a choke. Protection of VBUS can usually be accomplished through the use of the USB required VBUS capacitor, C_{PORT} . The basic protection scheme is shown in Figure 1.

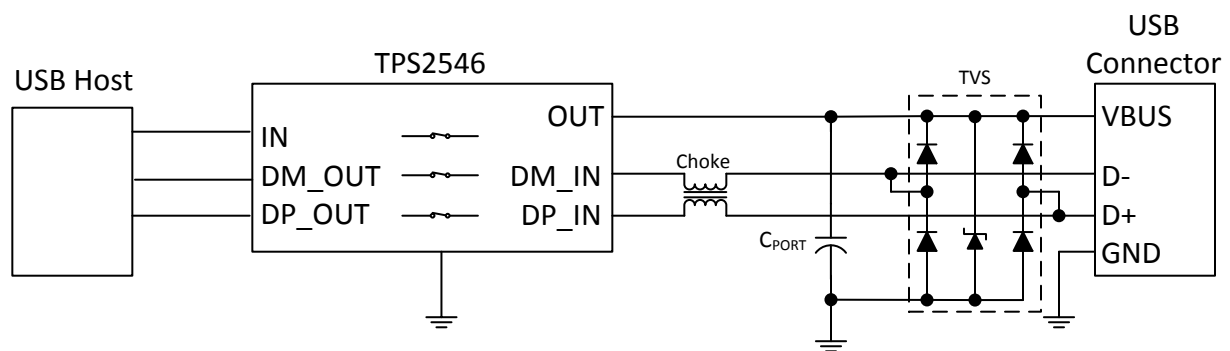

Copyright © 2016, Texas Instruments Incorporated


Figure 1. Basic USB ESD Protection Circuit

2 Choosing the TVS

The absolute maximum voltage rating of the TPS254x DP_IN and DM_IN pins with respect to GND ranges from -0.3 V to the lower of $V_{IN} + 0.3\text{ V}$ or 5.7 V . For example, if $V_{IN} = 5\text{ V}$, then the maximum rating is 5.3 V . The TVS should clamp the voltage on DP_IN and DM_IN within this voltage range for reliable operation in the presence of ESD surges.

The TVS configuration shown in Figure 1 is one example of an ESD diode array which can clamp D+ and D- between GND and VBUS. The TPD2E001 is used on TPS254x EVMs and benefits from the connection of the TPD2E001 VCC pin to VBUS (and C_{PORT}). For this case, the clamping voltage between GND and VBUS depends on the forward voltage drop of the clamping diodes at peak surge current.

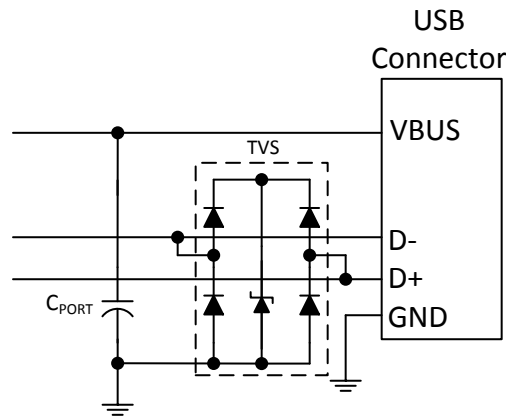There are alternative options such as the TPD2E2U06 which rely on the clamping voltage of the internal clamp only and do not benefit from a connection to VBUS (and C_{PORT}). An example is shown in Figure 2. This configuration may not protect the TPS254x as the clamping voltage is above the absolute maximum voltage rating of the TPS254x DP_IN and DM_IN pins.



Copyright © 2016, Texas Instruments Incorporated

Figure 2. Clamp Type USB ESD Protection Circuit

3 Data Line Choke

In some cases where the signal trace length is far away from the USB connector and TVS, a data line choke may be required. For example, TPS2540EVM-623 incorporates L1 (Coilcraft 0805USB-372ML or Würth 744231371) to provide additional ESD margin above IEC 61000-4-2, level 4 ($\pm 8\text{ kV}$ contact and $\pm 15\text{ kV}$ air discharge). TPS2543EVM-064 also incorporates the L1 choke, but can also meet IEC 61000-4-2, level 4 ESD requirements without the choke. The data line choke also helps suppress EMI generated by the local dc/dc converter.

4 PCB Layout and Routing

4.1 Signal Integrity Considerations

The DP_OUT/DM_OUT, DP_IN/DM_IN traces should be routed as controlled-impedance differential pairs per the USB-2.0 specification. Minimize the use of vias in the high-speed data lines. Place the TPS254x on the bottom side of the PCB so that the connections from DP_IN and DM_IN to the downstream USB connector do not cross. This yields a single via on each connection.

For TPS2543EVM-064, the data pairs are routed as edge-coupled micro-strips on the bottom layer with nominal differential impedance of 90 Ω. The reference plane is tied to GND and is on layer 3 of this four layer PCB. Ensure that the reference plane is void of cuts or splits above the differential pairs to prevent impedance discontinuities. Route through the choke and TVS in a manner that minimizes impedance discontinuities in the high speed traces. Refer to the TPS254xEVM-064 User Guide Layout Guidelines section for the layout example.

4.2 TVS Placement and Hookup

The TVS should be placed close to the downstream USB connector so that ESD energy is shunted back to chassis ground before it can find a discharge path within the end product's internal circuitry. The TVS should be directly connected to the TPS254x DP_IN/DM_IN pins without any vias. Placing the TVS on the same side of the PCB as the TPS254x can help minimize any impedance between the TVS pin and TPS254x pin. Figure 3 shows a poor, good, and best method for connecting TPS254x, TVS and USB connector.

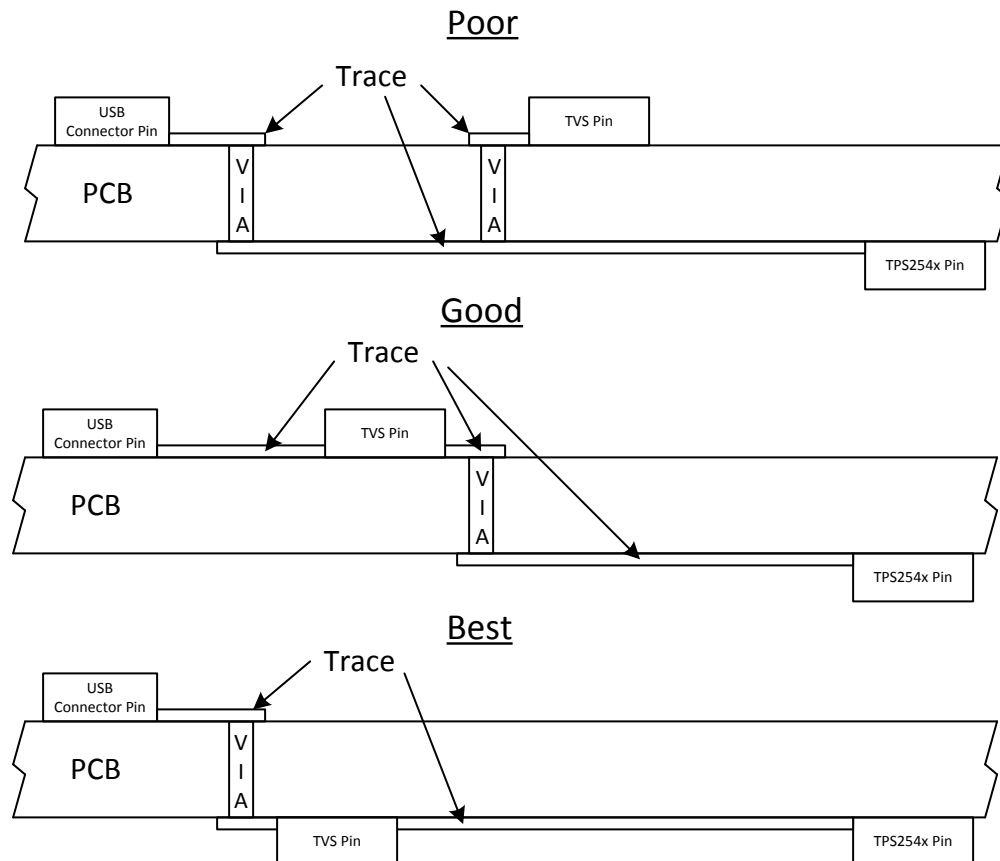


Figure 3. Examples of TVS Placement and Connectivity

Use a heavy connection from TVS VCC and GND pins to VBUS and ground plane respectively. Use multiple vias to make the connection when VBUS and ground are on internal layers.

5 Conclusion

The guidelines in this application report provide a robust solution for ESD suppression in USB charging based devices. Protection up to and above ± 8 kV contact and ± 15 kV air discharge are achieved by proper PCB layout and choice of the TVS.

6 References

1. Data Sheet: TPS2546 USB Charging Port Controller and Power Switch With Load Detection ([SLVSBJ2](#))
2. Application Report: ESD Protection Layout Guide ([SLVA680](#))
3. Application Report: Design Considerations for System-Level ESD Circuit Protection ([SLYT492](#))
4. User Guide: TPS254xEVM-064 ([SLVU660](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com