

Minimizing Switching Ringing at TPS53355 and TPS53353 Family Devices

Benyam Gebru

ABSTRACT

The system reliability of a high efficiency DC/DC converter with a fast slew rate is improved when switch node ringing is reduced. This document describes switching ringing reduction methods and lab bench test results with the 30-A TPS53355, and also applies to the pin compatible 20-A TPS53353. Both devices are well-suited for rack server, single board computer, and hardware accelerator applications that benefit from the fast transient response time of D-CAP™ control, or when multi-layer ceramic capacitors are undesirable for the output filter.

Contents

1	Introduction	2
2	Proper Measurement Method of Switch Ringing	2
3	Minimize the Switch Ringing by Adding RC Snubber and Bootstrap Circuit.....	5
4	Practical Design	8
5	Adding Bootstrap Resistor	11
6	Effects of Snubber on the Efficiency Performance	12
7	Summary	12
8	References	13
1	Changes from original to Nov 13, 2018	14

List of Figures

1	Single-Ended Probing	2
2	Probing Using 1-GHz Differential Probe	3
3	Typical Switching Ringing Waveform of TPS53355	4
4	RC Snubber Added Circuit With Parasitic Components	5
5	TPS53355EVM-743 RC Snubber Placements.....	5
6	Switching Ringing Waveform Rising and Falling Edges	6
7	Un-snubber Switching Node Ringing Waveform	8
8	Switching Node Ringing Waveforms (Blue: With 2.2-nF Capacitor Added, Green: No Snubber)	8
9	Switch Node Ringing Waveforms at 30-A Load (Blue: With Snubber 2.2nF + 1.47Ω, Green: No Snubber) ..	10
10	Rbst 2.05 Ω + 0.1 μF and 1.47 Ω + 2.2 nF Snubber	11
11	Rbst 0 Ω + 0.1 μF and 1.47 Ω + 2.2 nF Snubber	11
12	Boot Resistor Effects on Efficiency	11
13	Efficiency Comparison When Snubber Capacitance Cs Changes	12

List of Tables

1	TPS53355 and TPS53353: Comparing Ringing Voltage of Three Snubber and Bootstrap Resistors.....	10
---	--	----

Trademarks

SWIFT, D-CAP are trademarks of Texas Instruments Incorporated.
All other trademarks are the property of their respective owners.

1 Introduction

Due to high-voltage change (dv/dt) and current changes (di/dt) at the high-speed switching MOSFETs, a significant ringing and overshoot voltage can be observed at the switch node of the at synchronous buck converter while the high-side MOSFET is turn ON. Even though fast-switching speeds help reduce the switching loss, the buck converter efficiency would still suffer. This application note will focus on minimizing switching ringing at TPS53k family products of SWIFT™ synchronous step-down converter. First, this document will describe switch ringing measuring methods, how to minimize the switching ringing by adding an RC snubber circuit and bootstrap resistor, and the effect of snubber on efficiency performance of the synchronous buck converter.

2 Proper Measurement Method of Switch Ringing

How and where to measure fast switch ringing at buck regulators is very important. It is highly recommended to use 1-GHz differential probe, which should be probed as close as possible to the switch node and thermal pad-GND. The voltage probe should have the bandwidth of 500 MHz or more. [Figure 1](#) and [Figure 2](#) shows two different probing methods used at TPS53k family devices. A single-ended, P6139B, 500-MHz, passive probe is used in [Figure 1](#), and a TDP1000, 1-GHz differential probe is used in [Figure 2](#).

 


Figure 1. Single-Ended Probing

 


Figure 2. Probing Using 1-GHz Differential Probe

These probing techniques result in different ringing peak voltages. Because the single-ended probe has 6.5-in long ground wire loop, the probe can pick noises generated from neighboring device of the system board, which can couple to the switch node voltage. On the other hand, by placing the differential probe very close to the IC with two short leads reduces the measurement loop results with less noise coupling to the switch node. The optimal switch ringing can be obtain using this measurement method.

Figure 3 shows typical switching ringing waveform of TPS53355 using a single-ended probe with 6.5-in long ground wire loop that was taken at TPS53355EVM-743 evaluation module (EVM) at 12-V input voltage, 1.5-V output voltage with 30-A load and 500-kHz switching frequency. The switching peak voltage is 27.8 V; whereas, at the same test condition using differential probes, the peak switching voltage is 22.4 V. Therefore, improper measurement method can result in inaccurate ringing voltage.

 


Figure 3. Typical Switching Ringing Waveform of TPS53355

3 Minimize the Switch Ringing by Adding RC Snubber and Bootstrap Circuit

The addition of RC snubber will reduce the switch ringing voltage with a small impact on overall efficiency. This RC snubber is required to avoid excessive ringing that can cause damage to the devices and high-frequency EMI radiation. The RC snubber should be placed as close to the switch to ground pins as possible. Figure 4 and Figure 5 show the placement of RC snubber with the parasitic components.

 


Figure 4. RC Snubber Added Circuit With Parasitic Components

 


Figure 5. TPS53355EVM-743 RC Snubber Placements

The switch ringing occurs when the high-side MOSFET is on and the low-side MOSFET is off with internal MOSFETs parasitic capacitance and inductance, which creates a resonance circuit resulting in high-frequency switch ringing. Now to examine the switch-ON ringing rising edge, which is mostly determined by C_{oss} of low-side FET plus total parasitic inductance of both FET's switching loop (L_p on both MOSFETs, L_{traces} , C_{in_ESL}).

 


Figure 6. Switching Ringing Waveform Rising and Falling Edges

The parasitic inductance and capacitance R_s snubber values will depend on L_p and C_p components of the network. Because of the parasitic value for integrated MOSFETs, the layout parasitic and packaging parasitic, such as wire bond, is unknown. A quick and easy way to determine snubber component values is to measure the ringing frequency (F_{ring}) at the lab bench then characterize the impedance of the circuit. The following method is used to estimate the RC snubber components.

3.1 Methods of Designing RC Snubber

1. Measure the switch node ringing frequency (F_{ring}) of original circuit without snubber. Reduce the original ringing frequency in half by adding a small capacitor from switch to GND.

NOTE: Usually the added capacitance, which is snubber capacitor C_s , is chosen to be approximately three times larger than total parasitic capacitance, C_p . Therefore, the total resonance parasitic capacitor is approximately one third of the added capacitance.

2. Estimate the parasitic inductance L_p using the original ringing frequency—the ringing frequency after adding the snubber capacitor and two capacitances (C_p and C_p+C_s).
3. Estimate parasitic switch node capacitance C_p .
4. Finally, determine snubber resistor R_s required for optimal damping.

To estimate L_p , the parasitic inductance of the circuit, first measure the switch node ringing frequency (T_1) of original circuit without snubber. Next, add external C_s snubber capacitor in the circuit (from switch node to GND), and increase the value of the capacitor until the frequency of the ringing has been reduced by half (F_{ring_2}), which means the change of the period (T_2) doubled when changing the original parasitic capacitance C_p to C_p+C_s .

Estimate the C_p , parasitic the capacitance, and L_p , parasitic inductance, to calculate the snubber resistor R_s required for optimal damping. The damping factor, ξ , for damping response of LC circuit usually range $\xi < 1$ (underdamped) and $\xi = 1$ (critical damped). The value of the snubber resistor is equal to the characteristic impedance of the parasitic resonant circuit that provides near $\xi = 1$ damping.

The characteristics of impedances of L-C circuit can be expresses as following formulas:

[Equation 1](#) shows the natural resonate of L-C frequency.

$$\omega_n = \frac{1}{\sqrt{L_p C_p}} \quad (1)$$

[Equation 2](#) shows the resonate ringing frequency or period without adding external capacitor.

$$F_{ring_1} = \frac{1}{2\pi\sqrt{L_p C_p}}; T_1 = 2\pi\sqrt{L_p C_p} \rightarrow T_1^2 = 4\pi^2 L_p C_p \quad (2)$$

[Equation 3](#) shows the reduced ringing frequency by half (the period doubled) after adding C_s -small capacitor.

$$F_{ring_2} = \frac{1}{2\pi\sqrt{L_p (C_p + C_s)}}; T_2 = 2\pi\sqrt{L_p (C_p + C_s)} \rightarrow T_2^2 = 4\pi^2 L_p (C_p + C_s) \quad (3)$$

Subtract [Equation 2](#) from [Equation 3](#). Manipulate the two equations to find L_p then C_p .

$$L_p = \frac{T_2^2 - T_1^2}{4\pi^2 C_s} \text{ OR } L_p = \frac{1}{4\pi^2 (Fring_2 - Fring_1)^2 C_s} \quad (4)$$

$$C_p \approx \frac{1}{4\pi^2 (Fring_1)^2 L_p} \quad (5)$$

After knowing L_p and C_p , determine snubber resistor R_s that is required for optimal damping.

Setting is $\xi = 1$. The value for the snubber resistor can be calculated as [Equation 6](#).

$$\xi = \frac{1}{2R_s} \sqrt{\frac{L_p}{C_p}} \text{ Damping factor } R_s = \frac{1}{2\xi} \sqrt{\frac{L_p}{C_p}} \quad (6)$$

4 Practical Design

Figure 7 shows an example of the typical un-snubbed and $R_{bst} = 0\Omega$ switch ringing waveforms of TPS53355 D-CAP™ mode, 30-A synchronous buck converter that provides a fixed, 1.5-V output at up to 30 A from a 12-V input bus. The board is operated at 500-kHz switching frequency, 12-Vin, and 1.5-V, 30-A load. For this design example, the schematic from *Using TPS53355EVM-743, High-Efficiency 30A, Synchronous Buck Converter*[1] was used.

 


Figure 7. Un-snubber Switching Node Ringing Waveform

 


Figure 8. Switching Node Ringing Waveforms (Blue: With 2.2-nF Capacitor Added, Green: No Snubber)

Figure 8 shows the un-snubber switch node with the peak voltage of 27.8 V, and the ringing frequency (F_{ring_1}) of 151.5 MHz. To reduce this original ringing frequency, a small capacitor was added. The goal is to reduce the original ringing frequency to almost half by increasing the value of the capacitor. The 2.2-nF capacitor was chosen and placed from the switch node to GND, which reduced the original frequency to 62.5 MHz (F_{ring_2}) and the peak voltage to 24.8 V. Now estimate the parasitic inductance (L_p) using original ringing frequency (F_{ring_1}) and ringing frequency (F_{ring_2}) after adding the snubber capacitor (C_s).

By using Equation 4 the parasitic inductance, L_p, is 1.45 nH, and the parasitic capacitance, C_p, is approximately 761 pF.

$$L_p = \frac{1}{4\pi^2 (62.5 \text{ MHz} - 151.5 \text{ MHz})^2 \cdot 2.2 \text{ nF}} = 1.45 \text{ nH} \quad (7)$$

$$C_p \approx \frac{1}{4\pi^2 (151.5 \text{ MHz})^2 \cdot 1.45 \text{ nH}} = 761 \text{ pF} \quad (8)$$

NOTE: TPS53355 synchronous, step-down converter, low-side FET C_{oss} is 700 pF, which is very close to C_p = 761 pF. Therefore, one can say that this method of estimating the snubber capacitance is valid since the main component of parasitic capacitance, C_p, is C_{oss} of the low-side MOSFET.

Once L_p and C_p are determined, the snubber resistor (R_s) is required for optimal damping is 1.38 Ω, and because 1.38 Ω is not available, R_s = 1.47Ω has been used for this example.

$$R_s = \frac{1}{2} \sqrt{\frac{1.45 \text{ nH}}{761 \text{ pF}}} = 1.38 \Omega \quad (9)$$

With the RC value calculated above, the RC snubber network (1.47Ω + 2.2nF) was placed at switch node to ground, and the optimum switch node ringing was measured at different load conditions. For instance at 30-A load condition, the snubber circuit reduced the switch node ringing peak voltage to 23.85 V from 27.7 V.

Figure 9 shows ringing waveforms at 30-A load with snubber = 2.2 nF + 1.47 Ω and without snubber. Table 1 details different RC snubber configurations test data.

 


Figure 9. Switch Node Ringing Waveforms at 30-A Load (Blue: With Snubber 2.2nF + 1.47 Ω , Green: No Snubber)

Table 1. TPS53355 and TPS53353: Comparing Ringing Voltage of Three Snubber and Bootstrap Resistors

Vin = 12 V Vout = 1.5 V Temperature = 25°C Fsw = 500 kHz	Rbst = 0 Ω + 0.1 μ F No snubber		Rbst = 0 Ω + 0.1 μ F Snubber = 1.47 Ω + 2.2 nF		Rbst = 2.05 Ω + 0.1 μ F Snubber = 1.47 Ω + 2.2 nF		Rbst = 2.05 Ω + 0.1 μ F Snubber = 1.47 Ω + 1 nF	
	Vsw_pk	dV/dt (V/nsec)	Vsw_pk	dV/dt (V/nsec)	Vsw_pk	dV/dt (V/nsec)	Vsw_pk	dV/dt (V/nsec)
Load = 10 A	25.6	10.2	20.8	8	18.2	7	19.2	7.4
Load = 20 A	27.2	12.5	22.8	9	21	8.8	21.8	9
Load = 30 A	27.7	12.9	23.85	11	22.2	10	23.2	10.4

5 Adding Bootstrap Resistor

Another way to reduce the ringing is to include a boot resistor, R_{bst} , in series with boot capacitor, C_{bst} , as shown in Figure 4 to slow down the turn-on of the high-side MOSFET. To control the rising rate of switch node and reduce the V_{sw} ring, add $R_{bst} = 0\ \Omega$ resistor, and increase the R_{bst} resistance until the desired switch node ringing voltage is met. Table 1 shows V_{sw} ring comparison with boot resistor = $0\ \Omega$ and $2.05\ \Omega$ at different load conditions. For example, at 30-A load with $R_{bst} = 0\ \Omega$, the peak voltage of switch node voltage is 23.85 V and 11 V/nsec. On other hand, at 30-A load with $R_{bst} = 2.05\ \Omega$, the peak voltage of switch node voltage reduced to 22.2 V and rising edge reduced to 10 V/nsec. So, increasing the boot resistor affects the turn-on of the high-side MOSFET and the associated rising edge of the SW node voltage; however, as shown in Figure 11 a higher boot resistor does not affect the ringing frequency.

Figure 10 and Figure 11 show the effect of boot resistor on ringing frequency.

 


Figure 10. $R_{bst} = 2.05\ \Omega + 0.1\ \mu\text{F}$ and $1.47\ \Omega + 2.2\ \text{nF}$ Snubber

 


Figure 11. $R_{bst} = 0\ \Omega + 0.1\ \mu\text{F}$ and $1.47\ \Omega + 2.2\ \text{nF}$ Snubber

Adding the boost resistor of $2.05\ \Omega$ will have very small efficiency impact to the converter. As shown in Figure 12, the $2.05\text{-}\Omega$ boot resistor does not effect in the efficiency at light load current ($<6\ \text{A}$). Even at the load greater than 6 A, the boot resistor still has a little effect on the efficiency. With $R_{bst} = 2.05\ \Omega$, the efficiency at 20-A load current is 91.52%; however, with $R_{bst} = 0\ \Omega$, the efficiency at 20-A load current is 91.67%. Thus, because increasing the boot resistor will slow the MOSFET switch-on timing and increase switching power loss, the efficiency will suffer as a result.

 


Figure 12. Boot Resistor Effects on Efficiency

6 Effects of Snubber on the Efficiency Performance

From Philip Todd's classic paper[2], the power dissipated in the snubber resistor (R_s) can be estimated from peak energy stored in snubber capacitor (C_s).

$$P_{cs} = \frac{1}{2} C_s V_{sw}^2 \quad (10)$$

This amount is the energy dissipated in R_s when C_s is charged and discharged in each switching cycle. By principle of conservation of charge an amount of energy equal to that stored will be dissipated. This amount of power dissipation is independent of the snubber resistor; therefore, the average power dissipation at a given switching frequency (F_{sw}), snubber capacitance (C_s), and charging voltage (V_{sw}) can be estimated as:

$$P_{diss} \approx 2 \left(\frac{1}{2} C_s V_{sw}^2 \right) F_{sw} = F_{sw} C_s V_{sw}^2 \quad (11)$$

So the main factor of power loss in snubber circuit is the snubber capacitor, C_s . It is essential to keep the snubber capacitor as small as possible for small power loss. Increasing the snubber capacitance (C_s) will increase the power loss. For example, at 15-A load current using $C_s = 1$ nF, the efficiency is 92.29%, and at the same test condition load current = 15 A with $C_s = 2.2$ nF, the efficiency is 91.97%. It is more noticeable that at light load current using small snubber capacitor— $C_s = 1$ nF—improves the efficiency almost by 1%. The following data at Figure 13 shows the efficiency performance of TPS53355 converter using two different snubber capacitance configurations:

1. Snubber = 1.47 Ω + 2.2 nF, $R_{bst} = 2.05 \Omega$ + 0.1 μ F
2. Snubber = 1.47 Ω + 1 nF, $R_{bst} = 2.05 \Omega$ + 0.1 μ F

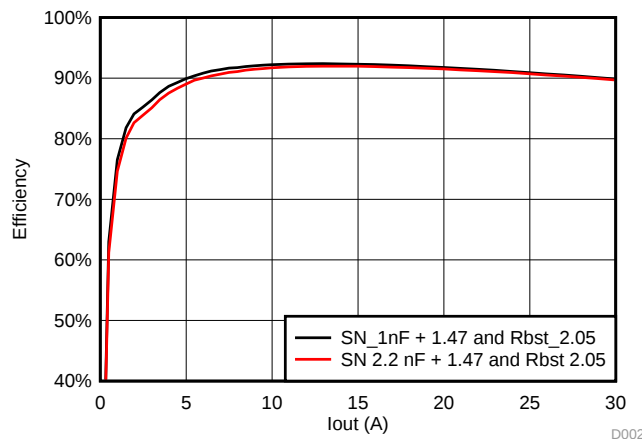


Figure 13. Efficiency Comparison When Snubber Capacitance C_s Changes

7 Summary

In this note, the proper measurement of switch node ringing, which shows that improper measurement can lead to switch node ringing voltage that is higher than desired, was discussed. The RC snubber design methods were introduced and examined to reduce both the amplitude and the ringing frequency of switch node voltage to acceptance levels. Moreover, this application note shown that the result of adding boot resistor, which is to slow down the turn on of the HS MOSFET and reduce the associated rising edge of the SW node voltage; however, the boot resistor does not affect the ringing frequency. Finally, this document has shown the effect of different snubber components values on efficiency performance of the synchronous buck converter.

8 References

1. Texas Instruments, [Using TPS53355EVM-743, High-Efficiency 30A, Synchronous Buck Converter](#), User's Guide (SLUU522)
2. Philip C. Todd, *Snubber Circuits: Theory, Design and Practice*, Unitrode Power Seminar 900 Topic 2, May 1993.
3. Rudy Severns, [Design of Circuits for Power Circuits](#), Application Note written for Cornell Dubilier Electronics, Inc.

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Original (July 2017) to A Revision

Page

!~Revision History

- 1 !~Changes from original to Nov 13, 2018**
!~Rewrite the abstract to include end equipment applications

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated