

TSW3725: Modifying to use the TRF3705 for Performance and BOM Improvements

Chris Pearson

RF and Radio Products

ABSTRACT

The goal of this document is to provide a basic description of the TSW3725EVM, modification requirements and results of replacing the TSW3725EVM's default I/Q modulator TRF370315 with the TRF3705.

Document History

Version	Date	Author	Notes
1.0	September 2012	C. Pearson	First release

Contents

1	TSW3725EVM Description.....	2
2	Hardware and Software Modification Requirements	4
3	TRF3705 versus TRF370315: LTE Band 1 ACPR Results.....	6

Figures

Figure 1.	TSW3725EVM Block Diagram	3
Figure 2.	TSW3725EVM Modification Area	5
Figure 3.	TSW3725EVM Component Changes	6
Figure 4.	TSW3725 Band 1 ACPR, TRF370315	7
Figure 5.	TSW3725 Band 1 ACPR, TRF3705	7

Tables

Document History	1
Table 1. BOM Changes.....	4

1 TSW3725EVM Description

The TSW3725EVM is a small-cell RF transceiver reference design and evaluation platform. It was designed to support the 2G/3G/4G LTE and WCDMA markets for signal bandwidths up to 20 MHz. The default configuration supports Band 1, but its flexibility allows it to support most other LTE & WCDMA Bands. For a complete small-cell development platform the TSW3725EVM mates with [Azcom's BTS digital reference design](#). The TSW3725EVM can also be evaluated as a standalone board with the TSW1400EVM family or with the TSW3100EVM as a digital source board and the TSW1200EVM as a digital capture board.

The TSW3725EVM supports a two transmit, two receive BTS architecture with a shared digital pre-distortion (DPD) observation receive path. Transmit path typical performance numbers for ACPR are less than -67 dBc and for EVM are less than 1% rms. Receive path typical performance numbers for EVM are less than 1% rms at very low input powers.

During the TSW3725EVM design phase the TRF3705 I/Q modulator was not available, however the board was designed to allow for an easy conversion to the TRF3705. As shown in the block diagram in Figure 1 the default schematic uses the TRF370315.

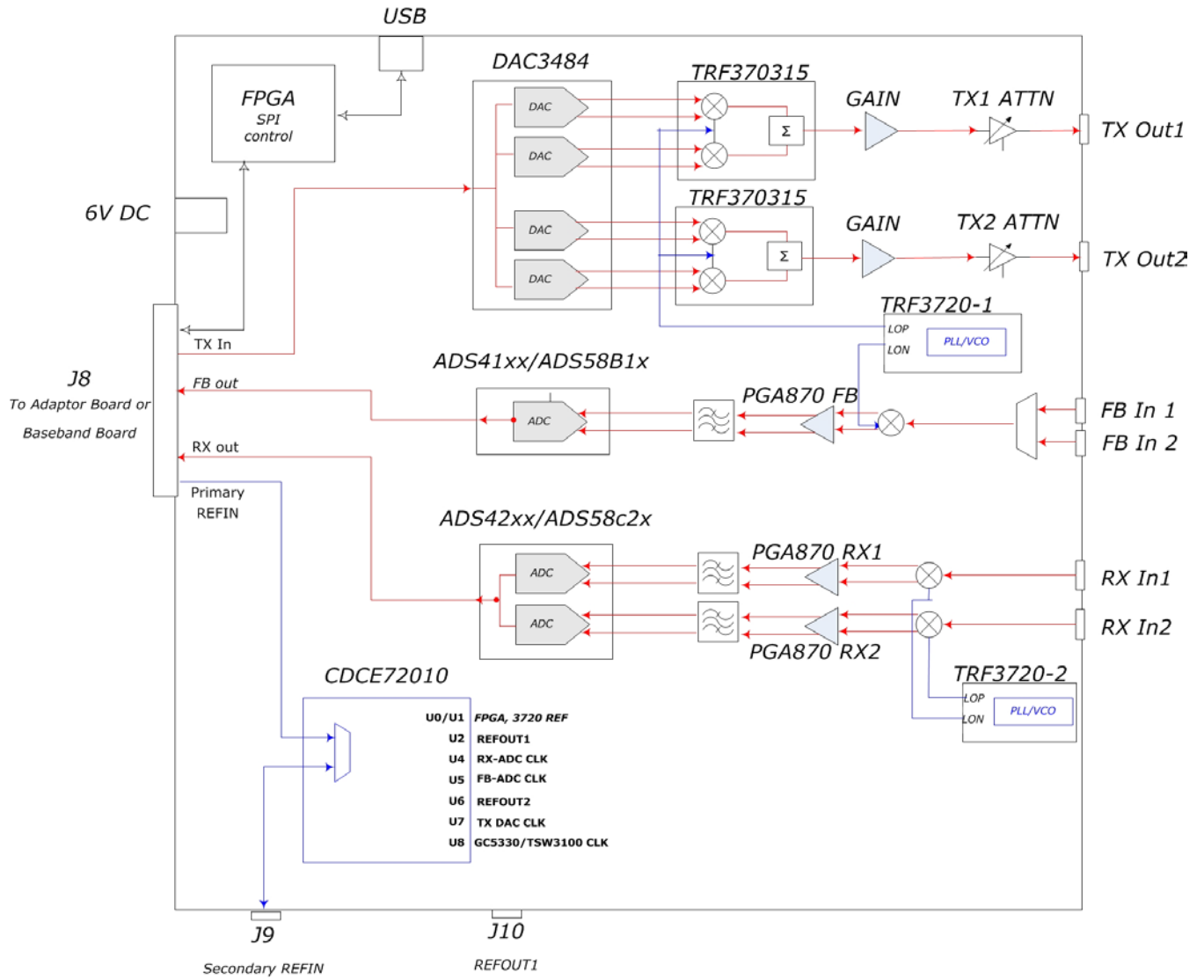


Figure 1. TSW3725EVM Block Diagram

Modifying the TSW3725 to use TRF3705 has the following advantages over the TRF370315:

- a. Improved linearity: the TRF3705 has better performance than the TRF370315 in common LTE bands.
- b. Higher output power and reduced BOM: the TRF3705's common mode input voltage (V_{cm}) of 0.25 V allows a seamless connection with the TSW3725's DAC3484. The TRF370315 common mode input voltage of 1.5 V requires a common mode voltage translation network between the DAC3484 and TRF370315. This translation network requires 24 SMT components and causes a 2.7 dB loss in baseband signal amplitude.
- c. The TRF3705 has additional digital pins for power down and gain control.

2 Hardware and Software Modification Requirements

To modify the TSW3725EVM for use with the TRF3705, the BOM changes shown in Table 1 are required. Figures 2 and 3 highlight in blue where these components are located on the TSW3725EVM. These changes account for the supply voltage, power down pin option, and common mode voltage differences between the TRF3705 and the TRF370315.

After these BOM changes are made, no software modifications are required when evaluating the TSW3725EVM as a standalone board using the TSW3725EVM GUI's default configuration. If the TSW3725EVM is being used in conjunction with other hardware, be aware these hardware modifications result in a 2 dB higher output power on the TX1 and TX2 ports. This increase in output power may or may not result in some software changes elsewhere in the system.

Please note the TSW3725EVM hardwires the TRF3705 power down pin (PD) to ground so that the TRF3705 is always on. Also, the TRF3705 also has a gain control (GC) pin that was not connected in the TSW3725EVM schematic. The GC pin has an internal pull down resistor that sets the TRF3705 to low gain mode on the TSW3725EVM. If creating a schematic with the TRF3705, please note that the high gain mode is enabled by setting the GC pin high. High gain mode provides 3 dB more output power. If high gain mode is desired, then account for it when selecting the proper gain stage to follow the TRF3705. The TSW3725's current fixed gain stage after the TRF3705 starts to degrade linearity performance with this increased input level.

Table 1. BOM Changes

Part Reference	Default BOM	BOM Changes for TRF3705	Change Description
U2, U3	TRF3703-15IRGE	TRF3705IRGE	I/Q Modulator Change
U7	TPS76750QPWP	TPS76733QPWP	5-V LDO to 3.3-V LDO
R22, R49	DNI	0 Ω (0402)	Accounts for TRF3705 PD pin
R12, R18, R28, R34, R39, R45, R55, R61	1 k Ω (0402)	0 Ω (0402)	Removes TRF370315 V_{cm} translation network
R13, R21, R29, R37, R40, R48, R56, R64	2.74 k Ω (0402)	DNI	Removes TRF370315 V_{cm} translation network
C50, C54, C71, C75, C76, C80, C97, C101	1 μ F (0402)	DNI	Removes TRF370315 V_{cm} translation network

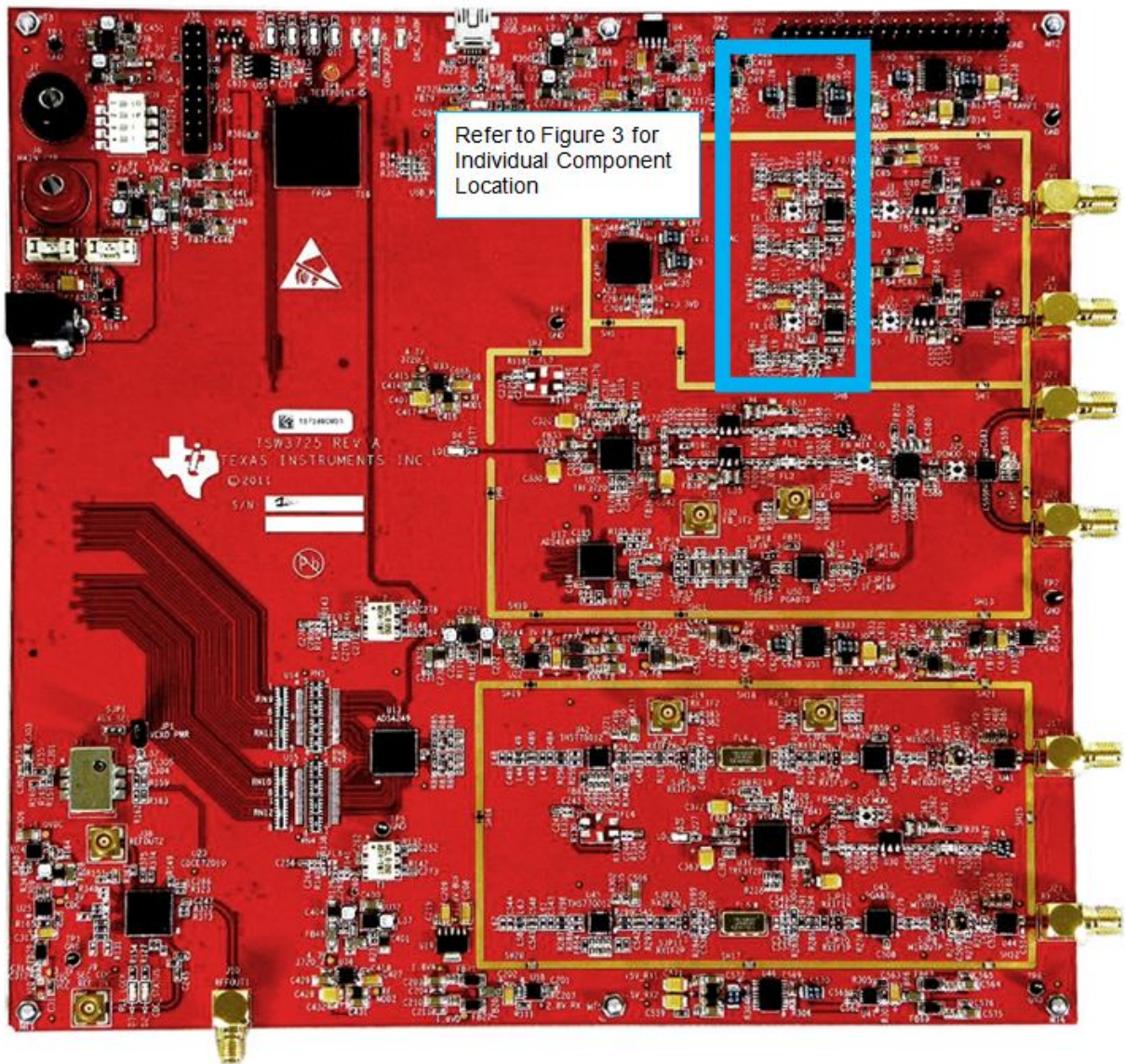


Figure 2. TSW3725EVM Modification Area

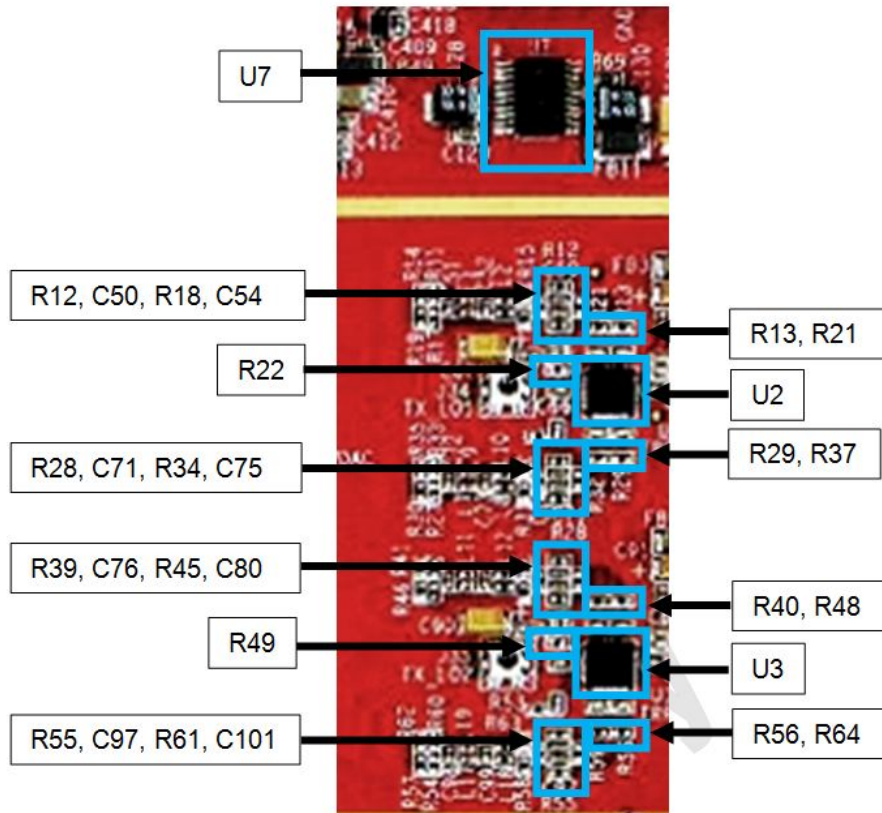


Figure 3. TSW3725EVM Component Changes

3 TRF3705 versus TRF370315: LTE Band 1 ACPR Results

Figures 4 and 5 compare ACPR results of the TRF370315 and TRF3705, respectively. These plots were created by following the LTE demonstration section in the TSW3725 User's Guide. The TRF3705 in Figure 5 provides 2-dB higher output gain and slightly better ACPR performance when compared to the TRF370315 in Figure 4.

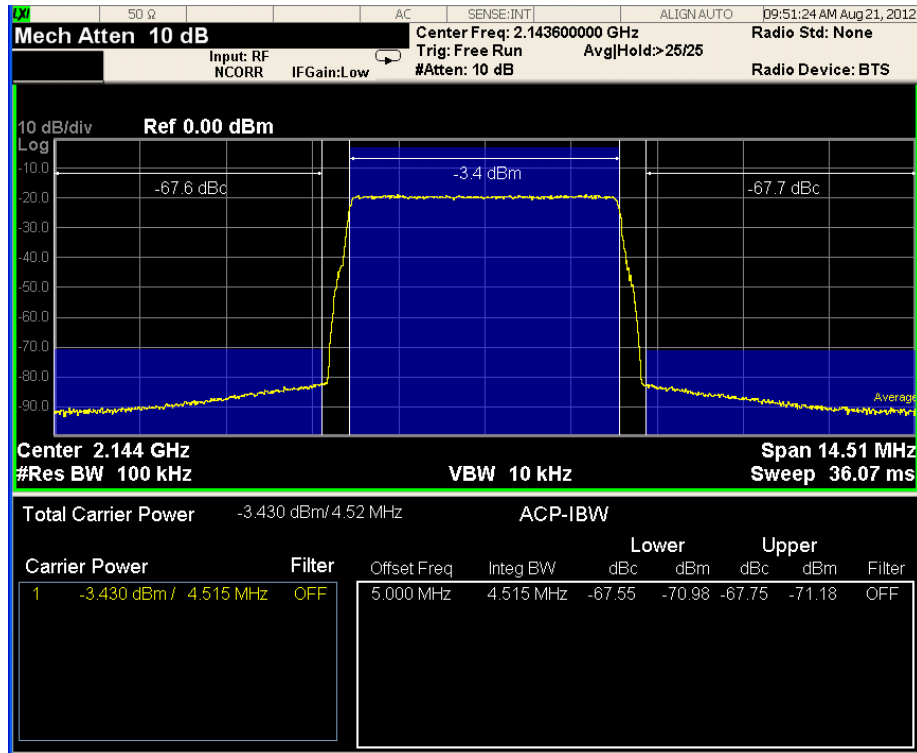


Figure 4. TSW3725 Band 1 ACPR, TRF370315

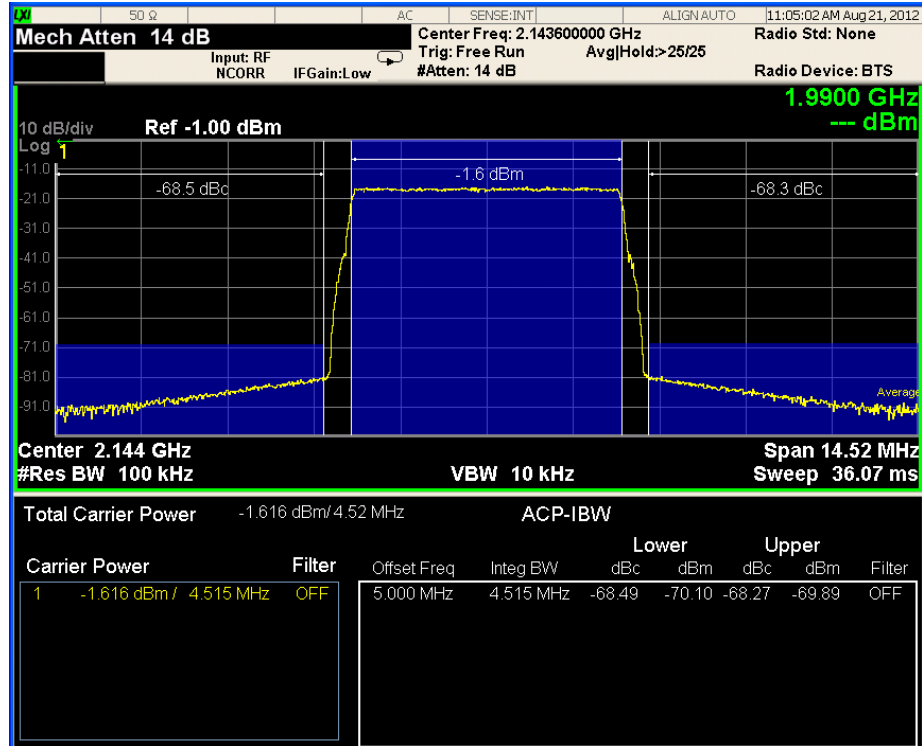


Figure 5. TSW3725 Band 1 ACPR, TRF3705

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com