

### UC3842A LOW COST START-UP AND FAULT PROTECTION CIRCUIT

This circuit optimizes control circuit performance to include:

- Low Start-up Current, Less Than 0.5 ma
- MOSFET Compatible Undervoltage Lockout Thresholds 16V Turn-on, 10V Turn-off
- Programmable Restart Delay HICCUP Fault Protection
- Auxiliary 5V Precision Reference
- Overvoltage/Overtemperature Protection

**CIRCUIT DESCRIPTION AND OPERATION:**


The UC3842A Controller is featured in this design *NOT* as the power supply control IC, but in a supervisory function to assist the principal PWM. It will be utilized to facilitate a low current start-up of less than 0.5 milliamp from the high voltage bulk supply. Additionally, the UC3842A features 16 volt turn-on and 10 volt turn-off thresholds, ideally suited for power mosfet gate drive circuits. The 1 amp output of the UC3842A is used to switch the auxiliary supply voltage to the principal PWM controller, a UC3825 or UC3846 for example.



The oscillator of the UC3842A is configured to generate a constant off time, corresponding to the desired restart delay interval. At the beginning of its operation, the UV

initiates a clock cycle and the PWM output at pin 6 goes high. This is fed to transistor Q<sub>1</sub> which pulls the R<sub>f</sub>/C<sub>t</sub> input at pin 4 low, thus "freezing" the oscillator, while keeping the PWM output high. Once a valid fault (greater than 1 volt) is received at the current sense input (pin 3), the output at pin 6 will go low. Transistor Q<sub>1</sub> is then turned off, and the oscillator generates an off period, or delay as programmed by the R<sub>f</sub>/C<sub>t</sub> components. This procedure will repeat as often as dictated by the fault conditions, but significantly reduces the average short circuit currents and power dissipation.

The UC3842A's current sense node is used as the fault input, and can be configured to provide numerous safeguards. Primary overvoltage protection is accomplished by using a simple resistor divider network or series string of zener diodes to the high voltage rail. Overtemperature protection is possible by including the UC3730 Precision Thermal Monitor IC, or a variable impedance thermistor. In a simple configuration, the fault circuit is designed to deliver a 1 volt input to pin 3 of the UC3842A when a fault response is necessary. The error amplifier can also be biased to accept lower amplitudes of valid fault inputs at the current sense input. A precision five volt auxiliary supply is made available at the IC's reference output, pin 8 and can supply 20 milliamps maximum.
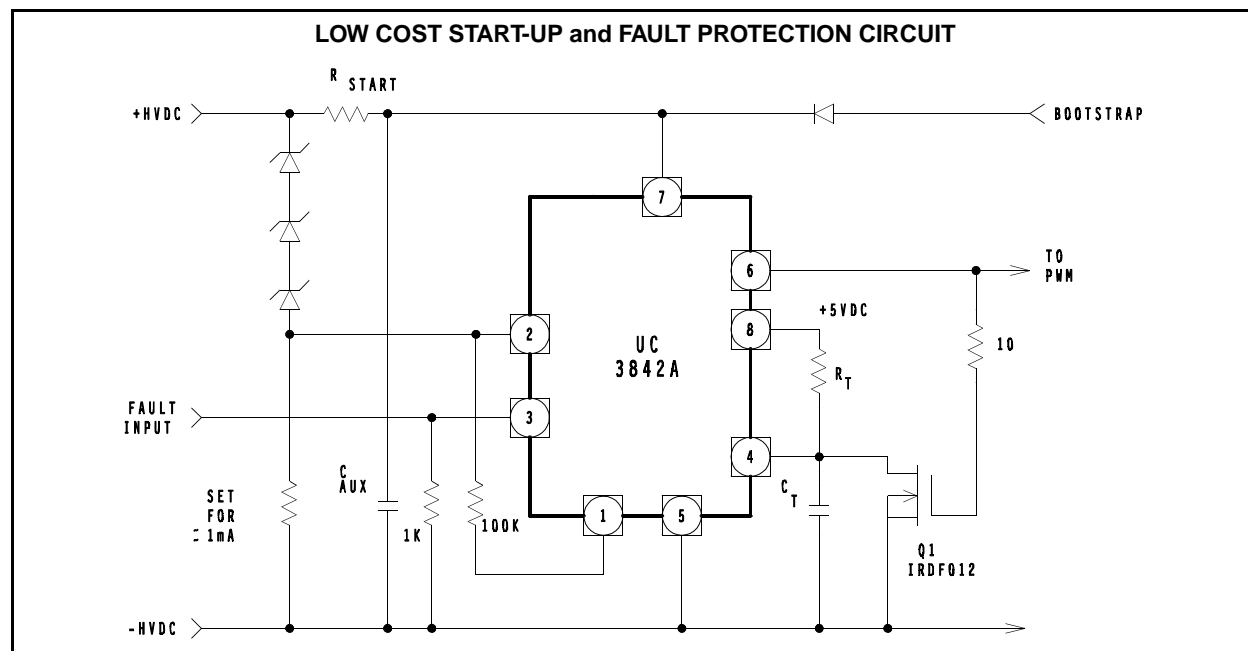
#### UC3842A Supervisory Function Circuits



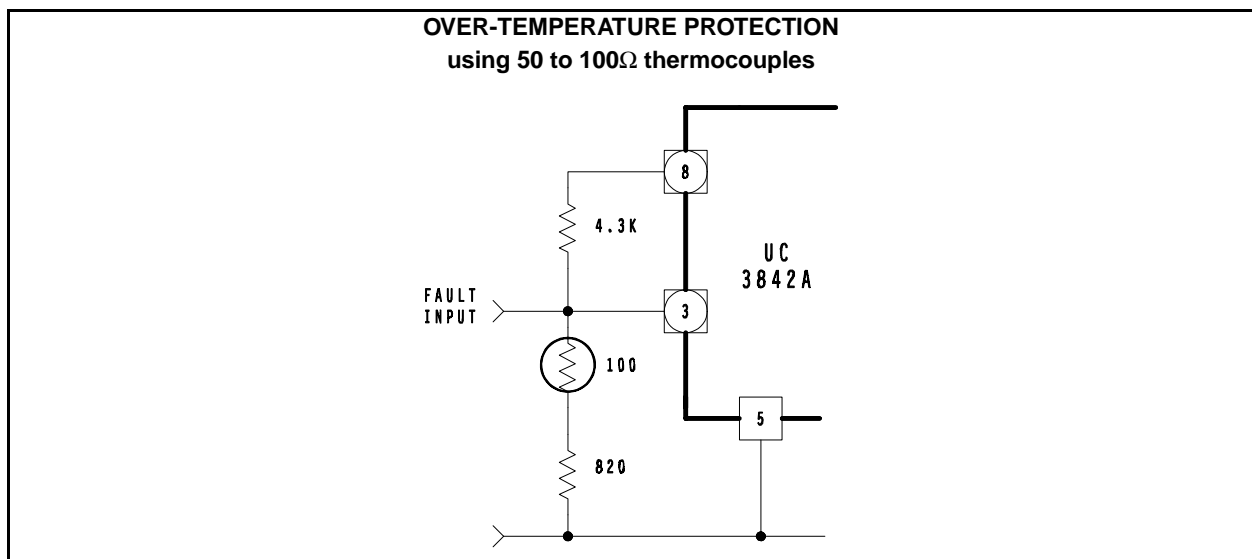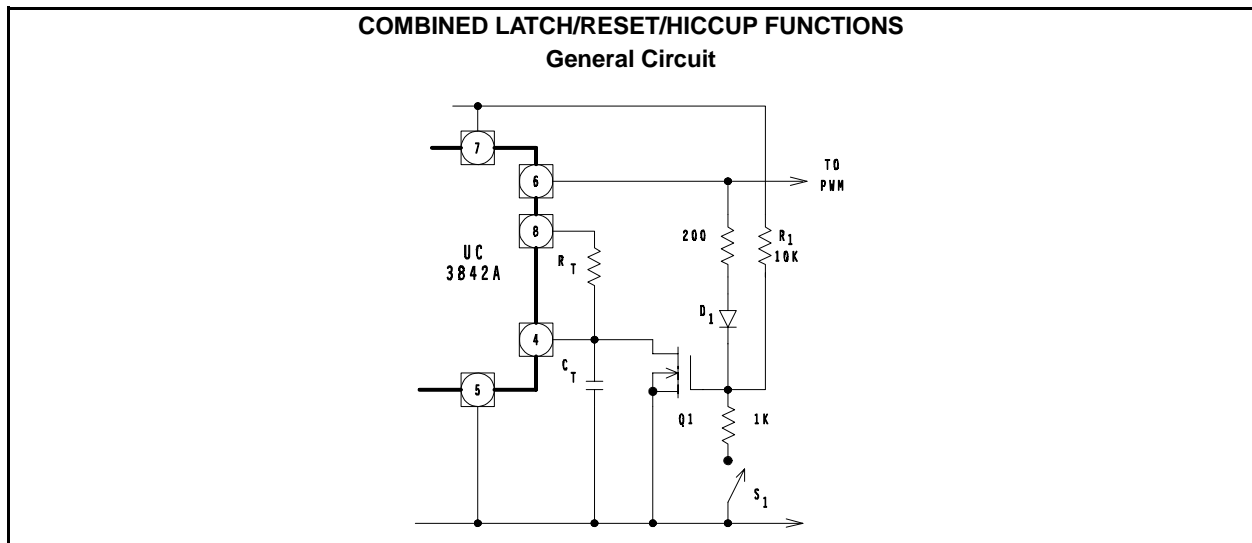

## IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF TI PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.