

Avoiding Audible Noise at Light Loads When Using Leading Edge Triggered PFC Converters

John Bottrill

ABSTRACT

This application note applies to the TI average current mode, leading edge modulation PFC controllers. See Applicable Device Table for part numbers.

When using a leading edge triggered PFC the designer may find that the converter, under extremely light-load conditions, will encounter an audible low noise.

The unit under these conditions can go into the Over Voltage Protection (OVP) state because of the extremely light load. When this happens, the output of the current error amplifier can fall to ground because of the input offset voltage variations and the residual current from MOUT.

When the unit comes out of the OVP state, the pulse width of the converter is going to start at a maximum. Because of the integrating nature of the error amplifier, these pulses will continue for a few milliseconds. This can cause the windings of the PFC inductor to physically oscillate resulting in a periodic burst of audible noise.

A single resistor from VREF to the positive input of the current error amplifier added to the circuit is sufficient to remove this problem.

The input offset voltage of the error amplifier and the multiplier zero current (IMOUT, zero current) are given in the data sheet. Divide the offset voltage by the value of the resistor connecting the positive input of the current error amplifier to ground and add to this the multiplier zero current.

This gives the current needed through the resistor to bias the positive input high under OVP conditions. Now divide the VREF voltage by this current to get the resistor needed to connect from VREF to the positive input of the current error amplifier.

The new resistor will bias the positive input high enough to keep the current error amplifier output high during OVP and because of the integrating nature of the current error amplifier, when OVP is released the unit will gradually increase the pulse width of the pulses as the current error amplifier output falls.

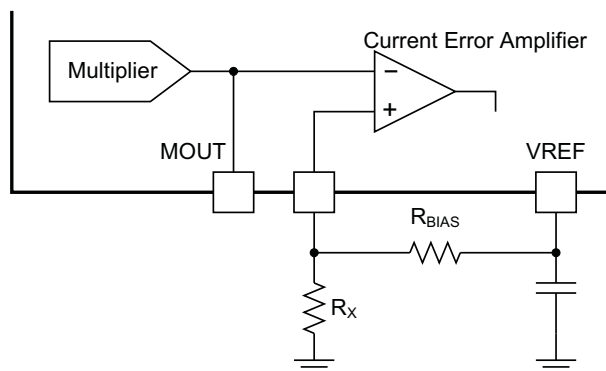


Figure 1. Schematic

Where R_x is the existing resistor from the positive input of the current error amplifier to ground,

$$I_{BIAS} = \left(\frac{V_{OFFSET}}{R_x} \right) \tag{1}$$


$$R_{BIAS} = \frac{V_{REF}}{(I_{BIAS} + I_{MOUT})} \tag{2}$$

where I_{MOUT} is at zero current

Select the nearest standard value lower than this for R_{BIAS} .

This additional resistor does add distortion at the zero crossing of the converter which might cause some problems in meeting the THD of certain designs.

With the addition of three resistors and a transistor it is possible to limit this distortion to extreme light load conditions. The schematic to accomplish this is shown below in [Figure 2](#).

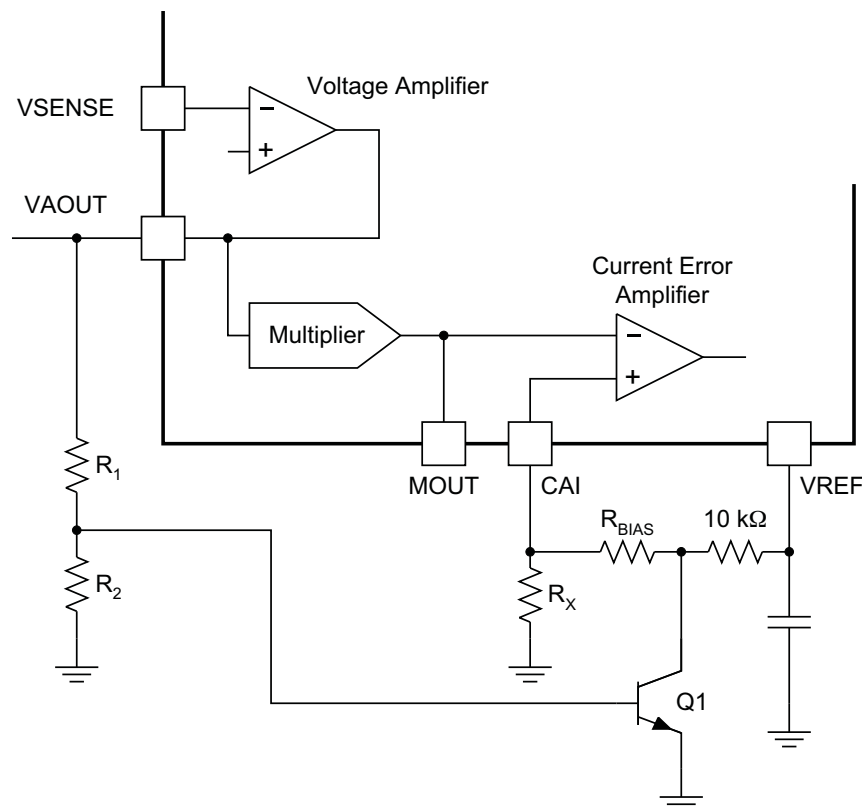

**Figure 2. Circuit to Remove Chirp
(without adding crossover distortion at nominal loads)**

The operation of the circuit is best described with the help of the above schematic and a review of the multiplier equation.

$$I_{MOUT} = \frac{(I_{IAC} \times (V_{VAOUT} - 1))}{(V_{VFF}^2 \times K)} \quad (3)$$

During operation as the output voltage increases the voltage on the VAOUT pin will decrease until at no load the voltage of VAOUT drops below 1 V as per the multiplier equation. At that point, from the multiplier equation, the circuit should be requiring no current.

By setting R1 and R2 so that their junction is slightly lower than the base-emitter junction voltage of Q1 with VAOUT equal to slightly greater than the 1-V level, the Q1 transistor is turned off and the collector voltage rises. This allows the application of the bias voltage to the CAI pin through the R_{BIAS} resistor.

When VAOUT goes higher as it will under any kind of significant load conditions, the Q1 transistor is turned on and the collector pulls the junction of R_{BIAS} and the 10-kΩ resistor to ground.

This removes the crossover distortion at any significant load that is present with the single resistor solution shown in [Figure 1](#).

Table 1. Applicable Devices

BiCMOS Power Factor Preregulators		BiCMOS PFC/PWM Combination Controllers	
UCC2817	UCC2817A	UCC28500	UCC28510
UCC2818	UCC2818A	UCC28501	UCC28511
UCC2819	UCC2819A	UCC28502	UCC28512
UCC3817	UCC3817A	UCC28503	UCC28513
UCC3818	UCC3818A	UCC38500	UCC28514
UCC3819	UCC3819A	UCC38501	UCC28515
		UCC38502	UCC28516
		UCC38503	UCC28517

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video
Wireless	www.ti.com/wireless-apps

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated