

# TPS650330-Q1 Image Sensor Selection



## Scalable PMICs Simplify Design for Automotive Camera Module Power Circuits

Automotive camera module designers have to balance reducing time to market while creating ever-smaller camera module designs that are scalable and reusable for various types of image serializers and sensors. This document examines key design challenges for automotive camera module designs, including design simplification and platform scalability.

## Simplify Design and Speed Time-to-Market with Scalable PMICs

Maintaining a common power design platform helps engineers reduce design time, and therefore time to market. Pin-to-pin and programmable power-management integrated circuits (PMICs) with an integrated voltage supervisor can scale from nonfunctional safety applications (such as surround-view cameras) to functional safety applications (such as driver monitoring, e-mirrors, and cameras in autonomous driving vehicles) without a power circuit redesign.

There are two types of programmable PMICs—software programmable PMICs and hardware programmable PMICs. Software programmable PMICs support fully scalable power management platforms while eliminating the need to redesign printed circuit boards (PCBs).

Figure 1 illustrates this point with the TPS650330-Q1 software programmable PMIC, which has an integrated tool set to support design reuse and simplify design. The TPS650330-Q1 also enables platform scalability through electrically erasable programmable read-only memory programming for output-voltage and power-sequencing settings, as well as adequate electrical current headroom to support image sensors of various resolutions. Because there's no need for a power circuit redesign, engineers can reuse power designs from image sensor to image sensor.

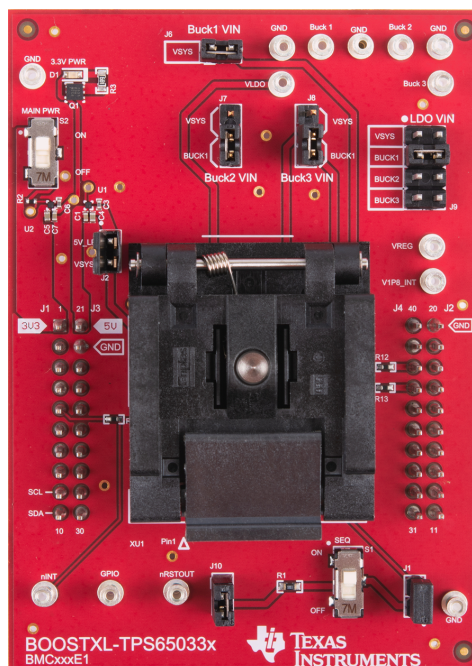


Figure 1. TPS650330-Q1 Programming BoosterPack™ EVM

The TPS650330-Q1 integrates a voltage supervisor and also supports pin-to-pin platform scalability from nonfunctional safety applications to functional safety applications without a power circuit redesign.

The same power board can support many types of image sensor boards with an approach that uses two stacked PCBs, found in some automotive camera modules. For example, engineers can upgrade the same power board to functional safety capable TPS650330-Q1 derivatives when the application must comply with the International Organization for Standardization's (ISO) 26262 functional safety standard by simply dropping in TPS650330-Q1 functional safety devices. For single PCB designs, engineers can also reuse the same power design by copying and pasting the same power design into multiple platforms.

Table 1 lists automotive image sensors that are supported by TI's TPS650330-Q1 PMIC.

## Conclusion

In addition to solution size, thermal performance, electromagnetic compatibility concerns, and power-supply rejection ratio performance, platform scalability is a critical factor to consider in automotive camera module power designs. Selecting a PMIC that allows platform scalability and reusability can reduce time to market and save development costs between platforms.

## Additional Resources

- Watch the [Design Challenges in Automotive Camera Modules](#) video.
- Review our [Available Reference Designs](#) for the TPS650330-Q1.
- Review the image sensor selection options for the TPS650330-Q1 on the [E2E Power Management Forum](#).

**Table 1. TPS650330-Q1 Image Sensor Selection Options**

Image Vendor	Image Device	PMIC	Supporting Technical Collateral
Sony®	IX019, IMX224, IMX290, IMX324, IMX390, IMX424	TPS650330-Q1	See <a href="#">Automotive 2-MP Camera Module Reference Design with MIPI CSI-2 Interface, PMIC, FPD-Link III and POC</a> for more details.
OmniVision®	OV97X6, OV1064/OX01A10, OX01B40, OV10650/OX02A10, OV2311, OV2775, OX01E/01F, OV4xx, OX08A/OX08B	TPS650330-Q1	See <a href="#">Automotive 2-MP Camera Module Reference Design for DMS and other Camera Modules</a> for more details.
Samsung®	S5K4A1, S5K3B5, S5K2G1, S5K3Bx	TPS650330-Q1	Contact TI for reference designs.
Aptina®	AR0132, AR0135, AR0136, AR0138, AR0140, AR0143, AR0144, AR0147, AR0160, AR0220, AR0230, AR0231, AR0233, AR0237, AR0330, AR0430, AR0431, AR0820	TPS650330-Q1	See <a href="#">Scalable Automotive 2-MP Camera Module Reference Design with Camera PMIC</a> for more details.

## 1 Trademarks

BoosterPack is a trademark of Texas Instruments.  
Aptina is a registered trademark of Aptina Imaging Corporation.  
OmniVision is a registered trademark of OmniVision Technologies.  
Samsung is a registered trademark of Samsung Electronics Co., Ltd.  
Sony is a registered trademark of Sony Corporation.  
All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2020, Texas Instruments Incorporated