

# Non-Isolated Point-of-Load Solutions for Tiger Lake in PC Applications



Richard Nowakowski

## ABSTRACT

Notebook, desktop, and industrial computers serve to improve business continuity, enhance consumer entertainment, and streamline industrial process control. Texas Instruments provides performance power-management solutions for these applications to improve performance and extend battery life. Advanced processors and platforms, such as the Intel® Tiger Lake micro-architecture, need point-of-load (POL) solutions for memory, low-power CPU rails, and 3.3 V and 5 V rail requirements from an array of rechargeable batteries, or a 12-V input bus. This document intends to highlight DC/DC converters and describe their features addressing general Tiger Lake power requirements. For specific information about Intel processors and their power requirements, log on to the Intel Resource and Design Center. Contact TI for information about multiphase controllers and power stages designed specifically for the Intel Mobile Voltage Positioning (IMVP) requirements.

## Table of Contents

1 Suggested Tiger Lake Point-of-Load Solutions.....	2
2 Light Load Efficiency (Eco-Mode™) and Low Quiescent Current (ULQ™).....	3
3 Voltage Identification (VID) Capability with TPS51215A.....	4
4 Fast Load Transient Response with D-CAP3™ and D-CAP2™ Control.....	4
5 Small IC Packaging.....	6
6 Conclusion.....	6
7 Resources.....	7
8 Revision History.....	7

## List of Figures

Figure 2-1. TPS51285A Efficiency Plot.....	3
Figure 4-1. TPS51395 Transient Waveform.....	4
Figure 4-2. TPS51215A Load Transient Waveform.....	5
Figure 5-1. TPS566335 in 2x3mm QFN Package.....	6

## List of Tables

Table 1-1. Suggested DC/DC Controllers, Converters and Power Modules for Tiger Lake.....	2
Table 4-1. TPS51215A Load Transient Test Results.....	5

## Trademarks

All trademarks are the property of their respective owners.

## 1 Suggested Tiger Lake Point-of-Load Solutions

Table 1-1 highlights the latest POL DC/DC converters with integrated MOSFETs and controllers suitable for Tiger Lake applications. The suggested devices are selected to accommodate different input voltage and control mode requirements over a wide range of output current. The featured devices in the left column accommodate a maximum input voltage of 22 V or greater, and are designed to achieve fast load-transient response with an adaptive on-time control mode, high light and full-load efficiency, and low quiescent current. Several devices include an integrated programmable voltage identification (VID) supporting the processor's adaptive voltage requirements. The alternate devices in the right column employ fixed-frequency current-mode control with frequency synchronization useful in noise-sensitive industrial applications, and operate up to a 17 V input. If VID is required with alternative devices, consider the LM10011 VID voltage programmer in addition to the converter's resistor divider network.

**Table 1-1. Suggested DC/DC Controllers, Converters and Power Modules for Tiger Lake**

Featured P/N <sup>(1)</sup>	Rail	Current	Type	Note	Alternate P/N <sup>(2)</sup>	Alternate P/N Power Module
<a href="#">TPS51285A</a>	V5A	≤20A & 100mA LDO each Rail	Dual Controller & 2 LDOs	System Power	<a href="#">TPS51220A</a>	<a href="#">TPSM41625</a>
	V3P3					
<a href="#">TPS51395</a>	V5A	≤8A & 100mA LDO	Converter & LDO	System Power	<a href="#">TPS543820</a>	<a href="#">TPSM84824</a>
<a href="#">TPS51393</a>	V3P3					
<a href="#">TPS51215A</a>	V <sub>CCIN_AU</sub> X	≤32A	Controller	I/O power, 2-bit VID (0V support)	-	-
<a href="#">TPS51372</a>	V1P8A, Optional bypass	≤6.5A	Converter	2-bit VID	<a href="#">TPS543620</a>	<a href="#">TPSM84424</a>
<b>General Purpose DC/DC Converters</b>						
<a href="#">TPS51219</a>	Various	≤25A	Controller	General	<a href="#">TPS543B20</a>	<a href="#">TPSM41625</a>
<a href="#">TPS51397A</a>	Various	≤10A	Converter	General	<a href="#">TPS542A52</a>	<a href="#">TPSM41615</a>
<a href="#">TPS51396A</a>	Various	≤8A	Converter	General	<a href="#">TPS543820</a>	<a href="#">TPSM84824</a>
<a href="#">TPS566335</a>	Various	≤6A	Converter	General	<a href="#">TPS543620</a>	<a href="#">TPSM84424</a>
<a href="#">TPS56339</a>	Various	≤3A	Converter	General	<a href="#">TPS543320</a>	<a href="#">TPSM84424</a>
<b>DDR Memory Power Solutions</b>						
<a href="#">TPS51486</a>	V <sub>DDQ</sub>	≤8A	Multi-Channel Converter	DDR4 Memory	<a href="#">TPS65295</a>	<a href="#">TPSM84824</a>
	V <sub>PP</sub>	≤1A				<a href="#">TPS82150</a>
	V <sub>TT</sub>	±1A				<a href="#">TPS82150</a>
	V <sub>TT_REF</sub>	10mA				-
<a href="#">TPS51487X</a>	V <sub>DD1</sub>	≤8A	Multi-Channel Converter	LPDDR4/X Memory	<a href="#">TPS65296</a>	<a href="#">TPSM84824</a>
	V <sub>DD2</sub>	≤1A				<a href="#">TPS82150</a>
	V <sub>DDQ_TX</sub>	≤1.5A				<a href="#">TPS82140</a>
<a href="#">TPS51716</a>	V <sub>DDQ</sub>	≤25A	Controller & LDO	DDR4 Memory	Consider General Devices with <a href="#">TPS51206</a>	<a href="#">TPSM41625</a>
	V <sub>TT</sub>	±2A				Use <a href="#">TPS51206</a>
	V <sub>TT_REF</sub>	10mA				Use <a href="#">TPS51206</a>
<a href="#">TPS51206</a>	V <sub>TT</sub>	±2A	LDO	DDR4 Memory	Use <a href="#">TPS51206</a>	Use <a href="#">TPS51206</a>
	V <sub>TT_REF</sub>	10mA				

- (1) Some featured 24-V devices require Mysecure access to download the data sheet. Click the device link to request access. Users will require their my.ti.com account information.
- (2) Alternate converters operate up to 17 V input with a fixed frequency control mode

## 2 Light Load Efficiency (Eco-Mode™) and Low Quiescent Current (ULQ™)

The POL regulators generating low voltages from an array of batteries must employ an energy-saving pulse-skipping technique now referred to as Eco-Mode. The inductor current in a synchronous-buck converter is a triangle wave. As the output current decreases from a heavy-load condition, the inductor current is reduced and the rippled valley of the triangle wave eventually touches the zero level at the boundary between continuous conduction-mode (CCM) and discontinuous conduction mode (DCM). With Eco-Mode, the rectifying MOSFET is turned off when the converter detects zero current in the inductor. As the load current further decreases, the on-time is held nearly constant so that the off-time is extended, and the switching frequency is reduced to maintain regulation. As a result, the power MOSFETs and inductor are idle for longer time periods and conduction losses are greatly reduced. DC/DC converters and controllers with low quiescent current will have improved light-load efficiency performance and extended battery run-time, since less power is dissipated within the IC. The TPS51825A features Ultra Low Quiescent current (ULQ) of 25- $\mu$ A for longer battery life in system stand-by mode. Figure 2-1 shows 90% efficiency with 7.4-V input and 5-V output at 1-mA, illustrating the combined affects of Eco-Mode and ULQ.

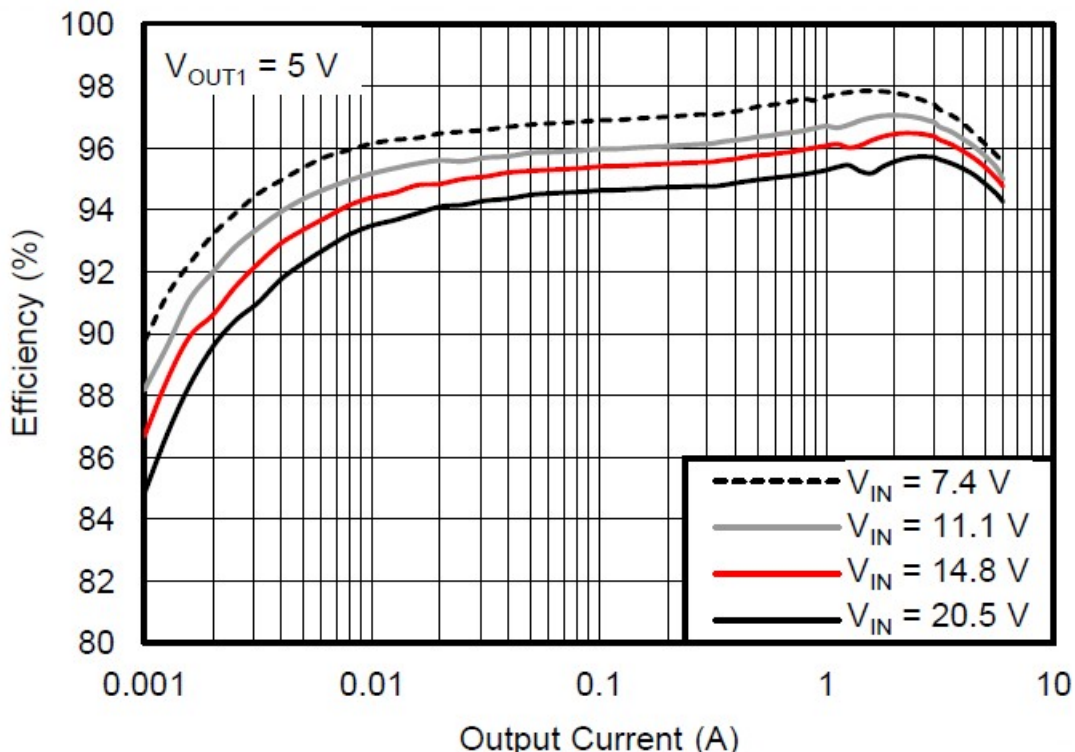



Figure 2-1. TPS51285A Efficiency Plot

### 3 Voltage Identification (VID) Capability with TPS51215A

The TPS51215A supports a 2-bit VID and Low Power Mode(LPM) to dynamically change the output voltage to satisfy Intel IMVP8/9 applications for VCCIN\_AUX, VCCIO\_0, and VCCIO\_1\_2 rails. A fixed 0-V output voltage and up to three voltage levels can be programmed externally with a voltage divider circuit. The device can also be configured to provide a 1-bit VID output voltage. Please see the TPS51215A data sheet for more information.

### 4 Fast Load Transient Response with D-CAP3™ and D-CAP2™ Control

Since the load profile can change dramatically in industrial PC applications, it is important to consider AC transient performance. Choosing a DC/DC converter with a fast transient response using non-linear control techniques, such as constant on-time or D-CAP3, allows a fast transient response with minimal output capacitance. A converter using D-CAP3 control mode has three primary considerations for deciding the value of the output capacitance: transient (which includes load step and slew rate of the load step), output ripple, and stability. In applications where the load transient is stringent, the output capacitance is predominantly driven by the transient requirement. For a D-CAP3 based design, there is a minimum capacitance requirement in terms of small signal stability. This requirement prevents subharmonic, multiple-pulsing behavior in the modulator. [Figure 4-1](#) shows the transient performance of the 8-A TPS51395 with a 5-V output, less than 100mV overshoot, and less than a 30μs recovery with output capacitance of 0.1 μF and 4x22 μF. The 0.8-A to 7.2-A load step has a slew rate of 2.5-A/μs.

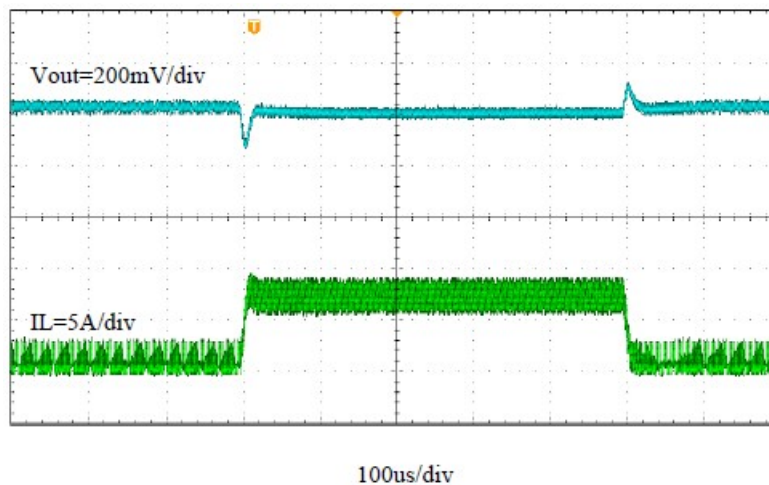

**Figure 4-1. TPS51395 Transient Waveform**

The TPS51215A supplying VCCIN\_AUX features adaptive on-time D-CAP2 control allowing ceramic output capacitors and achieves a fast load transient response shown in [Figure 4-2](#) under the noted conditions below the waveform. The over-voltage and under-voltage test results also meet the target design specification, and the results are shown in [Table 4-1](#) under the same conditions as the TPS51215A load transient waveform. The TPS51215A waveform conditions are  $V_{IN}=12.6V$ , slew rate=12A/μs,  $F_{SW}=600kHz$ ,  $L=0.22μH$ , and  $C_{OUT}=220μF + 22*12μF$ .

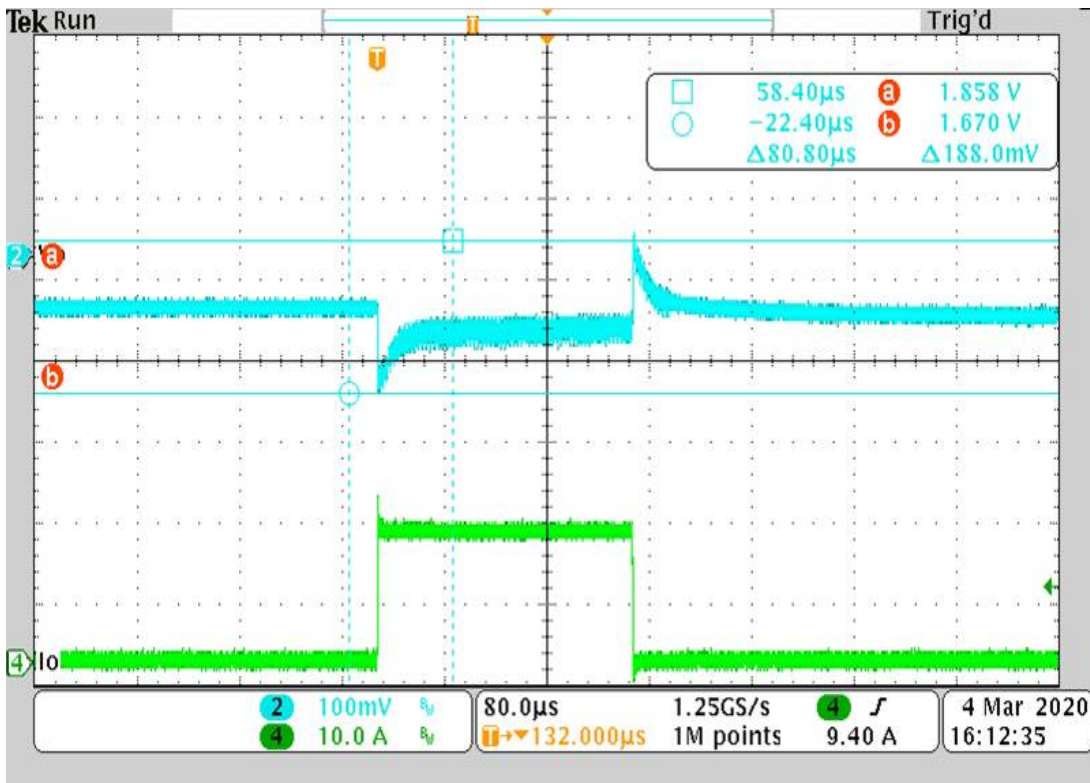


Figure 4-2. TPS51215A Load Transient Waveform

Table 4-1. TPS51215A Load Transient Test Results

Voltage Rail	Type	Load Transient	Validation Result (V)	Target (V)
1.8V	Undershoot	0A to 16A	1.67	1.62
	Overshoot	16A to 0A	1.858	1.89
1.8V	Undershoot	17A to 29A	1.678	1.62
	Overshoot	29A to 17A	1.882	1.89

## 5 Small IC Packaging

Integrated circuit packaging technology must keep pace with semiconductor wafer fabrication as process technology advances. TI has released flip-chip on leadframe packaging that reduce package footprint, power loss, and parasitic effects. Traditional bond wires are replaced with copper posts attached directly to the leadframe which shortens current path from the IC to the lead frame, which allows a larger die in the small package cavity, reduced package resistance, and reduced parasitic package inductance loops. Consider the 6-A TPS566335, housed in a small 2x3mm QFN package. Figure 5-1 shows ample pins for power conversion and I/O features while maintaining a 0.5mm pin pitch, allowing simplified circuit board manufacturing.

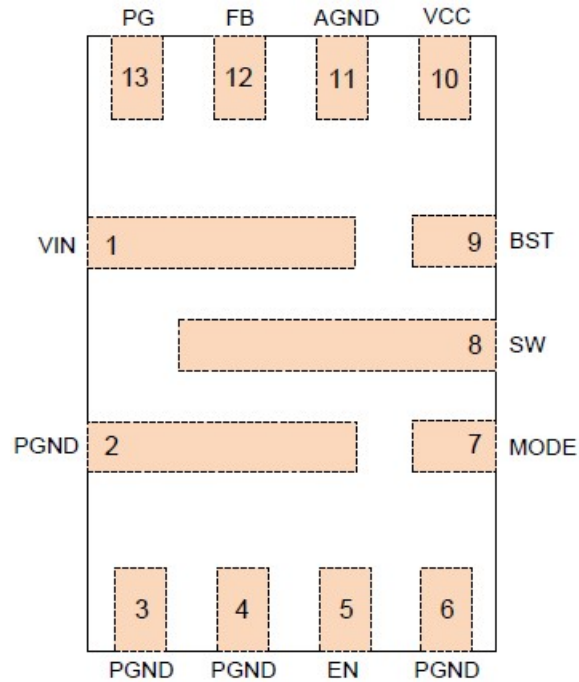


Figure 5-1. TPS566335 in 2x3mm QFN Package

## 6 Conclusion

Performance processors, such as the Tiger Lake platform in Notebook and Industrial PCs, need DC/DC converters that offer fast transient response, small packaging, low quiescent current, and high light and full-load efficiency. TI offers high performance point-of-load solutions to address these requirements while lowering the total system cost.

## 7 Resources

- Texas Instruments, [LM10011 VID Programmer Data Sheet](#)
- Texas Instruments, [Accuracy-Enhanced Ramp-Generation Design for D-CAP3 Modulation Application Report](#)
- Texas Instruments, [Power tips: Iq \(quiescent current\) and Light Load Efficiency](#)
- Texas Instruments, [HotRod QFN Package PCB Attachment Application Note](#)

## 8 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

---

### Changes from Revision A (May 2020) to Revision B (May 2021) Page

- Added newer DC/DC converters and additional suitable power modules throughout the document..... 2
- 

### Changes from Revision \* (May 2020) to Revision A (May 2020) Page

- Deleted Consider General Device with TPS 51206.....2
  - Added 24-V.....2
  - Changed subtitle from "Fast Load Transient Response with D-CAP3™ Control" to "Fast Load Transient Response with D-CAP3™ and D-CAP2™ Control".....4
  - Added cross-reference to TPS51395 Transient Waveform.....4
  - Added figure: TPS51395 Transient Waveform.....4
-

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated